

BJT AmplifiersOverview of DC Analysis of BJTCircuits & ModelsIntroduction to BJT Circuits & Models

- * Transistor is a 3 terminal device with the 3 terminals namely:
- * Emitter
- * Base
- * Collector.

Two types of transistors:



- 1) Unipolar: current conduction is due to one type of charge carriers.
- 2) Bipolar: current conduction is due to both type of charge carriers.


BJT: Current Controlled device,

the O/P current is controlled by i/p cur

Types of BJT based on construction:

- 1) n-p-n
- 2) p-n-p.

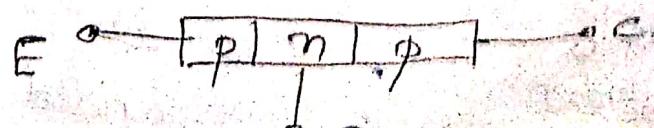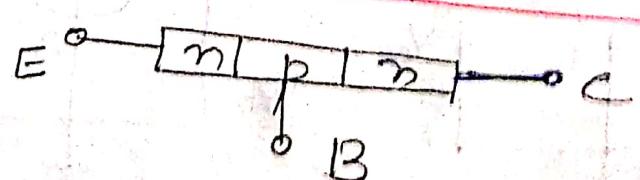

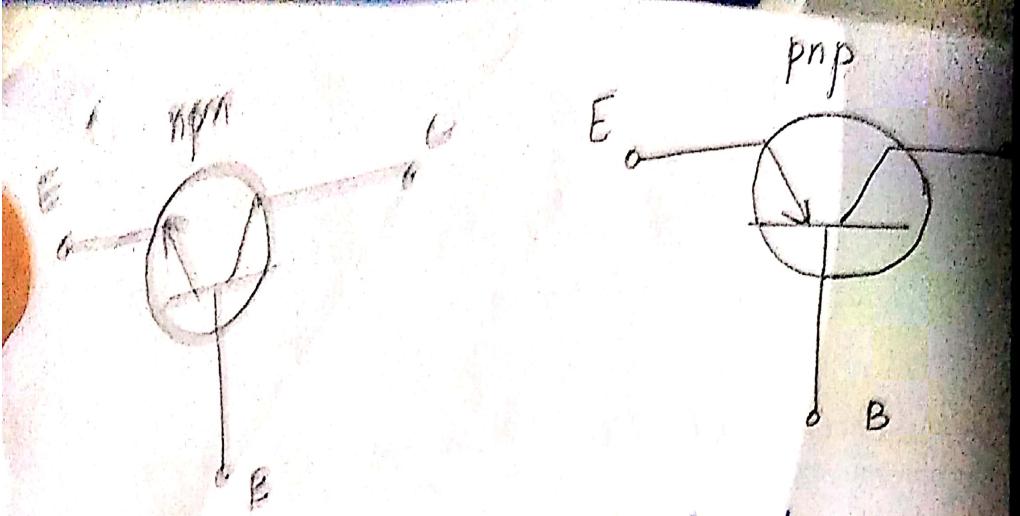

- * Base is thin & lightly doped.
 - * Emitter is heavily doped.
 - * Collector is large and moderately doped.
- Arrowhead indicates the conventional current direction which is opposite to the direction of electron current in emitter.

$$I_E = (1 + \beta) I_B$$

$$I_C = \beta I_B$$

$$I_E \approx I_C$$


BJT Configurations

There are 3 configurations


① Common Emitter

② Common Base


③ Common Collector

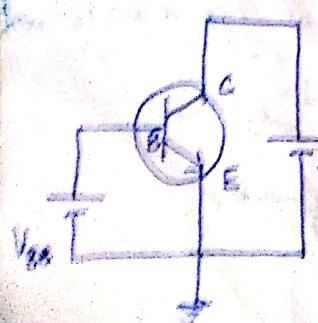

Emitter is grounded

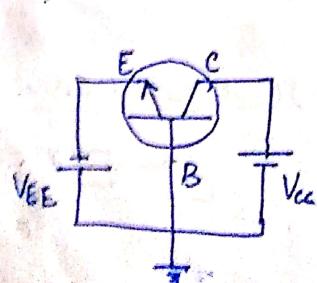

Base is grounded

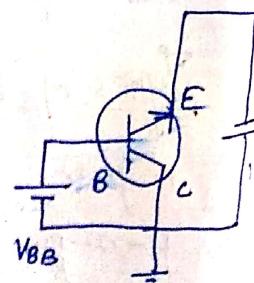

Collector is

* CE is the most popular configuration because of its high voltage and current gain.



Need for Biasing:

Application of dc voltages to establish a fixed level of current and voltage.

Operating / Quiescent point:

When we bias a transistor we establish a certain current and voltage conditions for the transistor. These conditions are called dc operating point.

DC Load line & Q-point

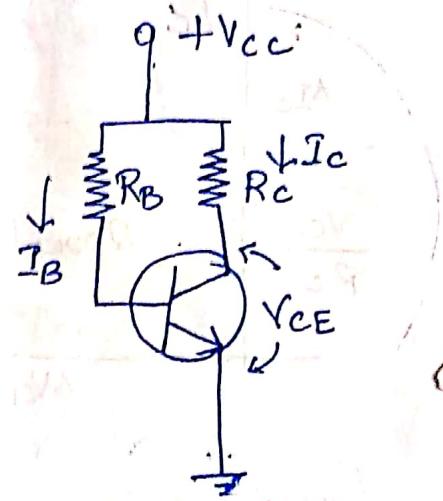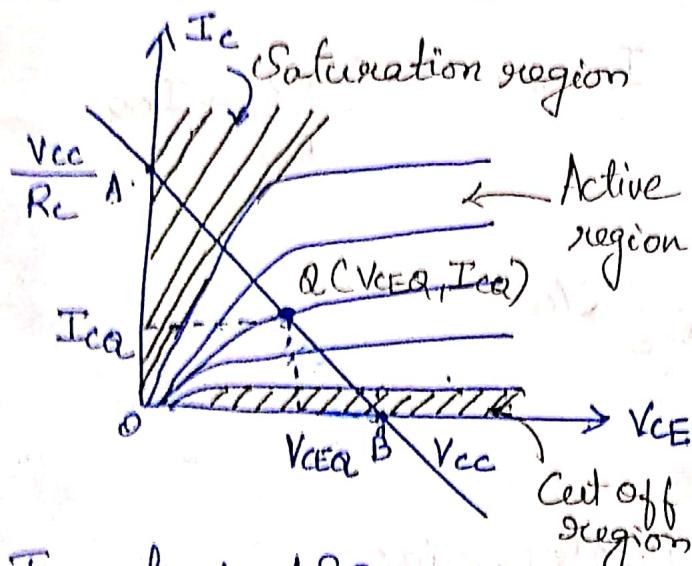

$$V_{CC} - I_C R_C - V_{CE} = 0$$

To find A & B : $V_{CC} - I_C R_C = V_{CE}$



(i) Let $V_{CE} = 0 \therefore V_{CC} = I_C R_C \& I_C = V_{CC}/R_C \rightarrow A$

(ii) Let $I_C = 0 \therefore V_{CE} = V_{CC} \rightarrow B$

Draw a line between A & B called the DC Load line.


Q point is at (V_{CEQ}, I_{CQ}) .

Ac Load line :-

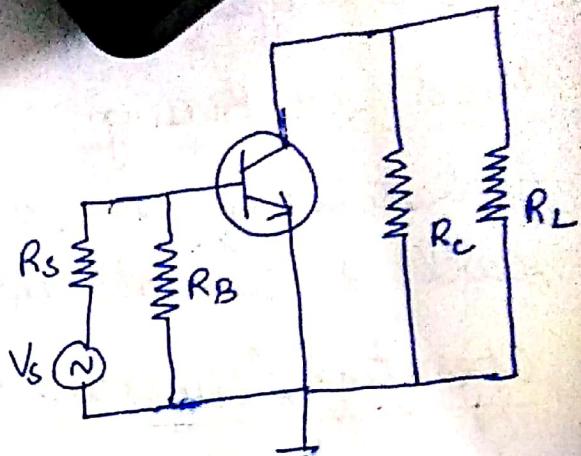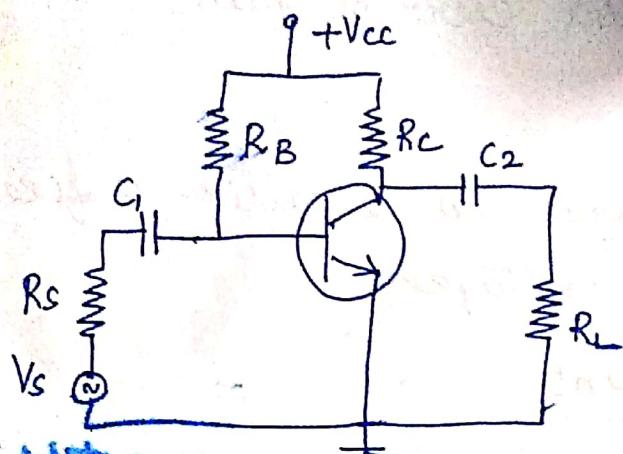

$$R_{ac} = R_C // R_L$$

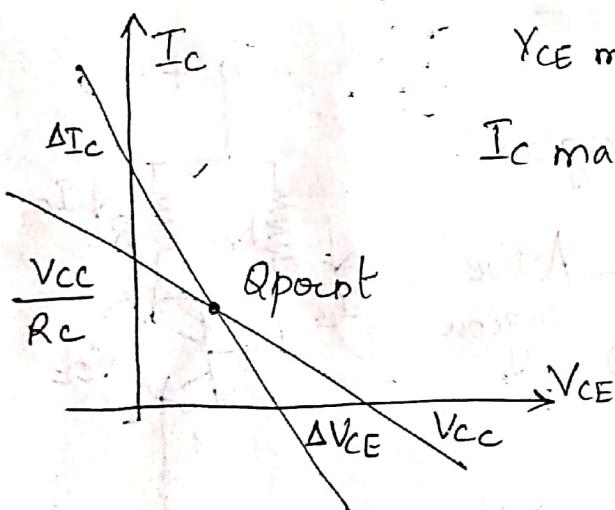- * For ac analysis coupling & bypass capacitors act as short circuit.
- * DC supply also replaced by short circuit.



$$V_{CE \text{ max}} = V_{CEQ} + I_{CQ} \cdot R_{ac}$$

$$I_{C \text{ max}} = \frac{V_{CEQ}}{R_{ac}} + I_{CQ}$$

Types of Biasing

- 1) Self Bias / Voltage Divider Bias
- 2) Fixed Bias
- 3) Collector to base bias
- 4) Emitter stabilised bias.

Stability



measure of sensitivity of a network to variations in its parameters:

I_C is sensitive

$$\textcircled{1} \text{ Price } S(\beta) = \frac{\Delta I_C}{\Delta \beta}$$

$$\textcircled{2} \text{ } V_{BE} \quad S(V_{BE}) = \frac{\Delta I_C}{\Delta V_{BE}}$$
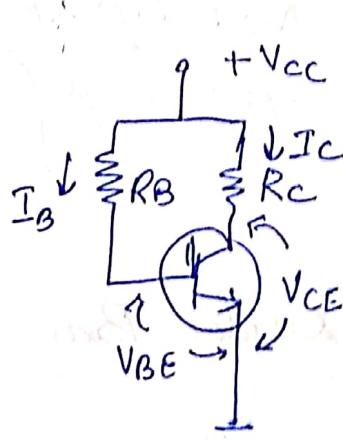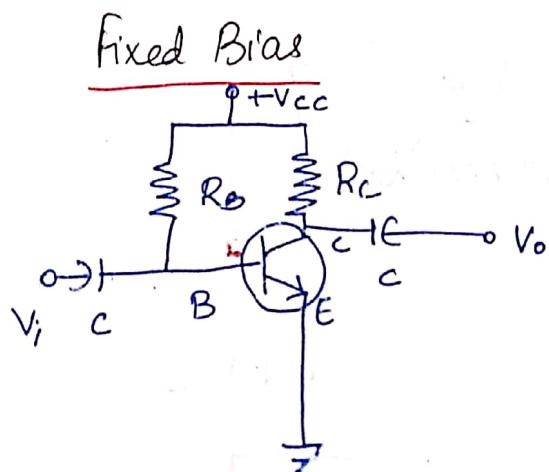
$$\textcircled{3} \text{ } I_{CO} \quad S(I_{CO}) = \frac{\Delta I_C}{\Delta I_{CO}}$$



To find Q-point:



$$V_{CC} - I_C R_C - V_{CE} = 0 \Rightarrow V_{CE} = V_{CC} - I_C R_C$$

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow I_C = \beta I_B \Rightarrow I_C = \beta \left[\frac{V_{CC} - V_{BE}}{R_B} \right]$$

$$S(I_{CO}) = \beta + 1$$

Emitter Bias Configuration

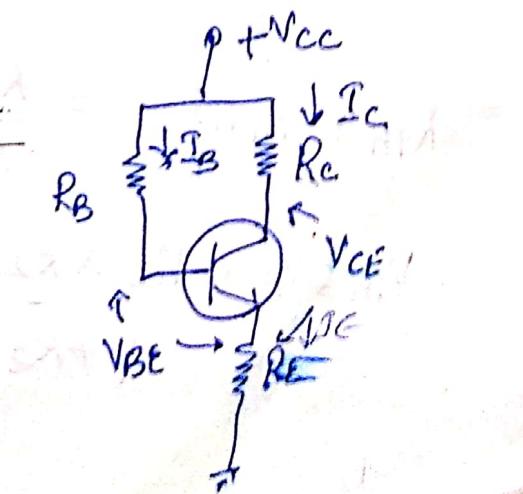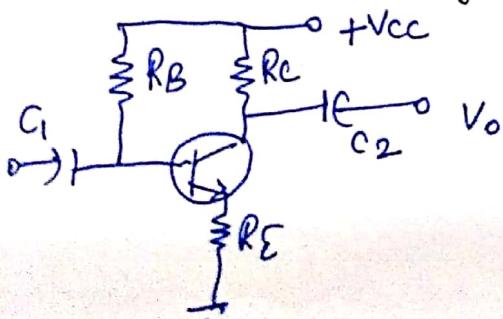

Q point

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0 \quad [I_E = (1+\beta) I_B]$$

$$V_{CC} - I_B R_B - V_{BE} - (1+\beta) I_B \cdot R_E = 0$$



$$I_B R_B + (1+\beta) I_B R_E = V_{CC} - V_{BE}$$

$$I_B [R_B + (1+\beta) R_E] = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E}$$


$$\therefore I_C = \beta I_B = \beta \left[\frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E} \right]$$

Voltage Divider Bias

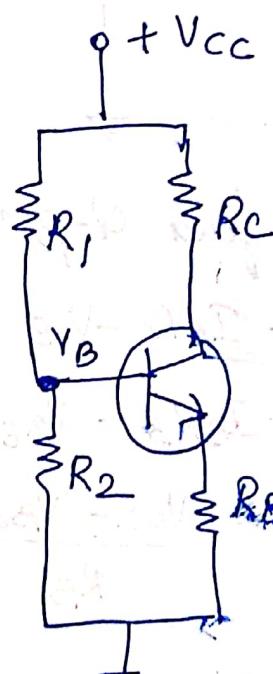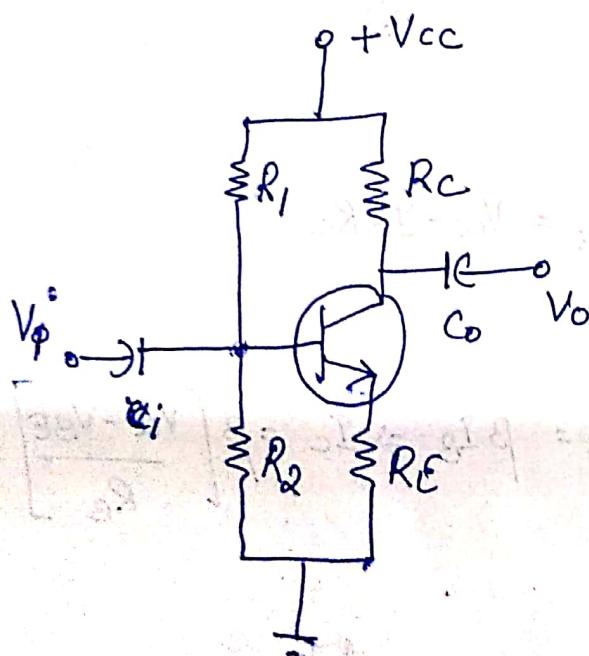

$$R_{Th} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$
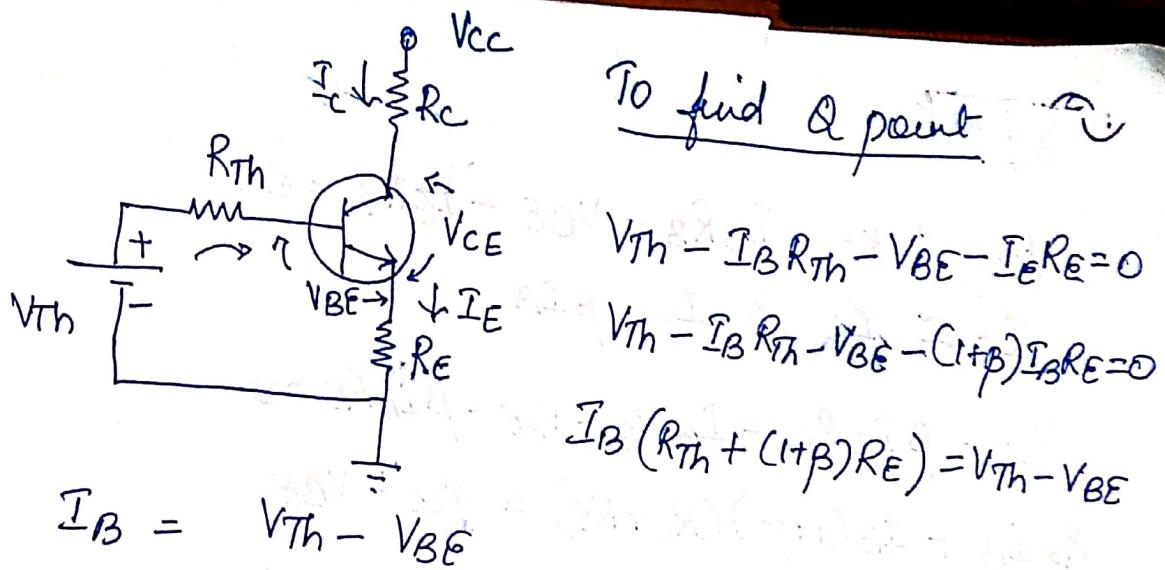
$$V_{Th} = V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$$



$$I_C = \beta I_B = \beta \left[\frac{V_{Th} - V_{BE}}{R_{Th} + (1+\beta) R_E} \right]$$



$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E \quad (I_E \approx I_C)$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$S = (\beta+1) \frac{1 + R_{Th}/R_E}{(1+\beta) + R_{Th}/R_E}$$

Collector Feedback Bias

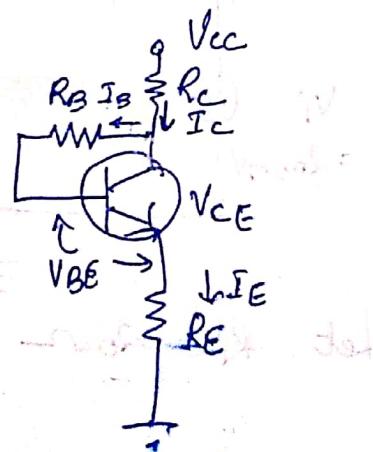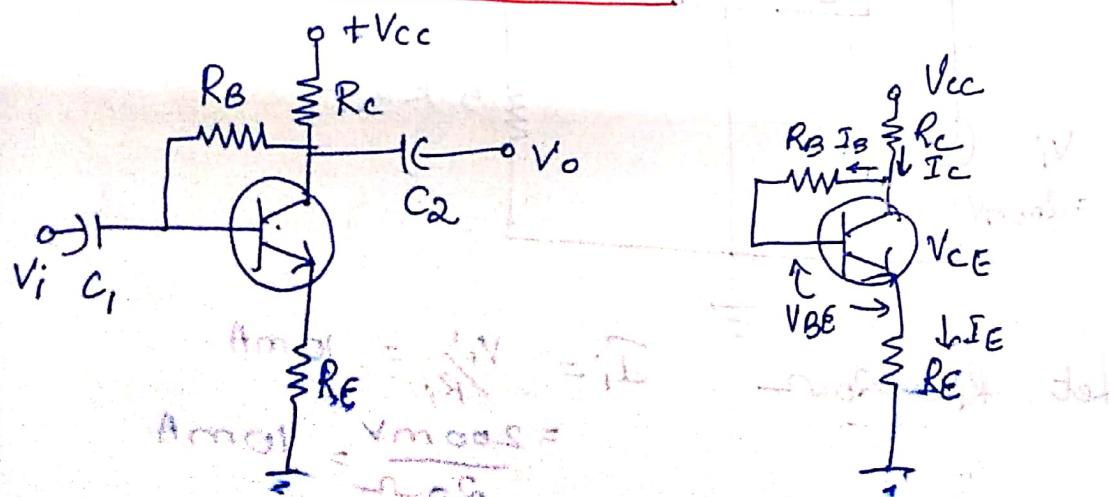

8 point

$$V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E \leq I_C \quad \& \quad I_C = \beta I_B$$

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

$$R_B I_B + I_B(1+\beta)(R_C + R_E) = V_{CC} - V_{BE}$$

$$I_B [R_B + (1+\beta)(R_C + R_E)] = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)(R_C + R_E)}$$


$$R_B + (1+\beta)(R_C + R_E)$$

$$\therefore I_C = \beta I_B = \beta \left[\frac{V_{CC} - V_{BE}}{R_B + (1+\beta)(R_C + R_E)} \right]$$

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

AC Analysis

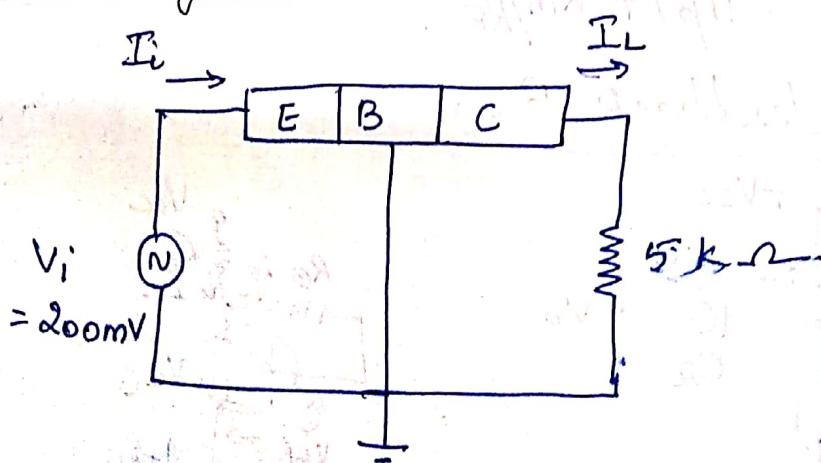

$$\text{Let } R_i = 20\Omega \quad I_i = \frac{V_i}{R_i} = 10 \text{ mA.}$$

$$= \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA.}$$

$I_i = 10 \text{ mA.}$

$$V_o = R_L \times I_L = 10mA \times 5k\Omega$$

$$V_o = 50V$$

$$\text{Gain} = \frac{V_o}{V_i} = \frac{50V}{200mA} = 250$$

An ac signal changes the i_{pp} current (i.e) of I_b ,

~~If I_c changes it, I_c changes Q point shifts.~~

Therefore ac analysis is necessary.

Ac analysis of a transistor network depends on the magnitude of the i_{pp} signal:

1) Small signal analysis

2) Large signal analysis

There are 3 models in small signal analysis:

1) π model


2) Hybrid equivalent model (H -parameters)

3) Hybrid π model.

Model:-

A model is a combination of circuit elements that best approximates the actual behaviour of a semiconductor device under specific operating conditions.

hybrid-parameter (h-model)

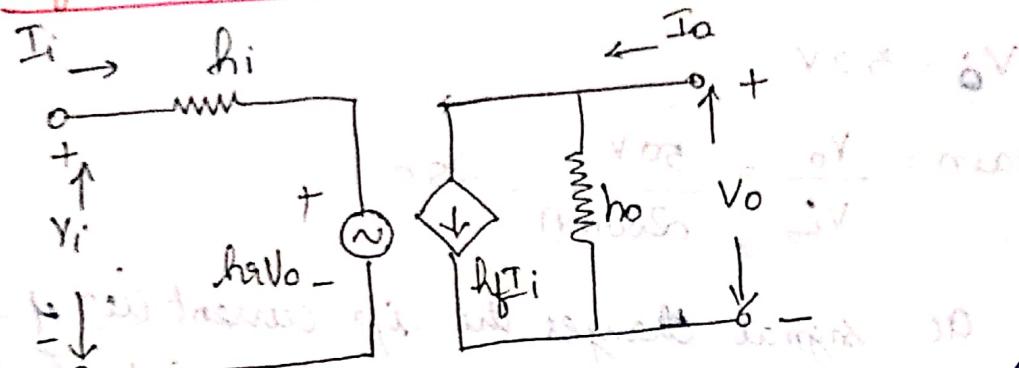

Used for d
when the
in the act
Hybrid h

* Popular
small

The hybrid model is suitable for small signals
at mid band & describes the action of transistor


$$h_i = \text{input resistance } \frac{V_i}{I_i} \text{ at } V_o = 0$$

$$h_r = \frac{V_i}{V_o} \text{ at } I_i = 0 \quad \text{reverse transfer voltage ratio}$$

$$h_f = \frac{I_o}{V_o} \text{ at } I_i = 0 \quad \text{forward transfer current ratio}$$

$$h_o = \frac{I_o}{V_o} \text{ at } I_i = 0 \quad \text{off conductance}$$

Approximate Model - hybrid-coupled

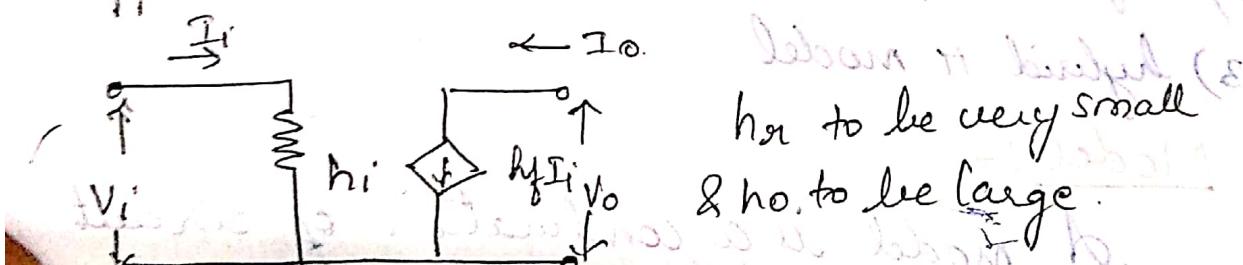

Ac Analysis of basic BJT Amplifier Configuration

Using classical discrete circuit bias arrangement

Small signal Ac Model

Linear Ac models are used for determining
The Q point, however an ac model is

$$\frac{V_{BE}}{I_c}$$

The I
approx
base
varic
The I
gm =

$$I_c$$

$$V_T$$


V
base
diffus
resist

(6)

Used for determining the voltage or power gains when the transistor is operated as an amplifier in the active region.

Hybrid π Model

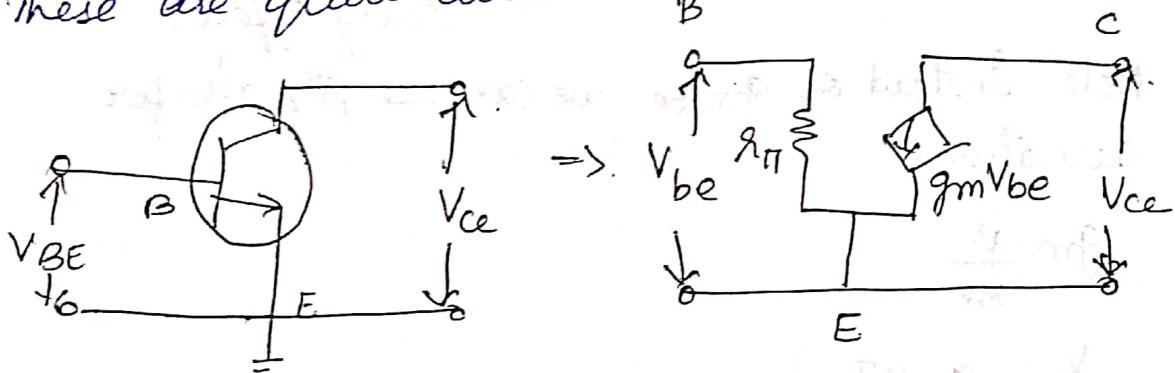- * Popular circuit model used for analysing small signal behaviour of BJT & FET.
- * These are quite accurate.



The hybrid π is a linearized 2 port network approximation to BJT using small signal base emitter voltage, V_{ce} , & i_b , i_c as dependent variables.

The various parameters are:

$$g_m = \frac{i_c}{V_{be}} \Big|_{V_{ce}=0} = \frac{I_c}{V_T} = \text{transconductance}$$

$I_c = I_{cq}$ = Quiescent collector current.

$$V_T = \frac{kT}{q} = \text{thermal voltage}$$

$K \rightarrow$ Boltzmann's constant

~~q~~ \rightarrow charge of electron e ~~walks except~~
~~T~~ \rightarrow temperature in kelvins, and subvols

$$V_T = 26 \text{ mV at room temperature}$$

base emitter resistor

$$r_{\pi} = \frac{V_{be}}{I_B} \Big|_{V_{ce}=0} = \frac{V_T}{g_m} = \frac{V_T}{\beta I_B}$$

$$\beta = g_m R_{\pi}$$

diffusion resistance R_b

$I_b = DC$ bias base current

$\beta_0 = \frac{I_c}{I_B}$ is current gain

$$g_m = \frac{v_{ce}}{i_c} \Big|_{v_{be}=0} \approx \frac{V_A}{I_c}$$

is the O/P

resistance due to
Early Effect


Note: Instead of $g_m v_{be}$ we can use βI_b also for derivations.

$$g_m = \frac{\beta}{r_T}$$

$$v_{be} = g_m \times I_b$$

$$\therefore g_m v_{be} = \frac{\beta}{r_T} \times g_m I_b = \beta I_b$$

Common Emitter Amplifier (AC Analysis)

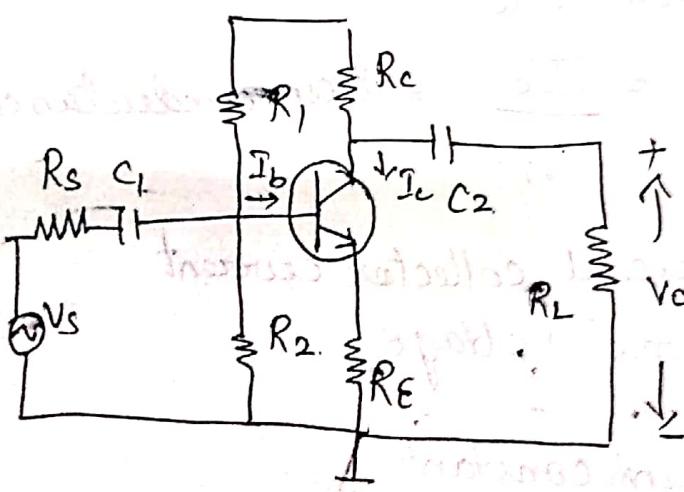

* Figure shows CE circuit with voltage divider bias. Emitter is at ground potential.

* The signal from source is coupled to the base of the transistor through

(1)

the Coupling capacitor → provides dc isolation between amplifier & signal source.

- * R_1 & R_2 → establish dc transistor biasing & is not disturbed when the source is capacitively coupled to the amplifier.
- * At high frequencies

$$|Z_{cl}| = \frac{1}{2\pi f C_C} \quad \text{which is very less. Hence}$$

capacitor is considered as short circuit.

- * Signal frequency is high enough to consider any coupling capacitor as short circuit & transistor capacitances as open circuit.

Steps involved in analyzing an amplifier

Circuit: ~~law of voltages and currents~~


- 1) Conduct a dc biasing analysis of the transistor circuit.
- 2) Determine the signal parameters g_m , ω_{HP} & ω_{LO} .
- 3) Determine the ac equivalent circuit of
- 4) Perform a small signal analysis to find R_i , A_{vo} & R_o .

at present question : $\frac{dV}{dT} = dI$


return to next slide

→ always good thinking

39 (1st part) + next part

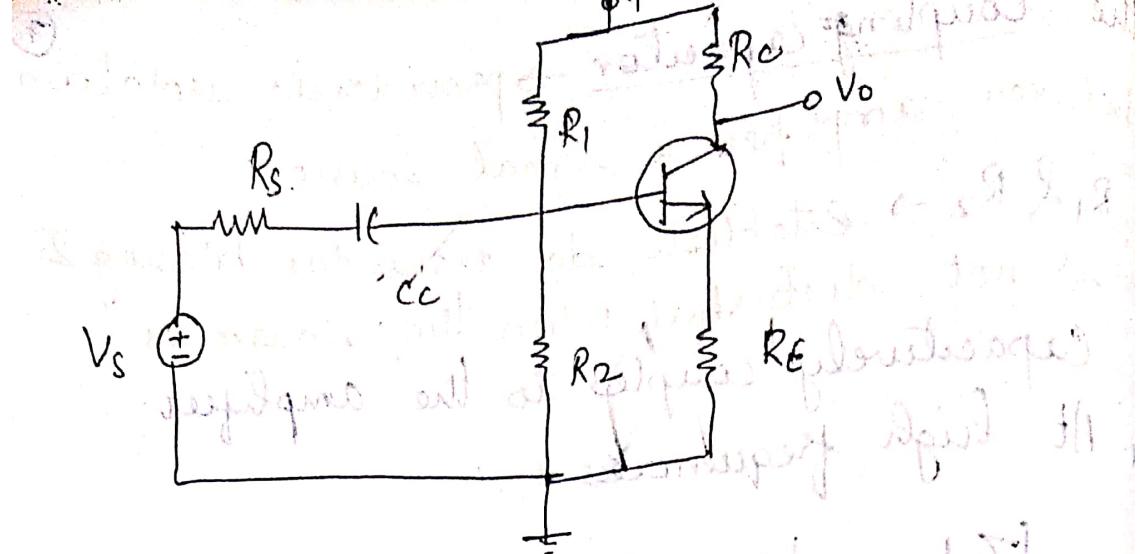

Equivalent Circuit

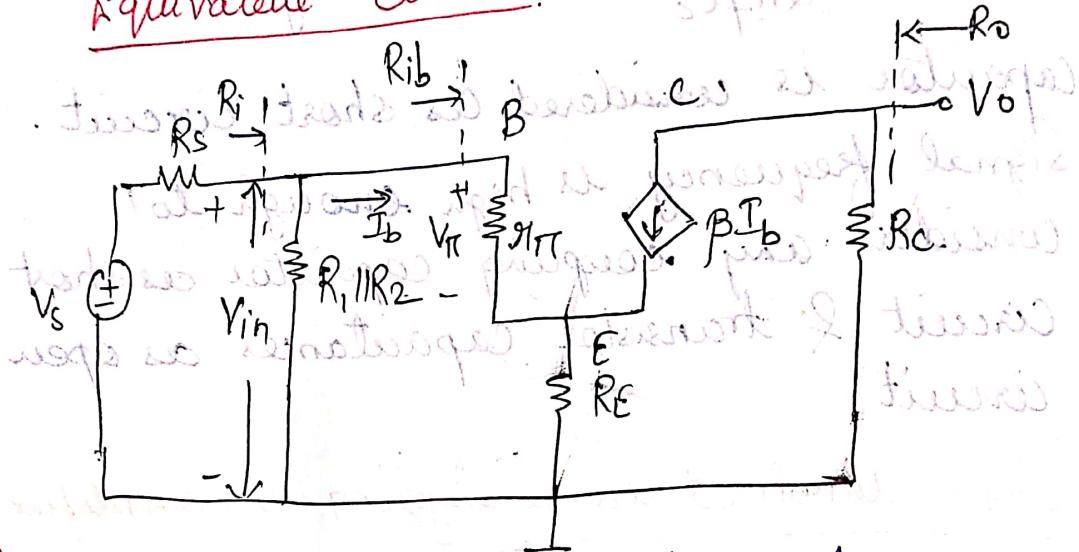

Current gain parameter β is used
 Ro is neglected since early effect voltage
 $V_A \approx \infty$.

$$R_o = \frac{V_A}{I_c} \approx \infty$$

1) Input Resistance R_i

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$R_{ib} = \frac{V_{in}}{I_b}$ = Input resistance looking into
 the base of transistor

Applying loop equations:-

$$V_{in} = I_b R_{ib} + (I_b + \beta I_b) R_E$$

$$\frac{V_{in}}{I_b} = R_{ib} = g_{\pi} + (1 + \beta) R_E$$

This is called as input resistance reflection rule. (8)

Input resistance to the amplifier is

$$R_i = R_1 \parallel R_2 \parallel r_{in} + (1+\beta)R_E$$

2) O/P resistance R_o

The o/p resistance is

$$R_o = R_C$$

3) Voltage Gain A_v

A_{vo} : Open Loop Voltage Gain (without R_S)

$A_{vo} = \frac{V_o}{V_{in}}$

$V_o = -\beta I_b R_C$

$$V_{in} = I_b r_{in} + (I_b + \beta I_b)R_E$$

$$V_{in} = I_b [r_{in} + (1+\beta)R_E]$$


$$\therefore \frac{V_o}{V_{in}} = A_{vo} = \frac{-\beta I_b R_C}{I_b [r_{in} + (1+\beta)R_E]}$$

$$A_{vo} = \frac{-\beta R_C}{r_{in} + (1+\beta)R_E}$$

If $r_{in} \ll (1+\beta)R_E$ then
 $A_{vo} = \frac{-\beta R_C}{1+\beta R_E} \approx -\frac{R_C}{R_E}$

Voltage gain including source resistance & V_S
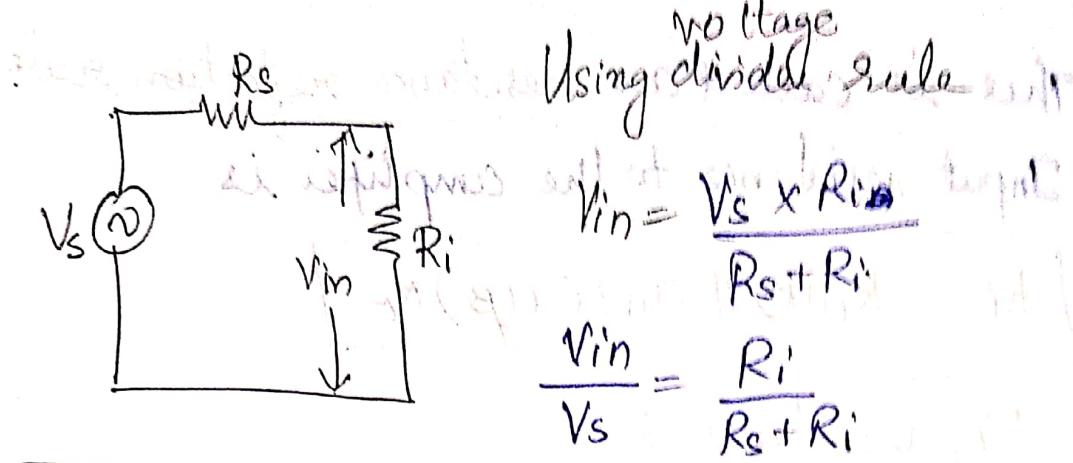
$$A_{vs} = \frac{V_o}{V_S} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_S}$$



$$A_{vs} = \frac{-\beta R_c}{r_{pi} + (1+\beta)R_E} \cdot \left(\frac{R_i}{R_s + R_i} \right)$$


A_{vo} can be made high by

- * Choosing large value of β_f
- * Choosing large value of R_c
- * Choosing low value of R_E ($R_E \approx 0$)

$$A_{vo} = -\frac{\beta_f R_c}{r_{pi}} = -\frac{g_m r_{pi} R_c}{r_{pi}} = -g_m R_c$$

Eg ① For the circuit shown, determine the value of R_i , R_o & A_{vo} for $\beta = 100$
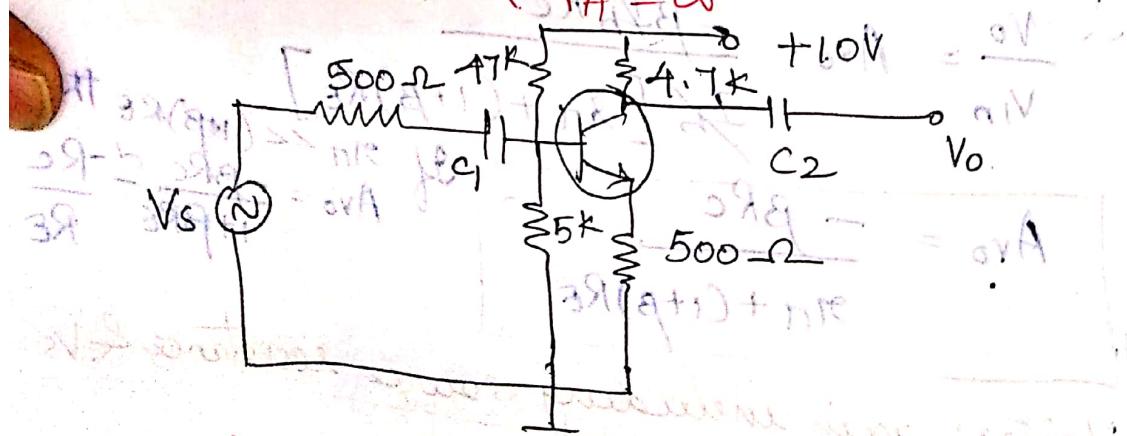
$$V_{BE} = 0.7V \quad \& \quad V_A = \infty$$



Solution :-

Find hybrid π parameters :-

$$\text{g}_{\pi} = \frac{V_T}{I_B} = \frac{V_T \times \beta_{\text{TPA},0}}{I_{CQ}} = \frac{20T}{320.0} = 5.49 \text{ k}\Omega \quad (9)$$

$$g_m = \frac{I_{CQ}}{V_T} \quad &$$

$$\text{g}_{\text{D}} = \frac{V_A}{I_{CQ} \cdot 0(\text{C}_0 + 1) + \text{TPA} \cdot 3} = 2.12$$

find I_{CQ}

To find I_{CQ} , do dc analysis

$$I_{CQ} = \beta \left[\frac{V_{Th} - V_{BE}}{R_{Th} + C(1+\beta)R_E} \right]$$

$$V_{Th} = \frac{V_{cc} \times R_2}{R_1 + R_2} = \frac{10V \times 5k}{5k + 47k} = 0.96V$$

$$R_{Th} = R_1 || R_2 = 47k || 5k = \frac{47k \times 5k}{47k + 5k} = 4.52k$$

$$\therefore \frac{I}{I_B} = \frac{V_{Th} - V_{BE}}{R_{Th} + C(1+\beta)R_E} = \frac{0.96 - 0.7}{4.52 + (1+100)0.5} = 0.07$$

$$I_B = 4.73 \mu A$$

$$I_{CQ} = \beta I_B = 100 \times 4.73 \mu A = 0.473 \text{ mA}$$

To find R_i , R_o & A_V

find g_{π} & g_m

$$1) \text{g}_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{0.026 \times 100}{0.473} = 5.49 \text{ k}\Omega$$

$$2) g_m = \frac{I_{CO}}{V_T} = \frac{0.473}{0.026} = 18.19 \text{ mA/V}$$

$$1) R_i = \underbrace{R_1 || R_2 || \frac{g_n + (1+\beta)R_E}{4.52k}}_{\text{in}} \rightarrow R_{ib} = \frac{g_n + (1+\beta)R_E}{4.52k}$$

$$\begin{aligned} R_{ib} &= g_n + (1+\beta)R_E \\ &= 5.497 + (1+100)0.5 \\ &= 56 \text{ k}\Omega \end{aligned}$$

$$R_i = 4.52k \parallel 56k = 4.18k\Omega$$

$$R_i = 4.18k\Omega$$

$$2) R_o = R_C = 4.7k\Omega$$

$$3) A_{V_o} = \frac{-\beta R_C}{g_n + (1+\beta)R_E} = \frac{5.497 \times 0.5}{5.497 + 9.99} = 0.39$$

$$A_{V_o} = \frac{100 \times 4.7}{5.497 + (1+100) \times 0.5} = 0.39$$


$$A_{V_o} = \frac{100 \times 4.7}{56} = 0.39$$

$$A_{V_o} = 0.39$$


② Determine the small signal voltage gain of a CE circuit with emitter resistor.

The transistor parameters are $\beta = 100$, $b = 0.519$, $V_{BE(ON)} = 0.7V$

$$V_H = 0.7V$$

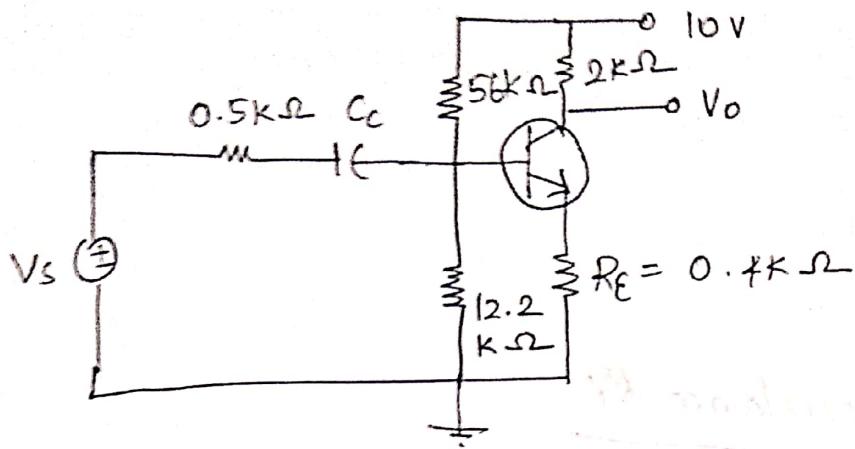

$$R_S = 0.5 \text{ k}\Omega$$

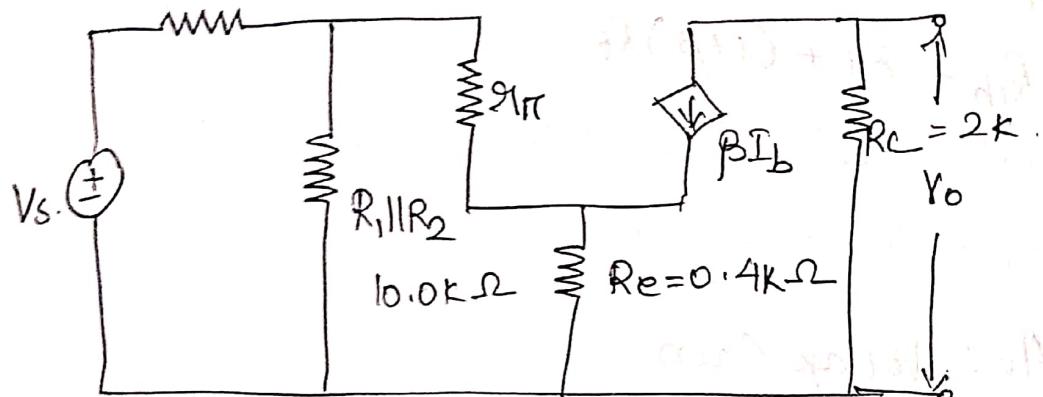

Solution :-

DC analysis to find I_{CQ} :-

$$V_{Th} = \frac{V_{cc} \times R_2}{R_1 + R_2} = \frac{12 \times 12.2}{56 + 12.2}$$

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{56 \times 12.2}{56 + 12.2}$$

$$I_{CQ} = \beta [V_{Th} - V_{BE}] = 2.16 \text{ mA}$$

$$\beta R_{Th} + (1 + \beta) R_E$$

Determine small signal hybrid π parameters :-

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{2.16} = 1.20 \text{ k}\Omega$$

$$g_m = \frac{I_{CO}}{V_T} = \frac{2.16}{0.026} = 83.1 \text{ mA/V.}$$

$$y_0 = \frac{V_A}{I_{CO}} = \infty$$

i) Input resistance R_i'

$$R_i' = R_1 \parallel R_2 \parallel R_{ib}$$

$$R_{ib} = r_{in} + (1+\beta)R_E$$

$$R_{ib} = 1.20 + (101)(0.4) = 41.6 \text{ k}\Omega$$

$$R_i' = 10 \parallel 41.6 = 8.06 \text{ k}\Omega$$

ii) A_v : Voltage Gain

$$A_v = \frac{-R_C(\beta)}{r_{in} + (1+\beta)R_E} \left[\frac{R_i'}{R_C + R_i'} \right]$$


$$= \frac{-2(100)}{1.20 + (101)(0.4)} \left[\frac{8.06}{8.06 + 0.5} \right] = -4.53$$

Using approximate analysis

$$A_v = \frac{-R_C}{R_E} = \frac{-2}{0.4} = -5.0$$


Conclusion:- By including R_E the gain is nearly independant of β .

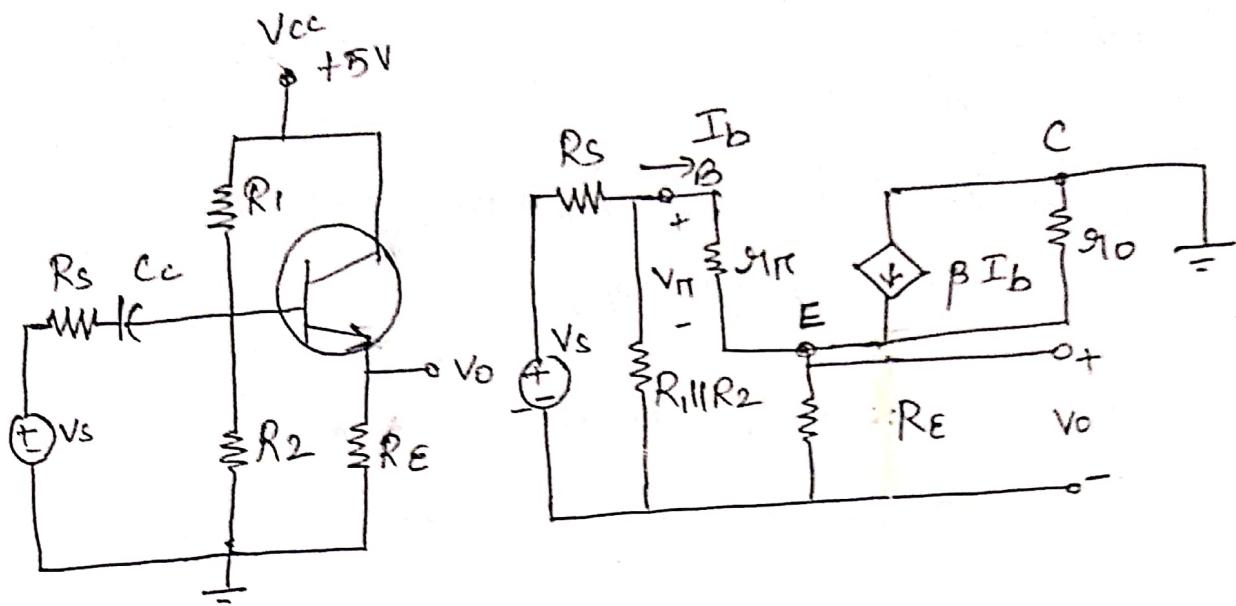Common Collector Amplifier / Emitter follower



- * The o/p is taken off the emitter with respect to ground & collector is connected to \$V_{CC}\$.
- * Since \$V_{CC}\$ is at signal ground in ^{ac} equivalent circuit, we have the name common collector.
- * It is known as emitter follower because the emitter voltage follows the voltage at the base terminal.
- * low o/p resistance & high i/p resistance.
- * Used as buffer b/w source & load.

Equivalent Circuit,

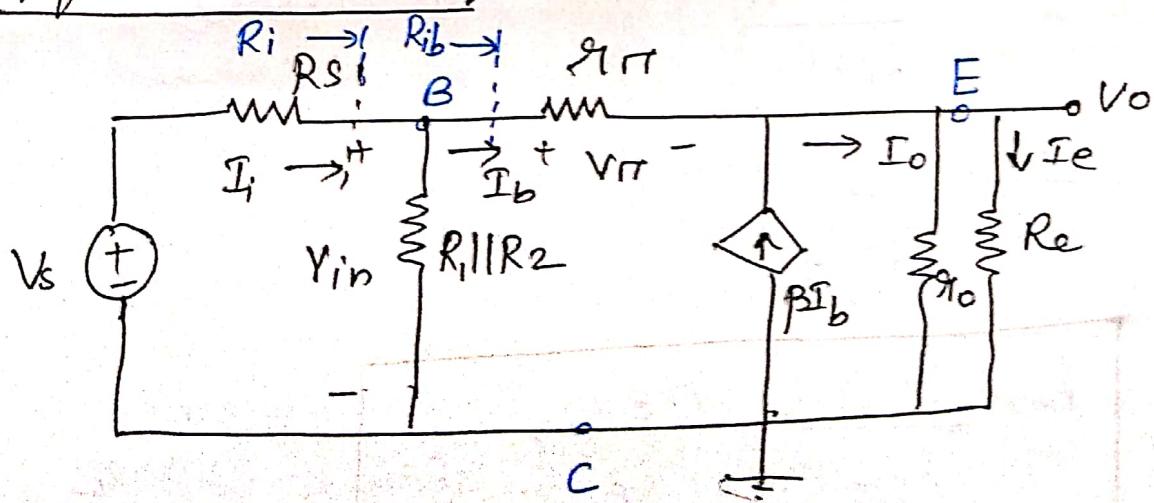

① Voltage Gain Av (open loop)

$$A_V = \frac{V_o}{V_{in}}$$

Vin.

$$V_o = I_o (\text{r}_o || R_E) = (I_b + \beta I_b) (\text{r}_o || R_E)$$

$$= I_b (1 + \beta) (\text{r}_o || R_E)$$


$$V_{in} = I_b \text{r}_T + I_o (\text{r}_o || R_E)$$

$$V_{in} = I_b \text{r}_T + I_b (1 + \beta) (\text{r}_o || R_E)$$

$$A_V = \frac{V_o}{V_{in}} = \frac{I_b (1 + \beta) (\text{r}_o || R_E)}{I_b [\text{r}_T + (1 + \beta) (\text{r}_o || R_E)]}$$

$$\boxed{A_V = \frac{V_o}{V_{in}} = \frac{(1 + \beta) (\text{r}_o || R_E)}{\text{r}_T + (1 + \beta) (\text{r}_o || R_E)}}$$

Closed Loop gain Avs

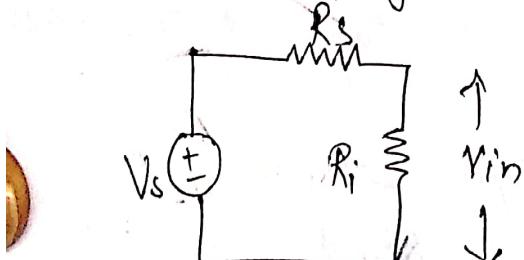

$$A_{vs} = \frac{V_o}{V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s}$$

$$V_{in} = \frac{V_s \times R_i}{R_i + R_s}$$

$$\therefore A_{vs} = \frac{V_o}{V_{in}} \left(\frac{R_i}{R_i + R_s} \right)$$

$$\therefore \frac{V_{in}}{V_s} = \frac{R_i}{R_i + R_s}$$

$$\boxed{A_{vs} = \frac{(1 + \beta) (\text{r}_o || R_E)}{\text{r}_T + (1 + \beta) (\text{r}_o || R_E)} \left(\frac{R_i}{R_i + R_s} \right)}$$

where

$$R_i = R_1 || R_2 || R_{\text{ab}}$$

Voltage gain is -ve, so O/P voltage at emitter is in phase with i/p voltage. O/P follows i/p.

a) Input Impedance

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$R_{ib} = \frac{V_{in}}{I_b}$$

$$V_{in} = I_b r_{in} + I_b (r_{o\parallel RE})$$

$$= I_b r_{in} + (I_b + \beta I_b) r_{o\parallel RE}$$

$$V_{in} = I_b [r_{in} + (1 + \beta) r_{o\parallel RE}]$$

$$\frac{V_{in}}{I_b} = r_{in} + (1 + \beta) (r_{o\parallel RE}) = R_{ib}$$


$$\therefore R_i = R_1 \parallel R_2 \parallel r_{in} + (1 + \beta) (r_{o\parallel RE})$$

This is called reflection rule multiplied.

Impedance in the emitter is $(1 + \beta)$

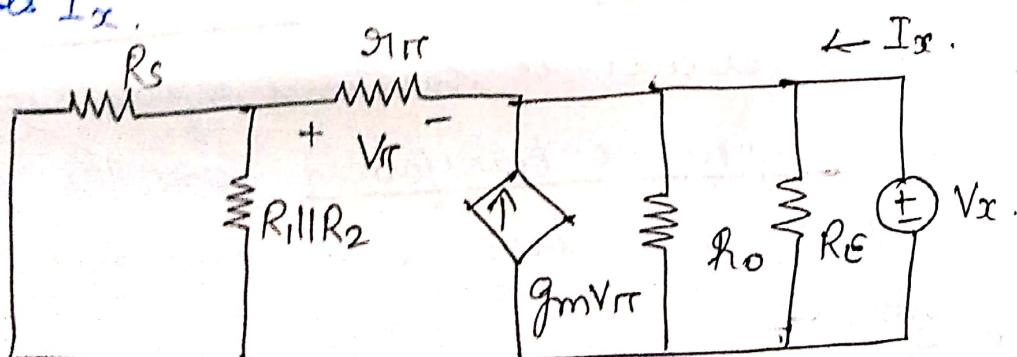b) Output Impedance R_o

The independant voltage source is set to zero ($v_s = 0$). A test voltage V_x is applied to the O/P terminals & the resulting test current is I_x .



$$\beta I_b = g_m V_{RE}$$

$$\beta I_b = \frac{1}{2} \left(\frac{V_{in}}{V_{RE}} \right)$$

$$g_m \times V_{RE}$$


$$R_o = \frac{V_x}{I_x}$$

Applying KCL at O/P:

$$I_{RE} + g_m V_{IF} = \frac{V_x}{R_E} + \frac{V_x}{s_0} + \frac{V_x}{s_0 + (R_s || R_1 || R_2)} \rightarrow (1)$$

$$V_{IF} = - \frac{V_x \times s_0}{s_0 + (R_s || R_1 || R_2)}$$

Substitute in (1)

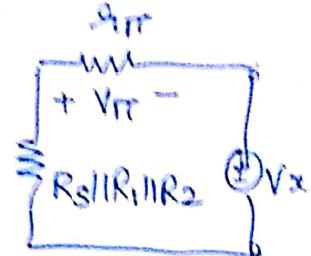

$$I_x = \frac{V_x g_m s_0}{s_0 + (R_s || R_1 || R_2)} + \frac{V_x}{R_E} + \frac{V_x}{s_0} + \frac{V_x}{s_0 + (R_s || R_1 || R_2)}$$

$$I_x = V_x \left[\frac{1}{R_E} + \frac{1}{s_0} + \frac{(1 + g_m s_0)}{s_0 + (R_s || R_1 || R_2)} \right]$$

$$I_x = V_x \left[\frac{1}{R_E} + \frac{1}{s_0} + \frac{1 + \beta}{s_0 + (R_s || R_1 || R_2)} \right]$$

$$\therefore R_o = \frac{V_x}{I_x} = R_E || h_o || \frac{s_0 + (R_s || R_1 || R_2)}{1 + \beta}$$


- * Emitter follower is sometimes referred to as an impedance transformer, since the i/p impedance is large & o/p impedance is small.
- * This makes it an ideal voltage source, so the o/p is not loaded when used to drive another load.
- * This is used as o/p stage in multistage amplifiers.

(1) Small signal Current gain A_i

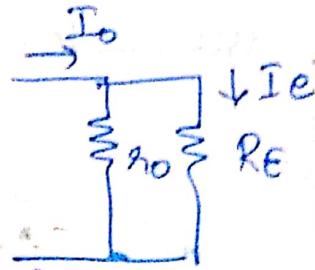(2)

$$A_i = \frac{I_e}{I_i}$$


$$I_e = \frac{I_o \cdot r_o}{r_o + R_E}$$



$$I_o = I_b + \beta I_b = (1 + \beta) I_b$$

$$I_e = (1 + \beta) I_b \left(\frac{r_o}{r_o + R_E} \right)$$

$$I_b = I_i \times \frac{R_1 || R_2}{R_{ib} + (R_1 || R_2)}$$

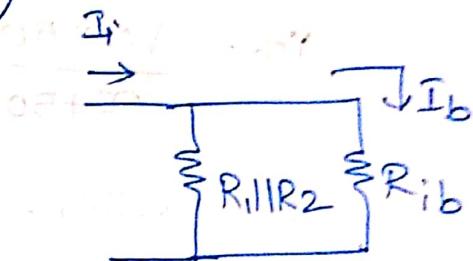

$$I_e = (1 + \beta) I_i \frac{R_1 || R_2}{R_{ib} + (R_1 || R_2)} \left(\frac{r_o}{r_o + R_E} \right)$$

$$\frac{I_e}{I_i} = (1 + \beta) \frac{(R_1 || R_2)}{R_{ib} + (R_1 || R_2)} \left(\frac{r_o}{r_o + R_E} \right)$$

$$A_i = \frac{I_e}{I_i} = (1 + \beta) \frac{R_1 || R_2}{R_{ib} + R_1 || R_2} \left(\frac{r_o}{r_o + R_E} \right)$$


$$R_1 || R_2 \gg R_{ib} \quad r_o \gg R_E$$

$$\therefore A_i \approx (1 + \beta)$$

The small signal current gain is greater than 1. \therefore the circuit produces a small signal power gain.

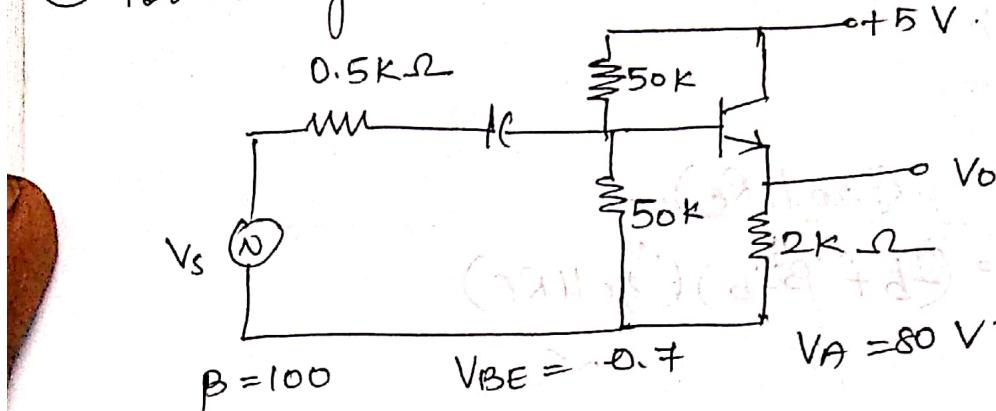Example:-

- ① For the given circuit calculate the A_v , A_i , R_o &



- ② Find I_{CQ}

$$V_{Th} = \frac{V_{CC} \times 50}{50 + 50} = \frac{5 \times 50}{50 + 50} = \frac{250}{100} = 2.5 \text{ V}$$

$$R_{Th} = R_1 || R_2 = 25 \text{ k}\Omega$$

$$I_{CQ} = \frac{V_{Th} - V_{BE}}{R_{Th} + (1+\beta) R_E} = \frac{2.5 - 0.7}{25 + (100) 2} = \frac{1.8}{225} = 1.8 \text{ mA}$$

$$\boxed{I_{CQ} = 0.793 \text{ mA}}$$

To calculate r_{in} , g_m & λ_0 :

$$r_{in} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.793} = 3.28 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.793}{0.026} = 30.5 \text{ mA/V}$$

$$\lambda_0 = \frac{V_A}{I_{CQ}} = \frac{80}{0.793} \approx 100 \text{ k}\Omega$$

To find R_i , R_o , A_v & A_o .

$$\underline{R_i} \quad R_i = R_1 || R_2 || R_{ib}$$

$$R_{oL} = r_{in} + (1+\beta) (\lambda_0 || R_E)$$

$$R_{ib} = 3.28 + (101)(100||2) = 201 \text{ k}\Omega \quad (1)$$

$$R_i = R_{ib} || R_1 || R_2 = 201 || 50 || 50 = 22.2 \text{ k}\Omega$$

(2) A_v

$$\begin{aligned} A_v &= \frac{(1+\beta)(R_o || R_E)}{R_{in} + (1+\beta)(R_o || R_E) + \left(\frac{R_i}{R_i + R_S} \right)} \\ &= \frac{(101)(100||2)}{3.28 + (1+100)(100||2)} = \frac{22.2}{22.2 + 0.5} \end{aligned}$$

$$A_v = 0.962$$

$$(3) \underline{R_o} = \left[\frac{R_{in} + R_i || R_2 || R_S}{1 + \beta} \right] || R_E || R_o$$

$$= \left[\frac{3.28 + 50 || 50 || 0.5}{101} \right] || 2 || 100$$

$$= 0.0373 || 2 || 100 = 0.0366 \text{ k}\Omega$$

$$R_o = 36.6 \Omega$$

(4) A_i




$$A_i = (1+\beta) \left(\frac{R_i || R_2}{R_i || R_2 + R_{in}} \right) \left(\frac{R_{in}}{R_o + R_E} \right)$$

$$= (101) \left(\frac{25}{25 + 22.2} \right) \left(\frac{100}{102} \right) = 52.4$$

$$A_i = 52.4$$

Common-Base Amplifier

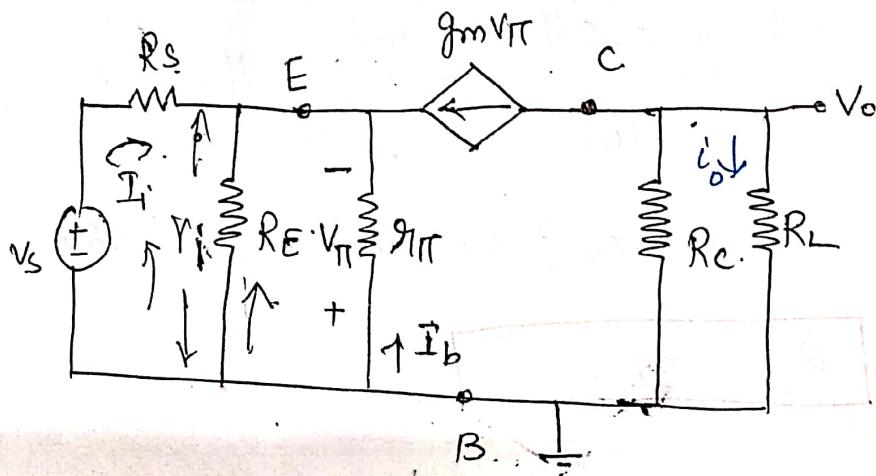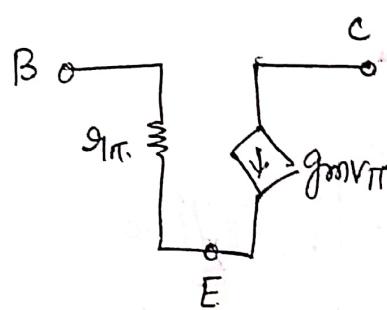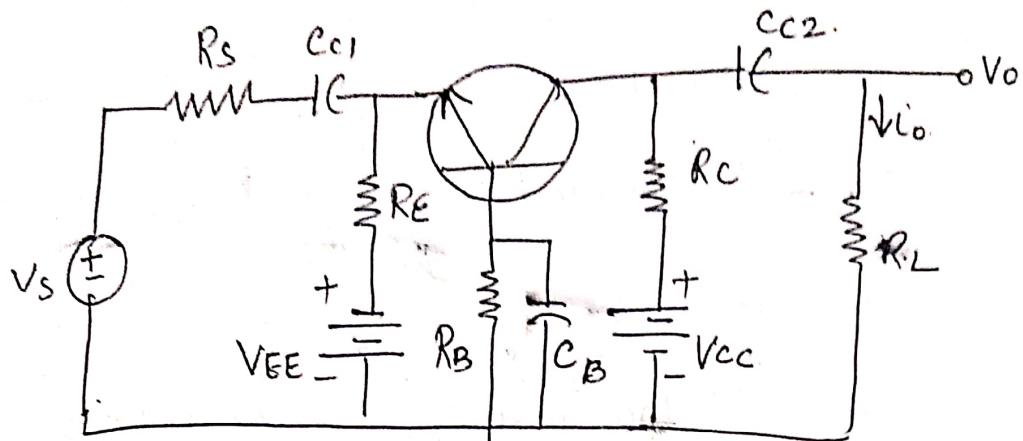- * Base is at signal ground & i/p is applied to emitter.
- * g_o is assumed to be infinite.



① Small signal voltage gain A_v :- $A_v = \frac{V_o}{V_{S0}}$

$$V_o = -g_m V_\pi (R_C || R_L) \rightarrow ①$$

KCL at the emitter node :-

$$g_m V_\pi + \frac{V_\pi}{g_\pi} + \frac{V_\pi}{R_E} + \frac{V_S + V_\pi}{R_S} = 0$$

$$V_{\pi} \left[g_m + \frac{1}{s_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S} \right] = - \frac{V_s}{R_S} \quad (1)$$

$$V_{\pi} \left[\frac{g_m s_{\pi} + 1}{s_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S} \right] = - \frac{V_s}{R_S}$$

$$V_{\pi} \left[\frac{1+\beta}{s_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S} \right] = - \frac{V_s}{R_S}$$

$$V_{\pi} = - \frac{V_s}{R_S} \left[R_S \parallel R_E \parallel \frac{s_{\pi}}{1+\beta} \right] \rightarrow (2)$$

Substituting (2) in (1).

$$V_o = - g_m \left(- \frac{V_s}{R_S} \left(R_S \parallel R_E \parallel \frac{s_{\pi}}{1+\beta} \right) \right)$$

$$A_v = \frac{V_o}{V_s} = g_m \left(R_S \parallel R_E \parallel \frac{s_{\pi}}{1+\beta} \right) (R_C \parallel R_L)$$

If $R_E = 0$

$$A_v \approx g_m (R_C \parallel R_L)$$

(2) Small signal current gain A_i

$$A_i = \frac{I_o}{I_i} \quad I_o = - g_m V_{\pi} \frac{R_C}{R_C + R_L} \rightarrow (3)$$

KCL at the i/p:

$$I_i + \frac{V_{\pi}}{R_E} + \frac{V_{\pi}}{s_{\pi}} + g_m V_{\pi} = 0$$

$$V_{\pi} \left[\frac{1}{R_E} + \frac{1}{s_{\pi}} + g_m \right] = - I_i$$

$$V_{\pi} \left[\frac{1}{R_E} + \frac{(1+\beta)}{2\pi} \right] = -I_i$$

$$V_{\pi} = -I_i \left[R_E \parallel \frac{2\pi}{1+\beta} \right] \rightarrow \textcircled{3}$$

Sub V_{π} from \textcircled{4} in \textcircled{3}

$$I_o = +g_m I_i \left[R_E \parallel \frac{2\pi}{1+\beta} \right] \left(\frac{R_C}{R_C + R_L} \right)$$

$$\boxed{\frac{I_o}{I_i} = A_i = g_m \left(R_E \parallel \frac{2\pi}{1+\beta} \right) \left(\frac{R_C}{R_C + R_L} \right)}$$

R_E approaches ∞ if $R_L = 0$.

$$\therefore A_{i0} = \frac{g_m 2\pi}{1+\beta} = \frac{\beta}{1+\beta} = \alpha.$$


$\alpha \rightarrow$ common base current gain of amplifier.

$A_v > 1$ & $A_i < 1$.

we have small signal power gain.

R_i : Input Impedance

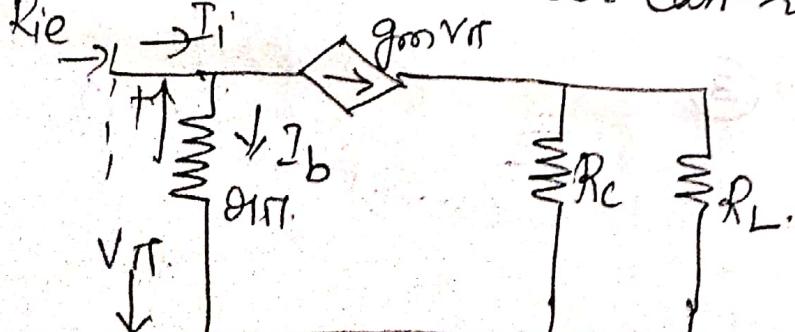for convenience we can reverse the polarities



$$R_{ie} = \frac{V_{rf}}{I_i}$$

(16)

$$I_i = I_b + g_m V_{RE}$$

$$I_i = \frac{V_{RE}}{g_m} + g_m V_{RE}$$

$$I_i = V_{RE} \left[\frac{1}{g_m} + g_m \right] = V_{RE} \left[\frac{1+\beta}{g_m} \right].$$

$$\boxed{\frac{V_{RE}}{I_i} = \frac{g_m}{1+\beta}} \approx g_m.$$


R_o : O/P Impedance

$$R_o \approx R_c.$$

Q) for a Common base circuit shown

calculate R_i , A_v , A_i & R_o .
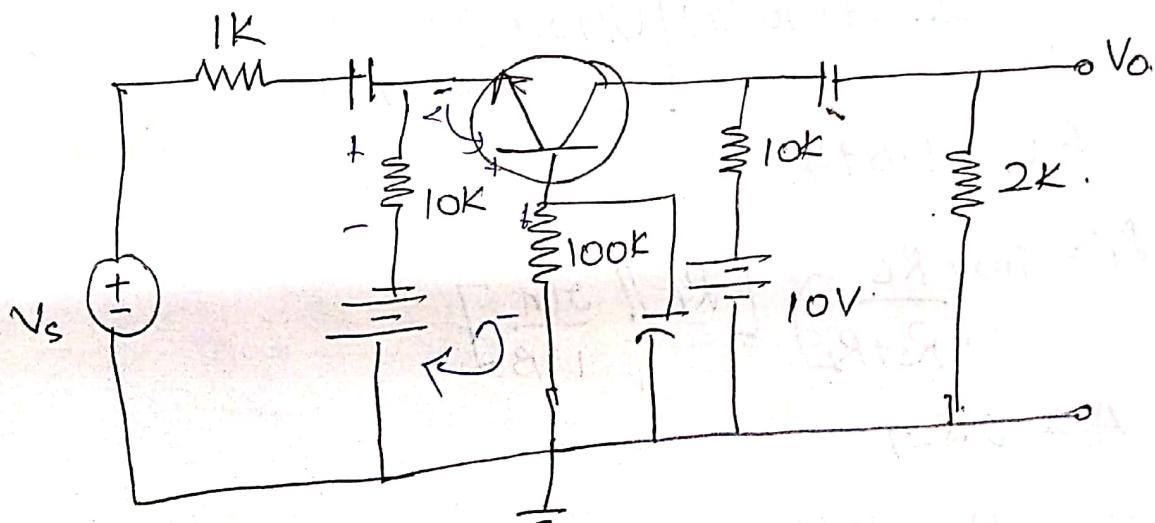
$$\beta = 100, V_{BE} = 0.7V, V_A = \infty$$



① find I_{CQ} :-

$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (1+\beta)R_E} = \frac{10 - 0.7}{100 + (1+100)10} = 8.378 \mu A.$$

$$\boxed{I_C = \beta I_B = 0.8378 mA.}$$

2) Determine α_{IT} , g_m & V_A :

$$\alpha_{IT} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{0.8378} = 3.1 K\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.8378}{0.026} = 32.223 \text{ mA/V}$$

$$\alpha_{IO} = \frac{V_A}{I_{CQ}} = \frac{\infty}{I_{CQ}} = \infty$$

③ Find R_i , A_V , A_i & R_o

$$1) R_i = \frac{\alpha_{IT}}{1+\beta} = \frac{3.1}{1+100} = 30.69 \Omega$$

$$2) A_V = \frac{g_m (R_C || R_L)}{R_S} \left[R_E || R_S \parallel \frac{\alpha_{IT}}{1+\beta} \right] \\ = 32.223 (10 || 2) \left[1 || 10 || \frac{3.1}{100+1} \right] \\ A_V = 1.594$$

$$3) A_i = g_m \left(\frac{R_C}{R_C + R_S} \right) \left[R_E \parallel \frac{\alpha_{IT}}{1+\beta} \right] \\ A_i = 0.82$$

$$4) R_o = R_C = 10K$$

Multistage Amplifiers

Need for Cascading:-


- When amplification of single stage amplifier is not sufficient, or

2). When
Correct
two or
Such
stages

Limita

1) The α_{IO}
always
amplify

2) Non linear
amplify
Two s

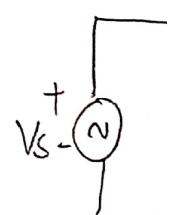

O/P of
stage e

A_V


$|A_V|$

2). When the i/p or o/p impedance is not of correct magnitude for a particular application two or more stages are connected in cascade. Such an amplifier with two or more stages is known as multistage amplifier.

Limitations of multistage amplifiers

- 1) The bandwidth of multistage amplifier is always less than that of a single stage amplifier.
- 2) Non linear distortion is more in a multistage amplifier.

Two stage cascaded amplifier

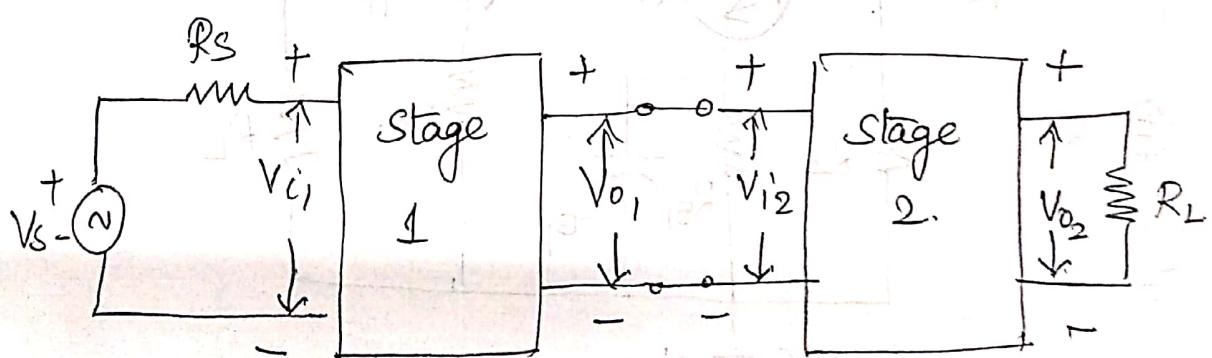

O/P of first stage is connected to the i/p of 2nd stage.

$$A_v = \frac{V_o 2}{V_i 1} = \frac{V_o 2}{V_i 2} \times \frac{V_i 2}{V_i 1} \quad [V_o 1 = V_i 2]$$

$$= \frac{V_o 2}{V_i 2} \times \frac{V_o 1}{V_i 1}$$


$$\boxed{A_v = A_{v2} \cdot A_{v1}}$$

* voltage gain of multistage amplifier is the product of voltage gains of the individual stages.


2 stage CE Amplifier

Figure shows the cascade configuration of 2 CE circuits.

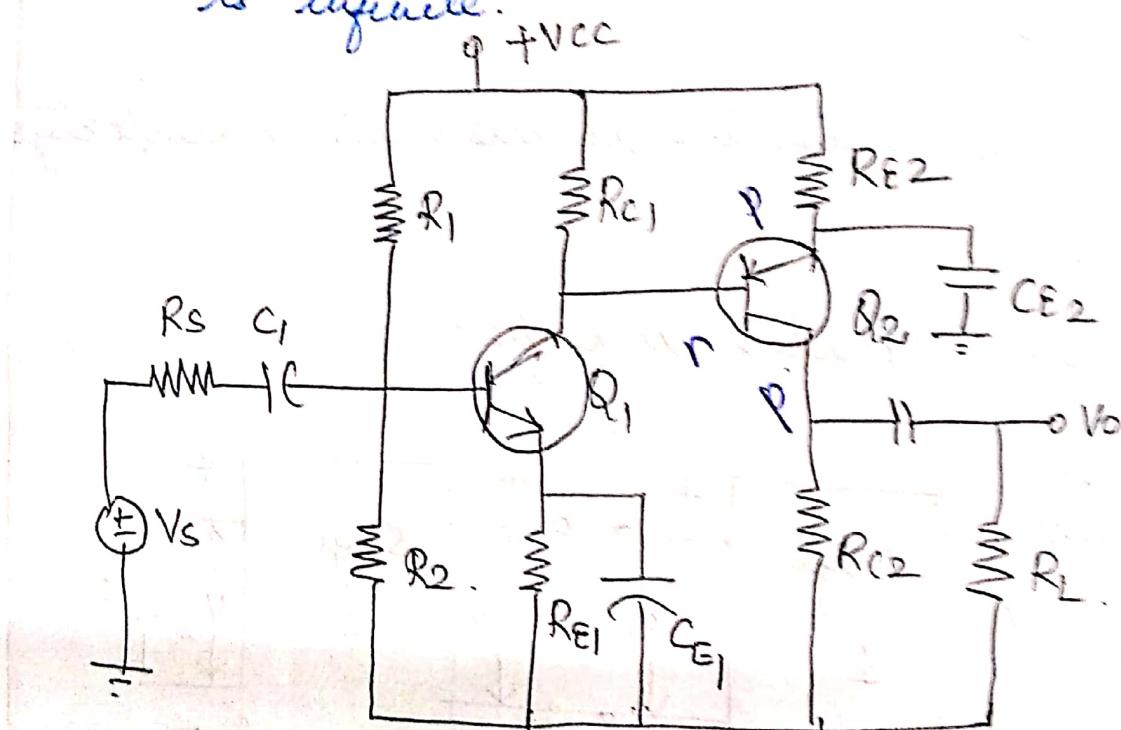for ac analysis all capacitors are shorted & each transistor off resistance is infinite.



Ac Equivalent Circuit

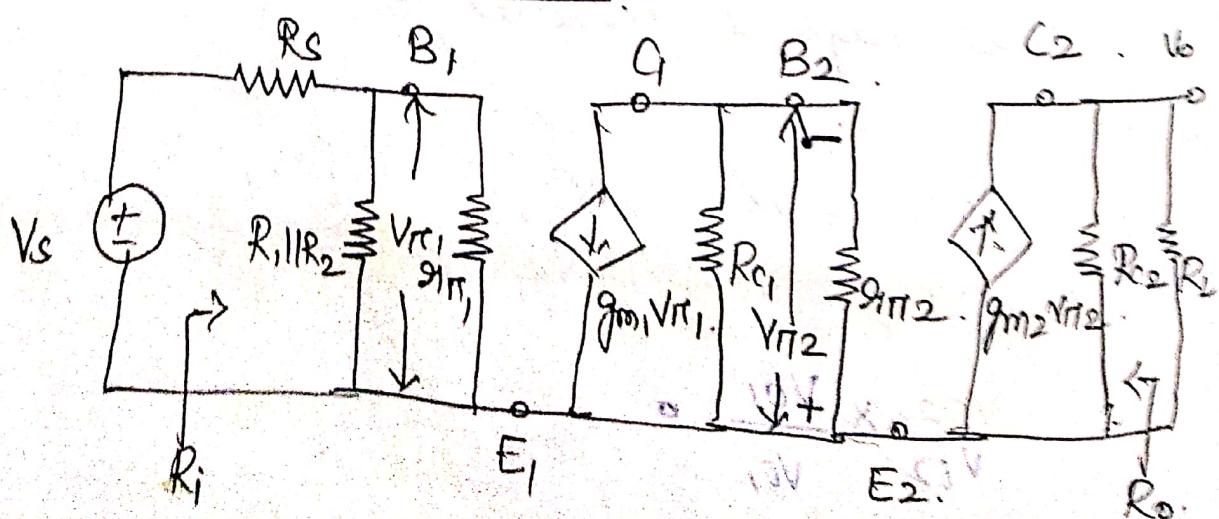

Op impedance of one stage is shunted by
the op impedance of the next stage.

Stage 2:-

1) Input impedance R_{i2}

$$R_{i2} = g_{m2} \times R_L = g_{m2} \times \frac{V_o}{A_{v2}}$$

2) Voltage gain A_{v2}

$$A_{v2} = \frac{V_o}{V_{T2}} = g_{m2} (R_{C2} || R_L)$$

~~$$A_{v2} = \frac{V_o}{V_{T2}} = g_{m2} (R_{C2} || R_L)$$~~

Stage 1

1) Input impedance R_{i1}

$$R_{i1} = R_1 || R_2 || s_{re1}$$

2) Voltage gain A_{v1}

$$A_{v1} = \frac{V_{T2}}{V_{T1}}$$

$$V_{T2} = g_{m1} V_{T1} (R_{C1} || s_{re2})$$

$$A_{v1} = \frac{V_{T2}}{V_{T1}} = g_{m1} (R_{C1} || s_{re2})$$

Total voltage gain (open loop) A_{v0}

$$A_{v0} = \frac{V_o}{V_{T1}} = \frac{V_o}{V_{T2}} \times \frac{V_{T2}}{V_{T1}} = A_{v1} \times A_{v2}$$

$$A_{VS} = g_{m1}(R_o + R_{in2})g_{m2}(R_{o2} + R_L)$$

$$A_{VS} = \frac{V_o}{V_s} = \frac{V_o}{V_{in2}} \times \frac{V_{in2}}{V_{in1}} \times \frac{V_{in1}}{V_{S, \text{input}}}$$

$$A_{VS} = A_{V2} \times A_{V1} \times \underline{R_L}$$

(Output load R_L is not included)


$$A_{VS} = g_{m1} g_{m2} (R_o + R_{in2}) (R_{o2} + R_L) \underline{R_L}$$


O/P resistance R_o

$$R_o \approx R_{o2}$$

Darlington Transistor

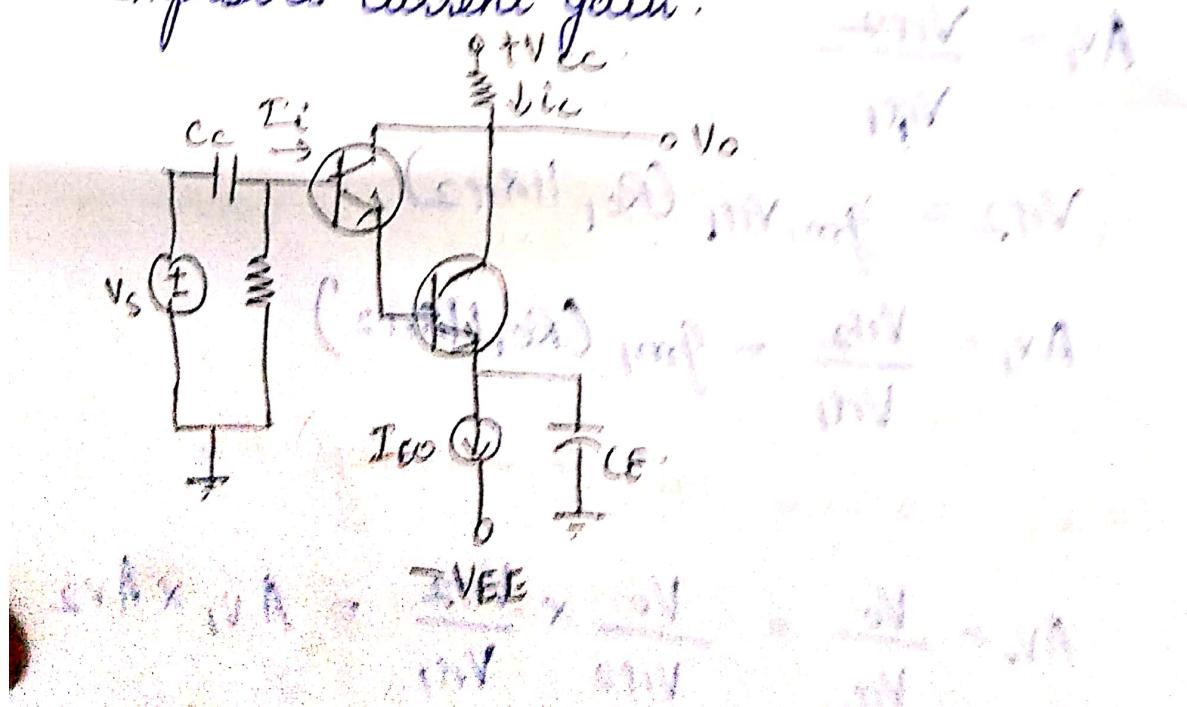- * High input resistance
- * Improves current gain.



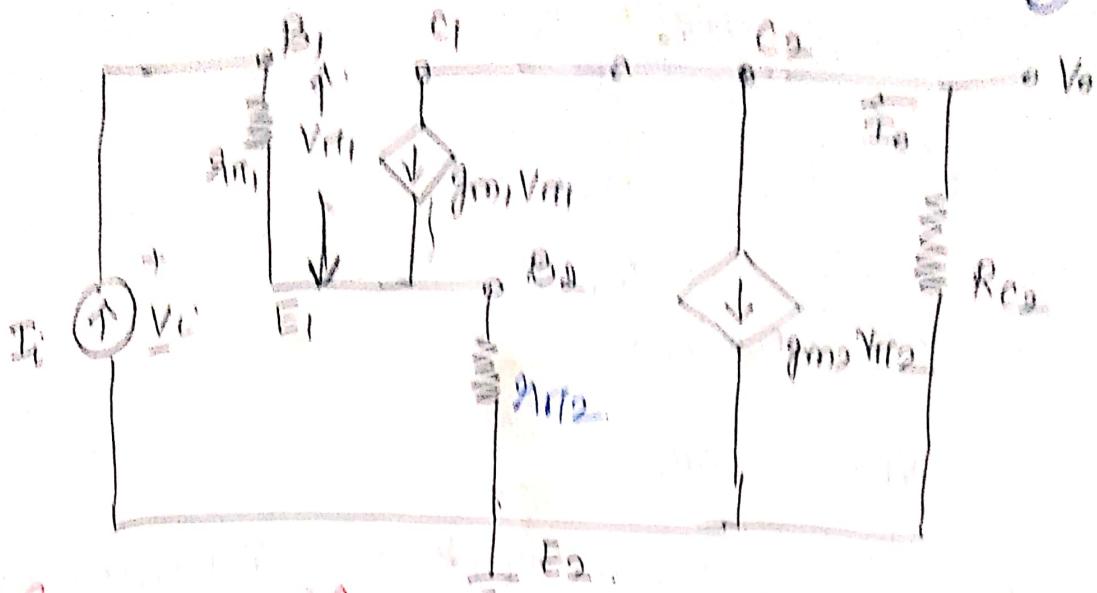

Small signal current gain (line)

$$A_i = \frac{I_o}{I_i}$$

(at 1KHz) if $V = 0V$

$$I_o = g_m 2 V_{BE2} + g_m 1 V_{BE1}$$

$$V_{BE1} = I_i \delta r_{e1}$$

$$\begin{aligned} V_{BE2} &= (I_i + g_m 1 V_{BE1}) \delta r_{e2} \\ &= (I_i + I_i g_m 1 \delta r_{e1}) \delta r_{e2} \\ &= (I_i + I_i \beta_1) \delta r_{e2}. \end{aligned}$$

$$V_{BE2} = I_i \delta r_{e2} + I_i \beta_1 \delta r_{e2}.$$

Sub V_{BE1} & V_{BE2} in I_o

$$\begin{aligned} I_o &= g_m 2 (I_i \delta r_{e2} + I_i \beta_1 \delta r_{e2}) + g_m 1 I_i \delta r_{e1} \\ &= I_i g_m 2 \delta r_{e2} + I_i \beta_1 g_m 2 \delta r_{e2} + I_i \delta r_{e2} g_m 1 \\ &= I_i [\beta_2 + \beta_1 \beta_2 + \beta_1] \end{aligned}$$

$$A_i = \frac{I_o}{I_i} = \beta_1 + \beta_2 + \beta_1 \beta_2. \quad \text{The overall current gain of a Darlington pair is the product of individual current gains.}$$

$$A_i \approx \beta_1 \beta_2.$$

Output Resistance R_i

$$R_i = \frac{V_i}{I_i}$$

$$V_i = V_{\pi 1} + V_{\pi 2}$$

$$V_{\pi 1} = I_i r_{\pi 1}$$

$$V_{\pi 2} = (I_i + g_m V_{\pi 1}) r_{\pi 2} = (I_i + g_m I_i r_{\pi 1}) r_{\pi 2}$$

$$V_{\pi 2} = I_i (1 + \beta_1) r_{\pi 2}$$

$$V_{\pi 2} = I_i (1 + \beta_1) r_{\pi 2}$$

Sub $V_{\pi 1}$ & $V_{\pi 2}$ in V_i

$$\therefore V_i = I_i r_{\pi 1} + I_i (1 + \beta_1) r_{\pi 2}$$

$$V_i = I_i [r_{\pi 1} + (1 + \beta_1) r_{\pi 2}]$$

$$\therefore R_i = \frac{V_i}{I_i} = [r_{\pi 1} + (1 + \beta_1) r_{\pi 2}]$$

$$r_{\pi 1} = \frac{\beta_1}{g_m} = \frac{\beta_1 V_T}{I_{CQ1}} \quad \text{Let } I_{CQ1} \approx \frac{I_{CQ2}}{\beta_2}$$

$$\therefore r_{\pi 1} = \frac{\beta_1 V_T}{I_{CQ2}} \beta_2$$

$$r_{\pi 1} = \beta_1 r_{\pi 2}$$

$$\therefore R_i = \beta_1 r_{\pi 2} + (1 + \beta_1) r_{\pi 2}$$

$$R_i \approx 2\beta_1 r_{\pi 2}$$

The input resistance of Darlington pair is large because of β multiplication.

Cascade Amplifier

* It has a common emitter stage in series with a common base amplifier.

* $Q_1 \rightarrow CE$



$Q_2 \rightarrow CB$.


Features :-

- 1) It provides high input impedance.
- 2) High voltage gain
- 3) Improved i/p o/p isolation as there is no direct coupling from o/p to i/p. This eliminates Miller effect & thus provides much BW.
- 4) High O/P resistance.
- 5) High slew rate & stability

Disadvantages:

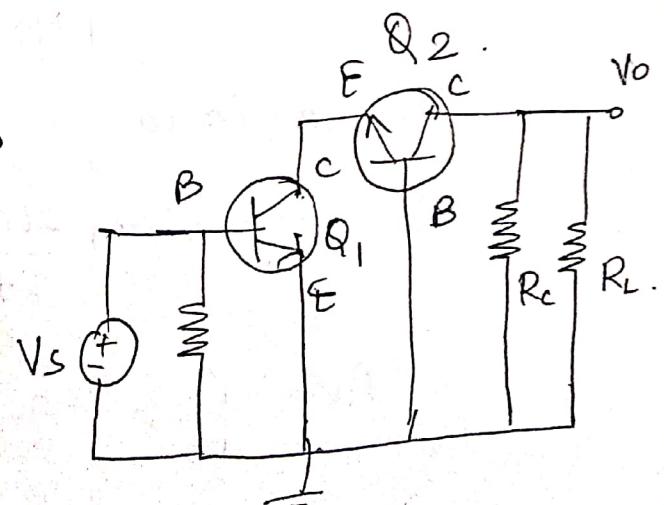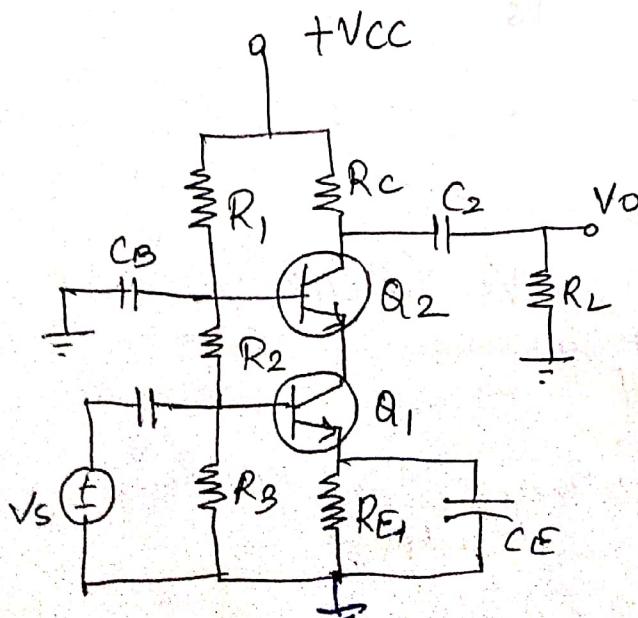- 1) high supply voltage is required &
- 2) need for 2 transistors.



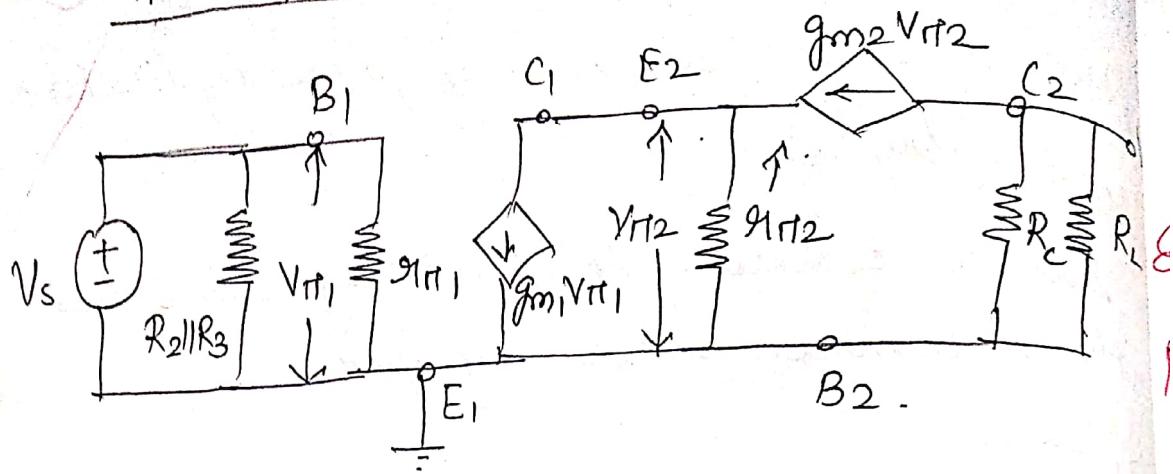

To find voltage gain Av.

$$Av = \frac{V_o}{V_s} = -g_{m2} V_{pi2} (R_c || R_L)$$

$$V_s = V_{pi1}$$

Apply KCL to E₂.

$$g_{m2} V_{pi2} + \frac{V_{pi2}}{g_{m2}} = g_{m1} V_{pi1} = g_{m1} V_s$$

$$\therefore V_{pi2} \cdot \left[\frac{1 + \beta_2}{g_{m2}} \right] = g_{m1} V_s$$

$$V_{pi2} = g_{m1} \frac{g_{m2}}{1 + \beta_2} V_s$$

Sub V_{pi2} in V_o

$$V_o = -g_{m2} g_{m1} \frac{g_{m2}}{1 + \beta_2} V_s \cdot (R_c || R_L)$$

$$\therefore Av = \frac{V_o}{V_s} = -g_{m1} g_{m2} \frac{g_{m2}}{1 + \beta_2} (R_c || R_L)$$

$$Av = \frac{V_o}{V_s} = -g_{m1} \frac{\beta_2}{1 + \beta_2} (R_c || R_L)$$

$$A_V \approx -g_m (R_C || R_L) \quad \left\{ \because \frac{\beta_2}{1+\beta_2} \approx 1 \right\}$$

Eg. ① for a cascode amplifier, $I_{CQ} = 0.5 \text{ mA}$, $\beta = 100$, $V_{BE} = 0.7$, $V_A = \infty$, $R_C = 7.5 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$.
Find A_V . (for both transistors)

Determine r_{in} & g_m :

$$r_{in} = r_{in2} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.5} = 5.2 \text{ k}\Omega$$

$$g_{m1} = g_{m2} = \frac{I_{CQ}}{V_T} = \frac{0.5}{0.026} = 19.23 \text{ mA/V}$$

$$r_o = r_{o1} = r_{o2} = \infty$$

Calculate A_V :


$$\begin{aligned} A_V &= \frac{V_o}{V_s} = -g_{m1} g_{m2} \left(\frac{r_{in2}}{1+\beta_2} \right) (R_C || R_L) \\ &= -(19.23)(19.23) \left(\frac{5.2}{1+100} \right) (7.5 || 2) \\ \therefore A_V &= -30.06 \end{aligned}$$

Frequency Response Analysis of Basic BJT CE Amplifier

Amplifier Frequency response

- * All amplifier gain factors are functions of signal frequency.
- * we have

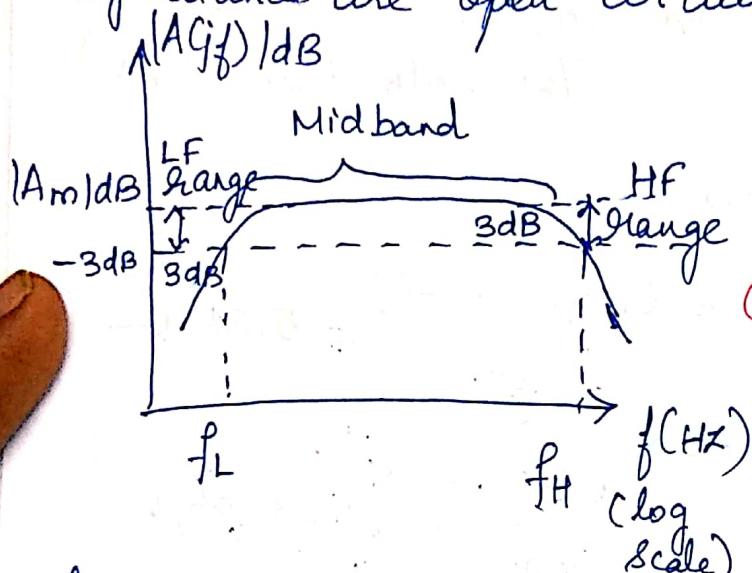high enough that coupling & bypass capacitors can be treated as short circuit and at the same time signal frequency is low enough such that transistor capacitors & stray capacitances are open circuit.



Three ranges of
frequency

① Low frequency range :-

$f < f_L$, the gain decreases as

because of coupling & bypass capacitors effects.

② High frequency range ($f > f_H$): stray capacitance & transistor capacitance effects cause gain to decrease as the frequency increases.

③ Mid band range: Coupling & bypass capacitors act as short circuit & stray \rightarrow transistor 'c' act as open circuit, Gain is constant.

* Gain at f_H & f_L is 3dB less than the max. midband gain.

$$BW = f_A - f_L$$

Equivalent Circuits: Each capacitor is important to only one end of frequency spectrum. We can develop equivalent circuits that apply to 1) HF 2) LF

1) LF range 2) HF range & 3) Midband range

bypass & coupling → short
bypass & coupling Stray & transistor → considered.
→ taken into consideration.

Stray & transistor C


→ open circuit

bypass & coupling
→ short
stray & transistor

Frequency response: Transistor amplifier with Capacitor circuit

- * Coupling } At low frequencies
- * Bypass } At high frequencies
- * Load capacitor. \rightarrow At high frequencies.

I/P Coupling capacitor for CE Circuit

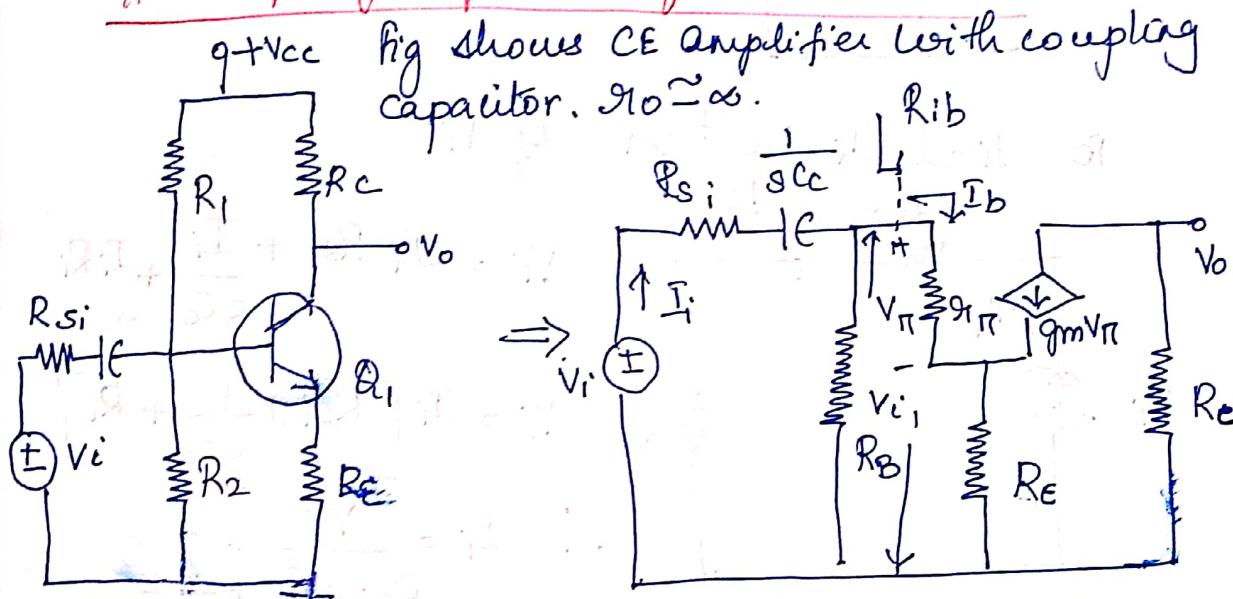

To determine the transfer function $A_v(s) = \frac{V_o(s)}{V_i(s)}$.
To find $A_v(s)$ highpass network

$$A_v(s) = \frac{V_o(s)}{V_i(s)}$$

(ie) At high frequencies, C_c acts as short ckt & i/p to

$V_o(s) = -g_m V_{\pi} R_c$
we know that $V_{\pi} = I_b R_{\pi}$. coupled through
From the i/p circuit Q_1 to o/p. if it is
 $R_i = R_1 || R_2 || R_{ib}$ low $O/P \approx 0$.


$$R_{ib} = \frac{V_{i1}}{I_b} \Rightarrow Y_{i1} = Y_{\pi} + (I_b + g_m V_{\pi}) R_E$$

$$= I_b R_{\pi} + (I_b + g_m I_b R_{\pi}) R_E$$

$$\therefore R_{ib} = \frac{Y_{i1}}{I_b} = R_{\pi} + (1 + \beta) R_E = I_b [R_{\pi} + (1 + \beta) R_E]$$


$$\therefore R_i = R_1 \parallel R_2 \parallel g_m + (1 + \beta)R_E$$

To find I_b in terms of I_i

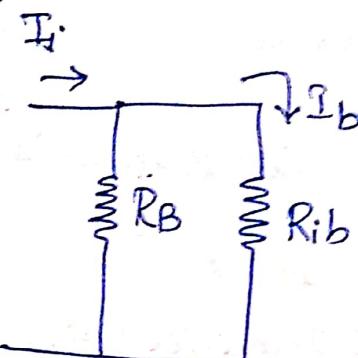

$$I_b = I_i \times \frac{R_B}{R_B + R_{ib}}$$

To find I_i in terms of V_i

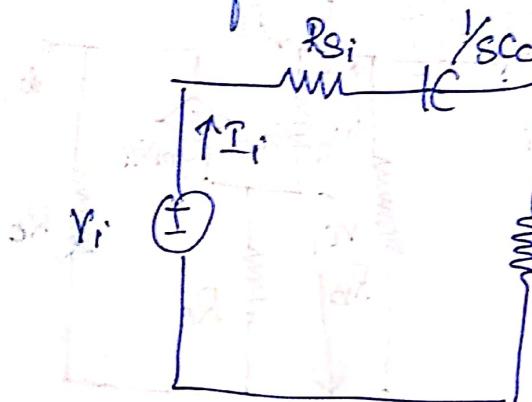

$$V_i = I_i R_{si} + \frac{I_i}{S_C} + I_C$$

$$V_i = I_i \left[R_{si} + \frac{1}{S_C} + R_i \right]$$

$$\therefore I_i = \frac{V_i}{R_{si} + R_i + \frac{1}{S_C}}$$

Sub. V_i in V_o :

$$\therefore V_o = -g_m R_C T_b g_m$$

Sub I_b in V_o

$$\therefore V_o = -g_m R_C I_i \frac{R_B}{R_B + R_{ib}} \cdot g_m$$

Sub. I_i in V_o .

$$\therefore V_o = -g_m R_C \frac{V_i}{R_{si} + R_i + \frac{1}{S_C}} \cdot \frac{R_B}{R_B + R_{ib}} \cdot g_m$$

$$= -g_m g_m R_C \frac{V_i (S_C)}{1 + S_C (R_{si} + R_i)} \cdot \frac{R_B}{R_B + R_{ib}}$$

$$A_V = \frac{V_o}{V_i} = -g_m R_i \frac{S C_c}{1 + S C_c (R_s + R_i)} \frac{R_B}{R_B + R_i}$$

Let $\tau_s = C_c (R_i + R_{s,i})$.

$$\therefore A_V = \frac{V_o}{V_i} = -g_m R_i \frac{R_C}{1 + \tau_s} \frac{R_B}{R_B + R_i}$$

$\times 2$ divide by τ_s

$$\therefore A_V = \frac{V_o}{V_i} = -g_m r_e R_C \times \frac{s C_c \tau_s}{1 + \tau_s} \frac{R_B}{R_B + R_i}$$


$$\therefore A_V(s) = -g_m r_e R_C \left(\frac{\tau_s}{1 + \tau_s} \right) \left(\frac{R_B}{R_B + R_i} \right)$$

$\tau_s \rightarrow$ determines the corner frequency
lower cut off frequency

$$f_L = \frac{1}{2\pi \tau_s} = \frac{1}{2\pi (R_i + R_{s,i}) C_c}$$

$$\left| A_{V\max} \right|_{dB} = 20 \log \left(g_m r_e R_C \right) \left(\frac{R_B}{R_B + R_i} \right)$$

Coupling & Load Capacitors Effect :-

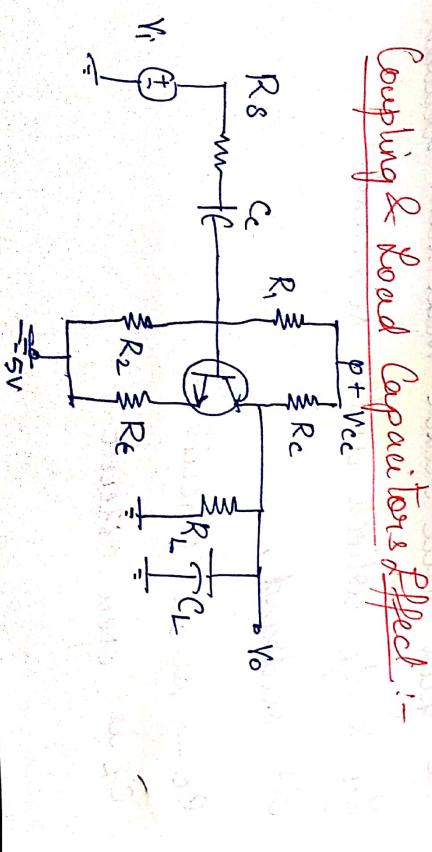

The values of coupling & load capacitor differ by orders of magnitude, the corner frequencies are far apart and can be treated separately.

Lower corner frequency

$$f_L = \frac{1}{2\pi\tau_s} \quad \leftarrow \text{lower corner frequency}$$

$\tau_s \leftarrow$ time constant associated with coupling capacitor

$$\tau_s = (R_s + R_1 || R_2 || R_i) C_c$$

Upper corner frequency

$$f_H = \frac{1}{2\pi\tau_p}$$

$f_H \rightarrow$ upper corner frequency

$\tau_p \rightarrow$ time constant associated with load capacitor

$$\tau_p = (R_o || R_L) C_L$$


Calculation of mid band gain

The gain will reach maximum between f_H & f_L , which is the mid band.

At midband,

$R_C \rightarrow$ short circuit &

C_L is open circuit.

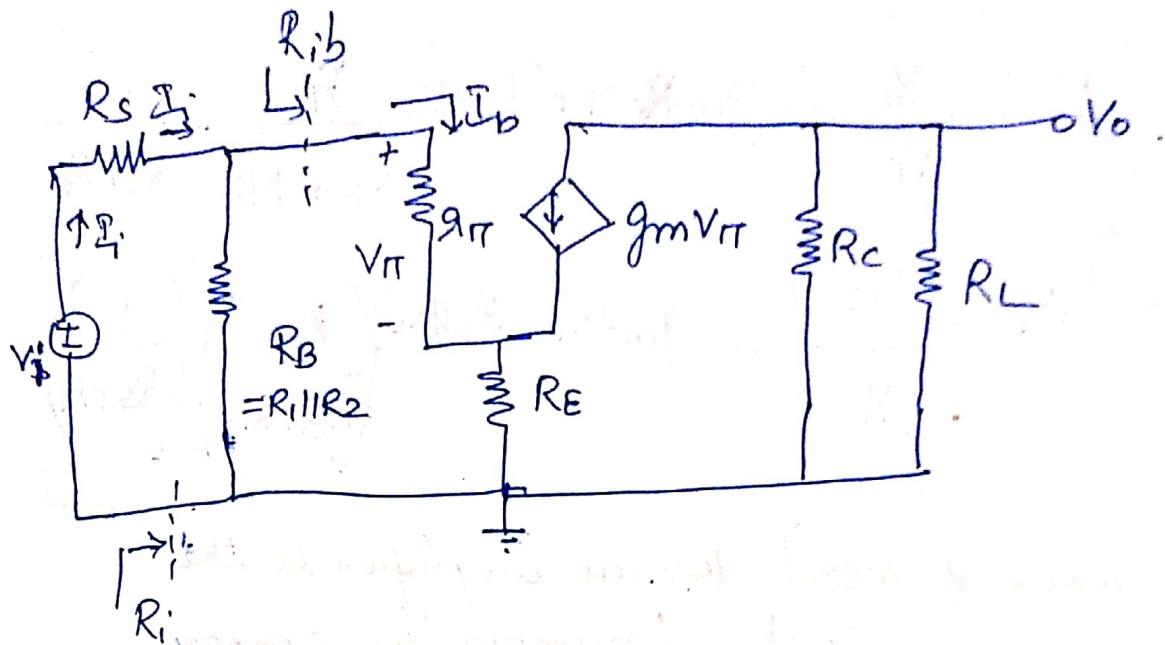

Midband gain $A_v = \frac{V_o}{V_i}$

$$V_o = -g_m V_{\pi} (R_C || R_L) = -g_m I_b g_{\pi} (R_C || R_L)$$

$$V_{\pi} = I_b g_{\pi}$$


$$I_b = I_i \times \frac{R_B}{R_B + R_{ib}}$$

where $R_{ib} = g_{\pi} + (1+\beta) R_E$

Sub I_b in V_o .

$$V_o = -g_m g_{\pi} (R_C || R_L) I_i \frac{R_B}{R_B + R_{ib}}$$

To find I_i in terms of V_i

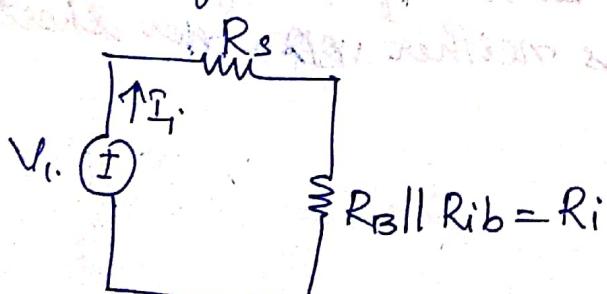

$$\therefore V_i = I_i (R_s + R_i)$$

$$I_i = \frac{V_i}{R_s + R_i}$$

$$\text{Sub in } V_o = -g_m g_{\pi} (R_C || R_L) \frac{V_i}{R_s + R_i} \frac{R_B}{R_B + R_{ib}}$$

$$A_v = \frac{Y_o}{Y_i} = -g_m R_{st} (R_C || R_L) \frac{R_B}{R_B + R_{ib}} \cdot \frac{1}{R_{st}}$$

$$|A_v| = \left| \frac{Y_o}{Y_i} \right| = g_m R_{st} (R_C || R_L) \left(\frac{R_B}{R_B + R_{ib}} \right) \left(\frac{1}{R_{st}} \right)$$


A figure of merit for an amplifier is the gain-BW product. Assuming the corner frequencies are far apart, BW is

$$f_{BW} = f_H - f_L \approx f_H$$

$$G_B = |A_v|_{\max} \cdot f_H$$

Bypass Capacitor Effects

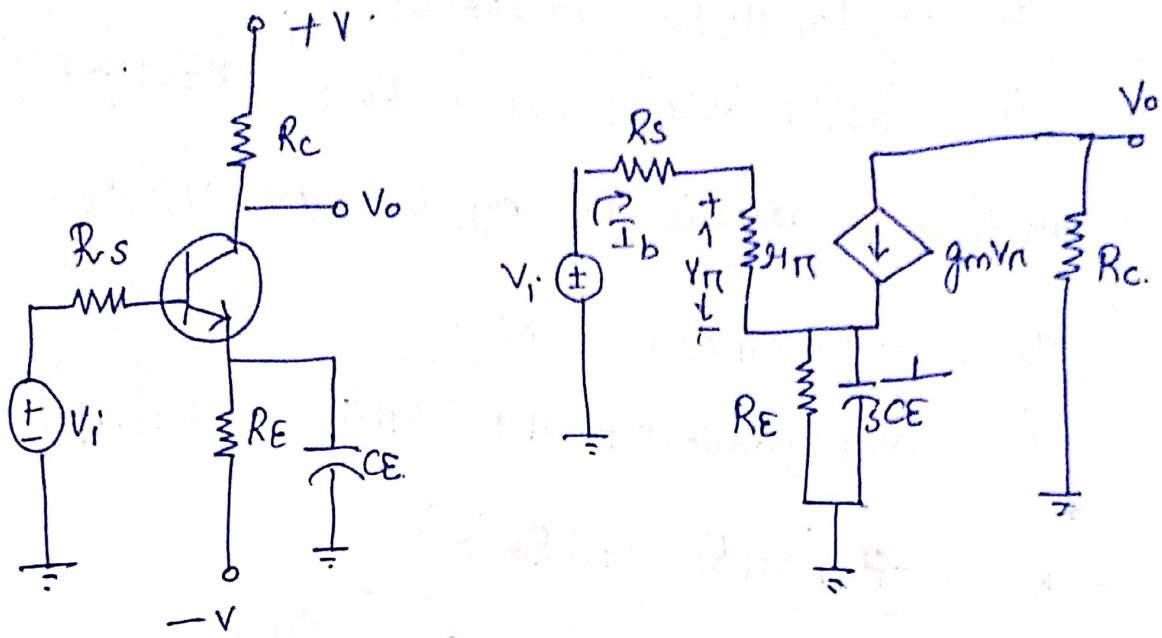- * By pass capacitors are included to stabilize Q point without sacrificing the small signal gain.
- * To choose a bypass capacitor we must determine the circuit response in the frequency range where these capacitors neither open nor short circuit.



The transfer function

$$A_v = \frac{V_o(s)}{V_i(s)}$$

$$V_o = -g_m V_{\pi} (R_c) = -g_m I_b r_{\pi} R_c$$

$$V_{\pi} = I_b r_{\pi}$$

$$V_i = I_b \left[R_s + r_{\pi} + \left(R_E \parallel \frac{1}{\beta C_E} \right) (1 + \beta) \right]$$

$$\Rightarrow I_b = \frac{V_i}{R_s + r_{\pi} + \left(R_E \parallel \frac{1}{\beta C_E} \right) (1 + \beta)}$$

Sub in

$$V_o = -g_m r_{\pi} R_c \frac{V_i}{R_s + r_{\pi} + \left(R_E \parallel \frac{1}{\beta C_E} \right) (1 + \beta)}$$

$$\frac{V_o}{V_i} = -g_m r_{\pi} R_c \frac{1}{R_s + r_{\pi} + \frac{R_E \times \frac{1}{\beta C_E}}{R_E + \frac{1}{\beta C_E}} (1 + \beta)}$$

$$= -g_m r_{\pi} R_c \frac{1}{R_s + r_{\pi} + (1 + \beta) \frac{R_E / \beta C_E}{R_E C_E + 1 / \beta C_E}}$$

$$\frac{V_o}{V_i} = \frac{-g_m g_{mT} R_C (1 + S R_E C_E)}{R_S (1 + S R_E C_E) + g_{mT} (1 + S R_E C_E) + R_E (1 + \beta)}$$

Multiply & divide the by $R_S + g_{mT} + (1 + \beta) R_E$.

$$\frac{V_o}{V_i} = \frac{-g_m g_{mT} R_C (1 + S R_E C_E)}{R_S + S R_S R_E C_E + g_{mT} + S g_{mT} R_E C_E + R_E (1 + \beta)}$$

$$\rightarrow \frac{V_o}{V_i} = \frac{-g_m g_{mT} R_C (1 + S R_E C_E)}{R_S + g_{mT} + (1 + \beta) R_E + S R_E C_E (R_S + g_{mT})}$$

Take $R_S + g_{mT} + (1 + \beta) R_E$ in Dr outside.

$$\frac{V_o}{V_i} = \frac{-g_m g_{mT} R_C (1 + S R_E C_E)}{R_S + g_{mT} + (1 + \beta) R_E \left[1 + \frac{S R_E C_E (R_S + g_{mT})}{R_S + g_{mT} + (1 + \beta) R_E} \right]}$$

$$\therefore A_v = \frac{-g_m g_{mT} R_C (1 + S \zeta_A)}{R_S + g_{mT} + (1 + \beta) R_E (1 + S \zeta_B)}$$

$$\text{where } \zeta_A = R_E C_E$$

$$\zeta_B = \frac{R_E C_E (R_S + g_{mT})}{R_S + g_{mT} + (1 + \beta) R_E}$$

At $\omega \rightarrow 0$, C_E tends to open circuit.

$$\therefore |A_v|_{\omega \rightarrow 0} = \frac{g_m g_{mT} R_C}{R_S + g_{mT} + (1 + \beta) R_E}$$

At $\omega \rightarrow \infty$ C_E is short circuit


$$|A_V| \omega \rightarrow \infty = \frac{g_m 2\pi R_C}{R_S + 2\pi}$$

R_E is shorted by C_E .


Corner frequencies

$$f_B = \frac{1}{2\pi C_B}$$

$$f_A = \frac{1}{2\pi C_A}$$

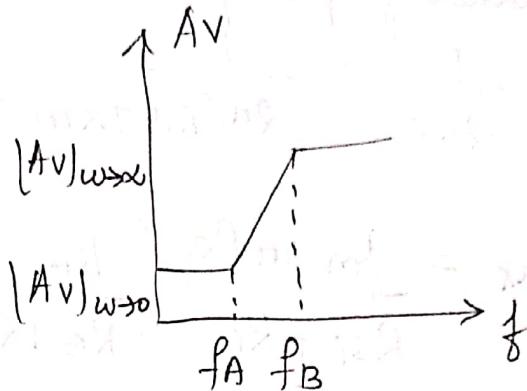

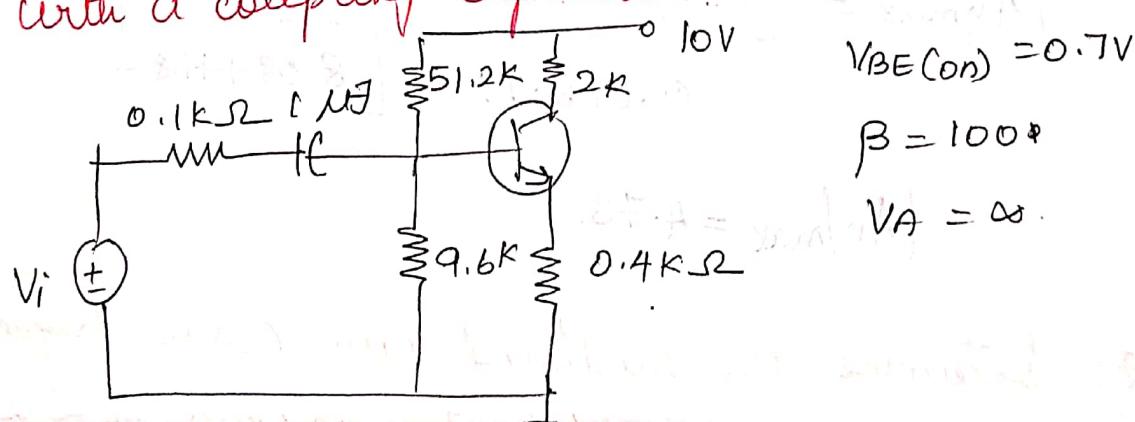① Calculate the corner frequency & maximum gain of a bipolar common emitter circuit with a coupling capacitor.



Solution : $I_{CQ} = 1.81 \text{ mA}$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.81}{0.026} = 69.6 \text{ mA/V}$$

$$2\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.81} = 1.44 \text{ k}\Omega$$

$$R_i = R_1 \parallel R_2 \parallel 2\pi + (1+\beta) R_E$$

$$= 51.2 \parallel 9.6 \parallel [1.44 + (101)(0.4)] = 6.77 \text{ k}\Omega$$

$$\tau_s = (R_{si} + R_i) C_c = (0.1 \times 10^3 + 6.77 \times 10^3) (1 \times 10^{-9})$$

$$\tau_s = 6.87 \times 10^{-9} \text{ s}$$

$$\tau_s = 6.87 \text{ ms}$$

The corner frequency:

$$f_c = \frac{1}{2\pi\tau_s} = \frac{1}{2\pi(6.87 \times 10^{-9})} = 23.2 \text{ Hz}$$

$$|Av|_{\max} = \frac{g_m \cdot \pi \cdot R_E}{R_{si} + R_i} \left(\frac{R_B}{R_B + R_{ib}} \right)$$

$$R_{ib} = g_m + (1+\beta) R_E = 1.44 + (101)(0.4)$$


$$R_{ib} = 41.8 \text{ k}\Omega$$

$$|Av|_{\max} = \frac{(69.6)(1.44)(2)}{0.1 + 6.77} \left[\frac{8.08}{8.08 + 41.8} \right]$$

$$|Av|_{\max} = 4.73$$

② Determine the midband gain, corner frequency & BW of a circuit containing both C_c & C_L .
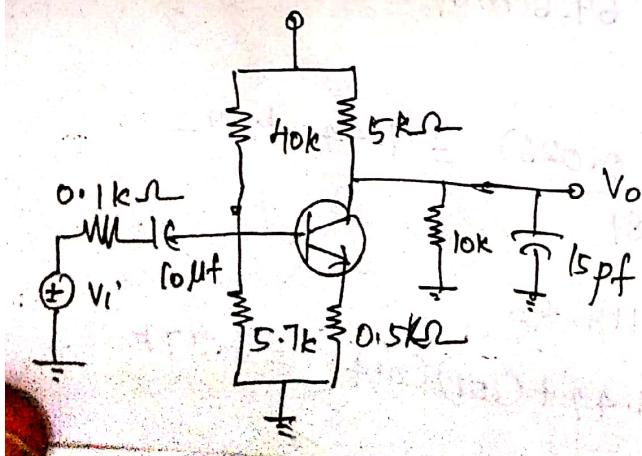
$$V_{BE(\text{CON})} = 0.7 \text{ V} \quad \beta = 100 \quad V_A = \infty$$



Solution

$$I_{CQ} = 0.99 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.99}{0.026}$$

$$g_m = 38.1 \text{ mA/V}$$

$$\theta_H = \frac{\beta VT}{I_{CQ}} = \frac{(100)(0.026)}{0.99} = 2.63 \text{ k}\Omega$$

$$R_i = \theta_H + (1+\beta) R_E = 2.63 + (101)(0.5) = 53.1 \text{ k}\Omega$$

$$|Av|_{\max} = \left| \frac{V_o}{V_i} \right|_{\max} = g_m \theta_H (R_C || R_L) \left[\frac{R_1 || R_2}{R_1 || R_2 + R_1} \right] \left[\frac{1}{R_s + (R_1 || R_2 || R_i)} \right]$$

$$= (38.1)(2.63)(5 || 10) \left[\frac{40 || 5.7}{40 || 5.7 + 53.1} \right] \left[\frac{1}{0.1 + (40 || 5.7) / 53.1} \right]$$

(or)

$$|Av|_{\max} = 6.16$$

The time constant τ_S is

$$\tau_S = (R_s + R_1 || R_2 || R_i) C_C$$

$$= (0.1 \times 10^3 + (5.7 \times 10^3) / (40 \times 10^3)) / (53.1 \times 10^3)$$

$$(10 \times 10^{-6}) = 4.66 \times 10^{-2} \text{ sec.}$$

$$\boxed{\tau_S = 46.6 \text{ ms.}}$$

The time constant τ_P is

$$\tau_P = (R_C || R_L) C_L = (5 \times 10^3 / (10 \times 10^3)) 15 \times 10^{-12}$$

$$\tau_P = 5 \times 10^{-8} \text{ sec.}$$

$$\Rightarrow \boxed{\tau_P = 50 \text{ ns.}}$$

The lower corner freq

$$f_L = \frac{1}{2\pi\tau_S}$$

$$= \frac{1}{2\pi(46.6 \times 10^{-3})} = 3.42 \text{ Hz}$$


The upper corner freq.

$$f_H = \frac{1}{2\pi\tau_P} = \frac{1}{2\pi(50 \times 10^{-9})}$$

$$f_H = 3.18 \text{ MHz}$$

$$BW = f_H - f_L = 3.18 \text{ MHz} - 3.4 \text{ Hz} \approx 3.18 \text{ MHz}$$

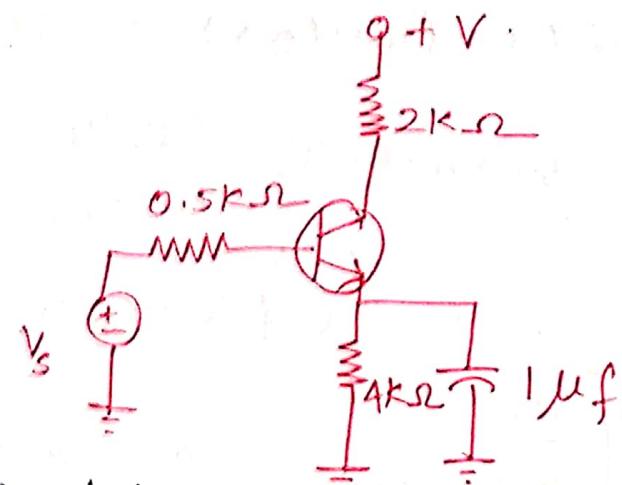③ Determine the corner frequencies & limiting horizontal asymptotes of CE amplifier with β .



$$I_{CQ} = 1.06 \text{ mA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$\beta = 100$$

$$g_{10} = \infty$$

Solution :-

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.06}{0.026} = 40.8 \text{ mA/V}$$

$$r_{m} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.06} = 2.45 \text{ k}\Omega$$

$$\tau_A = R_E C_E = (4 \times 10^3)(1 \times 10^{-6}) = 4 \times 10^{-3} \text{ sec.}$$

$$\tau_B = \frac{R_E (R_s + r_m) C_E}{R_s + r_m + (1+\beta) R_E} = \frac{(4 \times 10^3)(0.5 \times 10^3 + 2.45 \times 10^3)}{0.5 \times 10^3 + 2.45 \times 10^3 + (101)}$$

$$\tau_B = 2.90 \times 10^{-5} \text{ sec.}$$

$$f_A = \frac{1}{2\pi\tau_A} = \frac{1}{2\pi(4 \times 10^{-3})} = 39.8 \text{ Hz}$$

$$f_B = \frac{1}{2\pi\tau_B} = \frac{1}{2\pi(2.90 \times 10^{-5})} = 5.49 \text{ kHz}$$

Limiting low frequency horizontal asymptote is:

$$|Av|_{\omega \rightarrow 0} = \frac{g_m r_m R_C}{R_s + r_m + (1+\beta) R_E} = \frac{(40.8)(2.45)(2)}{0.5 + 2.45 + (101)} = 0.49$$

$$(Av)_{\omega \rightarrow 0} = 0.49 \quad \text{Limiting high frequency low asymptote}$$

$$|Av|_{\omega \rightarrow \infty} = \frac{g_m r_m R_C}{R_s + r_m} = \frac{(40.8)(2.45)(2)}{0.5 \cdot 2.45} = 67.8$$