

## 15EC202 Electronic Circuits

### Unit - I : BJT Amplifiers

1. DC analysis & DC load line of BJT ckt
2. AC analysis & AC load line of BJT ckt
3. Small-Signal operation & hybrid- $\pi$  model
4. T-Model
5. Characterizing amplifiers
6. Single-Stage BJT amplifiers
  - a. CE ampr.
  - b. CB ampr.
  - c. CC ampr.
7. Multi-Stage BJT amplifiers
  - a. CE+CE
  - b. CE+CB (cascode)
  - c. CE+CC
  - d. CC+CC (Darlington)
8. Single-Tuned Ampr.      Low-freq response
9. Freq. Response of CE ampr.      High-freq response

# Analysis of common-Emitter BJT amplifier

(1)

- amplifier is an electronic circuit which provides amplification.
- amplification is a process of raising the strength of a weak signal without any change in the shape of the signal.
- BJT can be employed for amplification.
- BJT can be connected in circuit <sup>in</sup> 3 ways.
  1. CE connection
  2. CB connection
  3. CC connection.

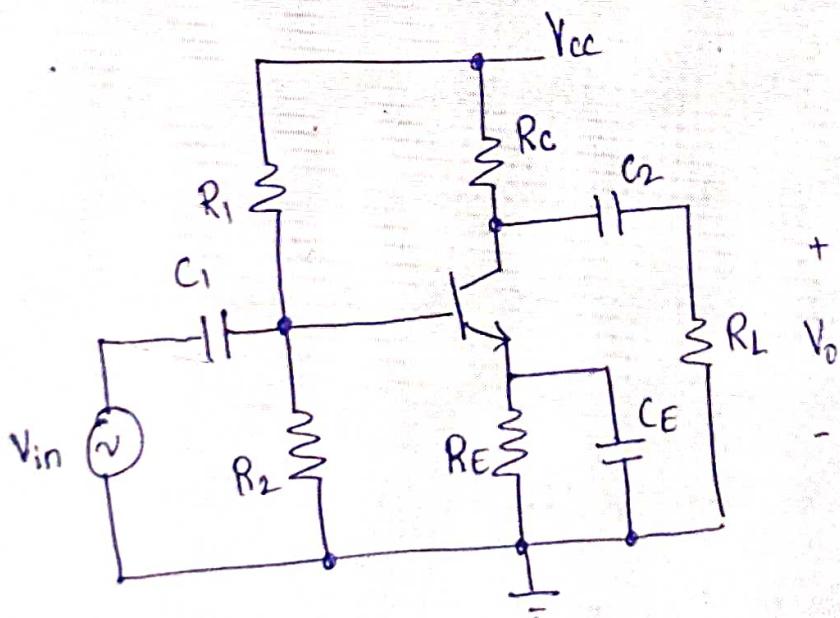


Fig.1 : CE BJT amplifier.

- Signal source is capacitor-coupled to the circuit i/p terminal
- a load resistor is also capacitor coupled to the circuit o/p terminal.

- Capacitor-coupling ensures that the source and the load do not affect the dc bias conditions in the circuit.
- Emitter resistor  $R_E$  is bypassed using a capacitor  $C_E$  to prevent ac degeneration (ie, loss in voltage gain of the circuit due to negative feedback)
- analysis is of two types: dc analysis and ac analysis.

### DC analysis

- To Perform DC analysis
  1. Turn-off AC sources
  2. Open-circuit all the capacitors
- the resultant p/w is a DC p/w, and only dc conditions (ie, dc voltages and dc currents) prevail in the p/w.

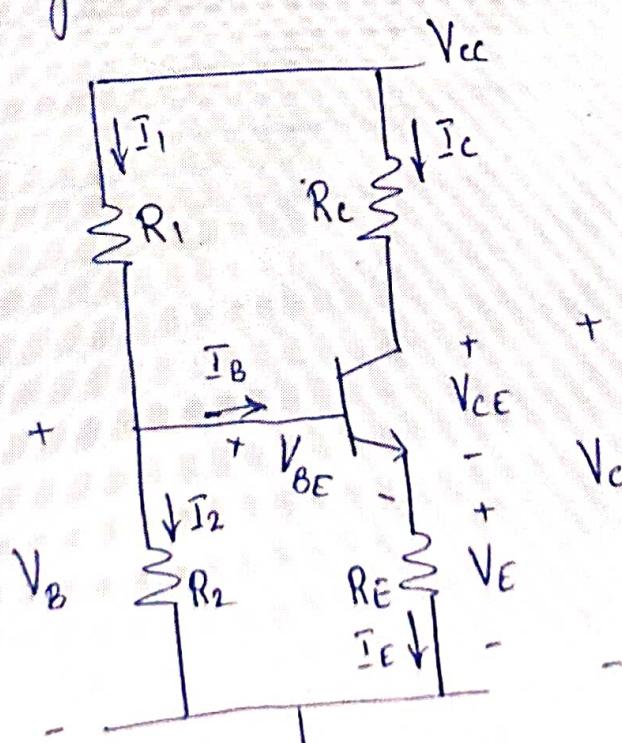


Fig.2: Voltage-divider biasing circuit

- This ckt. is called voltage-divider bias circuit for BJT
- The basis for the name of the ckt. stems from the fact that resistors  $R_1$  and  $R_2$  constitute a voltage divider that divides the supply voltage  $V_{cc}$  to produce base voltage  $V_B$ . (3)

Applying KVL in the i/p loop,

$$V_B = V_{BE} + V_E \quad \text{--- (1)}$$

$$\text{i.e., } V_E = \frac{V_B - V_{BE}}{R_E} \quad \text{--- (2)}$$

$$\text{i.e., } \beta I_E = \frac{V_B - V_{BE}}{R_E} \text{ where } V_B = \frac{V_{cc} \times R_2}{R_1 + R_2} \quad \text{--- (4)}$$

$$\text{and, } I_C \approx I_E \quad \text{--- (5)}$$

$$I_B = \frac{I_C}{\beta} \text{ where } \beta \text{ is the dc current gain.}$$

Applying KVL in the o/p portion of the n/w,

$$V_{cc} = I_C R_C + V_{CE} + I_E R_E$$

$$\text{i.e., } V_{CE} = V_{cc} - I_C (R_C + R_E) \text{ if } I_E \approx I_C \quad \text{--- (6)}$$

The other transistor branch currents and voltages can be computed as:

$$\left. \begin{aligned} V_C &= V_{CE} + V_E \\ V_{BC} &= V_B - V_C \\ V_E &= I_E R_E \approx I_C R_E \end{aligned} \right\} \quad \text{--- (7)}$$


- The zero-signal (pl. note the absence of signal source) values of transistor current and voltages is called Quiescent current and voltages.
- Particularly, the zero-signal values of  $V_{CE}$  and  $I_C$  is called Quiescent point, or Q-point, or Silent point.
- Quiescent means 'Silent'; Silent means 'no signal'.
- Q-point is also called as operating point.

### DC load line

Recall the expression

$$V_{CE} = V_{CC} - I_C(R_C + R_E) \quad \text{--- (6)}$$

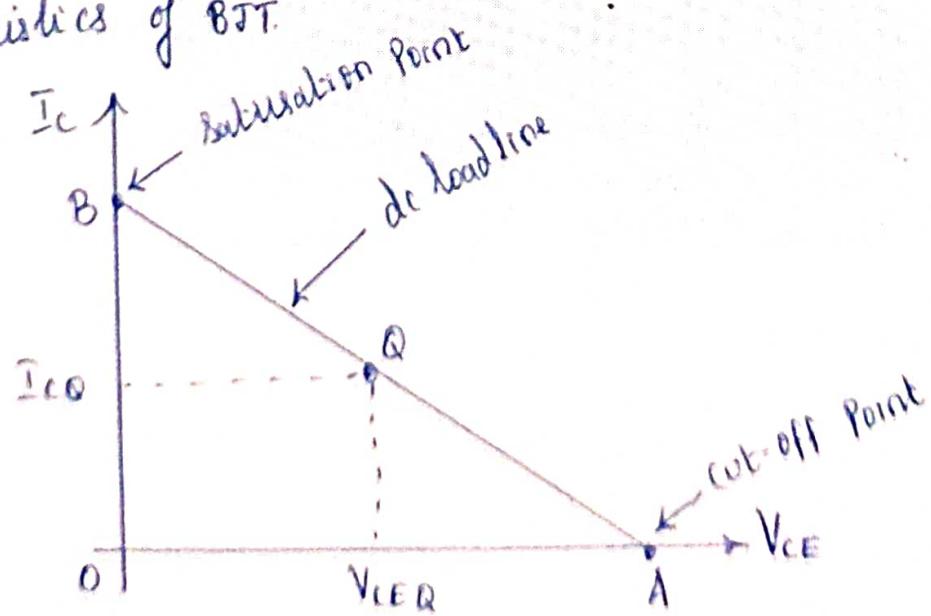- When  $I_B$  changes,  $I_C$  changes and  $V_{CE}$  changes
- ie, when  $I_B$  changes, Q-point changes but along a sloping straight line, since eq. (6) is an eq. of a st. line.
- this st. line is called dc loadline, and is draw on the o/p characteristics of BJT.



To draw dc load line.

(5)

\* Put  $I_C = 0$  in eq. ⑥

$$\Rightarrow V_{CE(\text{off})} = V_{CC}$$

This point  $(V_{CC}, 0)$  on the characteristics curve of the BJT is called cut-off point, meaning that transistor is off because of  $I_C = 0$ . This pt. is marked 'A'.

\* Put  $V_{CE} = 0$  in eq. ⑥

$$\Rightarrow I_C(\text{sat}) = \frac{V_{CC}}{R_E + R_C}$$

This pt.  $\Rightarrow (0, \frac{V_{CC}}{R_E + R_C})$  on the charac. curve is called saturation point, meaning that the voltage drop across the transistor (ie, between C & E terminals) is zero, and hence transistor is saturated by a large current flow through it. This point is marked 'B'.

\* Connect the points A & B using a straight line, which is called dc load line, whose slope is  $-\frac{1}{R_E + R_C}$ .

\* Q-point can be plotted, and is on the dc load line.

\* When  $I_B$  changes, Q-point changes and moves along the load line.

\* The region along the loadline including all points between saturation and cut-off is generally known as the linear region of the transistor's operation. As long as the tr. is operated in this region, the o/p voltage is ideally a linear reproduction of the i/p.

## Ac analysis

- once the DC analysis is completed, the ac response can be determined using ac analysis.
- To perform Ac analysis
  - \* Turn-off  $V_{cc}$ , ie,  $V_{cc}$  is at ac ground
  - \* short-circuit all the capacitors, because  $X_C \approx 0$  at signal frequencies (assumed)
- the resultant n/w is called AC equivalent circuit, and only ac conditions prevail in the circuit.


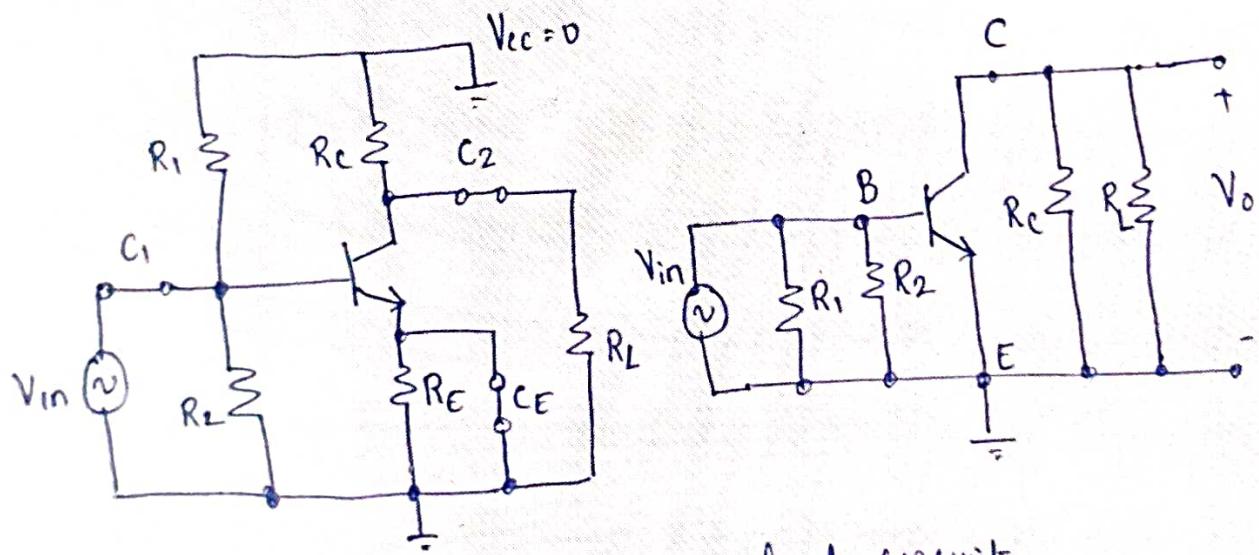


Fig. 3: AC equivalent circuit

- once the ac equivalent circuit is obtained, the BJT device is replaced by its equivalent model and then the circuit analysis is performed to determine the desired quantities of the n/w.
- of the various models available, hybrid-II model is extensively used, and its simplified version is discussed in the next section.
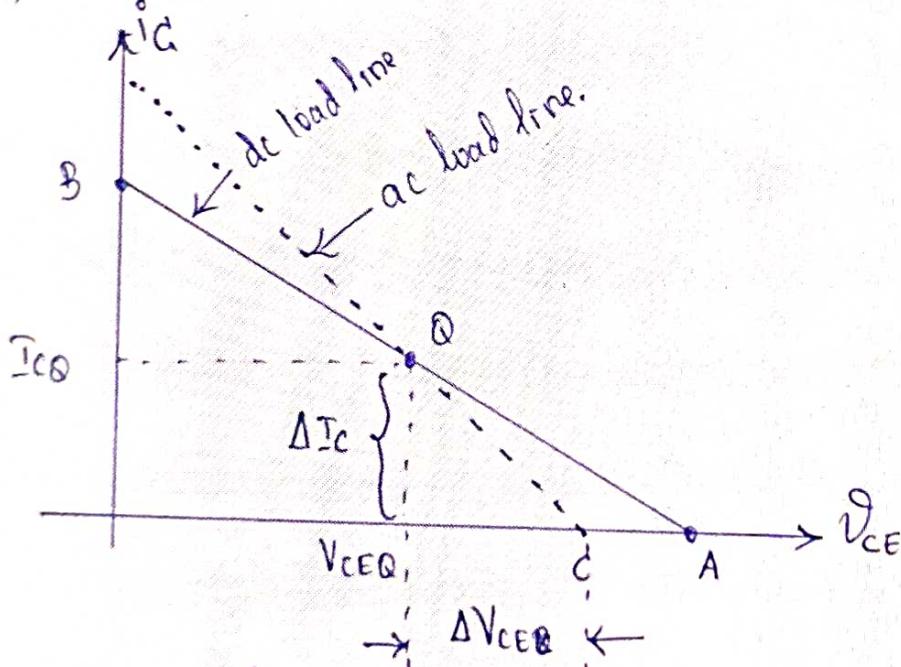
## Ac load line

- Ac loadline is a new load line drawn on the OIP Charac. curve of the transistor to describe the circuit performance when signal is applied.
- Recall that the total dc load of the tr. w/ is  $(R_C + R_E)$ , and consequently dc load line is drawn with a slope of  $(-\frac{1}{R_C + R_E})$ .
- From fig. 3, it is understood that  $R_E$  is not a part of the ac w/, and hence the ac load of the w/ is  $(R_L \parallel R_E)$ .




- When no signal is applied, the tr. current & voltage conditions are as indicated at the Q-pt. on the dc load line. When ac signal is applied, the tr. current and voltage vary above and below Q-pt. So, Q-point is common to both load lines.
- another pt. is found on the ac load line by taking a convenient collector current change (usually  $\Delta I_c = I_{CQ}$ ) and then calculate corresponding collector-emitter voltage  $\Delta V_{CEQ} = \Delta I_c \times (R_L \parallel R_E)$ . Mark this pt. as 'c'.
- connect pts. Q & c to draw ac load line and extend it to meet the y-axis.

(7)
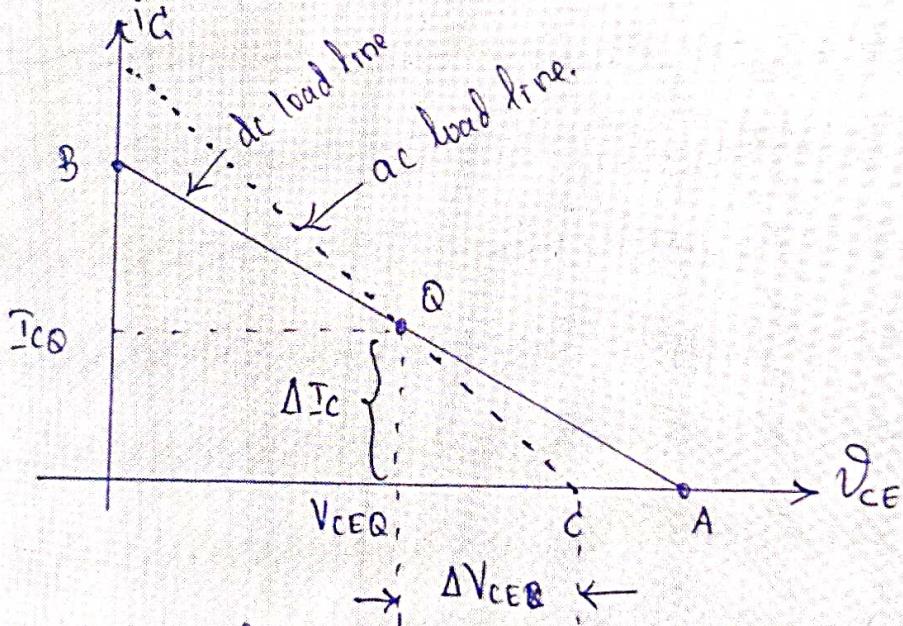
## Ac load line

- Ac loadline is a new load line drawn on the OIP charac. curve of the transistor to describe the circuit performance when signal is applied.
- Recall that the total dc load of the tr. o/p is  $(R_C + R_E)$ , and consequently dc load line is drawn with a slope of  $(-\frac{1}{R_C + R_E})$ .
- From fig. 3, it is understood that  $R_E$  is not a part of the ac o/p, and hence the ac load of the o/p is  $(R_C \parallel R_L)$ .



- When no signal is applied, the tr. current & voltage conditions are as indicated at the Q-pt. on the dc load line. When ac signal is applied, the tr. current and voltage vary above and below Q-pt. So, Q-point is common to both load lines.
- another pt. is found on the ac load line by taking a convenient collector current change (usually  $\Delta I_c = I_{CQ}$ ) and then calculate corresponding collector-emitter voltage  $\Delta V_{CEQ} = \Delta I_c \times (R_C \parallel R_L)$ . Mark this pt. as 'c'.
- connect pts. Q & c to draw ac load line and extend it to meet the y-axis.

AvM

## Small-Signal operation and hybrid-II model

Consider a conceptual circuit to illustrate the operation of the TA as an amp.

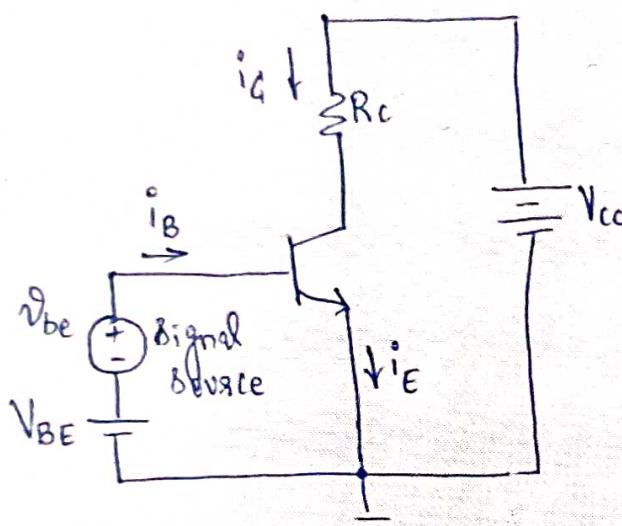


Fig. 4(a): Basic small-signal ampl.

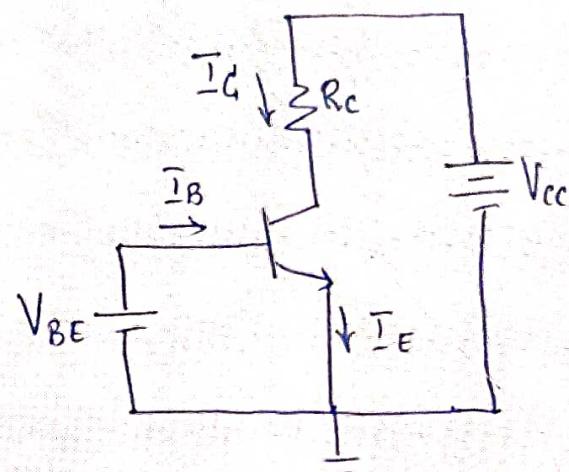


Fig. 4(b): Ckt. with signal source eliminated for dc analysis.

- DC power supply voltages  $V_{BE}$  and  $V_{CC}$  established fw/bias and rev. bias to EB jn and CB jn respectively.
- an i/p signal  $v_{be}$  which is to be amplified is superimposed on  $V_{BE}$

When no signal is applied, i.e.,  $v_{be} = 0V$ , we can write the following relationships for the dc currents and voltages.

$$\left. \begin{aligned} I_C &= I_S e^{\frac{V_{BE}}{V_T}} \\ V_C &= V_{CE} = V_{CC} - I_C R_C \\ I_C &= \beta I_B \\ I_C &= \alpha I_E \end{aligned} \right\} - \textcircled{8}$$

where  $V_T = \text{volt-equivalent of temperature} = \frac{kT}{q} \approx 26mV$   
 $\alpha = \text{current gain of CB connected TA.}$   
 $\beta = \text{current gain of CE connected TA.}$

(9)

## The collector current and the transconductance

when ac signal is applied, the total instantaneous base-emitter voltage becomes

$$v_{BE} = V_{BE} + v_{be} \quad - (9)$$

correspondingly, the total instantaneous collector current will be

$$\begin{aligned} i_C &= I_S e^{\frac{v_{BE} + v_{be}}{V_T}} = I_S e^{\frac{(V_{BE} + v_{be})}{V_T}} \\ &= I_S e^{\frac{V_{BE}}{V_T}} e^{\frac{v_{be}}{V_T}} \\ &= I_C e^{\frac{v_{be}}{V_T}} \end{aligned} \quad - (10)$$

if  $v_{be} \ll V_T$ , we can approximate,

$$\begin{aligned} \hat{i}_C &= I_C \left(1 + \frac{v_{be}}{V_T}\right) \\ &= I_C + I_C \frac{v_{be}}{V_T} \\ &= I_C + i_c \end{aligned}$$

This approximation  $v_{be} \ll V_T$ , ie,  $v_{be} \leq 10\text{mV}$  is referred to as small-signal approximation and hence, the name small-signal ampl.

where  $i_c$  is the small-signal collector current, and is given by

$$\hat{i}_c = I_C \frac{v_{be}}{V_T} \quad - (11)$$

$$\text{ie, } \boxed{\hat{i}_c = g_m v_{be}} \quad - (12)$$

where  $g_m$  is the transconductance, and is given by

$$\boxed{g_m = \frac{I_C}{V_T}} \quad - (13)$$

The base current and the ilp resist. @ the base

The total instantaneous base current is given by

$$i_B = \frac{i_C}{\beta} = \frac{\bar{I}_C + \dot{i}_C}{\beta} = \frac{\bar{I}_C}{\beta} + \frac{\dot{i}_C}{\beta} = \bar{I}_B + \dot{i}_b$$

where  $\dot{i}_b$  is the small-signal base current, and is given by

$$\dot{i}_b = \frac{\dot{i}_C}{\beta} = \frac{1}{\beta} \bar{I}_C \frac{V_{be}}{V_T} \quad \text{from eq. (11)}$$

$$\text{ie, } \dot{i}_b = \frac{g_m}{\beta} V_{be} \quad \text{--- (14)}$$

$$\text{ie, } R_{\pi} = \frac{V_{be}}{\dot{i}_b} = \frac{\beta}{g_m} \quad \text{--- (15)}$$

where  $R_{\pi}$  is the small-signal ilp resistance between base and emitter.

$$\text{also, } R_{\pi} = \frac{\beta}{\bar{I}_C / V_T} = \frac{V_T}{\bar{I}_B} \quad \text{--- (16) from eq. (13)}$$

The emitter current and the ilp resist. @ the emitter

The total instantaneous emitter current is given by

$$i_E = \frac{i_C}{\alpha} = \frac{\bar{I}_C + \dot{i}_C}{\alpha} = \frac{\bar{I}_C}{\alpha} + \frac{\dot{i}_C}{\alpha} = \bar{I}_E + \dot{i}_e$$

where  $\dot{i}_e$  is the small-signal emitter current, and is given by

$$\dot{i}_e = \frac{i_C}{\alpha} = \frac{1}{\alpha} \frac{\bar{I}_C}{V_T} V_{be} \quad \text{--- (17) from eq. (13)}$$

$$\text{ie, } \dot{i}_e = \frac{g_m}{\alpha} V_{be}$$

$$\text{ie, } R_e = \frac{V_{be}}{\dot{i}_e} = \frac{\alpha}{g_m} \approx \frac{1}{g_m} \quad \text{--- (18)}$$

where  $r_e$  is called emitter resistance

(11)



$$\text{also, } r_e = \frac{\alpha}{g_m} = \frac{\alpha}{I_c/V_T} = \frac{V_T}{I_E} \quad \rightarrow (17) \text{ from eq. (3)}$$

from equations (14) and (18),

$$v_{be} = i_b r_{\pi} = i_e r_e$$

$$\text{ie, } r_{\pi} = \frac{i_e r_e}{i_b} = \frac{i_b + i_c}{i_b} r_e$$
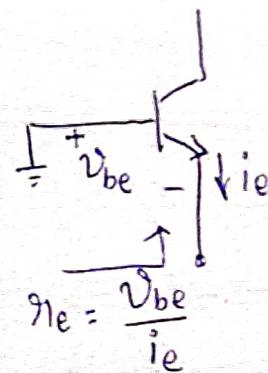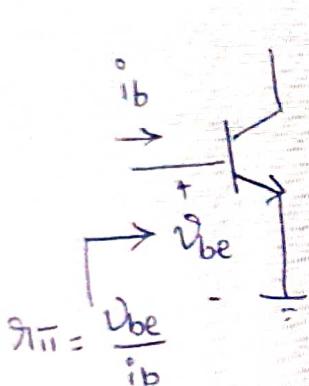
$$\text{ie, } r_{\pi} = (1 + \beta) r_e \quad \rightarrow (20)$$



### Voltage gain

$$\text{Eq. (12)} \Rightarrow i_c = g_m v_{be}$$

i.e., the transistor produces an o/p collector current proportional to the changes in the i/p base-emitter Voltage. To obtain an o/p voltage, force this o/p current to flow thru the resistor  $R_C$ . So,

$$\begin{aligned} V_C &= V_{CC} - i_c R_C = V_{CC} - (I_c + i_e) R_C \\ &= (V_{CC} - I_c R_C) - i_e R_C \\ &= V_C - V_e \end{aligned}$$

while  $V_C$  is the total instantaneous o/p collector voltage, given by

$$V_C = -i_C R_C$$

$$= -g_m V_{BE} R_C \quad \text{from eq. (12)}$$


it,  $A_V = \frac{V_C}{V_{BE}} = -g_m R_C$  is the voltage gain of this amp.

Because  $g_m$  is directly proportion to collector bias current, the voltage gain of the amp will be as stable as the collector current.

also,  $A_V = -g_m R_C = -\frac{i_C R_C}{V_T}$
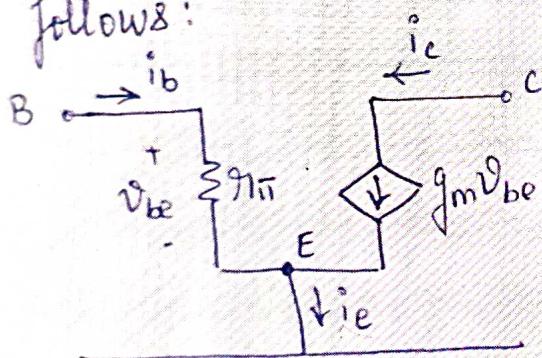
## The Hybrid- $\pi$ model

- in the previous section, we have developed the equivalent circuit of the CE BJT amplifier.
- the BJT in that circuit is replaced by its small-signal equivalent model.
- one such model is the hybrid- $\pi$  model, which is closely related to the physics of the transistor.
- using the parameters  $g_m$ ,  $\pi_{\pi}$ ,  $\pi_e$ ,  $\beta$  and  $\alpha$ , <sup>as</sup> discussed in the previous section, we can develop a simplified small-signal hybrid  $\pi$  equivalent circuit as follows:



$$\pi_{\pi} = \frac{\beta}{g_m}$$

$$g_m = \frac{I_c}{V_T}$$

This model

- represents BJT as a voltage-controlled current source, and
- includes the  $r_{IP}$  resistance looking into the base,  $\pi_{\pi}$ .

An expression for  $i_e$  can be found as

$$i_e = i_b + i_c = \frac{v_{be}}{\pi_{\pi}} + g_m v_{be} = \frac{v_{be}}{\pi_{\pi}} (1 + g_m \pi_{\pi})$$


$$= \frac{v_{be}}{\pi_{\pi}} (1 + \beta) = \frac{v_{be}}{\left(\frac{\pi_{\pi}}{1+\beta}\right)}$$

=  $\frac{v_{be}}{r_e}$ , where  $r_e$  = emitter resistance

$$= \frac{\pi_{\pi}}{1 + \beta}$$


A slightly different eq. ckt. can be obtained by replacing voltage-controlled current source with a current-controlled current source, as follows:
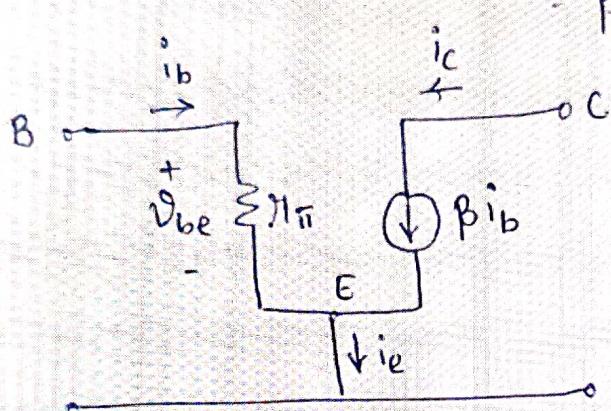
$$g_m v_{be} = g_m (i_b \gamma_{\pi}) = (g_m \gamma_{\pi}) i_b \\ = \beta \bar{i}_b \\ = \beta i_b$$



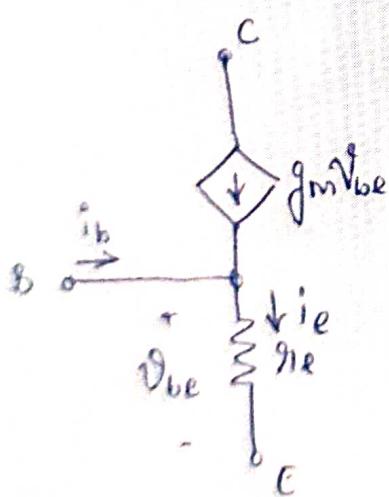
### The T-model

Although the hybrid- $\pi$  model can be used to carry out small-signal analysis of transistor circuits, there are situations in which an alternative model, known as T-model is much more convenient.



$$g_m = \frac{i_c}{V_T}$$
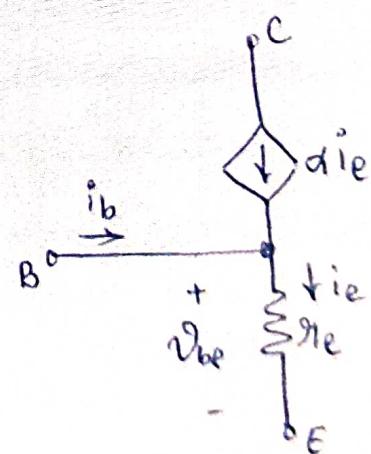
$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$



This model

- represents BJT as a voltage-controlled current source,  $g_m V_{be}$
- includes Hres. bet. base and emitter,  $\pi_e$

An expression for  $i_b$  can be found as


$$\begin{aligned} i_b = i_e - i_c &= \frac{V_{be}}{\pi_e} - g_m V_{be} = \frac{V_{be}}{\pi_e} (1 - g_m \pi_e) \\ &= \frac{V_{be}}{\pi_e} (1 - \alpha) = \frac{V_{be}}{\pi_e} \left(1 - \frac{\beta}{\beta+1}\right) \\ &= \frac{V_{be}}{(\beta+1)\pi_e} = \frac{V_{be}}{\pi_n} \end{aligned}$$

In the model, the current of the controlled source can also be expressed as in terms of the emitter current as follows:

$$\begin{aligned} g_m V_{be} &= g_m (i_e \pi_e) \\ &= (g_m \pi_e) i_e \\ &= \alpha i_e \end{aligned}$$

The Early Effect: its impact on the small-signal analysis

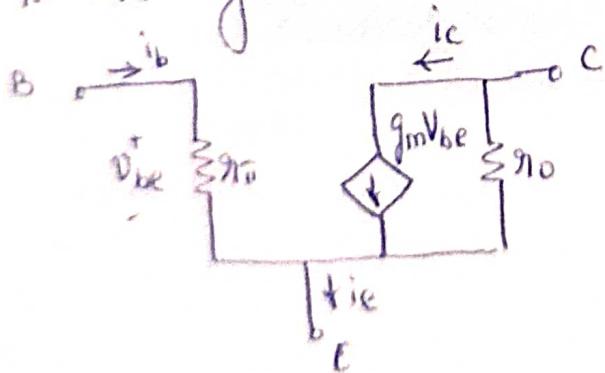The Early effect causes the  $I_c$  to depend not only on  $V_{BE}$  but also on  $V_{CE}$ . The dependence on  $V_{CE}$  can be modeled by assigning a finite output resistance  $\pi_o$  to the controlled current-source in the hybrid- $\pi$  model as follows:



Its value is given by  $\eta_0 = \frac{V_0 + V_{CE}}{I_C} \approx \frac{V_0}{I_C}$  where  $V_0$  = early voltage whose values ranges between 30V and 100V.

In the analysis of transistor circuits,  $\eta_0$  will not be included because it would complicate the analysis considerably. Also, it can be proved that the effect of  $\eta_0$  on the performance of discrete amplifier circuits is very small. This is not the case, however, for the IC form of the amplifier circuits, where effect of  $\eta_0$  is significant.

### Relationship between Various Small-signal parameters - a summary

Model parameters in terms of DC bias currents

$$g_m = \frac{I_C}{V_T}, \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C}, \quad r_{\pi} = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C}, \quad \eta_0 = \frac{V_A}{I_C}$$

In terms of  $g_m$

$$r_e = \frac{\alpha}{g_m}, \quad r_{\pi} = \frac{\beta}{g_m}$$

In terms of  $r_e$

$$g_m = \frac{\alpha}{r_e}, \quad r_{\pi} = (\beta+1)r_e, \quad g_m + \frac{1}{r_{\pi}} = \frac{1}{r_e}$$

Relationships between  $\alpha$  and  $\beta$


$$\beta = \frac{\alpha}{1-\alpha}, \quad \alpha = \frac{\beta}{\beta+1}, \quad \beta+1 = \frac{1}{1-\alpha}$$

## Characterizing Amplifiers

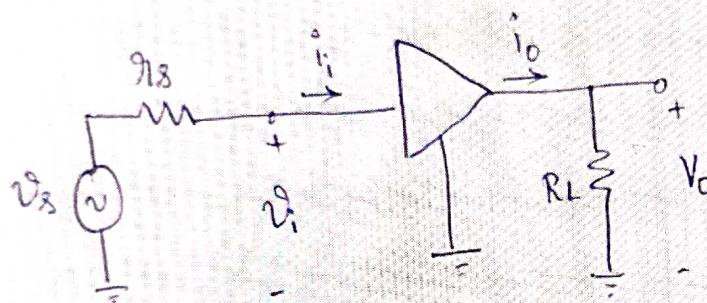(17)

Before the analysis of different BJT amp. configurations can be carried out, we shall understand how to characterize the performance of an amp. ckt.

Let us consider an amp. ckt represented by the block schematic as shown below:



- $r_{i\circ}$  is the internal resistance of the source  $v_s$ .
- $R_L$  is the load resist. connected to the o/p terminal.
- $R_L$  can be actual load resist. or the i/p resist. of a succeeding amp. stage.

The performance of the transistor can be characterized by using the following parameters:


### 1. The i/p Resistance, $R_{in}$

$$R_{in} = \frac{v_i}{i_i}$$

This  $R_{in}$  together with  $r_s$  forms a Voltage-divider which divides the source voltage  $v_s$ , producing  $v_i$ .

$$v_i = \frac{R_{in}}{R_{in} + r_s} v_s$$

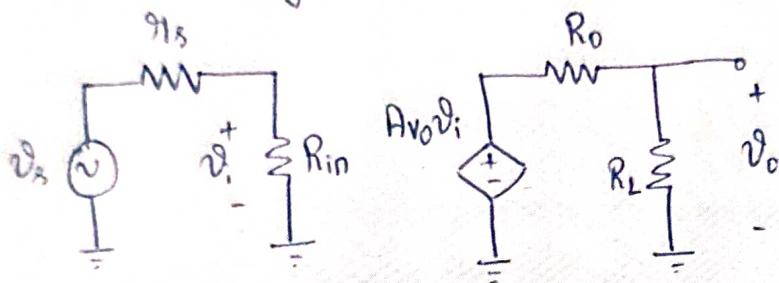The amp. block in the amp. block circuit shown above can be replaced by Thevenin's equivalent circuit model.




## 2. Open-circuit Voltage gain, A<sub>vo</sub>

$$A_{vo} = \frac{v_o}{v_i} \mid R_L = \infty$$
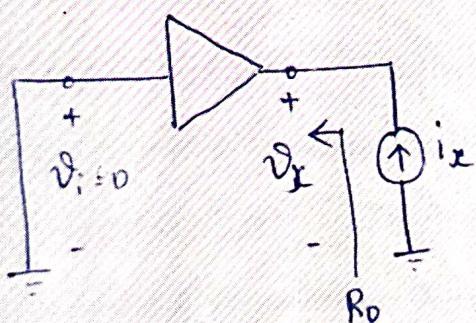
## 3. The o/p Resistance, R<sub>o</sub>

R<sub>o</sub> is the resistance seen looking back into the amp. o/p terminal with V<sub>i</sub> set to zero. conceptually,



$$R_o = \frac{v_x}{i_x}$$

From the eq. ikt. of the amp., we can also note that

$$v_o = A_{vo} v_i \times \frac{R_L}{R_o + R_L}$$


Thus, the voltage gain of the ampa. can be given by

$$A_V = \frac{V_O}{V_I} = A_{VO} \cdot \frac{R_L}{R_L + R_0}$$


The overall voltage gain,  $A_{VS}$  of the ampi. ckt can be given by

$$\begin{aligned} A_{VS} &= \frac{V_O}{V_S} = \frac{V_O}{V_I} \times \frac{V_I}{V_S} \\ &= A_V \cdot \frac{R_{in}}{R_{in} + g_{IS}} \end{aligned}$$

### The Common-Emitter (CE) Amplifier

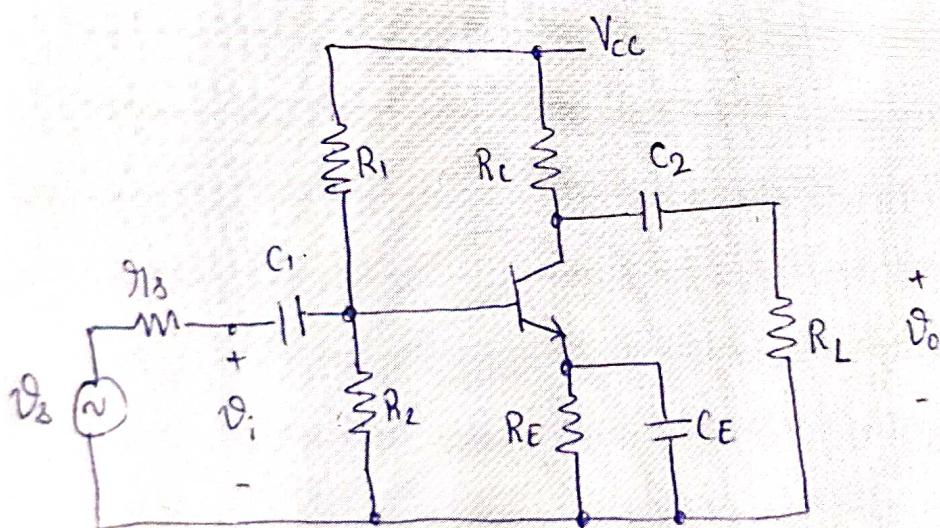

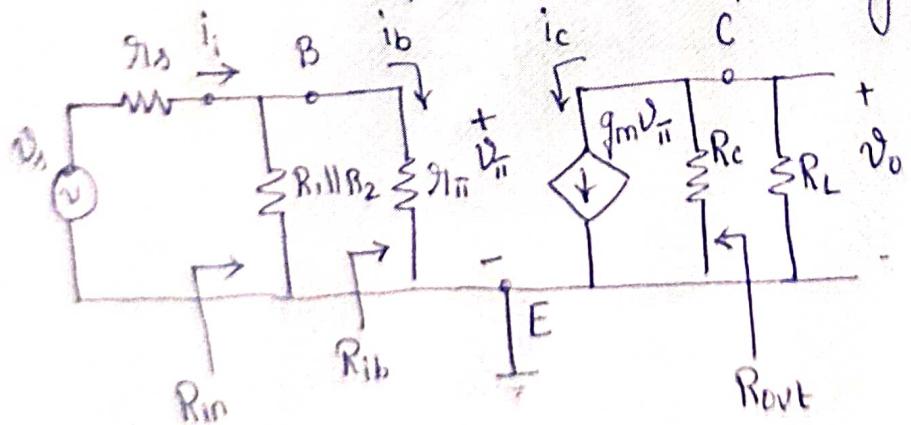The BJT in the ampi. ckt. can be replaced by its hybrid-II model.



### Input Resistance, $R_{in}$

$$R_{in} = \frac{V_i}{I_b} = R_1 \parallel R_2 \parallel R_{ib}$$

where  $R_{ib}$  is the resist. looking into the base.

$$R_{ib} = \mathcal{R}_{\pi}$$

Normally, we select  $R_1 \parallel R_2 \gg \mathcal{R}_{\pi}$ , resulting

$$R_{in} \approx R_{ib} = \mathcal{R}_{\pi}$$

### Output Resistance, $R_{out}$

The o/p resist can be found from the eq. ckt. by looking back into the o/p terminal with  $V_o = 0$ . This will result in  $V_{\pi} = 0$ , so

$$R_{out} = R_c \parallel R_L$$

### Voltage Gain

$$\begin{aligned} \text{open circuit Voltage gain, } A_{vo} &= \frac{V_o}{V_i} \Big|_{RL=\infty} \\ &= -g_m V_{\pi} R_c \\ &= -g_m R_c \end{aligned}$$

$$\begin{aligned} \text{Voltage gain of the ampl. block, } A_v &= A_{vo} \cdot \frac{R_L}{R_o + R_L} \\ &= -g_m R_c \times \frac{R_L}{R_c + R_L} \end{aligned}$$

$\therefore$  The overall voltage gain of the ampl. ckt. is given by

$$A_{vo} = \frac{V_o}{V_i} = A_v \times \frac{R_{in}}{R_{in} + \mathcal{R}_b} = \left( -g_m R_c \times \frac{R_L}{R_c + R_L} \right) \times \frac{\mathcal{R}_{\pi}}{\mathcal{R}_{\pi} + \mathcal{R}_b}$$

$$\text{ie, } A_{v8} = \frac{-g_m(R_C || R_L) \pi}{\pi + \pi_8}$$

$$= \frac{-\beta(R_C || R_L)}{\pi + \pi_8}, \text{ since } \beta = g_m \pi$$

Current gain,  $A_{i8}$


$$\begin{aligned} A_{i8} &= \frac{i_0}{i_i} = \frac{V_o/R_o}{V_8/R_i} = \frac{V_o}{V_8} \times \frac{R_i}{R_o} = |A_{v3}| \times \frac{R_i}{R_o} \\ &\approx \frac{\beta(R_C || R_L)}{\pi + \pi_8} \times \frac{\pi}{(R_C || R_L)} \\ &\approx \frac{\beta \pi}{\pi} , \text{ if } \pi_8 \ll \pi \\ &= \epsilon \beta \end{aligned}$$

### Inferences or Observations

1. The i/p resistance  $R_{in} = \pi = \frac{\beta}{g_m} = \frac{\beta V_T}{I_C}$  is moderate to low in value (typically, in the kilohm range).  $R_{in}$  is directly dependent on  $\beta$  and is inversely proportional to  $I_C$ . To obtain a higher i/p resist., the bias current  $I_C$  can be lowered, but this also lowers the gain. This is a significant design trade-off. If a much higher i/p resist. is desired, then a modification of the CE configuration, or an emitter-follower stage can be used.
2.  $R_{in}$  does not depend on the o/p side of the ampa. Hence, this ampa is said to be unilateral.


3. The o/p resist.  $R_o \approx R_c$  is moderate to high in value (typically in kilohm range). To obtain a lower o/p resist.,  $R_c$  can be lowered, but this is not a viable solution because the voltage gain is also lowered. If a much lower o/p resist. is desired, then an emitter-follower stage can be used.
4. The open-ckt voltage gain,  $A_{vo}$  is high, thus making CE configuration widely used for voltage amplification. unfortunately, however, the bandwidth of CE amps is severely limited.
5. To maintain a reasonably linear operation,  $V_i$  should not exceed about 5 mV to 10 mV, which poses a constraint on the value of  $V_B$ .
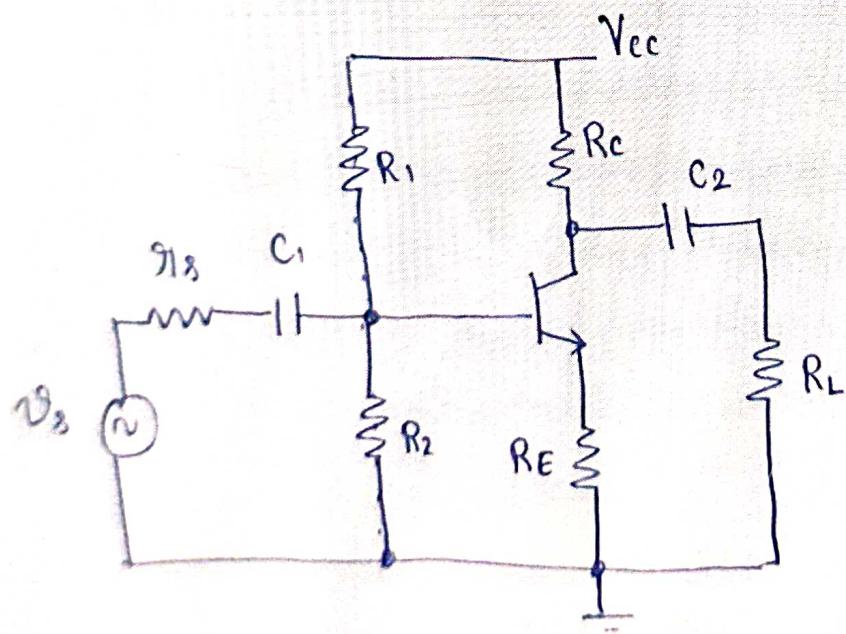
### The Common-Emitter Amplifier with unbypassed $R_E$



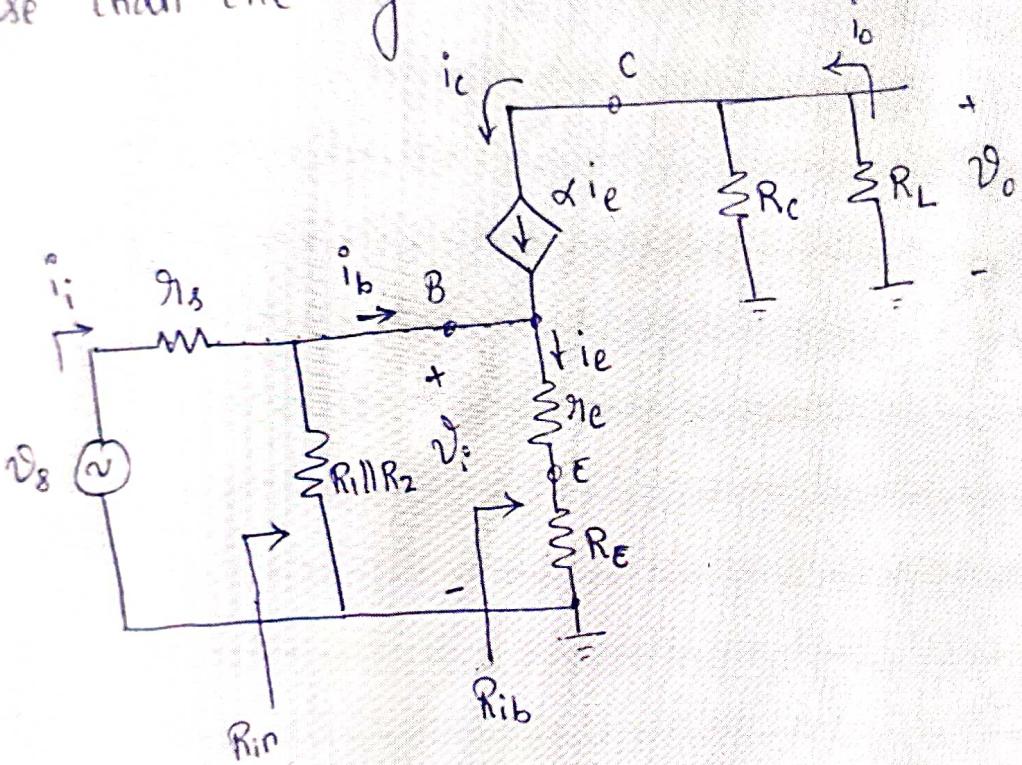(23)

Although hybrid-II model is used to perform ac analysis of this ampl. ckt., T-model is the most convenient for this type of circuit because  $R_E$  will appear in series with emitter resistor  $\mathfrak{r}_e$  of the T-model. In fact, whenever there is resistance in the emitter lead, the T-model should be more convenient to use than the hybrid-II model.



Input Resistance,  $R_{in}$

$$R_{in} = \frac{V_i}{i_i} = R_1 \parallel R_2 \parallel R_{ib}$$

where  $R_{ib}$  = resist. looking into the base terminal.

To determine  $R_{ib}$ , apply KVL in the loop consisting of  $V_i$ ,  $\mathfrak{r}_e$  &  $R_E$ .

$$V_i = i_e (R_E + \mathfrak{r}_e)$$

$$= (\beta + 1) i_b (R_E + \mathfrak{r}_e)$$

$$\Rightarrow R_{ib} = \frac{V_i}{i_b} = (\beta + 1) (R_E + \mathfrak{r}_e)$$

$$R_{in} = R_1 \parallel R_2 \parallel [(\beta + 1) (R_E + \mathfrak{r}_e)]$$

$$\approx (\beta + 1) (R_E + \mathfrak{r}_e), \quad \text{if } (R_1 \parallel R_2) \gg R_{ib}$$

$$\approx \beta (R_E + \mathfrak{r}_e) \approx \beta R_E, \quad \text{if } R_E \gg \mathfrak{r}_e$$

## Output Resistance, $R_{out}$

The  $\text{OIP}$  resist. can be found from the eq. ckt by looking back into the OIP terminal with  $V_S = 0$ . This will result in  $i_f = 0$ ,  $i_b = 0$ ,  $i_E = 0$ , and hence  $\alpha_{ie} = 0$ . So,

$$R_{out} = R_{\text{in}} \parallel R_L$$

## Voltage gain

$$\text{Open-circuit voltage gain, } A_{VO} = \left. \frac{V_O}{V_i} \right|_{R_L = \infty}$$

$$= \frac{-i_C R_C}{(\beta + 1) i_B (R_E + r_e)}$$

$$= \frac{-\beta R_C}{(\beta + 1)(R_E + r_e)}$$

$$\approx \frac{-R_C}{R_E + r_e}$$

$$\approx -\frac{R_C}{R_E} \quad \text{if } r_e \ll R_E$$

If  $R_i$  is connected to the amp, then voltage gain can be found as,

$$A_V = A_{VO} \times \frac{R_L}{R_o + R_L} = -\frac{R_C}{R_E} \times \frac{R_L}{R_C + R_L} = -\frac{R_{\text{in}} \parallel R_L}{R_E}$$

Taking into account the source resistance,  $r_s$ , the voltage gain can be expressed as

$$\begin{aligned} A_{VS} &= A_V \times \frac{R_{\text{in}}}{R_{\text{in}} + r_s} = -\frac{R_{\text{in}} \parallel R_L}{R_E} \times \frac{\beta R_E}{\beta R_E + r_s} \\ &= -\frac{\beta (R_{\text{in}} \parallel R_L)}{r_s + \beta R_E} \end{aligned}$$

Current Gain,  $A_{IS}$

$$A_{IS} = |Av_S| \times \frac{R_{in}}{R_{out}} = \frac{\beta(R_C||R_L)}{g_{IS} + \beta R_E} \times \frac{\beta R_E}{(R_C||R_L)}$$

$$= \frac{\beta}{\beta R_E} \times \beta R_E, \text{ if } g_{IS} \ll \beta R_E$$

$$\approx \beta$$

which is same as that of CE amp with  $R_E$  bypassed.

### Inferences or Observations

$$\frac{R_{ib} (\text{with } R_E \text{ included})}{R_{ib} (\text{without } R_E)} = \frac{(\beta+1)(R_E + r_e)}{g_{iI}} = \frac{(\beta+1)(R_E + r_e)}{(\beta+1)r_e}$$

$$= 1 + \frac{R_E}{r_e}$$

$$= 1 + g_m R_E, \text{ since } g_m \approx \frac{1}{r_e}$$

i.e., The i/p resist.  $R_{ib}$  is increased by a factor  $(1 + g_m R_E)$

$$2. A_{vo} = -\frac{R_C}{R_E + r_e} = -\frac{1}{r_e} \frac{R_C}{1 + R_E} = -\frac{g_m R_C}{1 + g_m R_E}$$

when compared to the CE amp. (without  $R_E$ ), the open-ckt voltage gain of this amp is reduced by a factor  $(1 + g_m R_E)$


3. For the same non-linear distortion, the i/p signal  $v_i$  can be increased by a factor  $(1 + g_m R_E)$

4. The overall voltage gain is less dependent on  $\beta$

5. The high freq response is significantly improved


6. The reduction in gain by a factor of  $(1 + g_m R_E)$  is due to the  $-ve$  feedback action of  $R_E$ , giving it the name 'emitter degeneration resistance'

# The Common-Base (CB) Amplifier

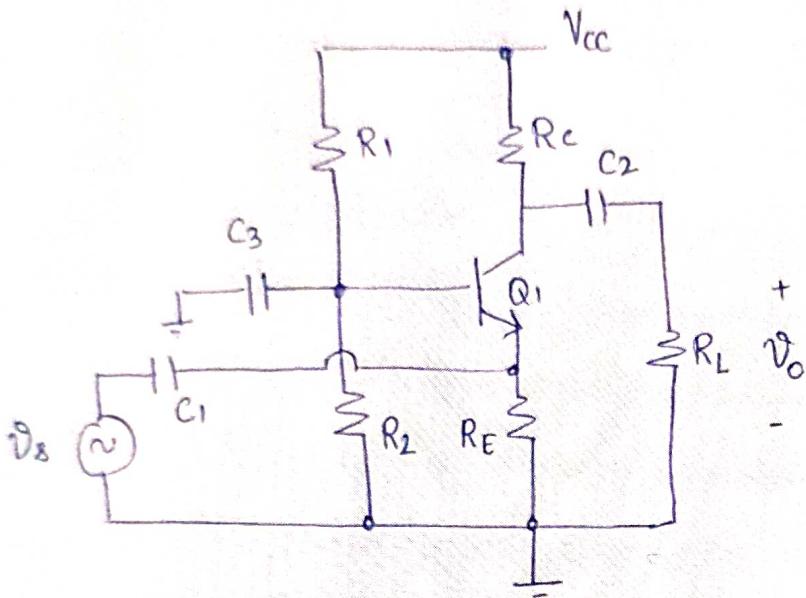


- Ifp signal is applied to the emitter, and the o/p is taken at the collector, with the base forming a common terminal between the input and output ports.
- also called as . grounded-base amplifier.

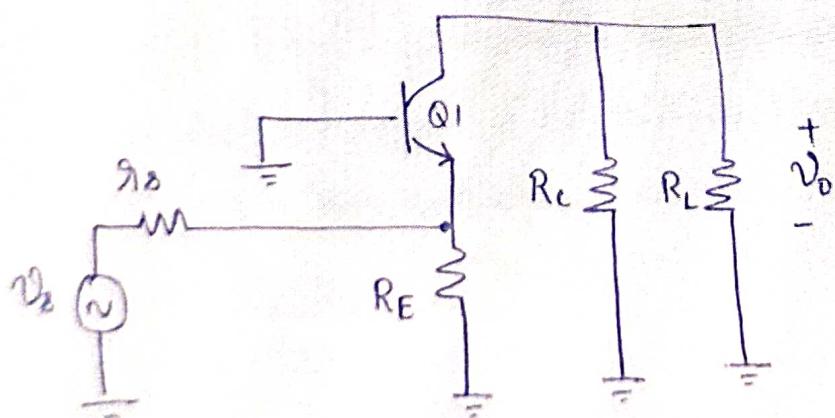The ac equivalent ckt. can be drawn by (i) shorting  $V_{cc}$  to ground, and (ii) shorting all the capacitors (ideal case of  $X_C \approx 0\Omega$  at mid-frequencies).




Since both the dc and ac voltages at the base are zero, the base is directly connected to ground, thus eliminating resistors  $R_1$  and  $R_2$  altogether during ac analysis.

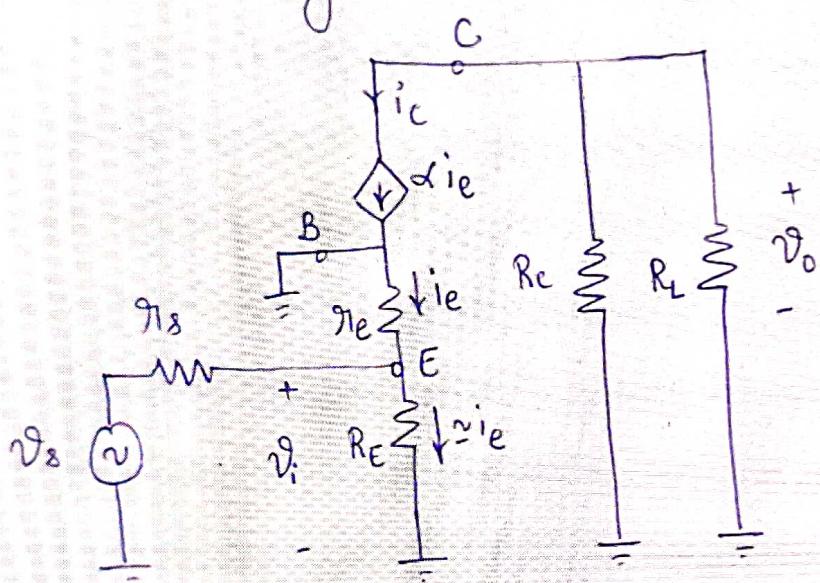Although hybrid- $\pi$  model can be used to perform ac analysis of this amp. ckt, T-model is the most convenient for this type of ckt because  $R_E$  will appear in series with emitter bias  $\eta_E$  of the T-model. In fact, whenever there is resistance in the emitter lead, the T-model should be more convenient to use than the hybrid- $\pi$  model.


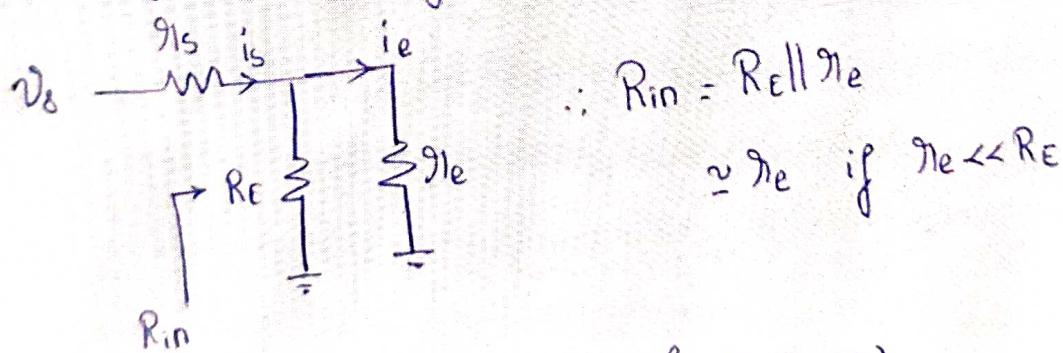
### Input Resistance, $R_{in}$

The i/p part of the small-signal eq. ckt. can be redrawn as




$$\text{Typically, } \eta_E \approx \frac{1}{g_m} = \frac{V_T}{I_C} = \frac{25 \text{ mV}}{1 \text{ mA}} \quad (\text{say for } I_C = 1 \text{ mA}) \\ = 25 \Omega$$

Thus, CB amp. has a low i/p resistance.
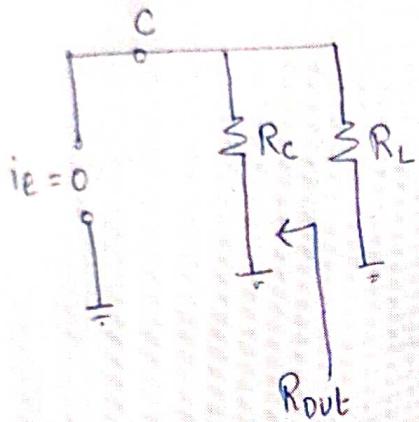
## Output Resistance, $R_{out}$

The  $\text{dc}$  res. can be found by inspection from the ckt. as



$$\therefore R_{out} = R_E \parallel R_L$$

which is similar to the case of  
CE ampr.

## Voltage Gain

$$\begin{aligned} \text{Open-circuit Voltage gain, } A_{vo} &= \frac{V_o}{V_i} \Big|_{R_L=\infty} = \frac{-i_o R_o}{-i_e (\beta \parallel R_E)} \\ &= \frac{\alpha i_e R_c}{i_e (\beta \parallel R_E)} \approx \frac{R_c}{\beta \parallel R_E} \quad \text{as } \alpha \approx 1 \\ &\approx \frac{R_c}{\beta E} \quad \text{if } \beta \ll R_E \\ &= g_m R_c \end{aligned}$$

This is identical to  $A_{vo}$  for the CE ampr. except that the CB ampr is non-inverting.

By taking into account the effect of  $R_L$ , the Voltage gain of the ampr. can be expressed as

$$A_v = A_{vo} \times \frac{R_L}{R_{out} + R_L} = g_m R_c \times \frac{R_L}{R_c + R_L} = g_m (R_c \parallel R_L)$$

(27)

By taking into account the effect of  $r_s$ , the voltage gain of the CB amp can be expressed as

$$A_{vs} = A_v \times \frac{R_{in}}{r_s + R_{in}} \approx g_m(R_{c||R_L}) \times \frac{r_e}{r_s + r_e}$$

$$\approx \frac{R_{c||R_L}}{r_s + r_e} \quad \text{since } g_m \approx \frac{1}{r_e}$$

The overall voltage gain  $A_{vs}$  is simply the ratio of the total resist. in the collector circuit to the total resistance in the emitter circuit. Also, the overall voltage gain is independent of  $\beta$ , which is a desirable property.

### Current gain, $A_{is}$


$$A_{is} = A_{vs} \times \frac{R_{in}}{R_{out}} = \frac{R_{c||R_L}}{r_s + r_e} \times \frac{r_e}{R_{c||R_L}} \approx 1, \text{ but slightly } < 1$$

Because of this property, the CB circuit can be used as a unity-gain current amp. or current buffer. It accepts an i/p signal current at a low o/p resist. and delivers a nearly equal current at a very high o/p resist. at the collector.


The CB amp has excellent high-freq performance, making it useful with other circuits in the implementation of high-freq. amplifiers.
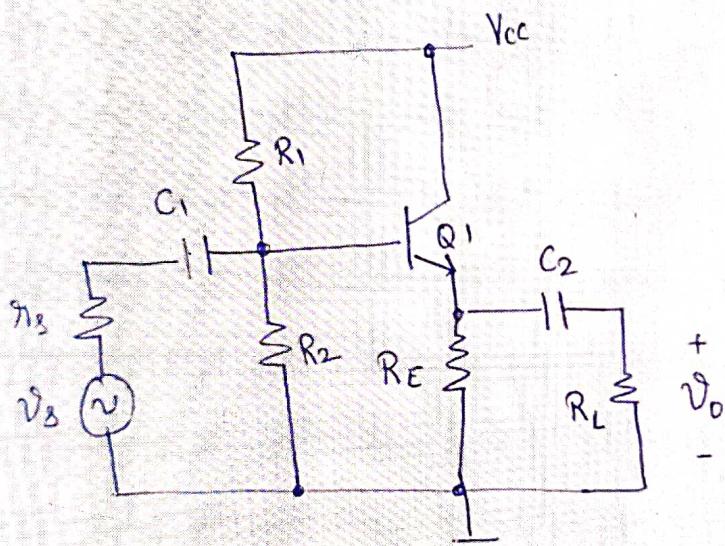
## The Common-Collector (CC) Amplifier

- The i/p signal is capacitively to the base, and the o/p signal is capacitively coupled from the emitter to a load resistor  $R_L$ , with the collector as the common terminal between i/p and o/p ports.
- also called as grounded-collector amps.
- more commonly known as emitter follower, since the voltage at the emitter ( $V_o$ ) follows very closely the voltage at the i/p.




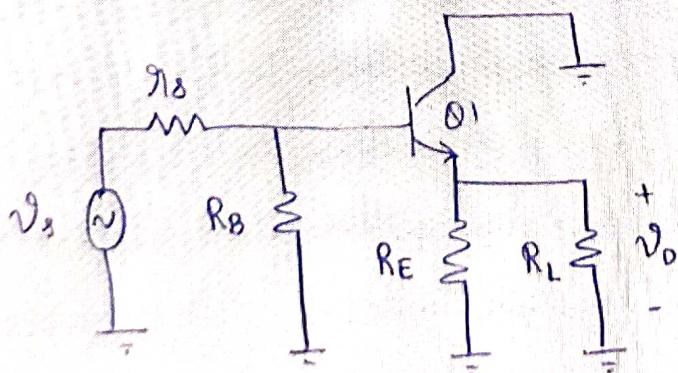The AC equi. ckt. can be drawn as (by making  $V_{cc} = 0 \& X_C \approx 0\Omega$ )



$$\text{where } R_B = R_1 \parallel R_2$$

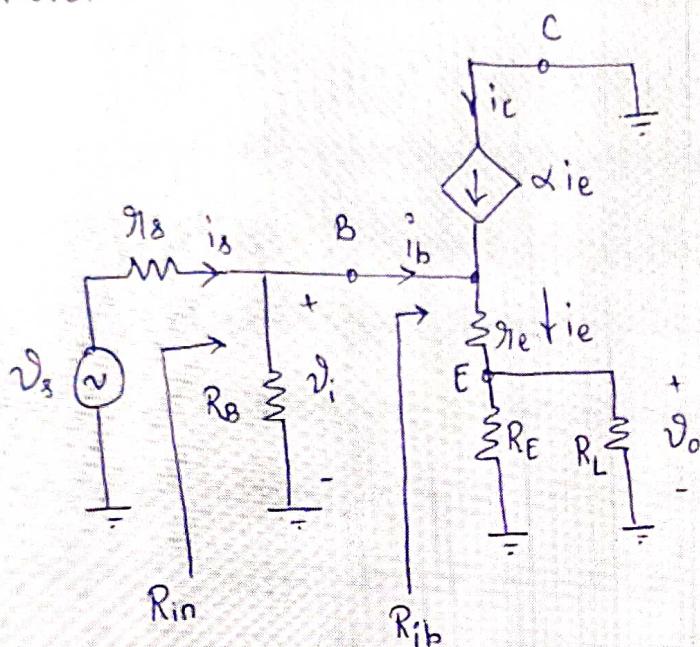Replace the BJT by its T-model to obtain the small-signal equivalent circuit of the emitter follower. T-model is preferred than hybrid- $\pi$  model as the T-model is more convenient to use whenever there is resist. in the emitter lead.



### Input Resistance, \$R\_{in}\$

By investigation of the i/p part of the n/w and applying KVL,

$$\begin{aligned} V_i &= i_e (r_e + R_E \parallel R_L) \\ &= (\beta + 1) i_b (r_e + R_E \parallel R_L) \end{aligned}$$

~~$$\frac{V_i}{i_b} = \beta r_e + R_E \parallel R_L$$~~

$$\begin{aligned} \text{i.e., } \frac{V_i}{i_b} &= R_{ib} = \beta r_e + \beta (R_E \parallel R_L) \quad \text{--- (1)} \\ &= \beta r_e \left( 1 + \frac{R_E \parallel R_L}{r_e} \right) \\ &= r_{\pi} [1 + g_m (R_E \parallel R_L)] \quad \text{--- (2)} \end{aligned}$$


The factor \$(1 + g\_m (R\_E \parallel R\_L))\$ refers to 'amount of -ve feedback introduced by \$R\_E\$'. By the property of -ve f/b, the i/p imp. @ the base (i.e., \$r\_{\pi}\$) is increased by a factor of \$(1 + g\_m (R\_E \parallel R\_L))\$.

## Voltage Gain


$$\text{From eq. ②, } v_i = i_b \times [\lambda_{II} + g_m \lambda_{II} (R_E \parallel R_L)]$$

$$= i_b \times [\lambda_{II} + \beta (R_E \parallel R_L)] \quad - \text{③}$$

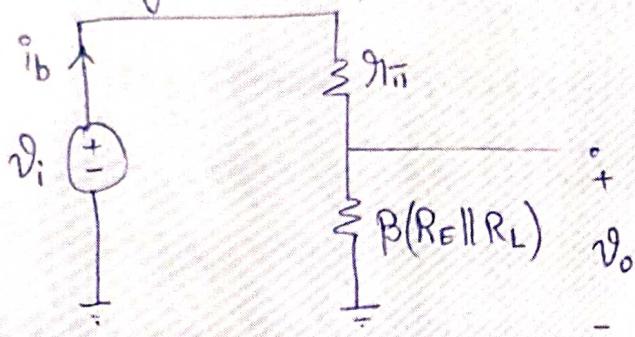The eq. ③ can be synthesized in the circuit form ④




Extending to the i/p part of the amp.,

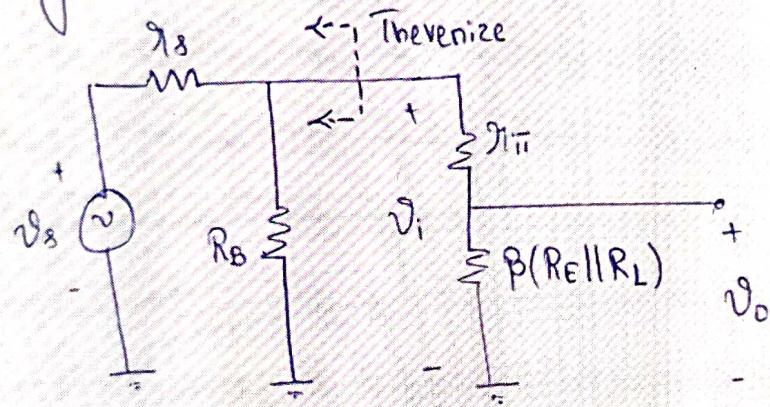

Applying Thevenin's theorem,
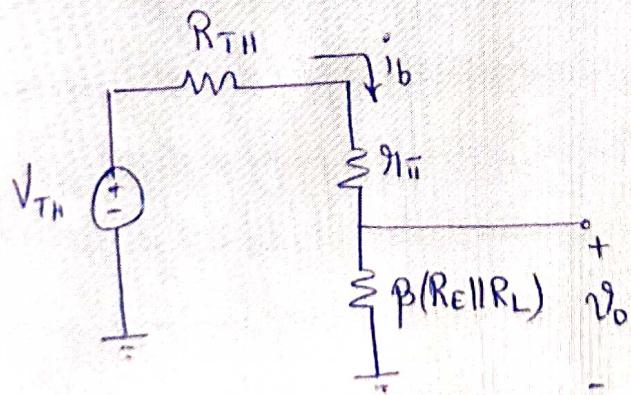
$$V_{TH} = v_s \times \frac{R_B}{g_m \lambda_{II} + R_B} \quad \text{and} \quad R_{TH} = g_m \lambda_{II} \parallel R_B$$



By voltage-divider formula,

$$V_o = \frac{V_{TH} \times \beta (R_E \parallel R_L)}{R_{TH} + g_{\pi} + \beta (R_E \parallel R_L)} = \frac{V_o R_B}{g_s + R_B} \times \frac{\beta (R_E \parallel R_L)}{(g_s \parallel R_B) + g_{\pi} + \beta (R_E \parallel R_L)}$$

$$\text{i.e., } \frac{V_o}{V_i} = A_{vS} = \frac{R_B}{g_s + R_B} \times \frac{\beta (R_E \parallel R_L)}{(g_s \parallel R_B) + g_{\pi} + \beta (R_E \parallel R_L)} \quad \text{--- (4)}$$

where  $A_{vS}$  is called overall voltage gain of the CC amplifier by including the effect of  $g_s$  and  $R_L$ .

If we choose to ignore the effect of  $g_s$ , then

$$A_{vS} \Big|_{g_s=0} = A_v$$

$$A_v = \frac{V_o}{V_i} \Big|_{g_s=0} = 1 \times \frac{\beta (R_E \parallel R_L)}{g_s + g_{\pi} + \beta (R_E \parallel R_L)} = \frac{R_E \parallel R_L}{\frac{g_s}{\beta} + (R_E \parallel R_L)}$$

$$= \frac{R_E \parallel R_L}{\frac{1}{g_m} + (R_E \parallel R_L)} = \frac{g_m (R_E \parallel R_L)}{1 + g_m (R_E \parallel R_L)} \approx 1, \text{ but slightly } < 1 \quad \text{--- (5)}$$


As mentioned earlier, the factor  $(1 + g_m (R_E \parallel R_L))$  refers to the 'amount of -ve fb' introduced by  $R_E$ , and because of this -ve fb, the gain of the ampr. is reduced by a factor of  $(1 + g_m (R_E \parallel R_L))$ .

$A_v \approx 1$  means that the signal at the emitter follows the signal at the base, and hence called as 'emitter follower'.


Because of this property, (ie,  $A_V \approx 1$ ), the ac circuit can be used as a unity-gain voltage amp or voltage buffer. It is useful in connecting a low-res. load to a high-res. source.
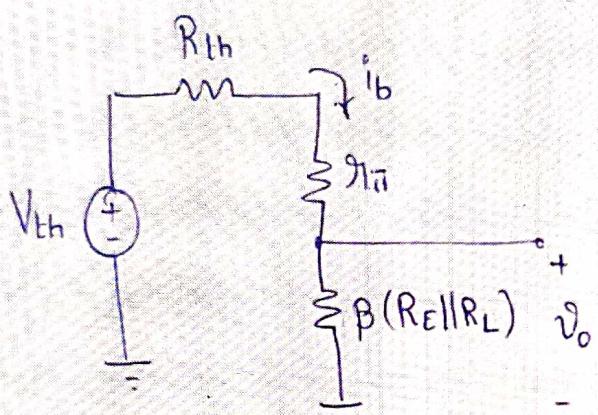
### Output Resistance, $R_{out}$

The circuit obtained in the derivation of Voltage gain of the amp is redrawn here:



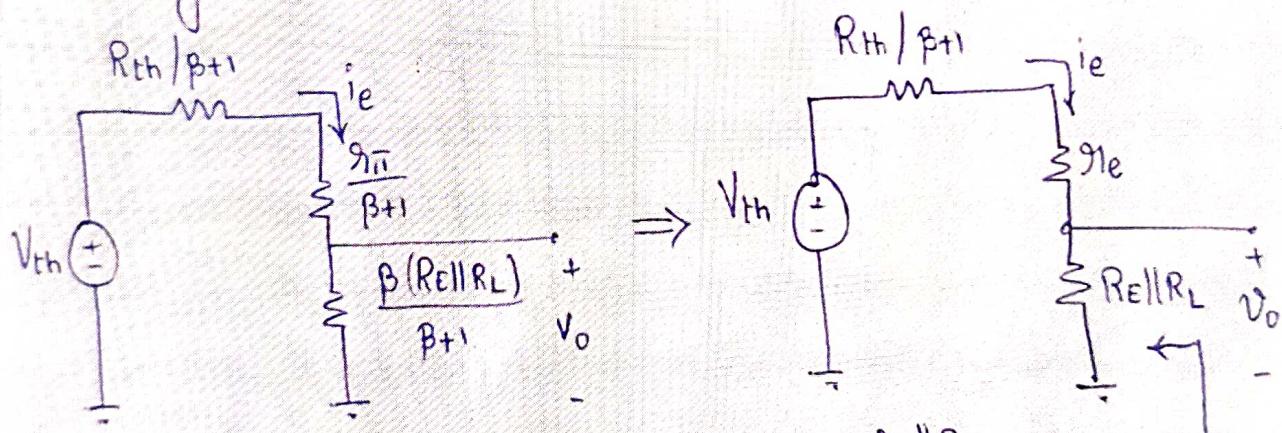Reflecting all base-circuit resistances to the emitter side,



$$R_{out} = (R_{load}) \parallel \left( r_e + \frac{r_s \parallel R_B}{\beta+1} \right) \quad \text{as } R_{th} = r_s \parallel R_B$$

$$\approx r_e + \frac{r_s \parallel R_B}{\beta+1}$$

$$\approx r_e$$

— (6)

$$\text{Typically, } \text{R}_e \approx \frac{1}{g_m} = \frac{V_T}{I_C} = \frac{25 \text{ mV}}{1 \text{ mA}} \quad (\text{say, for } I_C = 1 \text{ mA}) \\ \approx 25 \Omega$$

Thus, the o/p resist. of emitter follower is low, again as a result of its impedance transformation or buffering action, which lead to the division of  $(\text{R}_S \parallel R_B)$  by  $(\beta + 1)$ .

The o/p resist. of the ckt. can also be inferred as follows:

$$R_{\text{out}} = \frac{R_E \parallel R_L}{1 + g_m(R_E \parallel R_L)} \approx \frac{R_E \parallel R_L}{g_m(R_E \parallel R_L)} = \frac{1}{g_m} \approx \text{R}_e$$

i.e., the o/p resist.  $(R_E \parallel R_L)$  is reduced by a factor of  $[1 + g_m(R_E \parallel R_L)]$  due to -ve f/b.

### Current gain, A<sub>is</sub>

$$A_{\text{is}} = A_{\text{vs}} \times \frac{R_{\text{in}}}{R_{\text{out}}} \approx 1 \times \frac{\text{R}_e(1 + g_m(R_E \parallel R_L))}{g_e} = \beta(1 + g_m(R_E \parallel R_L))$$

i.e., the current gain  $\beta$  of the transistor is increased by a factor of  $(1 + g_m(R_E \parallel R_L))$  due to -ve f/b.


— \* —

Unlike the CE and CB circuits, the emitter-follower circuit is unilateral; i.e., the o/p resist. depends on  $R_L$ , and the o/p resist. depends on  $\text{R}_e$ . So, enough care must be taken while characterizing the emitter follower.

# MULTISTAGE AMPLIFIERS

(27)

## CC coupled Two-stage CC amplifier

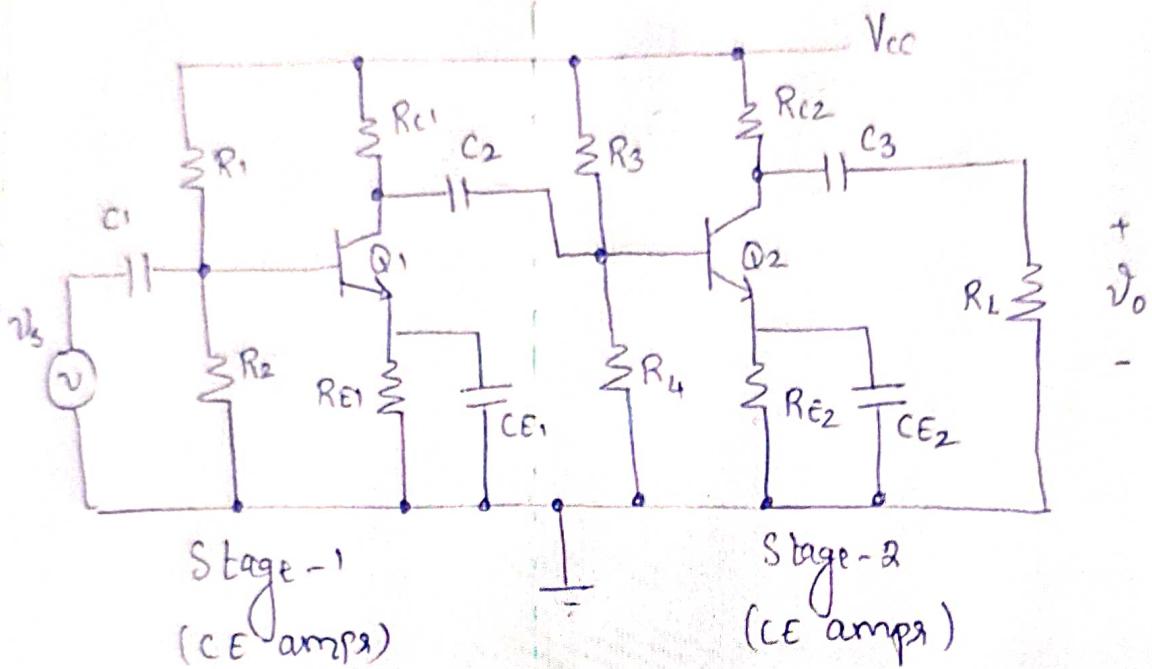


- Stage-1 and Stage-2 are similar to single-stage CE circuit
- Stage-1 is capacitor-coupled (Via  $C_2$ ) to the i/p of Stage-2
- The i/p signal is applied to the i/p of Stage-1 via  $C_1$ , and the load is coupled to the o/p of Stage-2 via  $C_3$ .
- The signal is first amplified by Stage-1, and the o/p of Stage-1 is amplified by Stage-2, so that the overall gain is much larger than the gain of a single-stage circuit.
- The signal is phase shifted by  $180^\circ$  by Stage-1, and then further phase shifted by  $180^\circ$  by Stage-2. Consequently, the overall phase shift of the o/p signal is  $0^\circ$  or  $360^\circ$ .

$$v_o = -v_{o1}$$

$$v_{o1} = -v_i$$

$$v_i = v_i$$

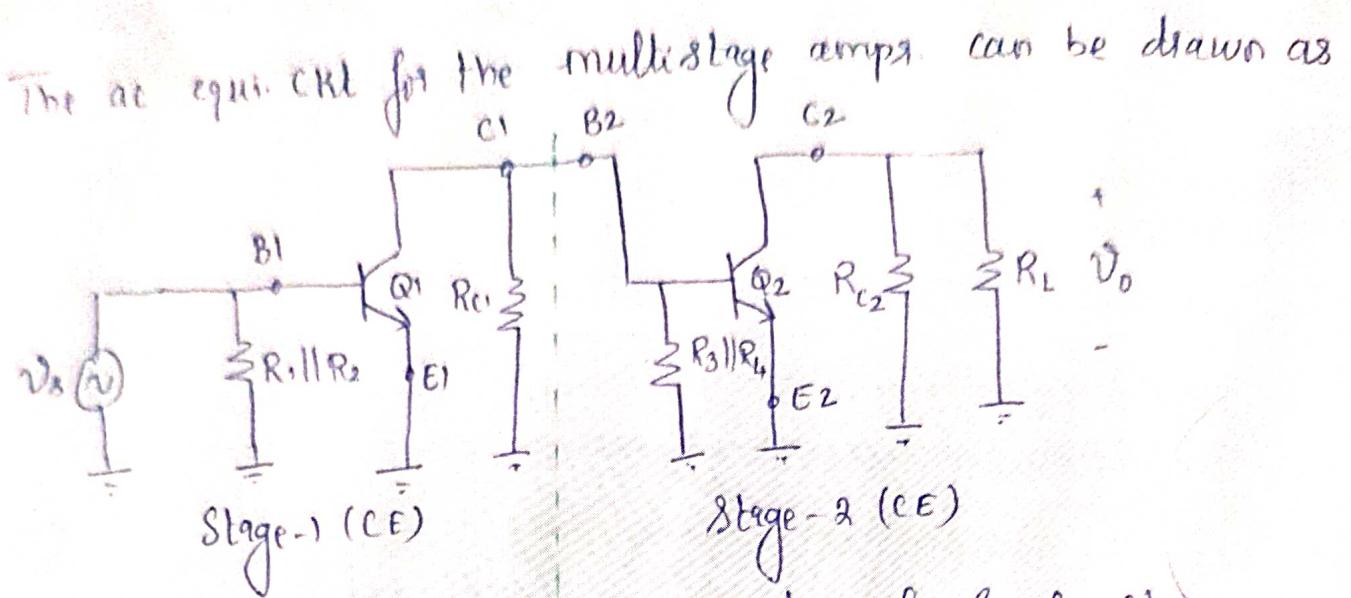

Using the results and discussion done for single-stage circuits, we can summarize the characteristics and parameters of this multistage ampa as :

### Input Resistance, $R_{in}$

$$R_{in1} = R_1 \parallel R_2 \parallel R_{ib1} \quad \text{where } R_{ib1} = g_{\pi}$$

$$R_{in2} = R_{c1} \parallel R_3 \parallel R_4 \parallel R_{ib2} \quad \text{where } R_{ib2} = g_{\pi}$$

### Output Resistance, $R_{out}$

$$R_{out1} = R_{in2}$$

$$R_{out2} = R_{c2} \parallel R_L$$

### Voltage gain

$$\begin{aligned} A_{v1} &= -g_m \times \text{effective resist. @ the collector of stage-1} \\ &= -g_m \times (R_{c1} \parallel R_3 \parallel R_4 \parallel R_{ib2}) \end{aligned}$$

$$A_{V2} = -g_m \times \text{effective resist. @ the collector of Stage-2}$$

$$= -g_m \times (R_{C2} \parallel R_L)$$

$\therefore$  The overall voltage gain of this multistage amp. is

$$A_V = A_{V1} \times A_{V2}$$

$$= g_m^2 \times (R_{C1} \parallel R_3 \parallel R_4 \parallel R_{ib2}) \times (R_{C2} \parallel R_L)$$


Current gain,  $A_i$

$$A_i = A_V \times \frac{R_{in}}{R_{out}}$$

$$= \frac{g_m^2 \times (R_{C1} \parallel R_3 \parallel R_4 \parallel R_{ib2}) (R_{C2} \parallel R_L) \times (R_1 \parallel R_2 \parallel R_{ib1})}{(R_{C2} \parallel R_L)}$$


$$= g_m^2 \times (R_{C1} \parallel R_3 \parallel R_4 \parallel R_{ib2}) (R_1 \parallel R_2 \parallel R_{ib1})$$
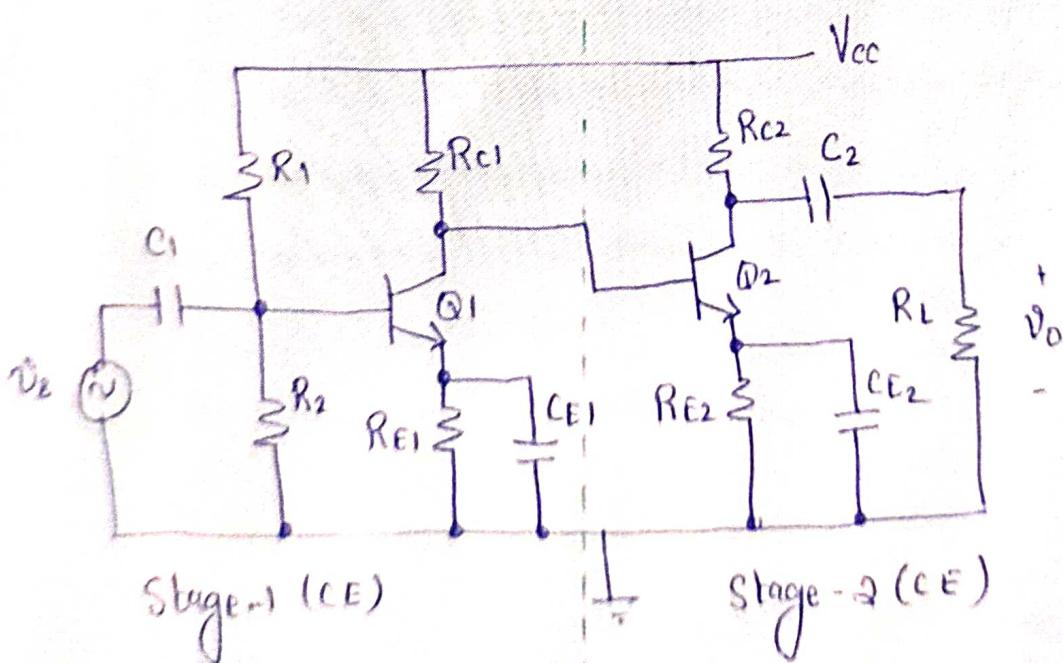
## Q. Direct-Coupled Two-Stage CE amplifier



- Stage-1 o/p is directly connected to stage-2 i/p, thereby eliminating the need for an interstage coupling capacitor and two bias resistors.
- The no. of components used in this ckt. is kept to minimum, and hence economical.

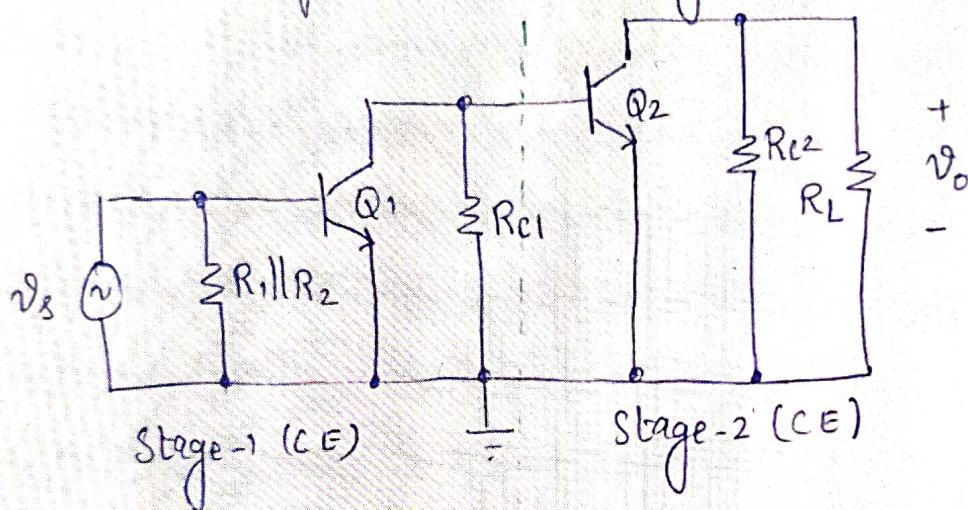The ac equi. ckt. for this multistage ampa. can be drawn as



### Input Resistance, $R_{in}$

$$R_{in1} = R_1 \parallel R_2 \parallel R_{ib1} \quad \text{where } R_{ib1} = \frac{V_T}{I_{C1}}$$

$$R_{in2} = R_{c1} \parallel R_{ib2} \quad \text{where } R_{ib2} = \frac{V_T}{I_{C2}}$$

### Output Resistance, $R_{out}$

$$R_{out1} = R_{in2}$$

$$R_{out2} = R_{c2} \parallel R_L$$

## Voltage Gain, $A_v$

$$A_{v1} = -g_m \times \text{eff. resist at collector of stage-1}$$

$$= -g_m \times (R_{c1} \parallel R_{ib2})$$

$$A_{v2} = -g_m \times \text{eff. resist. at collector of stage-2}$$

$$= -g_m \times (R_{c2} \parallel R_L)$$

$\therefore$  The overall voltage gain of the multistage amp is

$$A_v = A_{v1} \times A_{v2}$$

$$= -g_m (R_{c1} \parallel R_{ib2}) \times -g_m (R_{c2} \parallel R_L)$$

$$= +g_m^2 (R_{c1} \parallel R_{ib2}) (R_{c2} \parallel R_L)$$


## Current Gain, $A_i$

$$A_i = A_v \times \frac{R_{in}}{R_{out}} =$$

$$= \frac{+g_m^2 (R_{c1} \parallel R_{ib2}) (R_{c2} \parallel R_L) \times (R_1 \parallel R_2 \parallel R_{ib1})}{(R_{c2} \parallel R_L)}$$


$$= +g_m^2 (R_{c1} \parallel R_{ib2}) (R_1 \parallel R_2 \parallel R_{ib1})$$
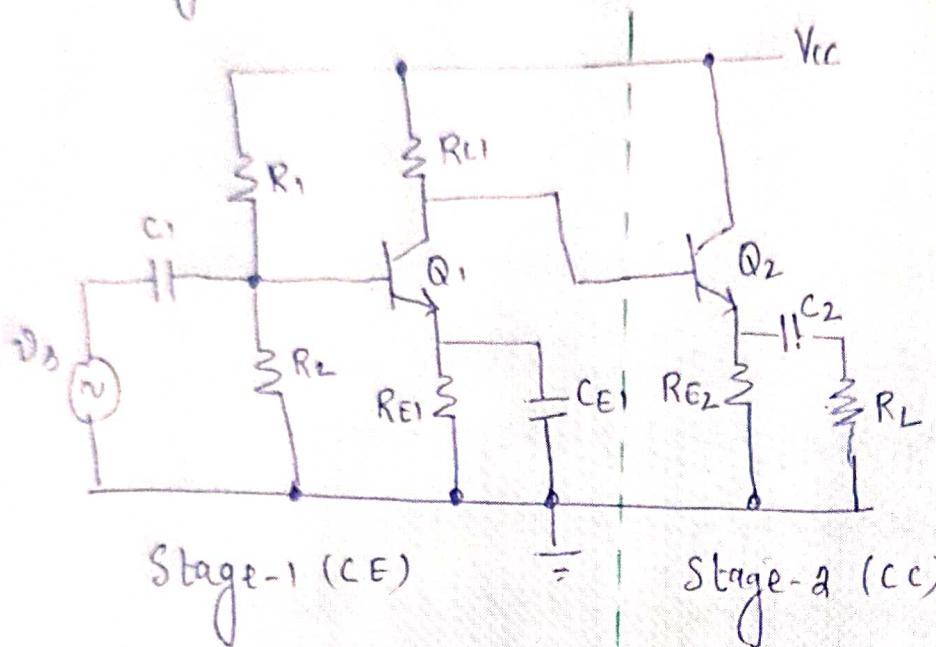
### 3. Two-stage Circuit with Emitter Follower o/p (Direct-coupled)



- Stage-1 is CE circuit, and Stage-2 is CC circuit.
- Stage-2 gives the circuit a very low o/p impedance, but has unity voltage gain.
- Stage-1 still has substantial voltage gain.

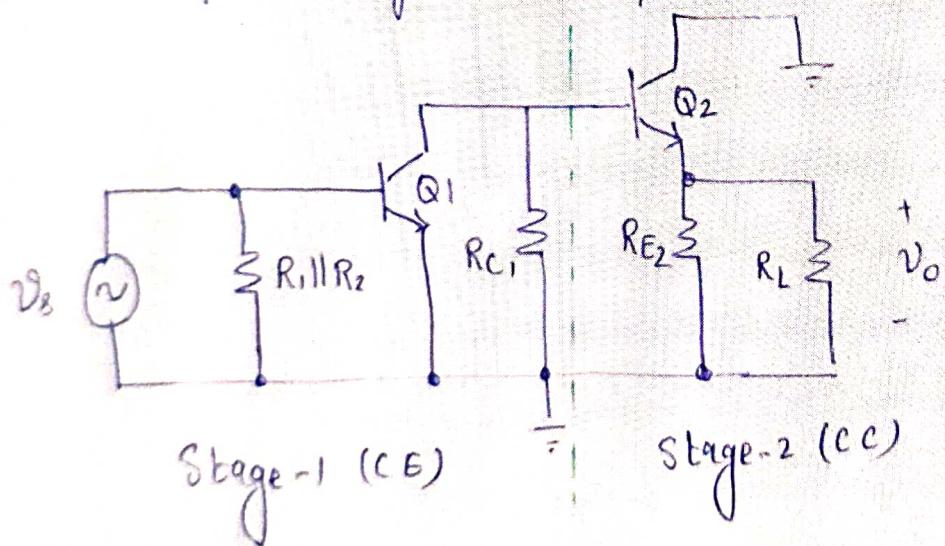The ac equi. ckt. for this ampa can be drawn as



## Input Resistance, $R_{in}$

$$R_{in1} = R_1 \parallel R_2 \parallel R_{ib1} \quad \text{where } R_{ib1} = r_\pi$$

$$R_{in2} = R_{c1} \parallel R_{ib2} \quad \text{where } R_{ib2} = r_\pi (1 + g_m (R_{e1} \parallel R_L))$$

## Output Resistance, $R_{out}$

$$R_{out1} = R_{in2}$$

$$R_{out2} \approx r_e$$

## Voltage Gain, $A_v$

$A_{v1} = -g_m \times \text{eff. resist. @ collector of stage-1}$

$$= -g_m (R_{c1} \parallel R_{ib2})$$

$$A_{v2} \approx 1. \quad (\text{for cc ckt.})$$

$\therefore$  The overall voltage gain is given by

$$A_v = A_{v1} \times A_{v2}$$

$$= -g_m (R_{c1} \parallel R_{ib2})$$

## Current Gain, $A_i$


$$A_i = A_v \times \frac{R_{in}}{R_{out}} = \frac{-g_m (R_{c1} \parallel R_{ib2}) \times (R_1 \parallel R_2 \parallel R_{ib1})}{r_e}$$

$$= -g_m^2 (R_{c1} \parallel R_{ib2}) (R_1 \parallel R_2 \parallel R_{ib1})$$

Since  $r_e \approx \frac{1}{g_m}$
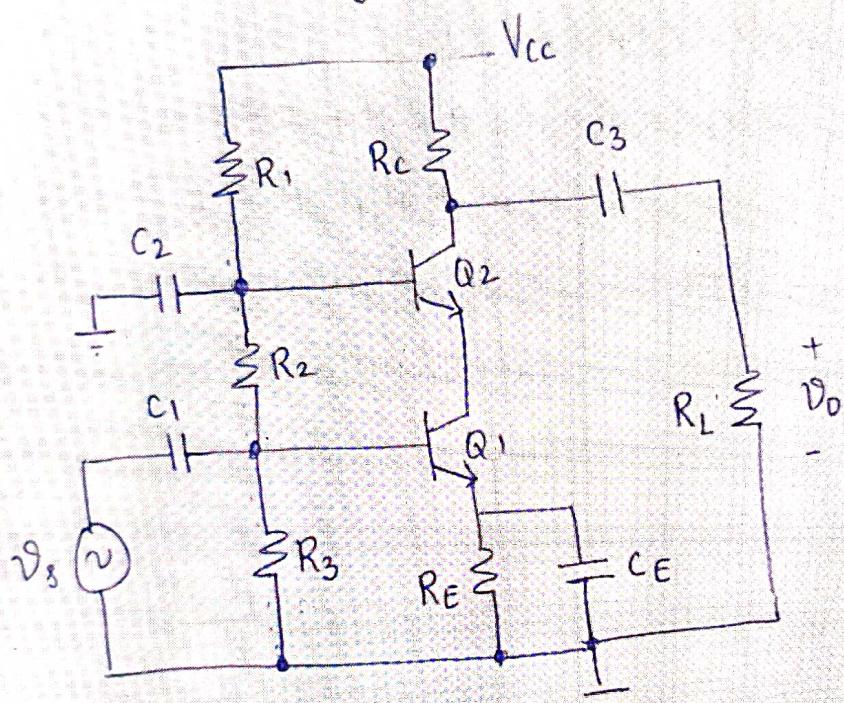
## b. cascode amplifier (CE+CB stages)


- The very low i<sub>OP</sub> impedance of a CB circuit (typically 25Ω) is a major disadvantage.
- To increase the circuit i<sub>OP</sub> impedance while retaining its high freq performance, the cascode amps can be used.
- It uses a CE stage driving a CB stage.



Transistor Q<sub>1</sub> and its associated components operates as a CE stage, while the circuit of Q<sub>2</sub> functions as a CB o/p stage.
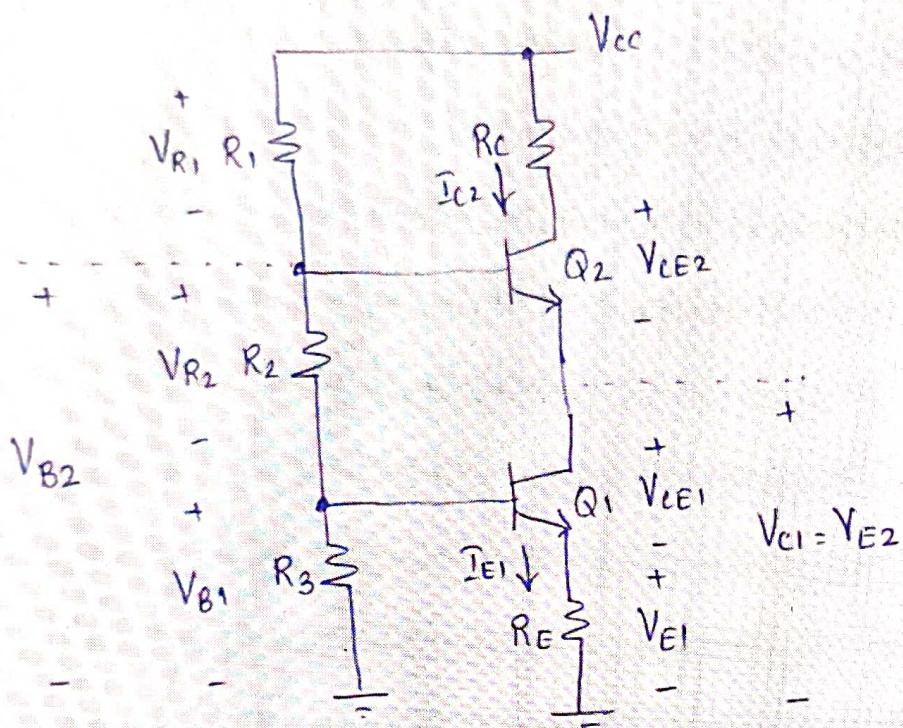
## Dc analysis

The DC equivalent for the cascode amplifier can be obtained by (i) open circuiting all capacitors, and (ii) omitting signal source, ie,  $V_s = 0$ .



The circuit analysis will yield the following results:

$$V_{B1} = V_{cc} \times \frac{R_3}{R_1 + R_2 + R_3}$$

also,  $V_{B1} = V_{BE} + V_{E1}$  using which

$$V_{E1} = V_{B1} - V_{BE}$$

$$I_{E1} R_E = V_{B1} - V_{BE}$$

$$I_{E1} \approx I_{C1} = I_{E2} \approx I_{C2} = \frac{V_{B1} - V_{BE}}{R_E}$$

$$V_{B2} = V_{cc} \times \frac{R_2 + R_3}{R_1 + R_2 + R_3}$$

also,  $V_{B2} = V_{BE} + V_{c1}$  where  $V_{c1} = V_{CE1} + V_{E1}$

$$\text{And, } V_{cc} = I_{C2} R_C + V_{CE2} + V_{CE1} + I_{E1} R_E$$


$$= I_{C2} R_C + 2V_{CE} + I_{C2} R_E \quad (\because V_{CE1} = V_{CE2} = V_{CE})$$

$$\Rightarrow V_{CE} = \frac{V_{cc} - I_{C2}(R_C + R_E)}{2}$$

When the voltage and current levels are selected/determined, the resistor values are easily determined.
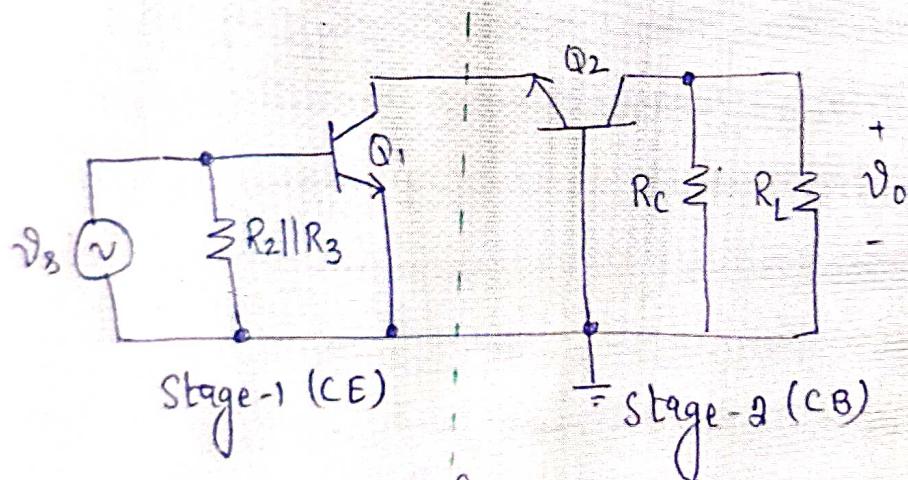
### AC analysis

The AC equivalent circuit of the Cascode amp. can be drawn



Please note that  $R_i$  has no significant effect in the performance of the amplifier circuit.

### Input Resistance, $R_{in}$

$$R_{in1} = R_2 || R_3 || R_{ib1} \quad \text{where } R_{ib1} = \frac{V_t}{I_{C1}}$$

$$R_{in2} \approx R_e$$

Output Resistance,  $R_{out}$

$$R_{out} = R_{in2}$$

$$R_{out2} = R_{c2} \parallel R_L$$

Voltage gain,  $A_v$

$$A_{v1} = -g_m \times \text{eff. resist. @ collector of stage-1}$$

$$= -g_m r_e \approx 1$$

$$A_{v2} = g_m \times \text{eff. resist. @ collector of stage-2}$$

$$= g_m (R_{c2} \parallel R_L)$$

$\therefore$  The overall voltage gain of the amp. is given by

$$A_v = A_{v1} \times A_{v2}$$

$$= g_m (R_{c2} \parallel R_L)$$

Current Gain,  $A_i$

$$A_i = A_v \times \frac{R_{in}}{R_{out}} = \frac{g_m (R_{c2} \parallel R_L) \times (R_2 \parallel R_3 \parallel R_{ib1})}{(R_{c2} \parallel R_L)}$$

$$= g_m (R_2 \parallel R_3 \parallel R_{ib1})$$