
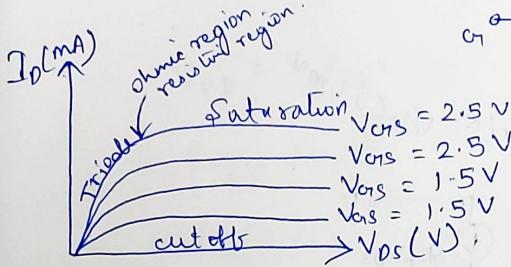
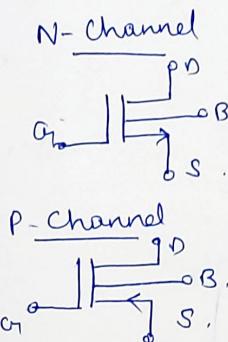


## Unit - II

### FET Amplifiers :-

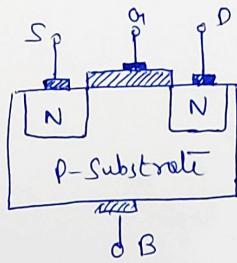

Cut off  
 $I_d = 0$

Triode Region

$$I_d = K_n (2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2)$$

for  $V_{DS} < V_{GS} - V_{TH}$



$$K_n = \frac{W H_n C_{ox}}{2L}$$

### MOSFET

Depletion type  
(Normally ON)

Enhancement Saturation Region.  
(Normally OFF)
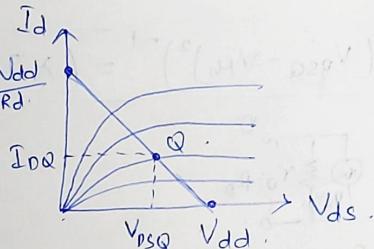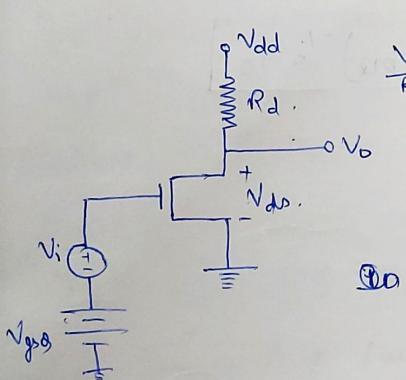
$$I_d = K_n (V_{GS} - V_{TH})^2 \text{ for } V_{DS} \geq V_{GS} - V_{TH}$$



In Saturation Region

$$I_d = K_n (V_{GS} - V_{TH})^2 \text{ for } V_{DS} \geq V_{GS} - V_{TH}$$

$$V_{TH} = V_{TN}$$

In triode Region.

$$I_d = K_n (2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2) \text{ for } V_{DS} < V_{GS} - V_{TH}$$

$$K_n = \frac{\mu_n C_{ox}}{2L} \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \rightarrow \text{permittivity}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \rightarrow \text{thickness}$$

$$g_m = \frac{I_d}{V_{GS}} = 2 K_n (V_{GSQ} - V_{TN}) \text{ (small signal equiv)}$$

From saturated current expression


$$(V_{gs} - V_{th})^2 = \frac{i_{DQ}}{K_n}$$

$$V_{gs} - V_{th} = \sqrt{\frac{i_{DQ}}{K_n}}$$

$$g_m = 2 K_n \sqrt{\frac{i_{DQ}}{K_n}}$$

$$\boxed{g_m = 2 \sqrt{K_n i_{DQ}}}$$

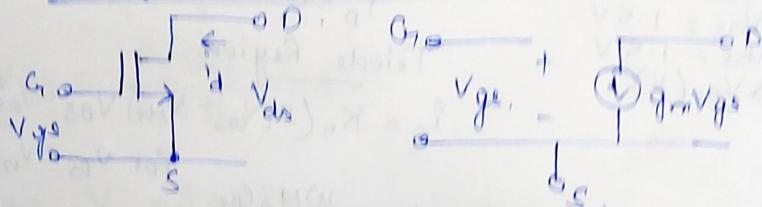(Small signal equivalent circuit with  $V_{ds}$ )




With channel length modulation effect


$$i_D = K_n [(V_{gs} - V_{th})^2 (1 + \lambda V_{ds})] \quad [\lambda = \text{channel length modulation factor}]$$

$$\gamma_0 = \left( \frac{\partial i_D}{\partial V_{ds}} \right)^{-1}$$
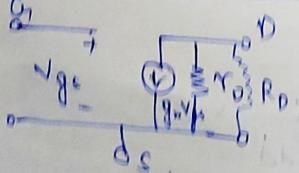
$$\therefore \boxed{\gamma_D = (\lambda K_n (V_{gs} - V_{th})^2)^{-1} = (\lambda I_{DQ})^{-1} = \gamma_0}$$




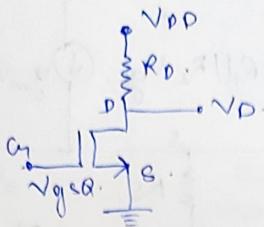Q) Find the load line and D point for a MOSFET circuit having  
 $V_{OSQ} = 2.12 \text{ V}$ ,  $V_{DD} = 5 \text{ V}$ ,  $R_D = 2.5 \text{ k}\Omega$ ,  $V_{tn} = 1 \text{ V}$ ,  $K_n = 0.80 \text{ mA/V}^2$



$$V_{DD} = I_D R_D + V_{DS}$$
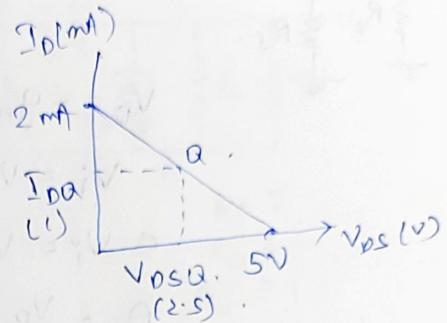
$$\begin{aligned} I_{DQ} &= K_n (V_{GSQ} - V_{tn})^2 \\ &= 0.80 (2.12 - 1)^2 \\ &= 0.8 (1.12)^2 \\ &= 1 \text{ mA} \end{aligned}$$



$$V_{DSQ} = V_{DD} - I_{DQ} R_D = 5 - 1(2.5) = 2.5 \text{ V}$$

Cut off pt

$$I_D = 0$$



$$V_{DD} = V_{DS} = 5 \text{ V}$$

Saturation pt.

$$V_{DS} = 0$$

$$I_D = \frac{V_{DD}}{R_D} = \frac{5}{2.5} = 2 \text{ mA}$$

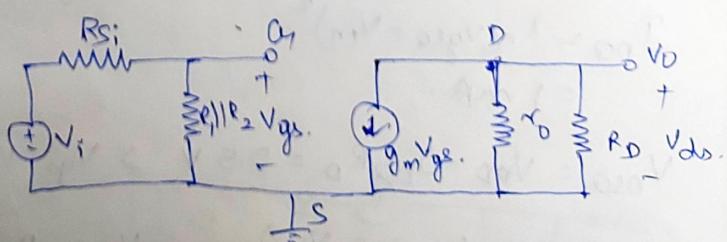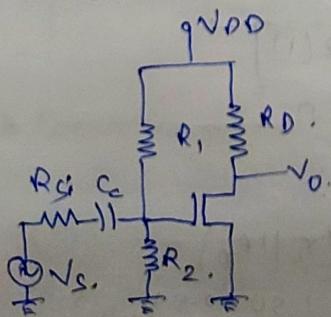Common Source Amp - (with bypass cap) ( $R_S$  x consider)  
without ( $R_S$  ✓ consider)





$$V_O = -g_m V_{GS} (r_o) R_D$$

$$V_{GS} = V_i \frac{R_1 || R_2}{(R_1 || R_2) + R_S}$$

$$A_V = \frac{V_O}{V_i} = -g_m (r_o || R_D) \left( \frac{R_1 || R_2}{R_S + R_1 || R_2} \right)$$

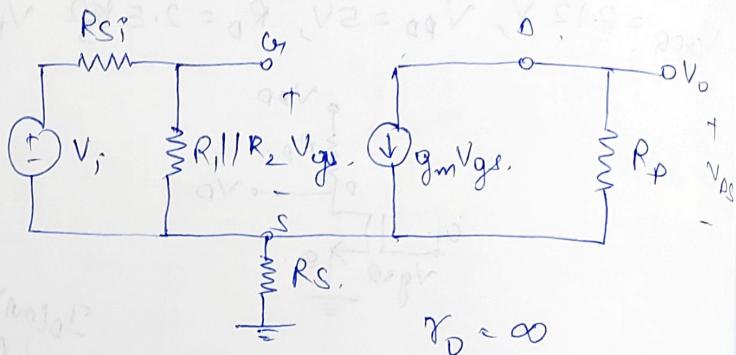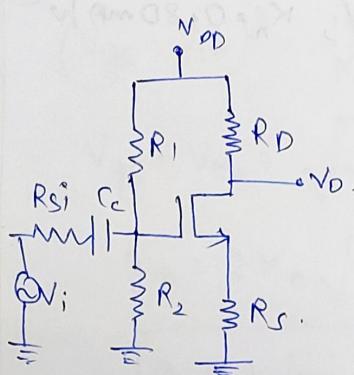► Common Source (without  $R_s$  / with  $R_s$ )



$$V_D = -g_m V_{gs} R_D$$

$$V_i = V_{gs} + g_m V_{gs} R_s$$

$$\Rightarrow V_i = V_{gs}(1 + g_m R_s)$$


$$A_v = \frac{V_o}{V_i} = \frac{-g_m V_{gs} R_D}{V_{gs}(1 + g_m R_s)}$$

$$= \frac{-g_m R_D}{1 + g_m R_s}$$

If  $g_m R_s \gg 1$

$$A_v = -\frac{R_D}{R_s}$$

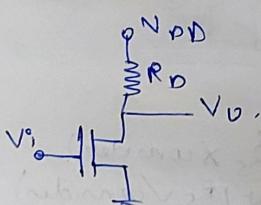Q) Find small  $A_v$  of MOSFET Amp.  $V_{gsQ} = 2.12 V$ ,  $V_{DD} = 5V$ ,  $R_D = 2.5 k\Omega$ ,  $V_{tn} = 1V$ ,  $K_n = 0.80 \text{ mA/V}^2$ ,  $\lambda = 0.02 \text{ V}^{-1}$  operate in saturation.



$$I_{DQ} = K_n (V_{gsQ} - V_{tn})^2$$

$$= 1 \text{ mA}$$

$$V_{DSQ} = V_{DD} - I_{DQ} R_D = 2.5 V > V_{gs} - V_{tn}$$

$$g_m = 2 K_n (V_{gsQ} - V_{tn})$$

$$= 2(0.80)(2.12 - 1)$$

$$= 1.6 \times 1.12$$

$$= 1.79 \text{ mA}$$

$$V_D = -g_m V_{gsQ} R_D$$

$$V_i = V_{gsQ} + g_m V_{gsQ}$$

$$r_o = (\lambda I_{DQ})^{-1}$$

$$= [0.02(1)]^{-1}$$

$$= 50 k\Omega$$



$$V_o = -g_m V_{gsQ} (r_o || R_D)$$

$$= -1.79 \times 2.12 \left( \frac{50 \times 2.5}{52.5} \right) \times 10^3$$

$$A_v = \frac{V_o}{V_{gs}} = -g_m (r_o || R_D) = -1.79 \times \frac{50 \times 2.5}{52.5} \times 10^3$$

$$= -4.26$$

## ► Source Follower! - (CD)

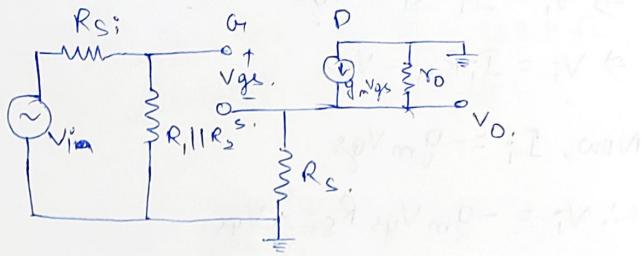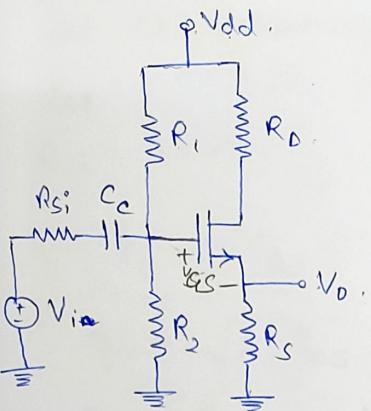

$$V_O = g_m V_{GS} (r_D || R_S)$$

$$\therefore V_{in} = V_{GS} + V_O$$

$$= V_{GS} + g_m V_{GS} (r_D || R_S)$$

$$\Rightarrow V_{GS} = \frac{V_{in}}{1 + g_m (r_D || R_S)}$$

$$V_{in} = \frac{V_i R_i}{R_i + R_{Si}} \quad [R_i = R_1 || R_2]$$

$$V_{GS} (1 + g_m (r_D || R_S)) = \frac{V_i R_i}{R_i + R_{Si}}$$



$$\Rightarrow V_i = \frac{V_{GS} [1 + g_m (r_D || R_S)] (R_i + R_{Si})}{R_i}$$

$$\therefore A_V = \frac{V_O}{V_i} = \frac{g_m V_{GS} (r_D || R_S) R_i}{V_{GS} [1 + g_m (r_D || R_S)] (R_i + R_{Si})}$$

$$\Rightarrow A_V = \frac{g_m (r_D || R_S) R_i}{[1 + g_m (r_D || R_S)] (R_i + R_{Si})} \quad \begin{cases} g_m (r_D || R_S) \gg 1 \\ R_{Si} \ll R_i \end{cases}$$

$\therefore A_V \approx 1$

## ► Common gate

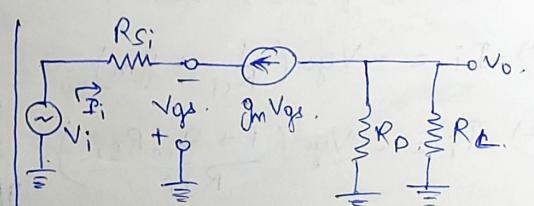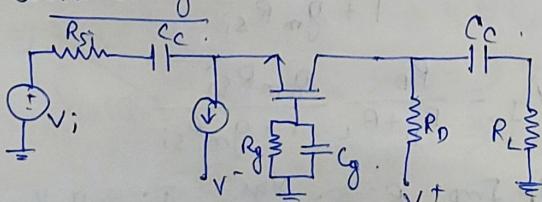

$$V_O = -g_m V_{GS} (R_D || R_L)$$

$$V_i - I_i R_{Si} - (-V_{GS}) = 0$$

P.T.O

$$\Rightarrow V_i - I_i R_{si} + V_{gs} = 0$$

$$\Rightarrow V_i = I_i R_{si} - V_{gs}$$

$$\text{Now, } I_i = -g_m V_{gs}$$

$$\therefore V_i = -g_m V_{gs} R_{si} - V_{gs}$$

$$\Rightarrow V_i = -V_{gs}(1 + g_m R_{si})$$

$$\Rightarrow -V_i = V_{gs}(1 + g_m R_{si})$$


$$\Rightarrow V_{gs} = \frac{-V_i}{1 + g_m R_{si}}$$

$$\therefore A_V = \frac{V_o}{V_i} = \frac{-g_m V_{gs}(R_D || R_L)}{-g_m R_{si} + 1) V_{gs}}$$

$$\Rightarrow A_V = \boxed{\frac{g_m(R_D || R_L)}{1 + g_m R_{si}}}$$

Using Norton's equiv. ckt.

To find  $A_I$

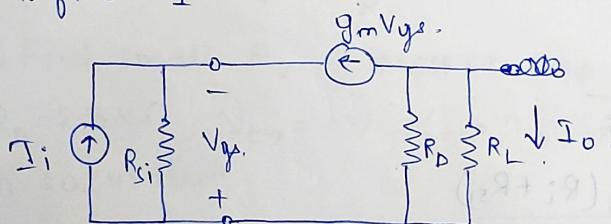

$$I_o = -g_m V_{gs} \left( \frac{R_D}{R_D + R_L} \right) \left( \frac{R_D}{R_D + R_L} \right)$$

At i/P KCL,

$$I_i - \left( \frac{V_{gs}}{R_{si}} \right) - \left( g_m V_{gs} \right) = 0$$

$$A_I = \frac{R_D}{R_D + R_L} \frac{g_m V_{gs}}{R_{si}}$$

$$\Rightarrow I_i + \frac{V_{gs}}{R_{si}} + g_m V_{gs} = 0$$

$$A_I = \frac{g_m (R_D + R_L) R_{si}}{1 + g_m R_{si}}$$

$$\Rightarrow I_i = -\frac{V_{gs}}{R_{si}} - g_m V_{gs}$$

$$A_I = \frac{R_D}{R_D + R_L} \frac{g_m R_{si}}{1 + g_m R_{si}}$$

$$\Rightarrow I_i = -V_{gs} \left( \frac{1}{R_{si}} + g_m \right)$$

$$\underline{\text{O/P Imp. }} R_i = -\frac{V_{gs}}{I_i}, I_i = -g_m V_{gs}$$

$$\Rightarrow I_i = -V_{gs} \left( \frac{1 + g_m R_{si}}{R_{si}} \right)$$

$$\underline{\text{O/P Imp. }} R_o = R_D$$

(Q) Calculate the small signal voltage gain of source follower.  
 Ckt. ckt. parameters are  $V_{DD} = 12V$ ,  $R_1 = 162 k\Omega$ ,  $R_2 = 463 k\Omega$ ,  
 $R_{SD} = 0.75 k\Omega$ ,  $V_{TH} = 1.5V$ ,  $K_n = 4 \text{ mA/V}^2$ ,  $\lambda = 0.01 \text{ V}^{-1}$ ,  
 $R_{SI} = 4 k\Omega$ .

$$r_o = (\lambda I_{DQ})^{-1}$$

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$I_{DQ} = K_n (V_{GS} - V_{TH})^2$$

$$g_m = 2 K_n (V_{GS} - V_{TH})$$

$$V_{OQA} = \frac{V_{DD} R_2}{R_1 + R_2}$$

$$= \frac{12 \times 463}{162 + 463}$$

$$\approx 8.88 \text{ V}$$

$$V_{OD} = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$I_{DQ} = 4(8.88 - 1.5)^2 \text{ mA} + g_m V = V_{GS} = V_{GS} + I_D R_S$$

$$= 217.8 \text{ mA}$$

$$= 0.217 \text{ A}$$

$$I_D = K_n (V_{GS} - V_{TH})^2$$

$$V_{GS} = V_{GS} + K_n (V_{GS} - V_{TH})^2 R_S$$

$$r_o = (\lambda I_{DQ})^{-1}$$

$$V_{GS} = V_{GS} + K_n (V_{GS}^2 + V_{TH}^2 - 2V_{GS}V_{TH}) R_S$$

$$= (0.01 \times 0.217)^{-1}$$

$$= 460.8$$

$$V_{GS} = \frac{463 \times 12}{463 + 162} \approx 8.89$$

$$V_{GS} = V_{GS} + K_n V_{GS}^2 R_S + K_n V_{TH}^2 R_S - 2K_n R_S V_{GS} V_{TH}$$

$$8.89 = V_{GS} + 4 \times 0.75 V_{GS}^2 + 16 \times 1.5 \times 1.5 \times 0.75 - 2 \times 4 \times 0.75 V_{GS}$$

$$\Rightarrow 8.89 - 16 \times 1.5 \times 1.5 \times 0.75 = V_{GS} [1 - (2 \times 4 \times 0.75) + (4 \times 0.75) V_{GS}] \times 1.5$$

$$\Rightarrow 8.89 - 27 = V_{GS} [(1 - 6) + 6 V_{GS}]$$

$$\Rightarrow -18.11 = V_{GS} [-5 + 6 V_{GS}]$$

$$\Rightarrow -18.11 = -V_{GS} (5 - 6 V_{GS})$$

$$\Rightarrow V_{GS} = 4.37$$

$$\Rightarrow 4.5 V_{GS} = (18.11 - 5)$$

$$V_{GSQ} = \frac{1}{2} (4.37) = 2.185 \Rightarrow 4.5 V_{GS} = -13.11$$

$$5 \pm \sqrt{4 \times 3 \times 2.14} = \frac{5 \pm 5.06}{6}$$

$$\Rightarrow V_{GS} = 2.91$$



$$= \frac{5 \pm \sqrt{4 \times 4.5 \times 18.11}}{2 \times 4.5} = \frac{5 \pm 18.05}{9}$$

$$= \frac{5 + \sqrt{325.98}}{9} = \frac{20}{9} = 2.22$$

$$= \frac{5 - \sqrt{325.98}}{9} = \frac{-5}{9} = -0.56$$

Q) For common gate amplifier determine  $V_o$ , if  $I_{DQ} = 1 \text{ mA}$ ,  
 $V^+ = 5V$ ,  $V^- = -5V$ ,  $R_g = 100K\Omega$ ,  $R_D = 4K\Omega$ ,  $R_L = 10K\Omega$ ,  $V_{th} = 1V$   
 $K_n = 1 \text{ mA/V}^2$ ,  $\lambda = 0$ ,  $R_s = 50K\Omega$ ,  $I_i = 100 \sin \omega t \text{ nA}$ .

### ► Frequency Response of CS amp.

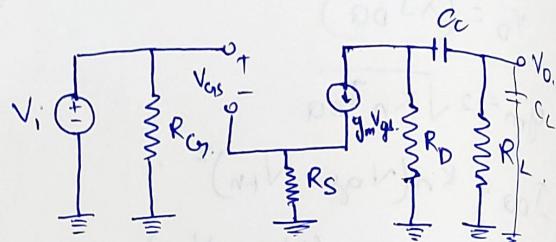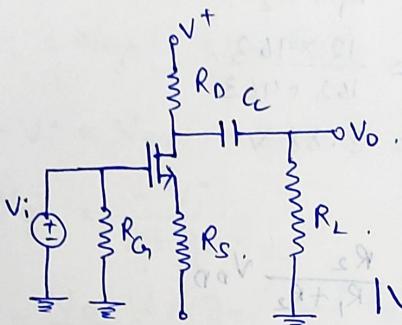

$$|V_{olmax}| = g_m V_{gs} (R_D || R_L)$$

$$-2g_m V_s + 2g_m V = V_i = V_{gs} + g_m V_{gs} R_s$$

$$2g_m (V - 2g_m V) \approx |AV|_{max} = \frac{|V_{olmax}|}{|V_{ilmax}|}$$

$$2g_m (V - 2g_m V) \approx V + 2g_m V = R_s V$$


$$2g_m (V - 2g_m V) \approx V + 2g_m V = R_s V = \frac{g_m V_{gs} (R_D || R_L)}{V_{gs} (1 + g_m R_s)}$$

$$2g_m V_{ilmax} + 2g_m V_{olmax} \approx |AV|_{max} = \frac{g_m (R_D || R_L)}{1 + g_m R_s}$$

$$T_s = (R_D + R_L) C_C \cdot f_L = \frac{1}{2\pi T_s}$$

$$T_p = (R_D + R_L) C_L$$

### ► High Frequency Response:

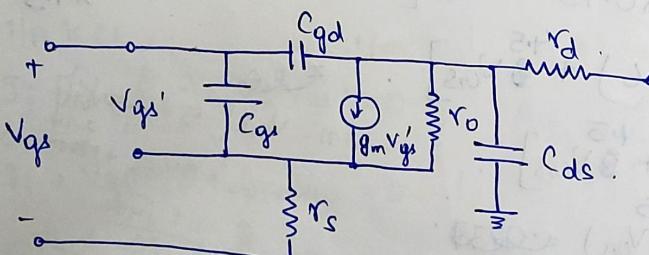

$$I_d = g_m V_{gs}'$$

$$V_{gs} = V_{gs}' + (g_m V_{gs}') R_s$$


$$\therefore V_{gs} = (1 + g_m R_s) V_{gs}'$$

$$\Rightarrow V_{gs}' = \frac{V_{gs}}{1 + g_m R_s}$$

$$\therefore I_d = g_m \left( \frac{V_{gs}}{1 + g_m R_s} \right)$$

$$= \left( \frac{g_m}{1 + g_m R_s} \right) V_{gs}' = g_m' V_{gs}'$$

## Short circuit current gain :-

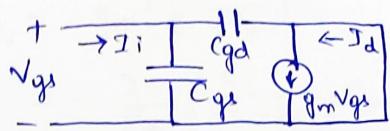

At input node, KCL.

$$I_i = \frac{V_{gs}}{1/j\omega C_{gs}} + \frac{V_{gs}}{1/j\omega C_{gd}}$$

$$= V_{gs} [j\omega(C_{gs} + C_{gd})]$$

At output node, KCL.

$$\frac{V_{gs}}{1/j\omega C_{gd}} + I_d = g_m V_{gs}$$

$$\Rightarrow V_{gs} j\omega C_{gd} + I_d = g_m V_{gs}$$

$$\Rightarrow I_d = V_{gs} (g_m - j\omega C_{gd})$$

$$I_i = \frac{I_d}{V_{gs}} \frac{j\omega(C_{gs} + C_{gd})}{g_m - j\omega C_{gd}}$$

$$\Rightarrow I_i = \frac{I_d [j\omega(C_{gs} + C_{gd})]}{g_m - j\omega C_{gd}}$$


$$\therefore A_I = \frac{I_d}{I_{0i}} = \frac{g_m - j\omega C_{gd}}{j\omega(C_{gs} + C_{gd})} \quad \text{where } \omega C_{gd} \ll g_m.$$

$$= \frac{g_m}{j\omega(C_{gs} + C_{gd})} = \frac{g_m}{j^2 \pi f T (C_{gs} + C_{gd})} = \frac{1}{j(f/f_T)}$$

$$\text{where } f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

If we consider miller capacitance,

$$C_m = C_{gd}(1 + g_m R_L)$$

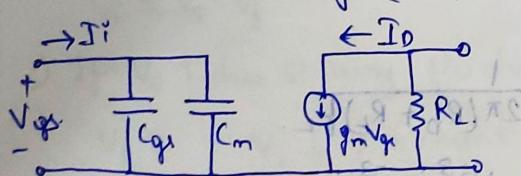



$$I_i = \frac{V_{gs}}{1/j\omega C_{gs}} + \frac{V_{gs}}{1/j\omega C_m}$$

$$I_i = V_{gs} j\omega(C_{gs} + C_m)$$

$$I_D = g_m V_{gs}$$

$$\therefore A_I = \frac{I_D}{I_i} = \frac{g_m V_{gs}}{V_{gs} j\omega(C_{gs} + C_m)} = \frac{g_m}{j\omega(C_{gs} + C_m)} = \frac{g_m}{2\pi f \omega(C_{gs} + C_m)}$$

## Bi FET Amp.

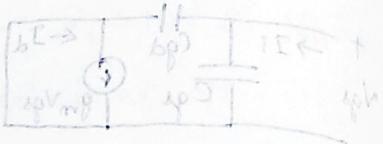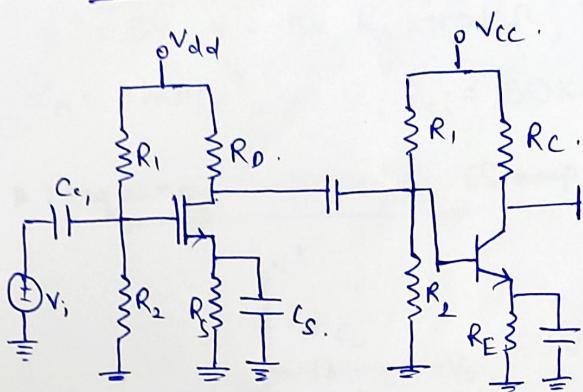

BiFET,  $A_v$  is less than 2 BJT.

It is preferred over BJT because BJT has  $\beta = bI + \frac{2pV}{bp\omega_i}$

1) Larger space

2) High Power consumption

3) Noisier

4) Speed ↑

$$f_{mf} = bI + bp\omega_i \frac{2pV}{bp} \ll$$

$$(bp\omega_i - m\beta) \frac{2pV}{bp} = bI \ll$$

It is preferred over MOSFET, because MOSFET has

$$(bp + 2p\beta) \omega_i \frac{2pV}{bp} bI = \beta I$$

$$(bp\omega_i - m\beta) \frac{2pV}{bp} \ll$$


$$\frac{(bp + 2p\beta) \omega_i bI}{bp\omega_i - m\beta} = \beta I \ll$$

5) Speed ↓

$$m\beta \gg bp\omega_i$$

$$\frac{bp\omega_i - m\beta}{(bp + 2p\beta) \omega_i} = \frac{\beta I}{\beta \omega_i} = IA$$

(Q)

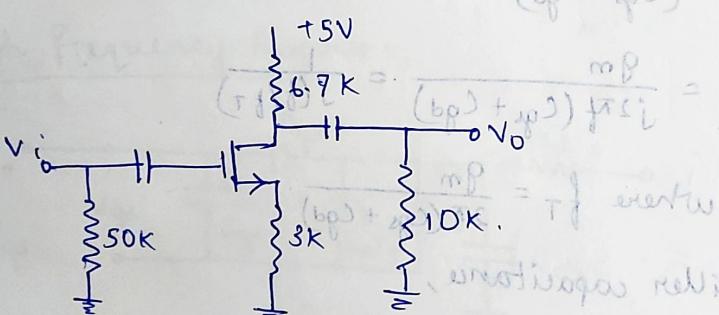

Find  $C_c$  if  $f_{TL} = 20 \text{ kHz}$ .

$$f_L = \frac{2\pi C_s}{2\pi f_{TL}}$$

$$f_L = \frac{(m + 2p\beta) \omega_i}{(m + 2p\beta) \omega_i} \frac{2pV}{bp} = \frac{1}{2\pi} \frac{1}{R_D + R_L} C_s$$

$$(4m\beta + 1) \frac{2pV}{bp} = m$$

$$C_s = \frac{1}{2\pi (R_D + R_L) f_{TL}} = \frac{10^3 \times 10^{-8}}{2 \times 3.14 \times 16.7 \times 20} \text{ F}$$

$$\frac{m\beta}{(m + 2p\beta) \omega_i} = \frac{m\beta}{(m + 2p\beta) \omega_i} = 0.00476 \times 10^{-8} = 4.76 \mu\text{A}$$

$$= 0.0048 \text{ nF}$$