

# ECE 261 Project Presentation 2

## 8-bit Booth Multiplier


Eric Wang  
Federico Gonzalez  
Bryan Flemming  
Jep Barbour

# Abstract

The purpose of this project is to create a 8 by 8 multiplier using Booth's multiplication algorithm. The 8-bit multiplicand and 8-bit multiplier are input signals into four Booth encoders/selectors. After applying Booth's algorithm to the inputs, simple addition is done to produce a final output.


Our main goal is to produce a working 8 by 8 bit multiplier with correct simulations and layout while attempting to maximize the speed in which the multiplier performs the calculation.

# Schematic Block Diagram



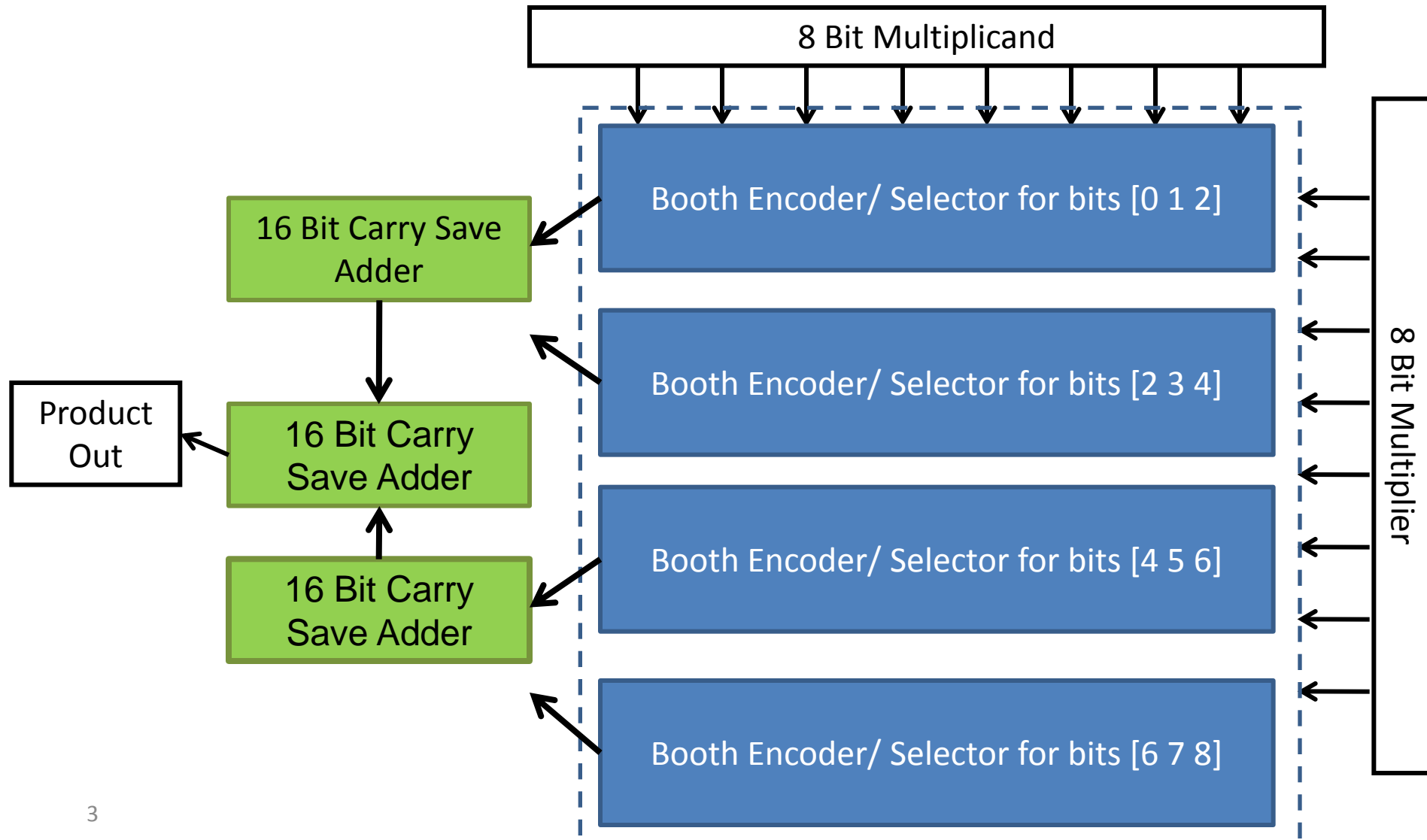


# Booth Encoder


## Schematic

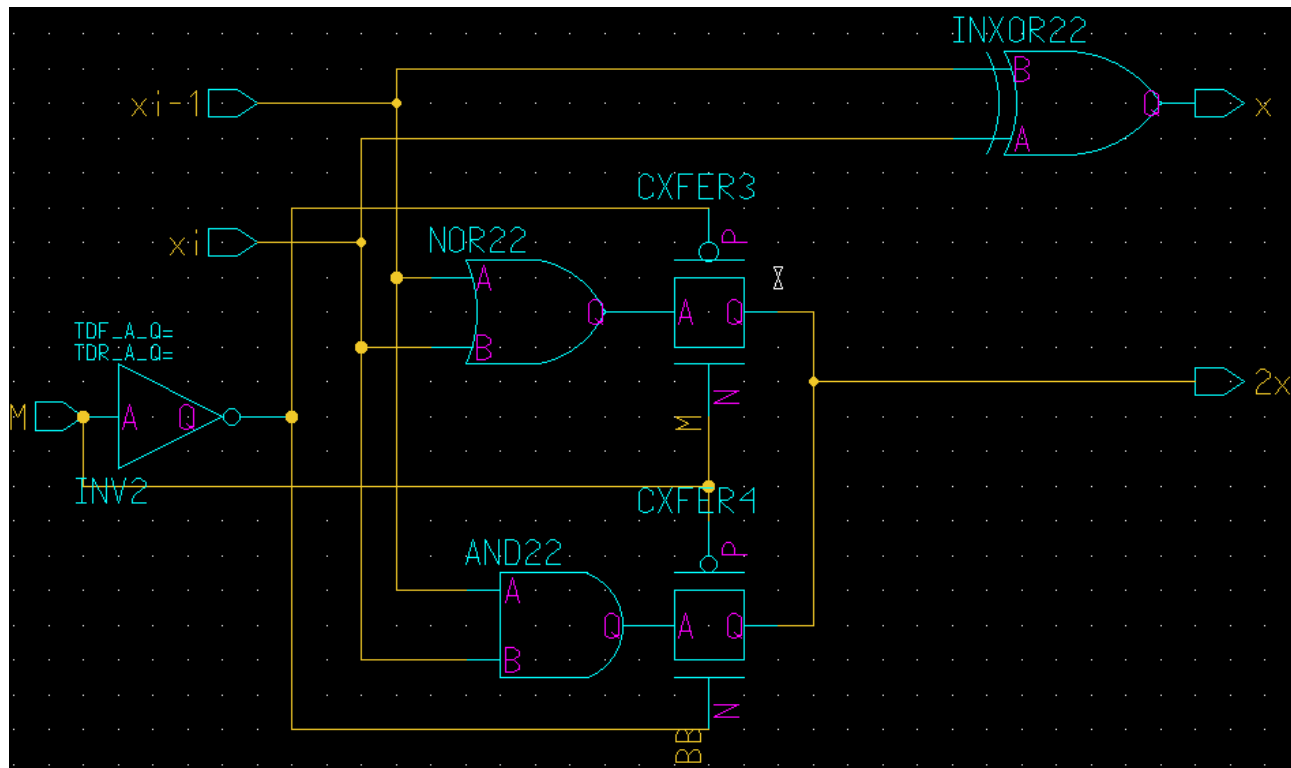


# Booth Encoder

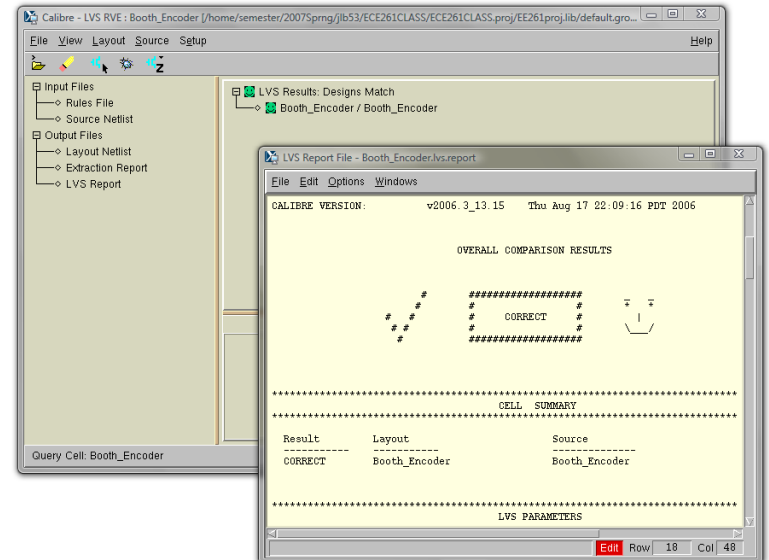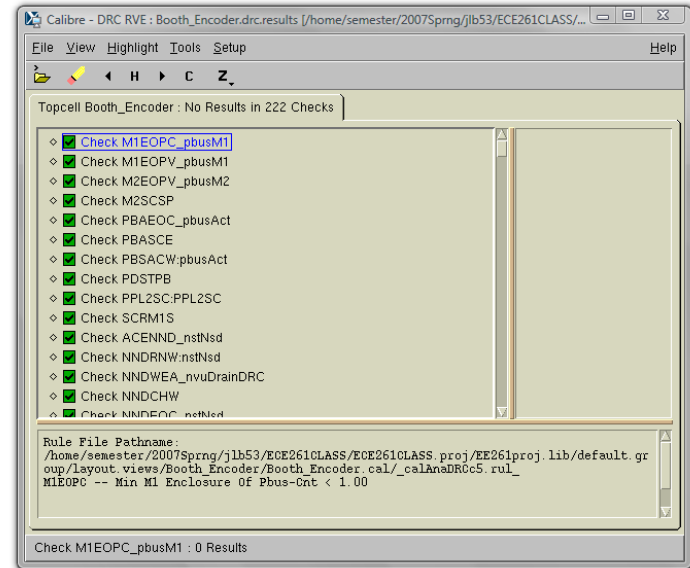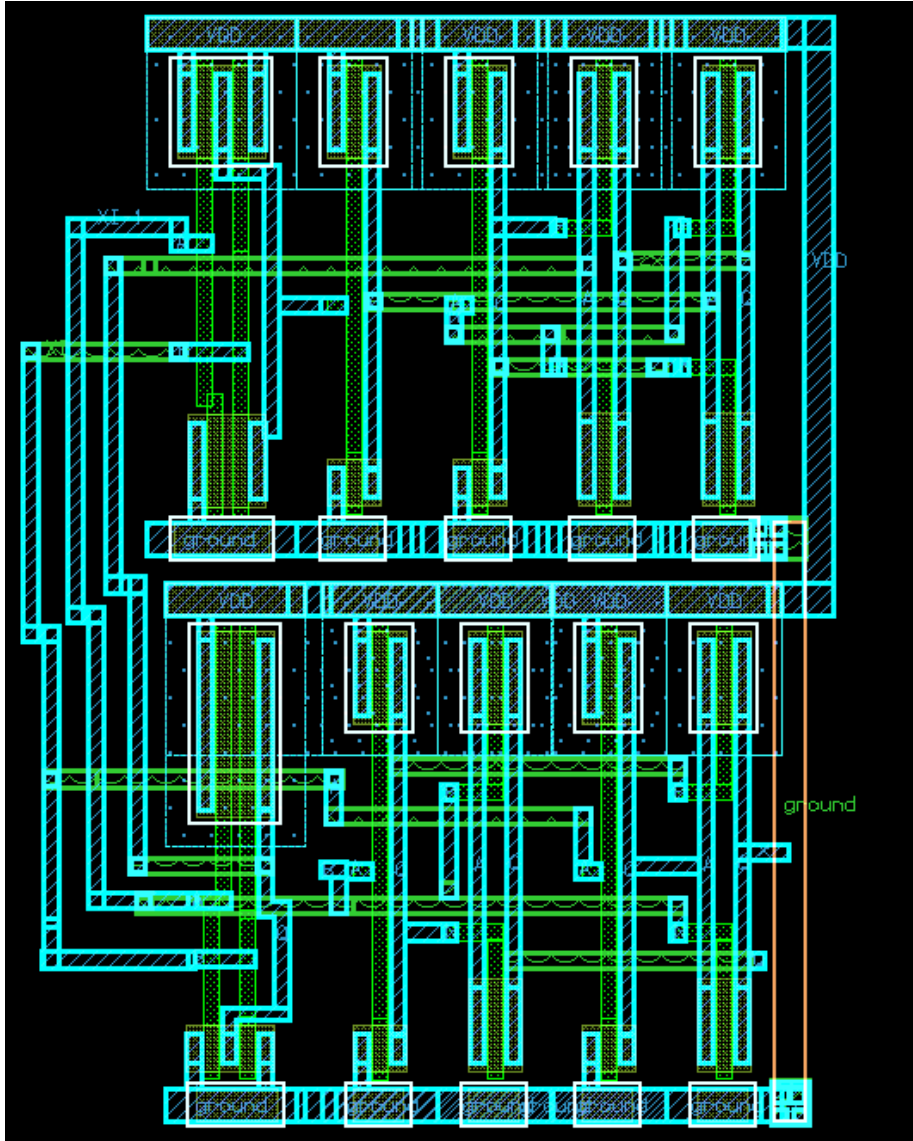

# Booth Decoder Schematic

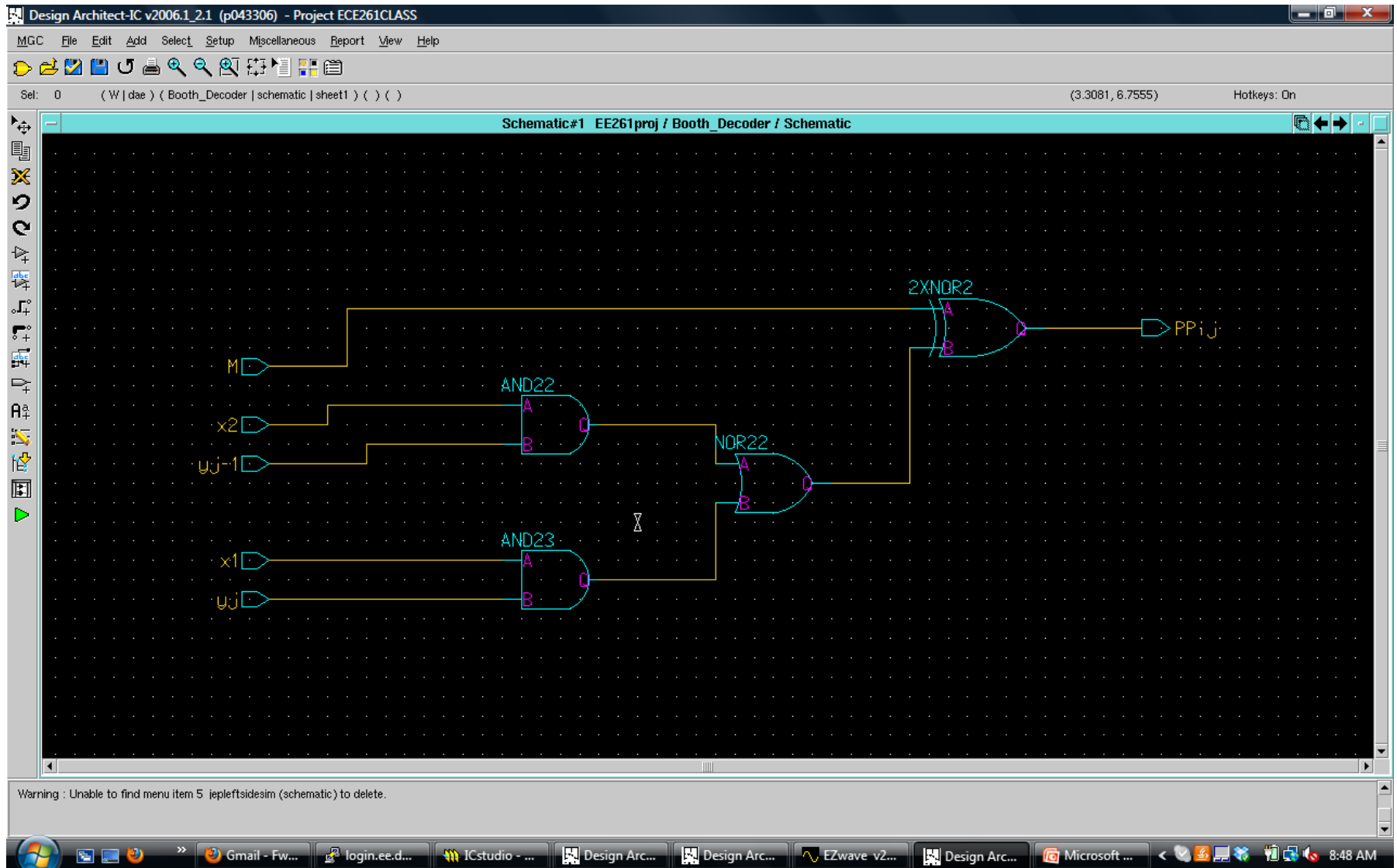


# Booth Decoder Layout

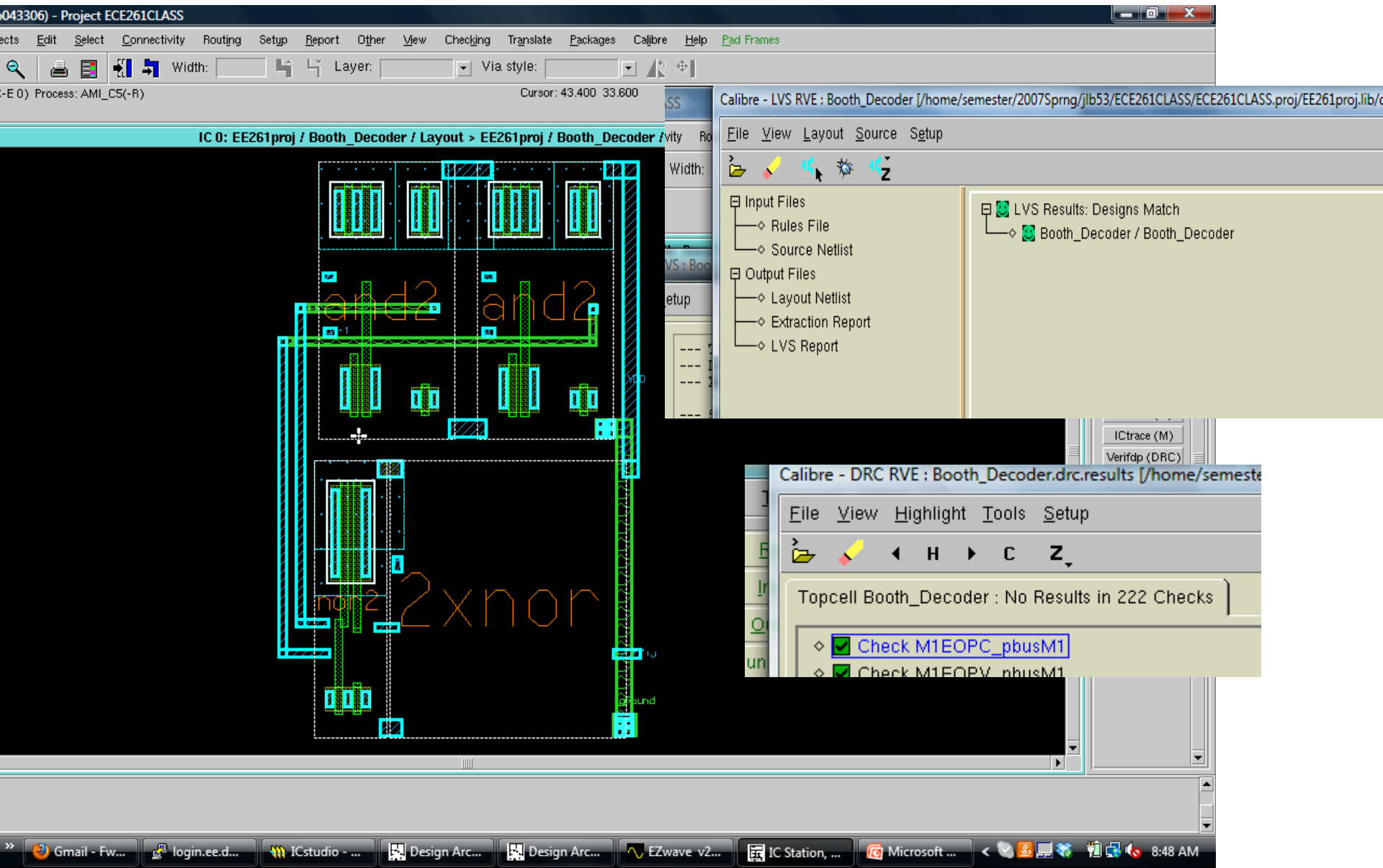




# Partial product generator

## Schematic




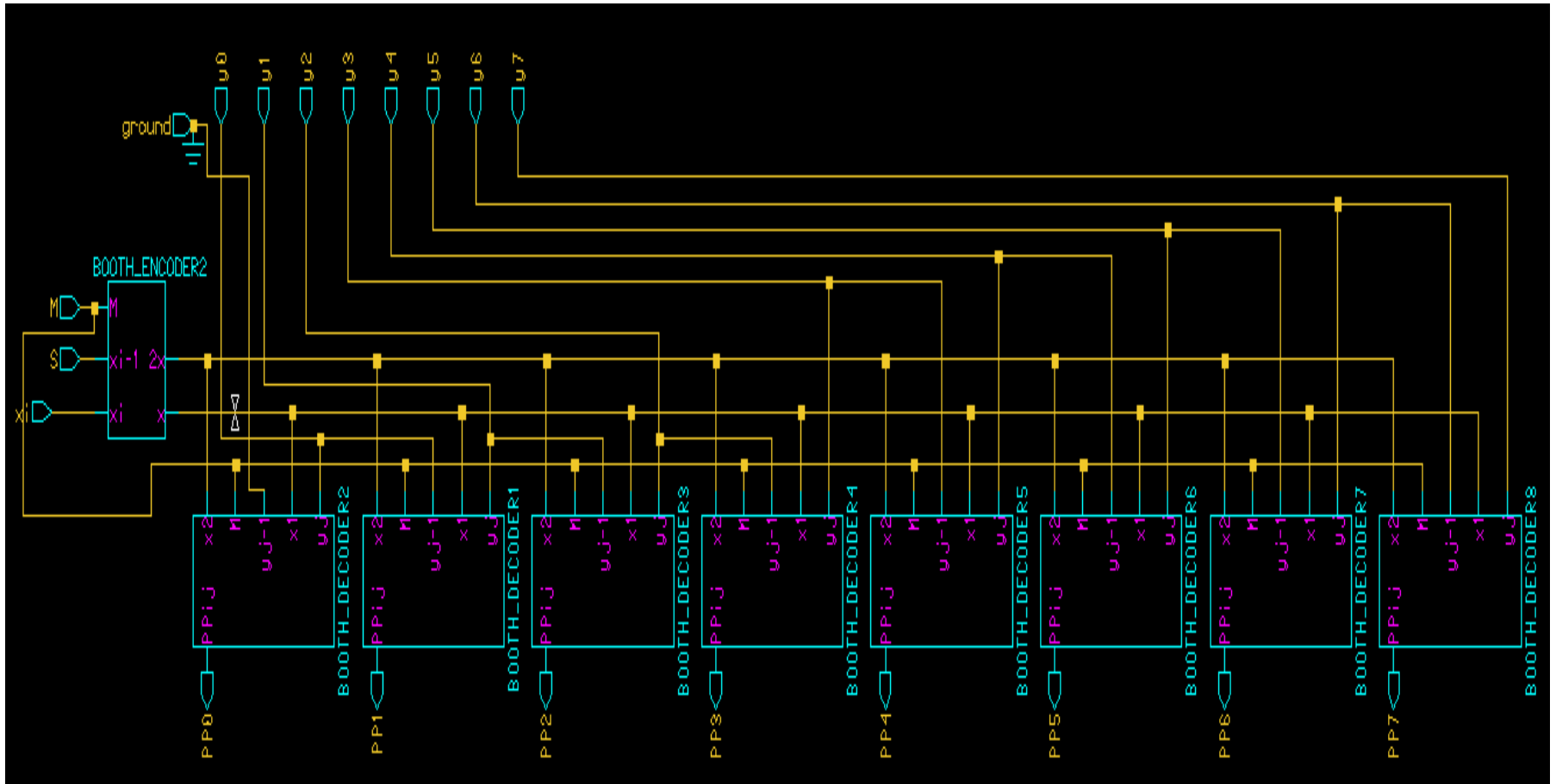





# Partial product generator

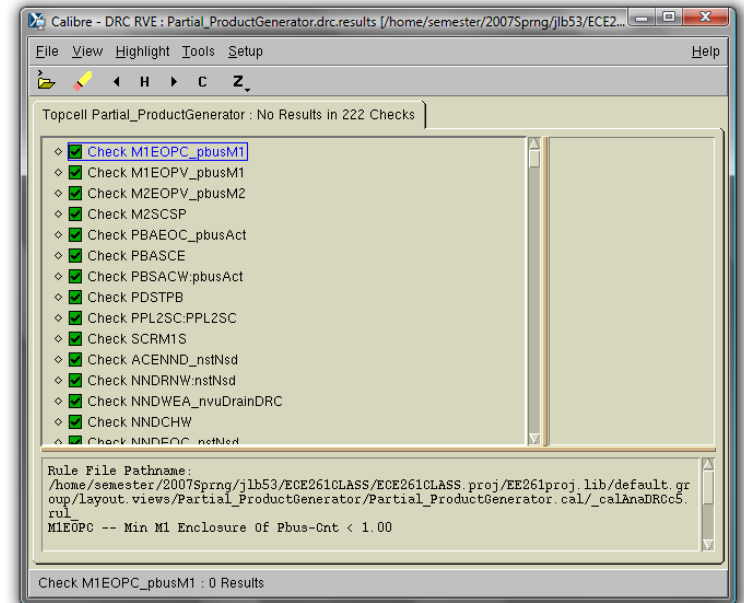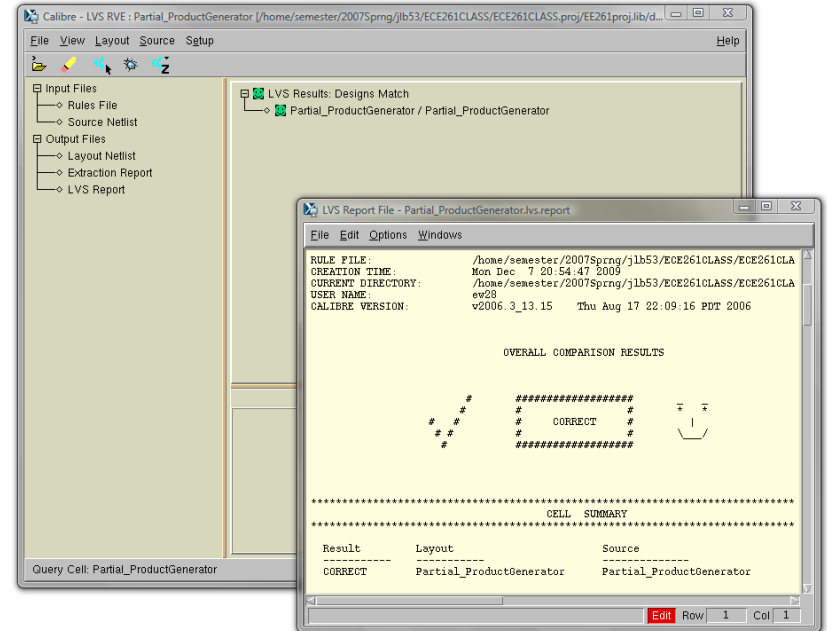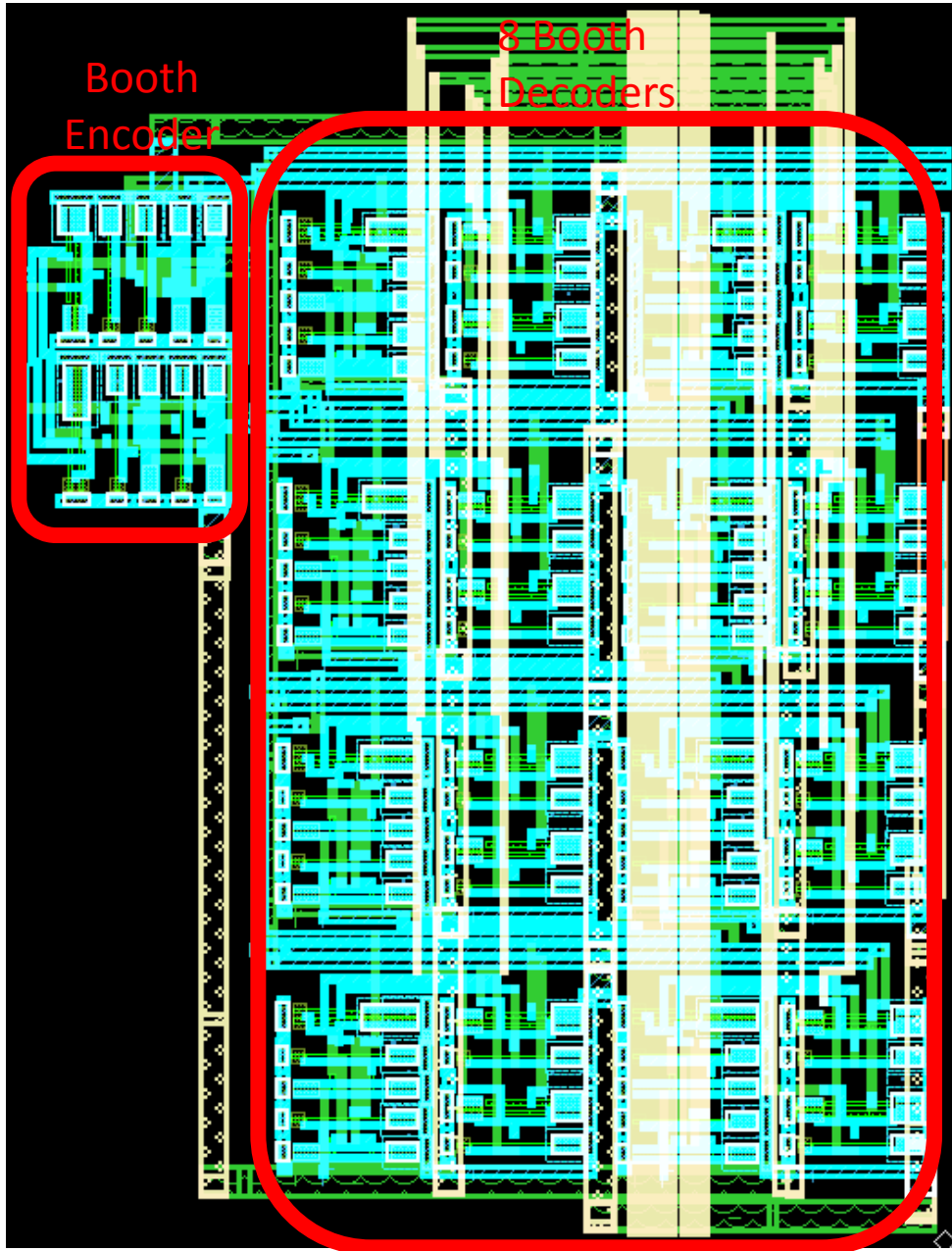


# Full Adder

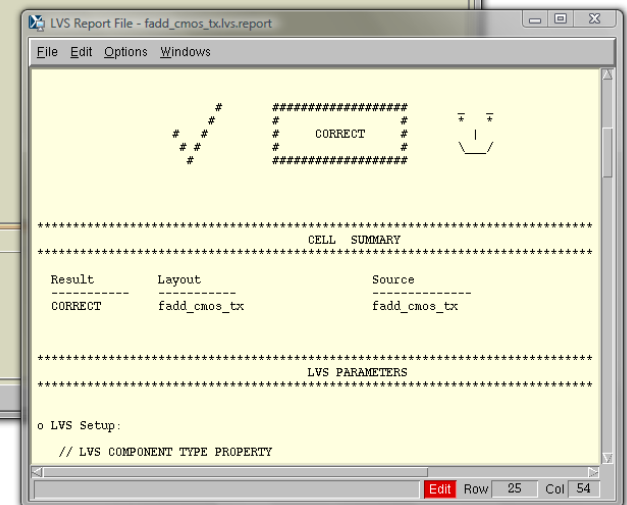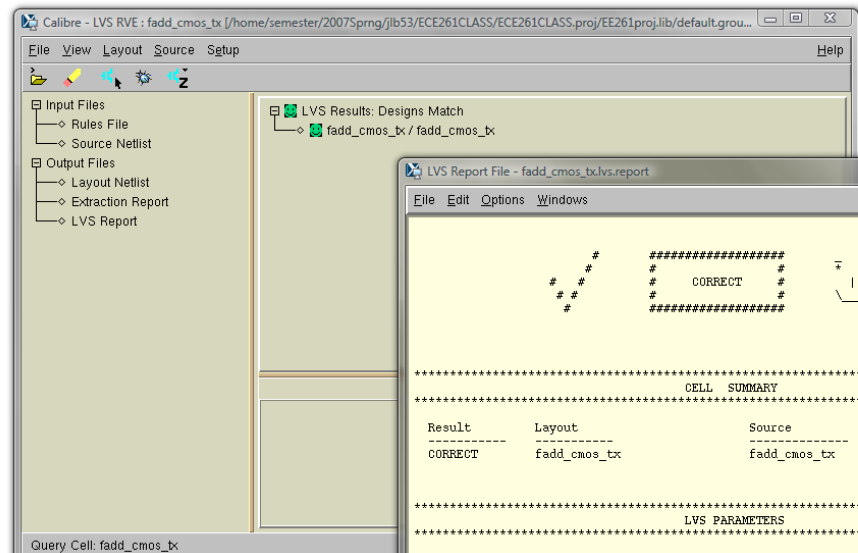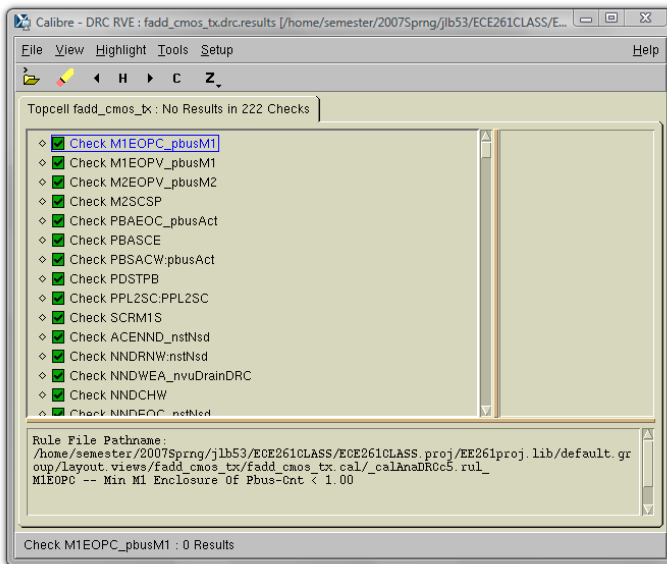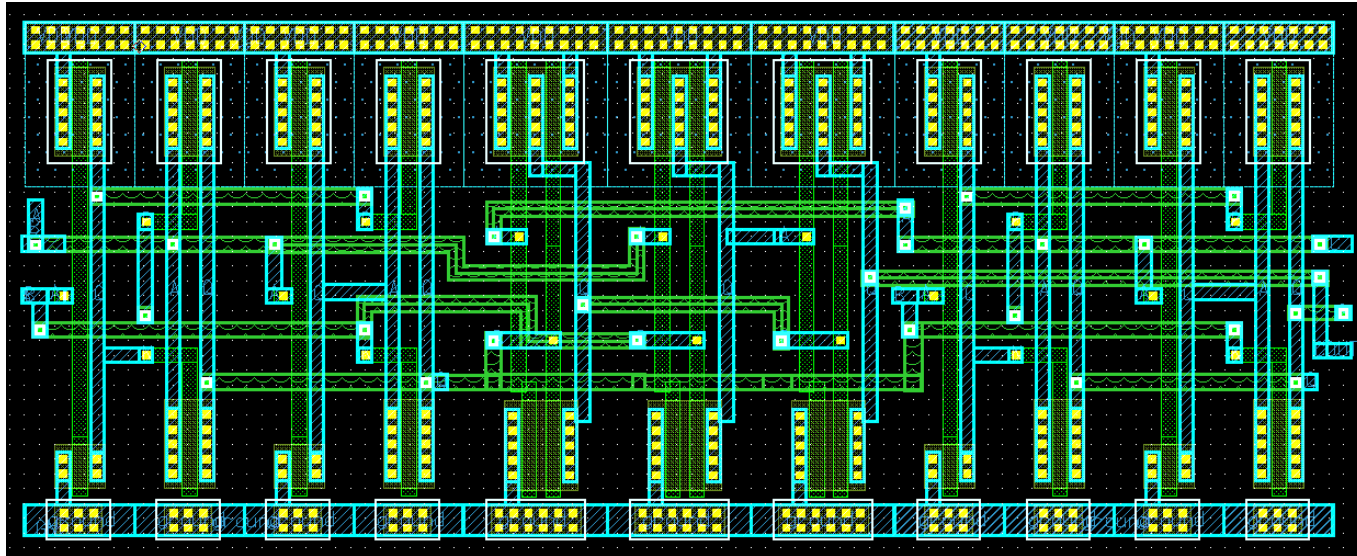



# Full Adder

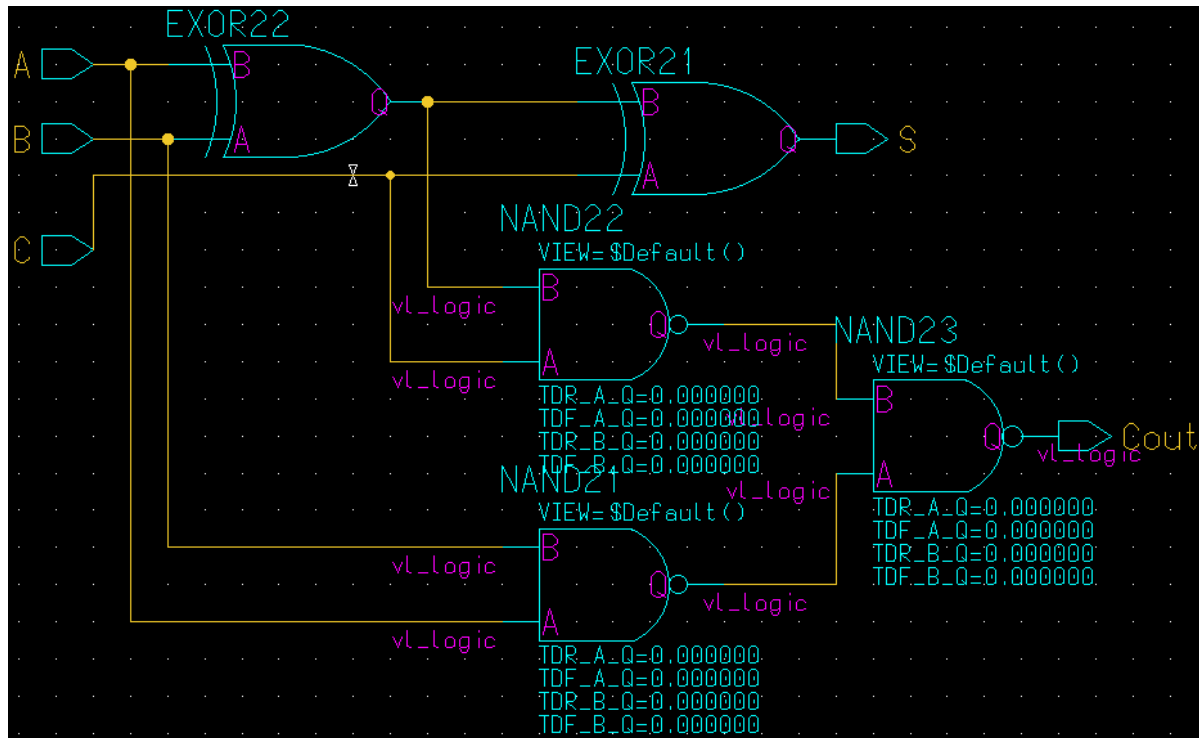


# 16 bit Carry Save Adder

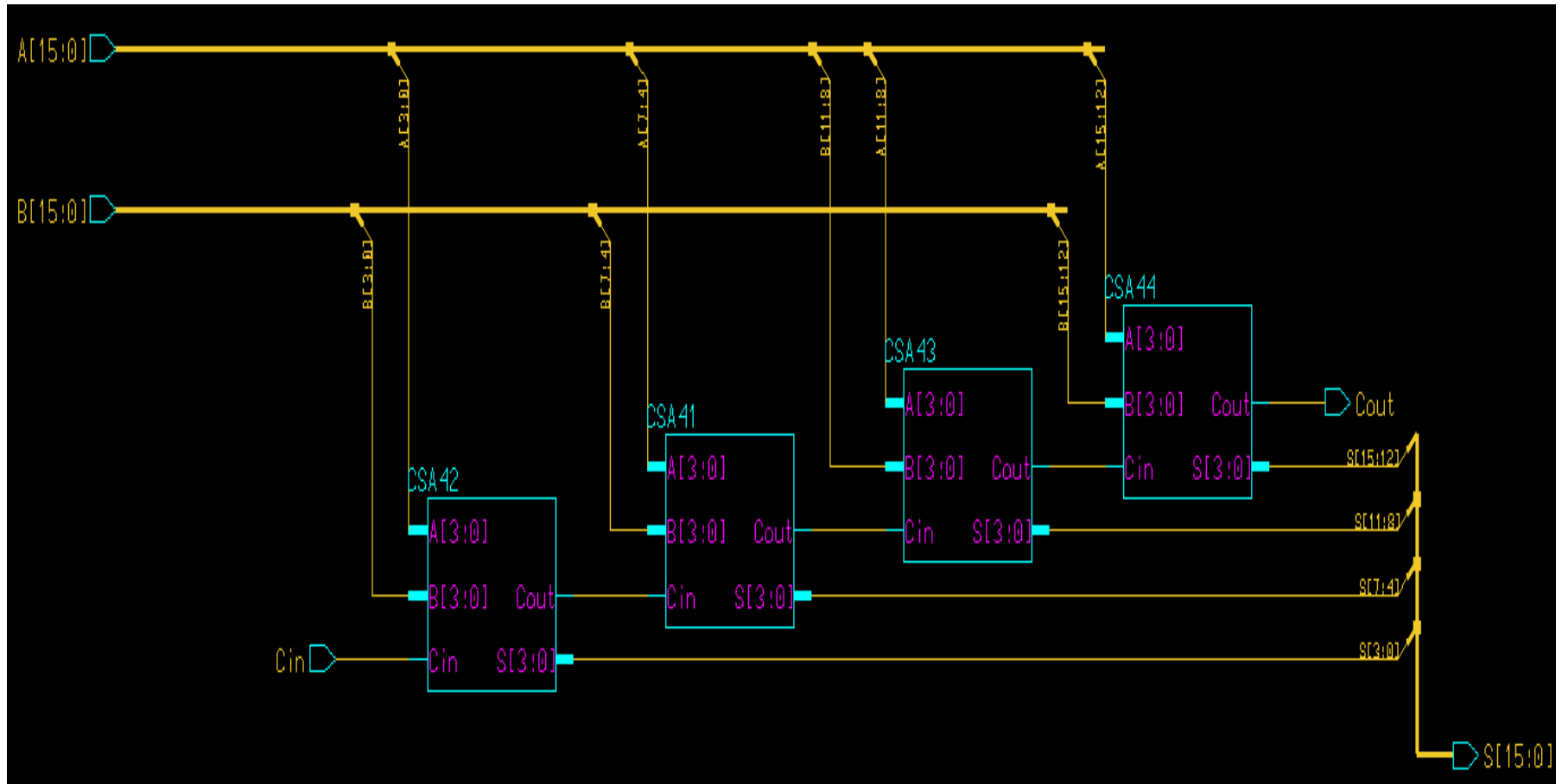

# 16 bit Carry Save Adder

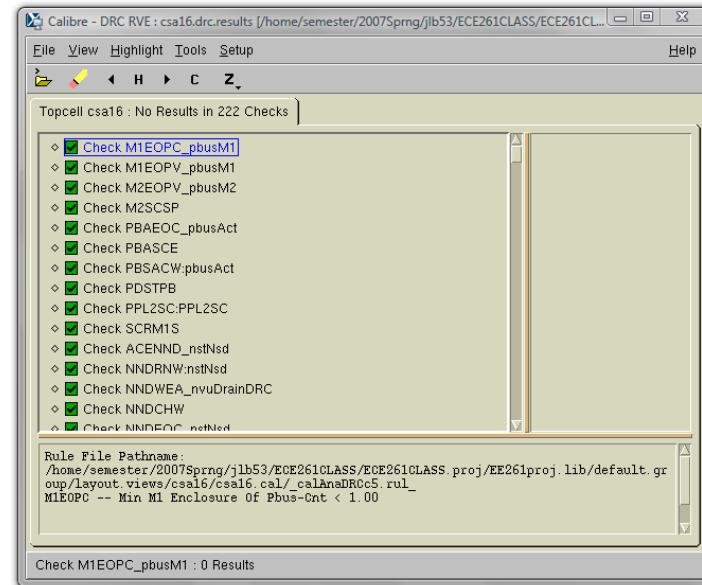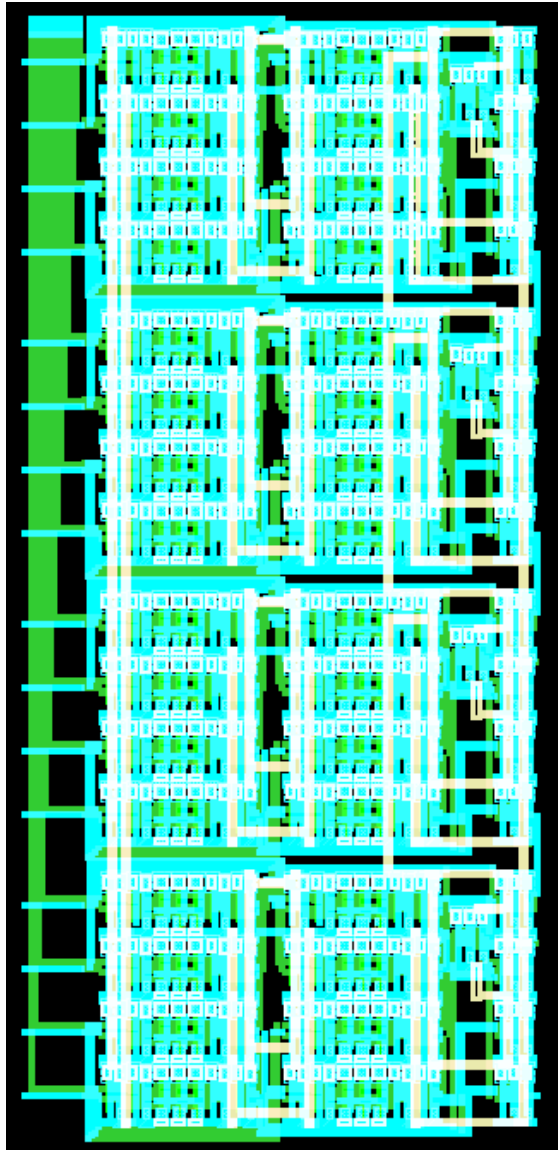


# 4 bit Carry Save Adder

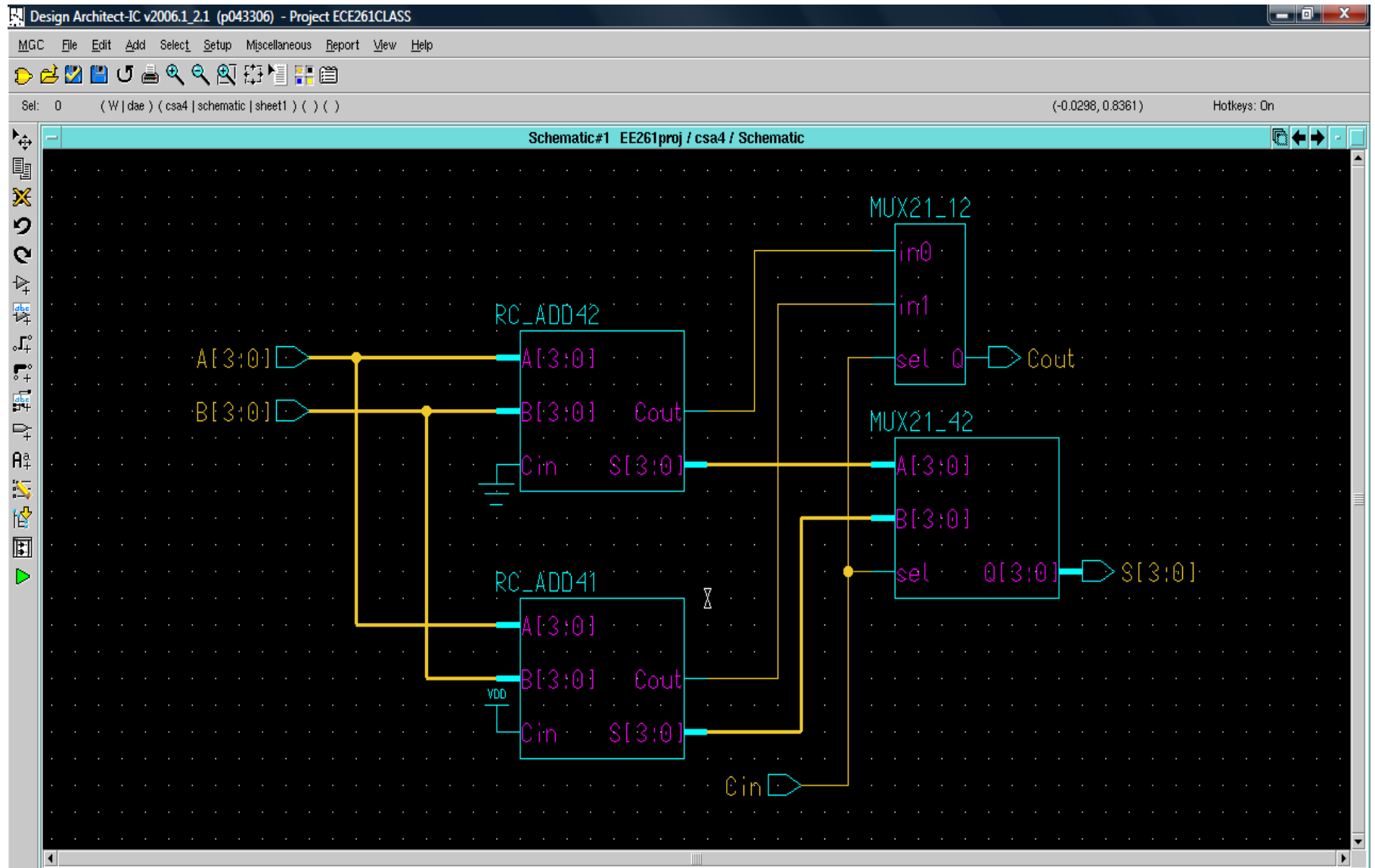


Warning : Unable to find menu item 5 jproc\_add4test (schematic) to delete.

# 4 bit Carry Save Adder

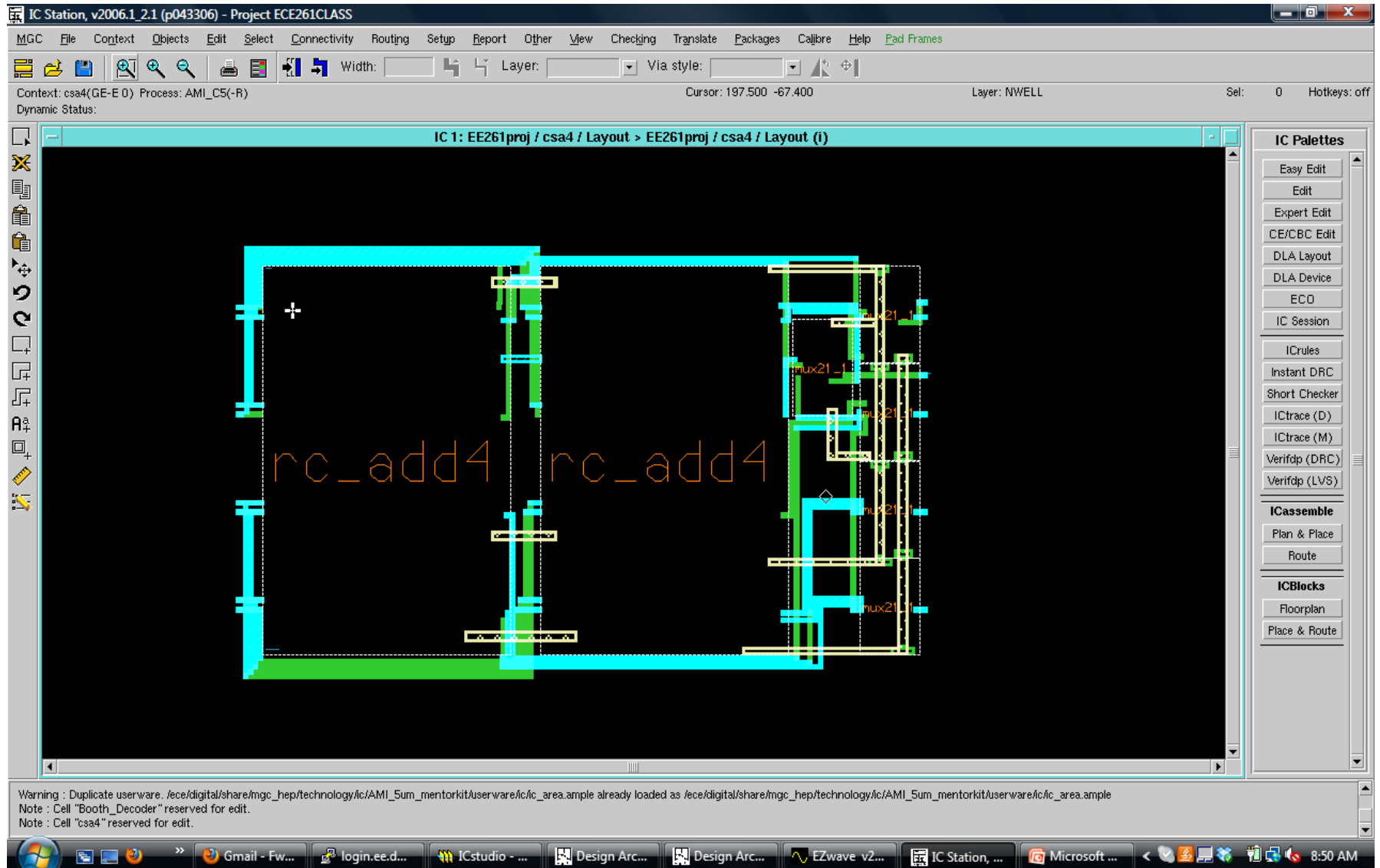


# Top Level Diagram

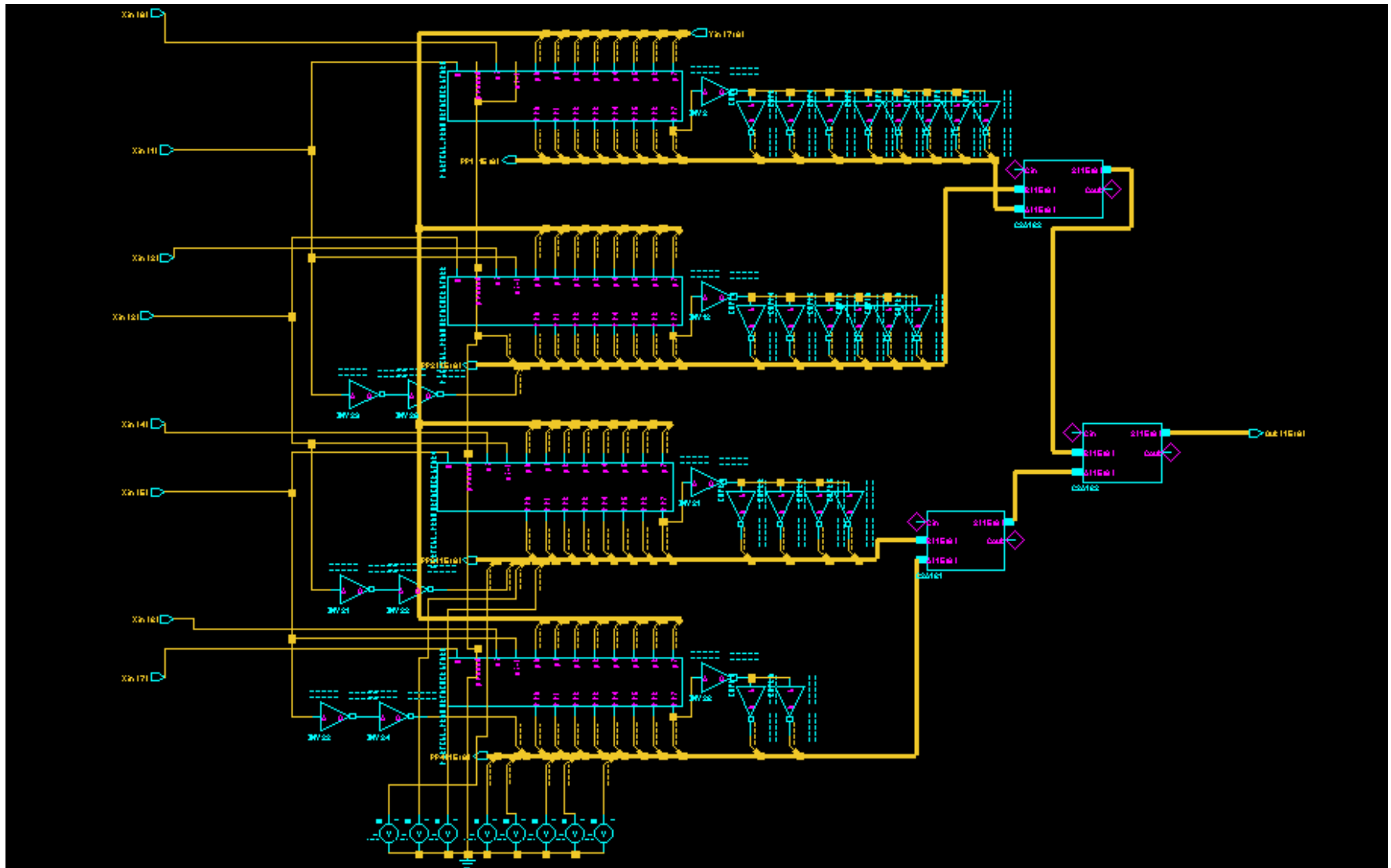



# Top Level Layout

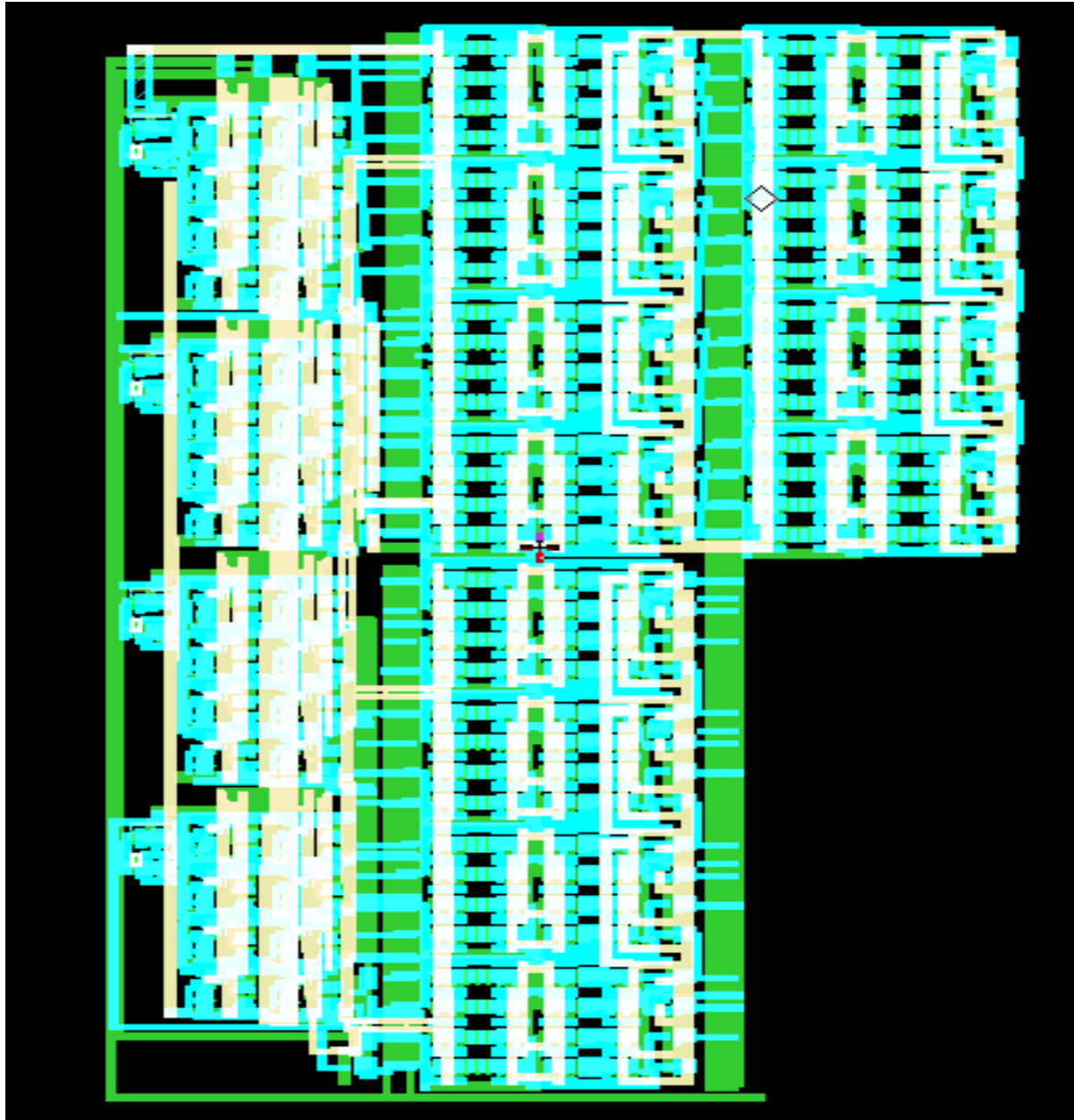

# Functional Simulations

- Our Eldo would not simulate the top level diagram with all three adders included
- Therefore, for simulations, we deleted the third adder, and took the outputs at the ends of the inner adders.
- To verify functionality through simulation, we simply took the two outputs we found and added them ourselves.

# Test 1:


- Multiplier input:  $00001010 = 10$
- Multiplicand input:  $00000101 = 5$
- Output 1:  $1111111111011110$
- Output 2:  $0000000001010100$
- Sum of outputs:  $0000000000110010 = 50$
- As we can see, the output equals the product of the two inputs

## Test 2

- Multiplier input:  $01011101 = 93$
- Multiplicand input:  $0001101010 = 26$
- Output 1:  $1111111110100110$
- Output 2:  $0000100111000100$
- Sum of outputs:  $0000100101101010 = 2418$
- Once again the final output is equal to the product of the inputs as expected.


# Timing Simulations

- Propagation time? Only 6ns worst case

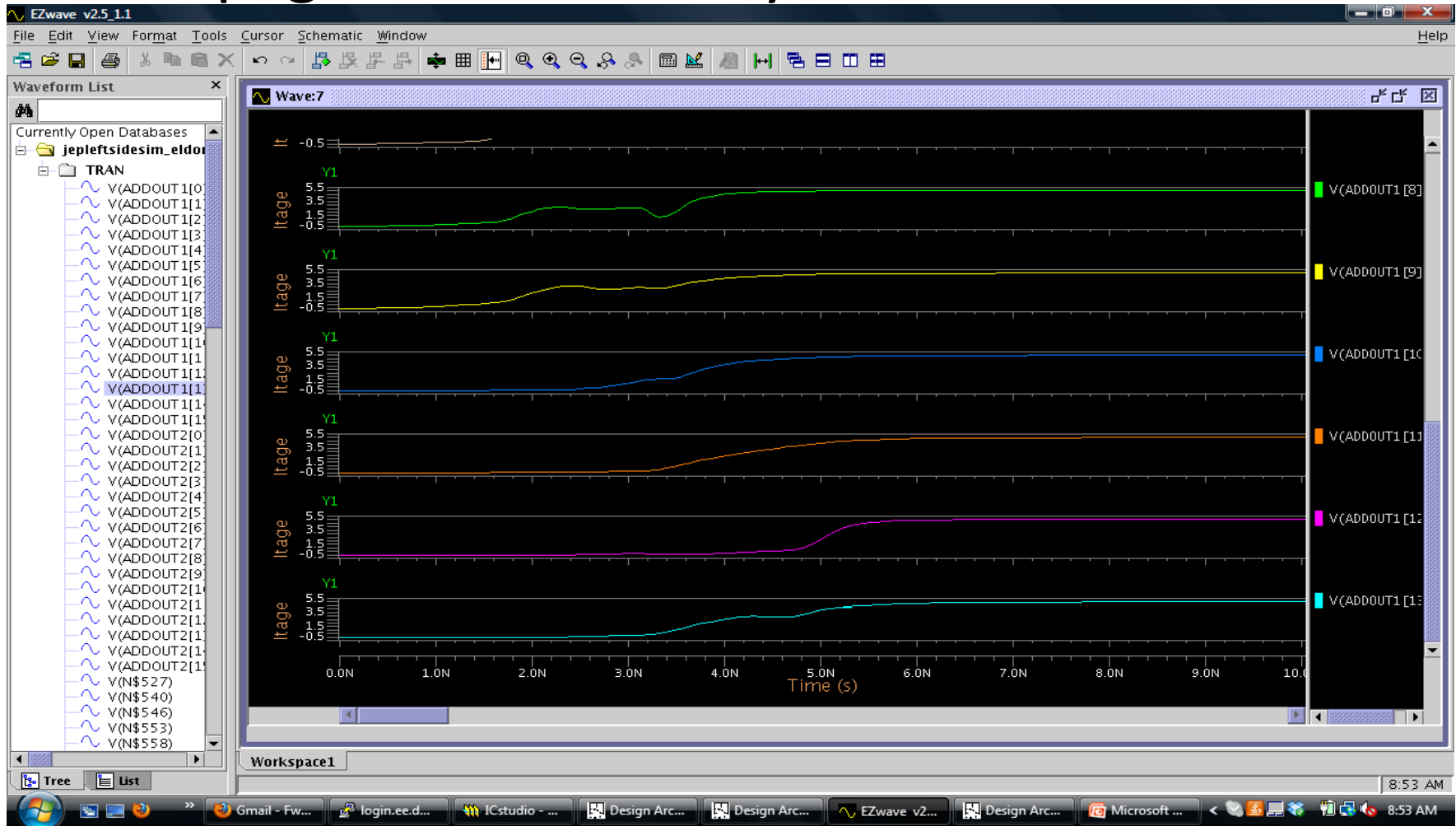
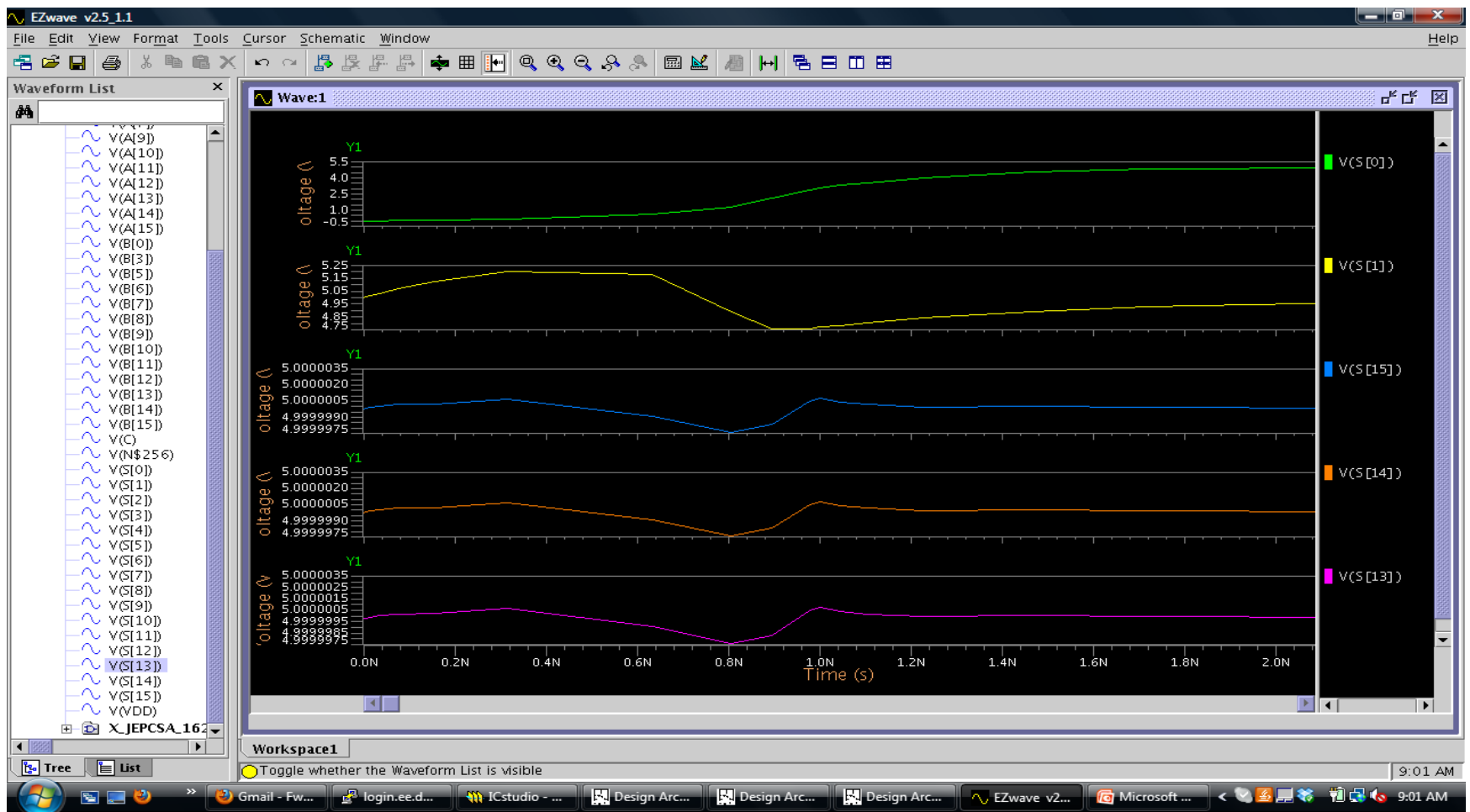
# Propagation Time continued

- Extra adder! 2ns additional propagation time.



# Power Consumption

- Simulation of top level block (minus the final adder of course) showed an average power consumption of 73.72 nano Watts.
- Simulation of the adder gave a power consumption of 21.24 nW.
- Therefore the total power consumption of our circuit is expected to be an average of 94.96nW.

