

Feedback Amplifiers

$$AV = -g_m \left(\frac{R_i}{R_i + R_S} \right) R_o = -\frac{I_o}{V_{in}^o} \frac{R_i}{R_i + R_S} \cdot R_o$$

$$= -\frac{I_o}{V_{in}^o} \cdot \frac{1}{R_i} \cdot R_o \quad [R_S = 0]$$

$$AV = -AI \cdot \frac{R_o}{R_i}$$

$$\text{If } A_I = 100, R_i = 1.1k, R_0 = 2.2k \quad A_V = -200.$$

$$q_f - V_i = 1 \text{ mV}$$

$$U_0 = |Av| \cdot U_i = 200 \text{ mV} = 200 \text{ mV}$$


If temp ↑, A[°]Tes to 110
men,

$$AV = 110 \cdot \frac{2 \cdot 2k}{1 \cdot 1k} = 220$$

$$V_0 = 220 \cdot 1mV$$

$$= 220 \text{ mV}$$

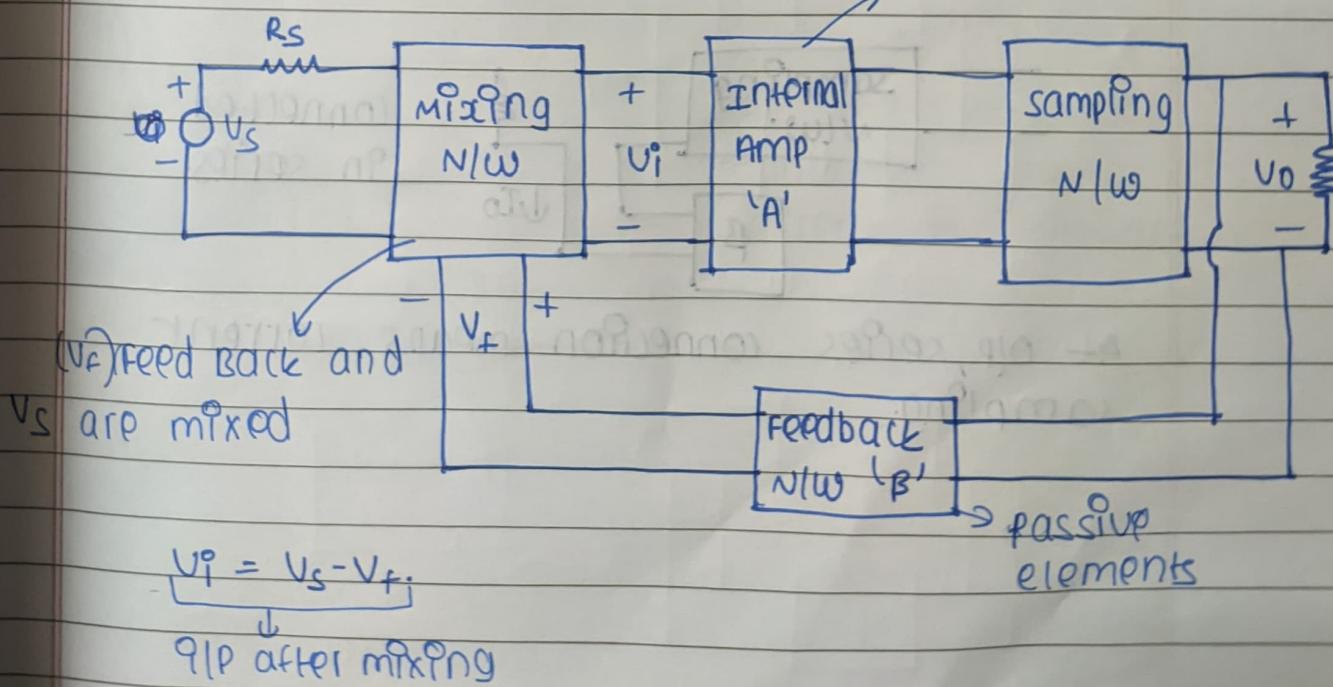(um) Feedback amp block diagram: A A_fs open loop gain




- * If $V_o \uparrow$ due to any fluctuations,
 $V_f \uparrow \therefore V_i \downarrow \Rightarrow$ brought down V_o to constant
- * If $V_o \downarrow, V_f \downarrow, V_i \uparrow \Rightarrow$ brought down V_o to constant

sampling:


(i) voltage sampling:

①

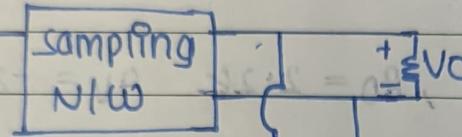


voltage sampling.

N/W-Network

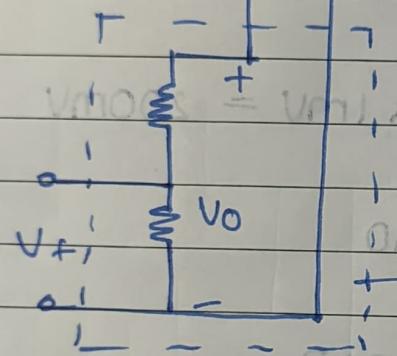


Voltage shunt sampling connection

(ii) current sampling

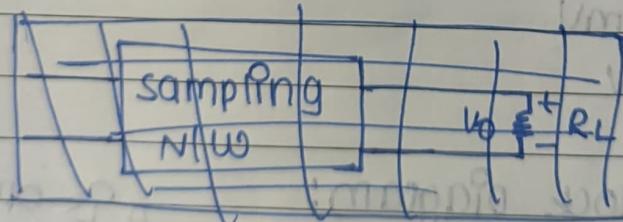

sampling N/W

connected in series.

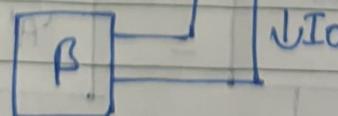


At O/P, series connection means current sampling.

- * when temp increase α_f increases which leads to increase βV_o (op voltage) so, β_f order to eliminate this effect and remove this instability a small sample of V_o is feed back into the transistor.
- * no sampled N/W can have both current (or) voltage.
- * feedback n/w β_s always made of passive elements. (RL -)


Mixing N/W

i) series mixing.

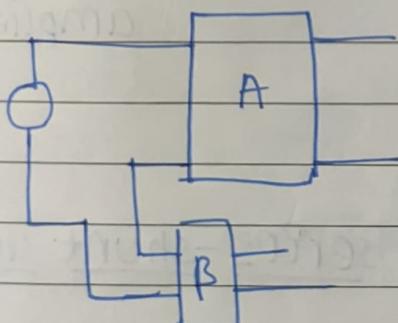

At the Q/P series connection means voltage β_s feed.


ii)

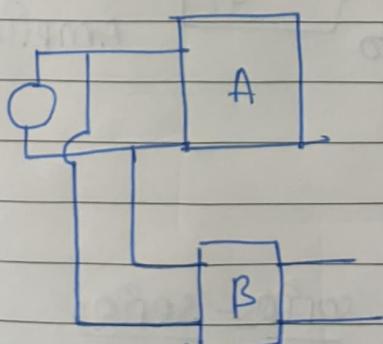

At the Q/P shunt connection means current β_s feedback

4 different types of sampling amplifiers

shunt-shunt-AMP

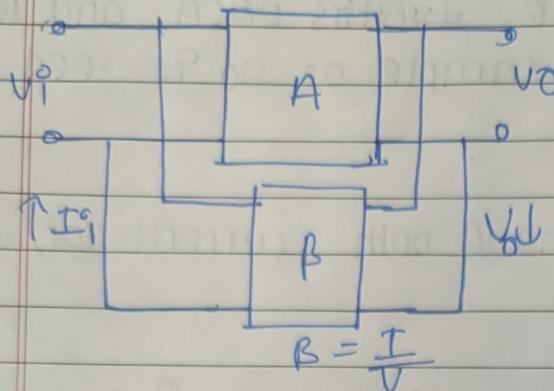

$$\beta = \frac{1}{A}$$

Voltage shunt

Feedback Amplifiers

$$A = \frac{V_o}{I_i} \rightarrow \text{Transistor amplifier}$$

Types


+ POSITIVE

+ NEGATIVE

so

current shunt FB amp:

shunt-series amp

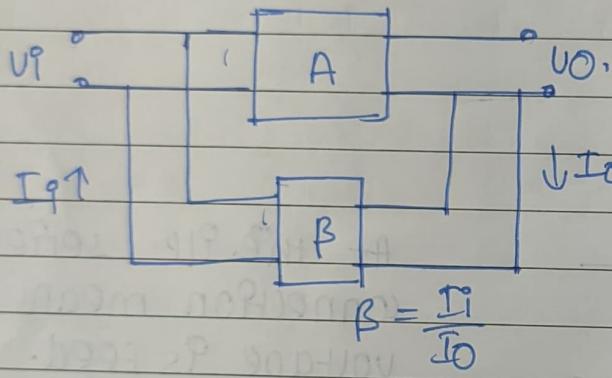

$$A = \frac{I_o}{I_i}$$

Current amplifier

so =

SFB =

SE =


SO =

ASI =

Afb

voltage - series FB amp:


series-shunt amp

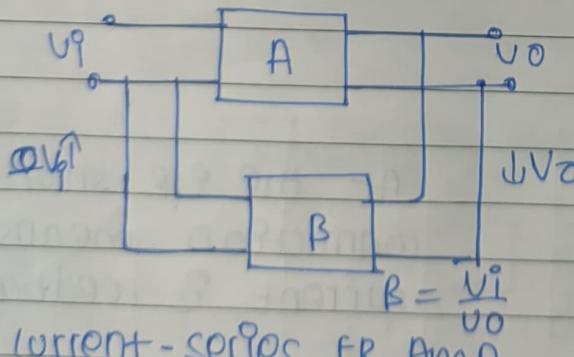

$$A = \frac{V_o}{V_i} \rightarrow \text{voltage amplifier}$$

current-series FB Amp

series-series

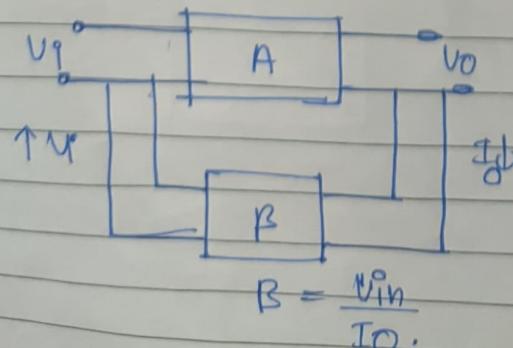


$$A = \frac{I_o}{V_{in}}$$

Transconductance amplifier

Af

Types of feedback:

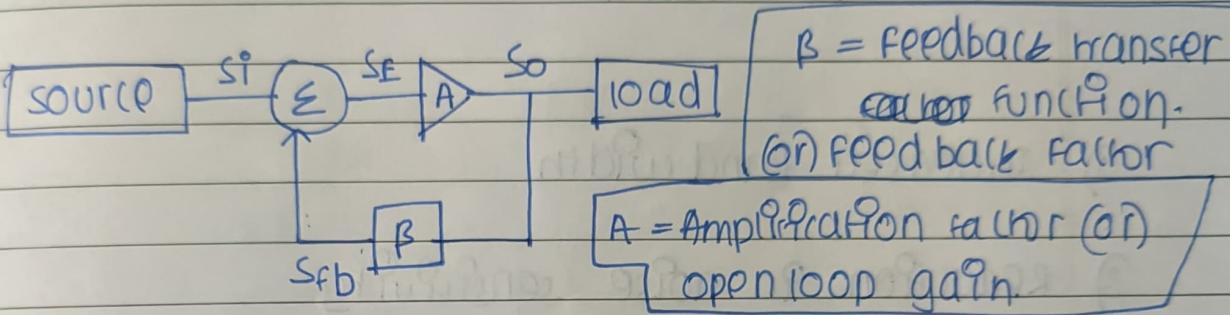- + Positive feedback → for oscillators
- + Negative feedback. → for amps.



$$S_O = A S_E$$

$$S_{fb} = \beta S_O$$

$$S_E = S_O - S_{fb}$$

$$S_O = A(S_O - S_{fb}) = A S_I - A \beta S_O$$

$$A S_I = S_O + A \beta S_O$$

$$A \beta = \text{loop gain}$$

$$A \beta \gg 1 \quad ; \quad A_{fb} = \frac{A}{A \beta} = \frac{1}{\beta}$$

$$A_{fb} = S_O / S_I = \frac{A}{1 + A \beta} \rightarrow \text{closed loop gain}$$

↓
negative feedback

$$A_{fb} = \frac{A}{1 - A \beta} \rightarrow \text{for positive feedback}$$

Advantages of feedback loop:

1) Reduction in gain sensitivity.

Sensitivity of V_o to temp and other factors is reduced.

2) Increased band width

3) Reduction in noise sensitivity

4) Reduction of non-linear distortions.

5) Good control over the impedance levels at IP and OIP sides.

Disadvantages

1) Gain will be reduced./overall gain is reduced.

$$A_{fb} \propto \frac{1}{B}$$

- (Q) calculate feedback transfer function β if $A = 10^5$, $A_F = 50$
Find β .

(A) ~~$A = 10^5$~~ ~~$A_F = 50$~~

$$A_F = \frac{A}{1+AB} = \frac{B}{A_F(B+A)}$$

$$\beta = \frac{A_F}{B}$$

$$A_F + A_F A B = A$$

$$\beta = \frac{A - A_F}{A_F A} = 0.01999$$

* Advantages of negative feedback

i) Reduction in gain sensitivity:

$$A_f = \frac{A}{1+AB}$$

$$\frac{dA_f}{A} = \frac{1}{1+AB} - \frac{A}{(1+AB)^2} \cdot B$$

$$\frac{dA_f}{A} = \frac{1}{(1+BA)^2}; \quad dA_f = \frac{dA}{(1+BA)^2}$$

$$\frac{dA_f}{A_f} = \frac{dA/(1+BA)^2}{A/(1+AB)} = \frac{1}{1+AB} \frac{dA}{A}$$


ii) Bandwidth Extension:

$$A(s) = \frac{AO}{1+s/\omega_H}$$

$$A_f(s) = \frac{A(s)}{(1+B(A(s))^2)} = \frac{AO}{(1+s/\omega_H)} \cdot \frac{1}{\left(1 + \frac{BAO}{(1+s/\omega_H)}\right)}$$

$$= \left(\frac{AO}{1+BAO}\right) \left(\frac{1}{1+s/\omega_H(1+BAO)}\right)$$

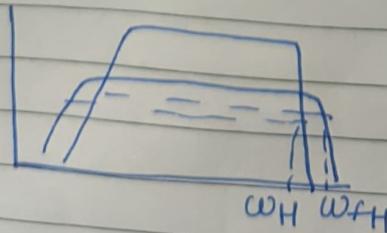i.e., ω_H is increased to $\omega_{HF} = \omega_H(1+BAO)$





(3) NOISE OF DISTORTION REDUCTION:

$$N_f = \frac{N}{1+\beta A} \quad D_f = \frac{D}{1+\beta A}$$

since gain is divided by $\frac{1}{1+\beta A}$
noise & distortion will also be divided.

(4) REDUCTION IN NON-LINEAR DISTORTION:

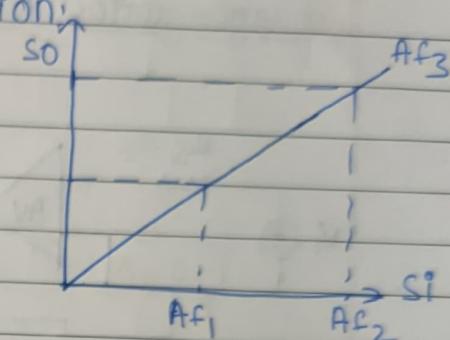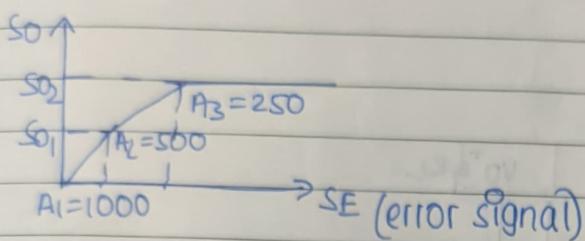

$$AF_1 = \frac{1000}{1 + (0.099)(1000)} = 10$$

$$AF_2 = \frac{500}{1 + (0.099)(500)} = 9.90$$

$$AF_3 = \frac{250}{1 + (0.099)(250)} = 9.7$$

NOISE:

- * It is caused due to random movement of charge carriers in the circuit.
This happens when there is ~~time~~ temperature change, when there are imperfection on the circuit etc.
- * It is internally created.



DISTORTION

- * Due to changes in the design of the transistor there will be an undesirable O/P. this is called Distortion

* The only disadvantage of negative feedback is that the gain is reduced.

series-shunt configuration

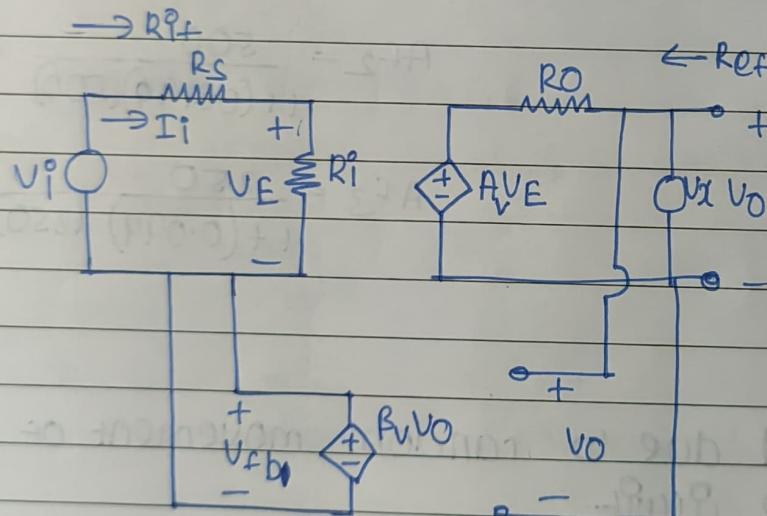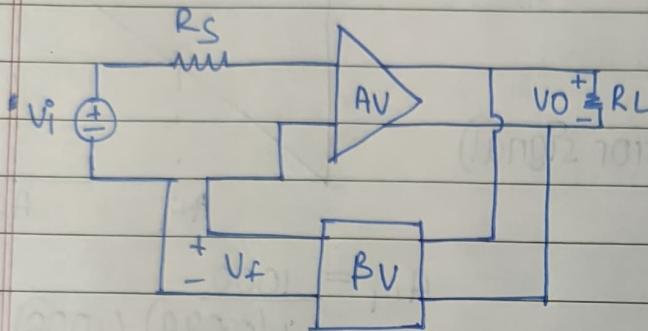voltage-series feedback amp (voltage amp)



$$V_O = A_V \cdot V_E, \quad V_{fb} = \beta_V V_O.$$

$$V_E = V_i - V_{fb}.$$

$$V_O = A_V (V_i - V_{fb}) \Rightarrow \frac{V_O}{V_i} = \frac{A_V}{1 + \beta_V A_V}$$

$$\textcircled{1} \quad V_O = A_V \cdot \frac{V_i}{V_{fb}} \Rightarrow V_O = \frac{A_V V_i}{\beta_V V_O} = A_{VF}$$

$$\frac{V_O}{V_i} = \left(\frac{A_V}{\beta_V} \right)$$

$$V_O =$$

$$V_i = V_E + V_{fb} \Rightarrow V_E + \beta_V V_o$$

$$V_i = (V_i - V_{fb}) + V_{fb}$$

$$V_i = V_E + \beta_V (A_v V_E)$$

$$V_E =$$

$$I_p = \frac{V_E}{R_i}$$

$$R_{of} = \frac{V_i}{I_p} = R_i (1 + \beta_V A_v)$$


O/P Impedance :-

$$V_E + V_{fb} = V_E + \beta_V V_x = 0 \quad \text{or} \quad 0$$

$$V_E = -\beta_V V_x$$

$$I_x = V_x - \frac{A_v V_E}{R_o} = -\frac{(V_x - A_v)}{R_o} \beta_V V_x + V_x$$

Current Amp (shunt-series Amp)

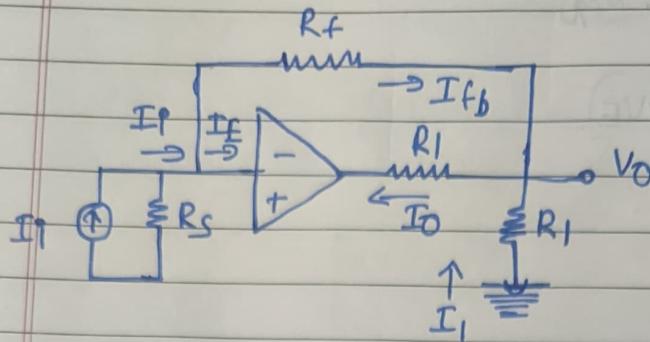

$$V_o = -I_{fb} R_f = -I_i R_f$$

$$I_i = -\frac{V_o}{R_f}$$

$$I_o = I_{fb} + I_i$$

$$= I_i + \left(-\frac{1}{R_f}\right) (-I_i R_f)$$

$$I_o = I_i \left(1 + \frac{R_f}{R_i}\right)$$


$$\frac{I_o}{I_i} = 1 + \frac{R_f}{R_i}$$

$$A_{if}^o \approx \frac{1}{\beta_i} = \frac{I_o}{I_i}$$

$$\therefore \beta_i = \frac{1}{\left(1 + \frac{R_f}{R_i}\right)}$$

Examples:-


CB Circuit:

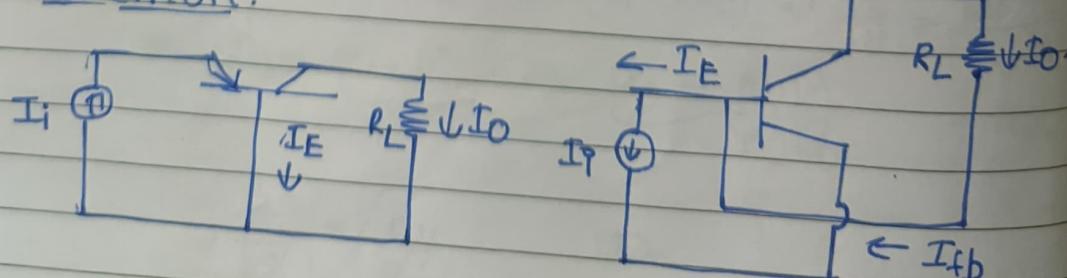


$$A_i^o = \frac{I_o}{I_E} = h_{fe}$$

$$\beta_i = \text{unity.}$$
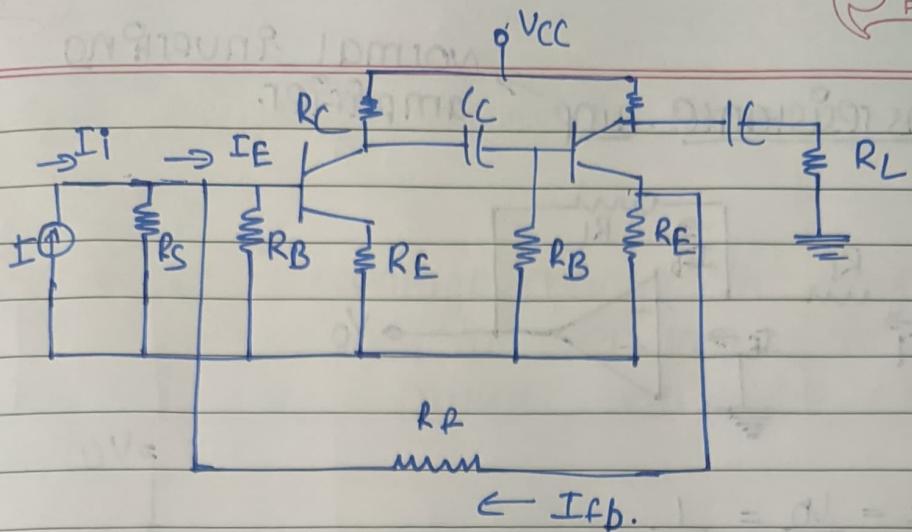
$$A_{if}^o = \frac{h_{fe}}{1 + h_{fe}} = \frac{A_i^o}{1 + A_i^o}$$



Transconductance Amp

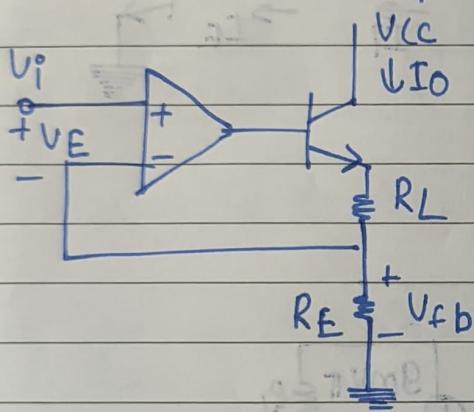


$$A_{gf} = \frac{I_O}{V_i} = \frac{1}{\beta_2}$$

$$V_i = V_{fb} - I_O R_E$$

$$A_{gf} = \frac{I_O}{V_i} = \frac{1}{R_E}$$

$$\beta_2 = R_E$$

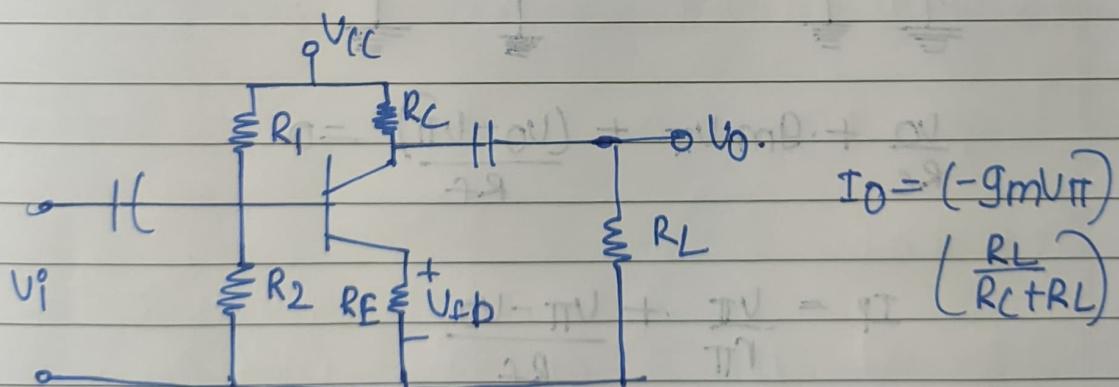


$$I_O = \frac{(-g_m V_{\pi})}{\left(\frac{R_L}{R_C + R_L} \right)}$$

$$V_{fb} = \left(\frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} \right) R_E$$

$$V_{\pi} = V_{\pi} + V_{TH} = V_{\pi} \left(1 + \left(\frac{1}{r_{\pi}} + g_m \right) R_E \right)$$

$$A_{gf} = \frac{I_O}{V_i} =$$

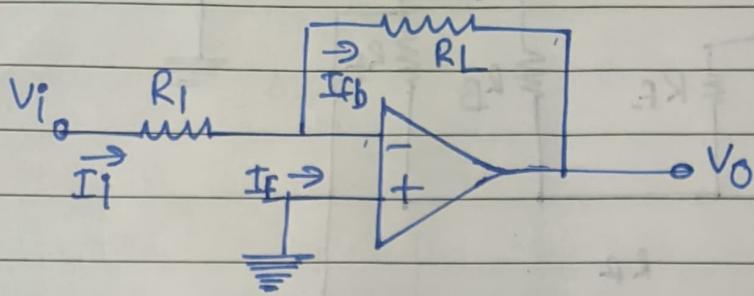trans resistance amp \rightarrow normal inverting amplifier.




$$A_{zf} = \frac{V_o}{I_g} = \frac{1}{B_g}$$

$$A_{zf} = -R_L$$

$$V_o = -I_{fb} R_L$$

$$B_g = -\frac{1}{R_L}$$

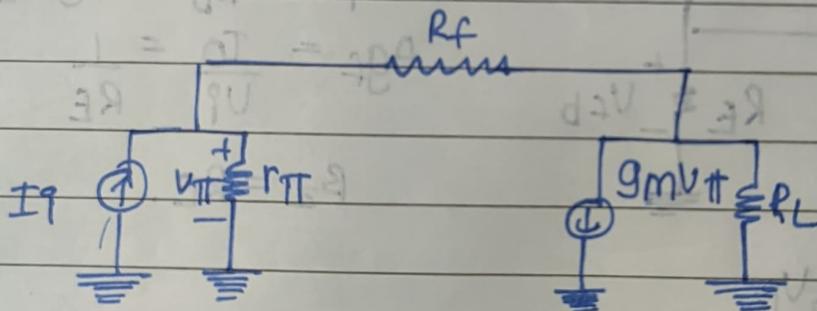

$$\frac{V_o}{R_C} + g_m V_T + \frac{(V_o - V_T)}{R_f} = 0$$

$$I_g = \frac{V_T}{r_T} + \frac{V_T - V_o}{R_f}$$

$$A_{zf} = \frac{V_o}{V_g} = -g_m \left(\frac{V_T}{r_T} + \frac{V_T - V_o}{R_f} \right)$$

$$(g_m \left(\frac{V_T}{r_T} + \frac{V_T - V_o}{R_f} \right) + 1) V_o = g_m V_T + V_o = V_T$$

* Example for current amp is common base amp.

Q) calculate the percentage change in closed loop gain A_f , given a change in open loop gain A .

$$\text{If } A = 10^5, \beta = 0.01999, \text{ and } dA = 10^4$$

$$A_f = 50$$

change closed loop gain: $\frac{dA_f}{A_f} - ?$


$$dA_f = \frac{A_f}{1 + \beta A} \cdot \frac{dA}{A}$$

$\underbrace{dA}_{\text{Differential gain}}$

$$dA_f = 2.5 \times 10^{-3}$$

$$\frac{dA_f}{A_f} = 0.0005 \times 10^{-5} \%$$

Oscillators

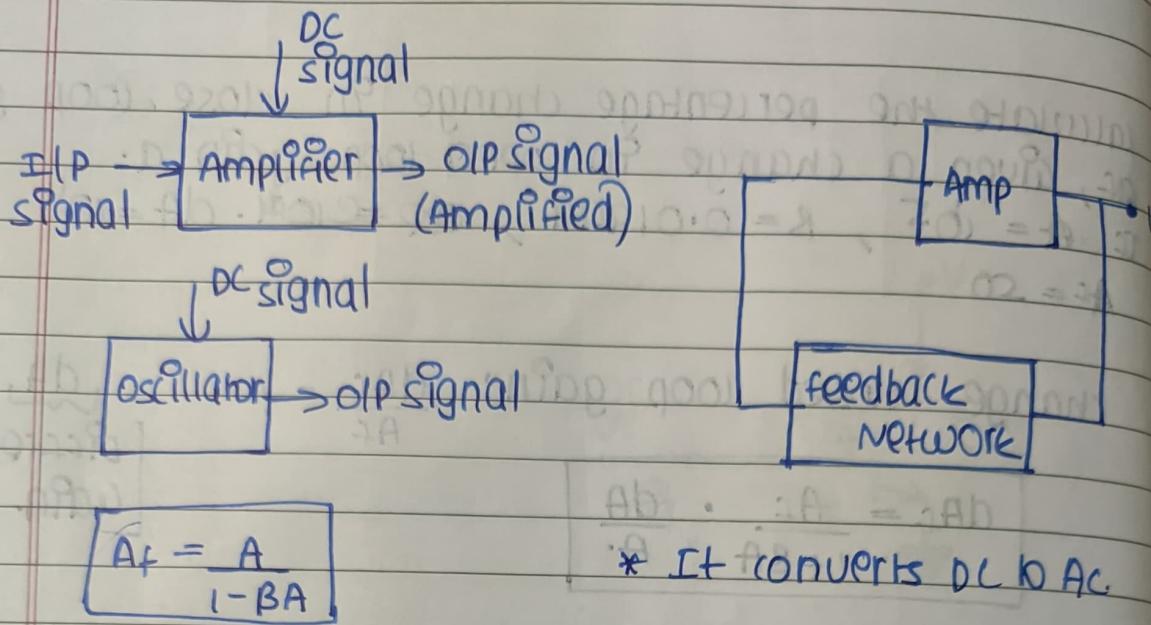

$$A_f = \frac{A}{1 - BA}$$

* It converts DC to AC.

If $BA = 1$ ($BA = \text{loop gain}$):

$$A_f = \frac{A}{1 - 1} = \frac{A}{0} = \infty$$

Condition for oscillator:

$$\beta A = 10^0$$

- i) $|\beta A| \geq 1$
 - ii) $\angle \beta A = 0^\circ \text{ or } 360^\circ$
- } Barkhausen criterion

Types:

- i) Sinusoidal or harmonic oscillator
- ii) Non-sinusoidal or relaxation oscillator. \rightarrow VR response

Under
Sinusoidal
oscillators

According to frequency of oscillation

- 1) Audio frequency oscillator \Rightarrow (20 Hz to 20 kHz)
- 2) Radio frequency oscillator.

\hookrightarrow Generate freq of osc beyond 20 kHz.

frequency stability

It depends on:

- * operating point
- * circuit components
- * supply voltage
- * output load
- * Int

* oscillator converts a DC signal into an AC signal without any input signal.

* audio free oscillators

RC phase shift

Wein bridge

* radio free oscillator


Hartley

Colpitt

Clapp

types of oscillations


1) damped. (overdamped/underdamped).

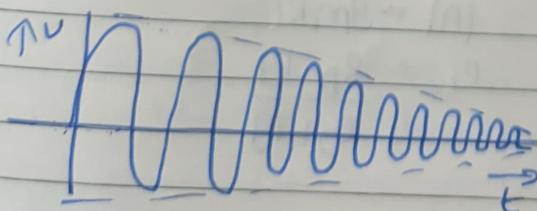

Oscillations

decrease over time

2) sustained / undamped

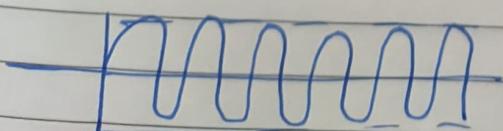


* const Amp

* const frequency.


* freq should be stable,

RC phase shift oscillator

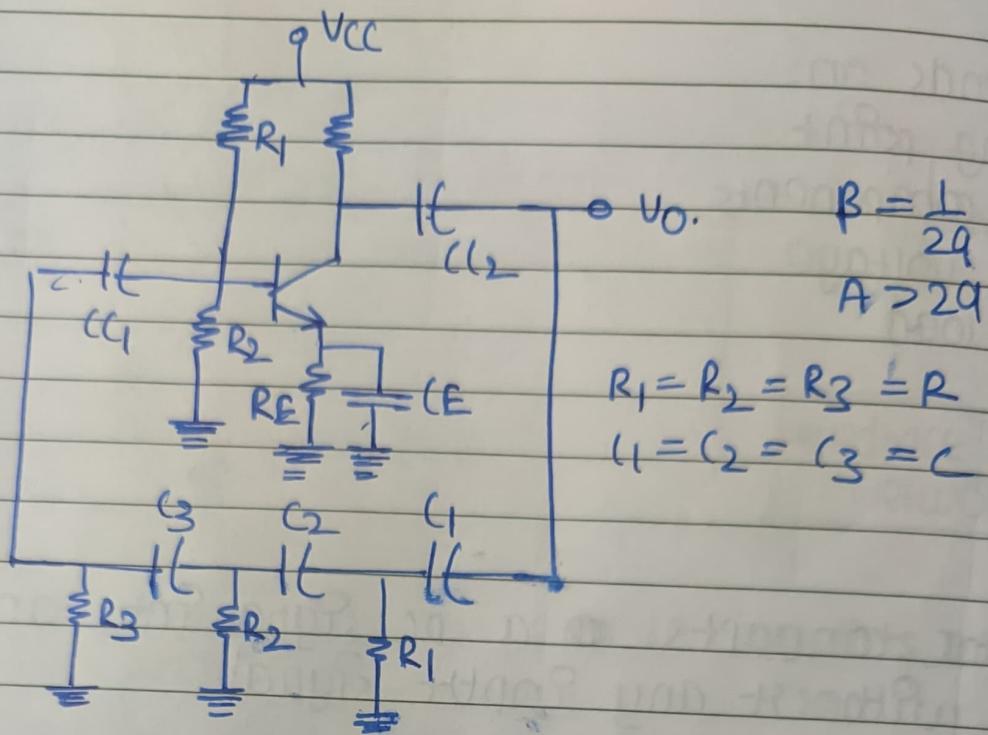

$$f = \frac{1}{2\pi RC} \cdot \frac{1}{\sqrt{6 + 4(RC/R)}}$$

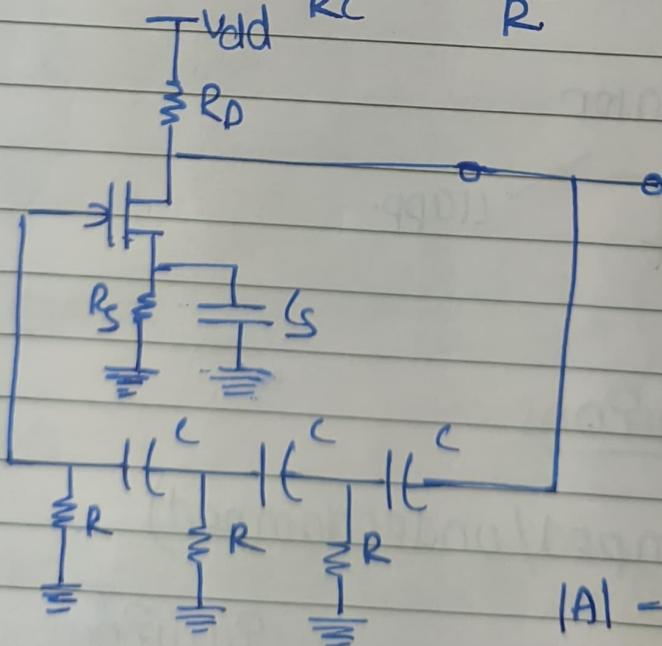
$$hfe > 23 + 2Q \frac{R}{RC} + \frac{4RC}{R}$$



$$f = \frac{1}{2\pi RC\sqrt{6}}$$

$$|A| = g_m R_L$$
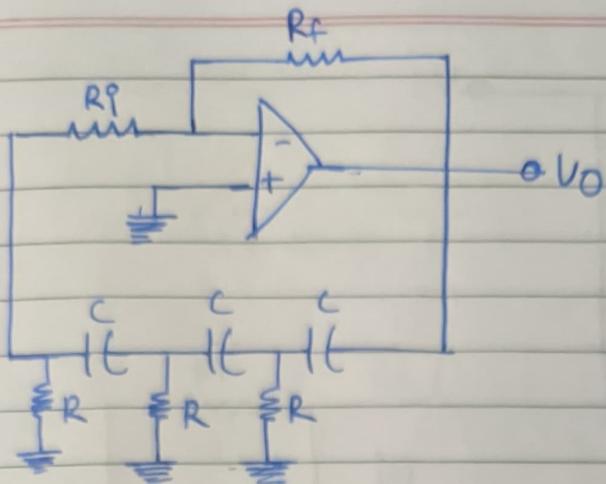
$$R_L = \frac{R_D \cdot r_d}{R_D + r_d}$$




* Explain RC phase shift oscillator:



- Bakhausen Crit

- Expression

- write point wise explanation & def by drawing
(ckt)

Hartley oscillator

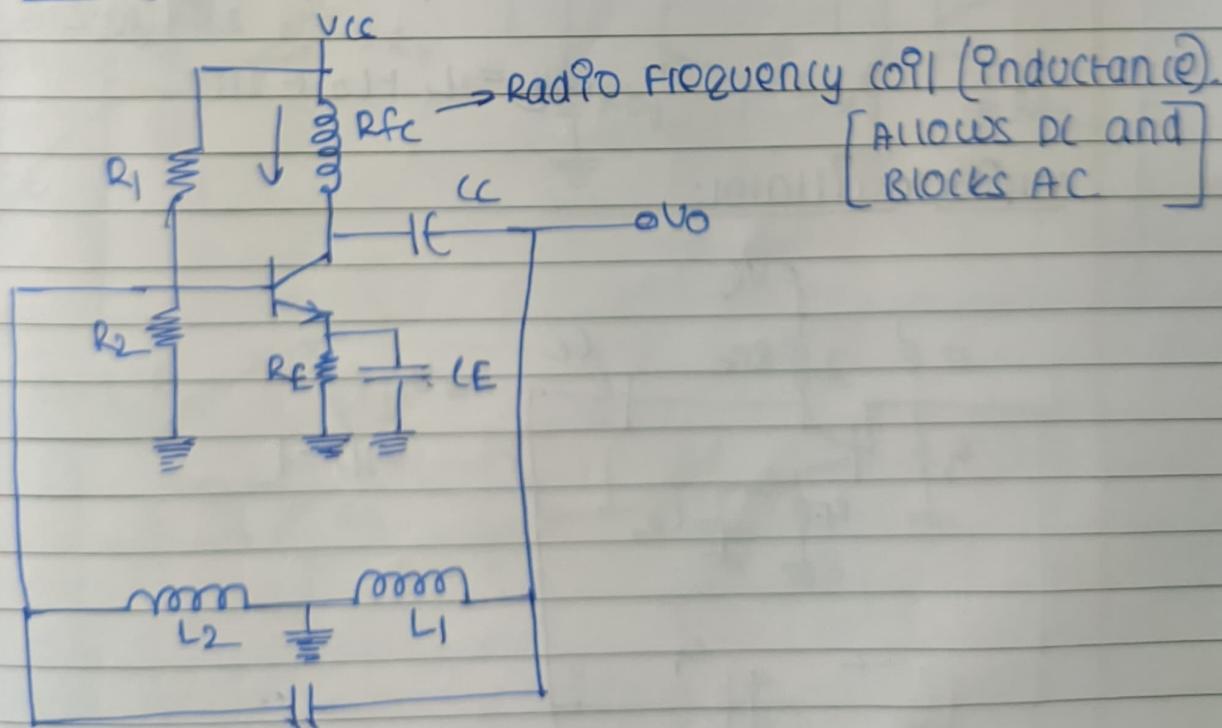

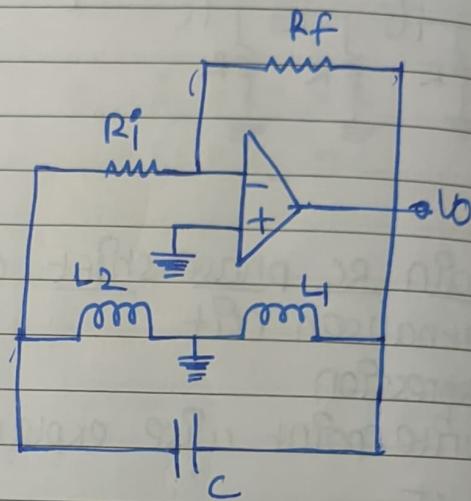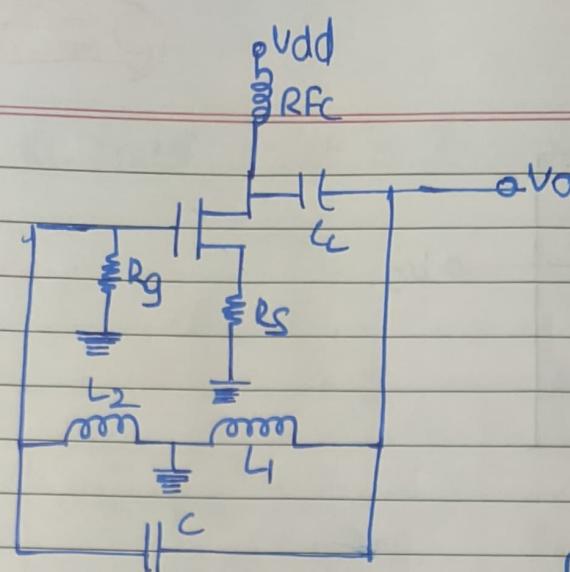


$$\beta = \frac{L_2}{L_1}$$

$$A = L_1 / L_2 \quad f_0 = \frac{1}{2\pi\sqrt{L_{eq} \cdot C}}$$

$$L_{eq} = L_1 + L_2 + 2m.$$

Colpitt oscillator:

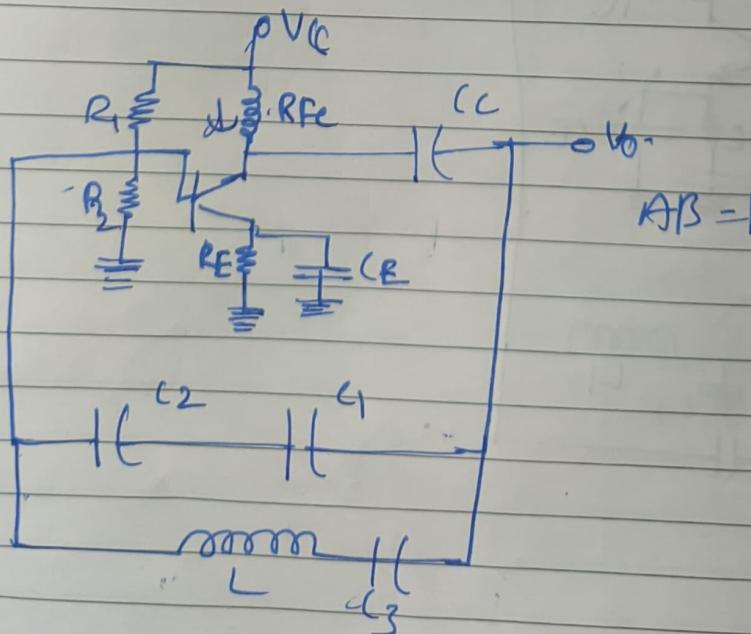

Clapp oscillator:

$$f_0 = \frac{1}{2\pi \sqrt{L_{C0}}}$$


$$eq = \left(\frac{1}{a} + \frac{1}{c_2} + \frac{1}{c_3} \right)$$

$C_3 = \text{small}$

$$f_0 \approx \frac{1}{2\pi\sqrt{LC_3}}$$



Wein Bridge oscillator:

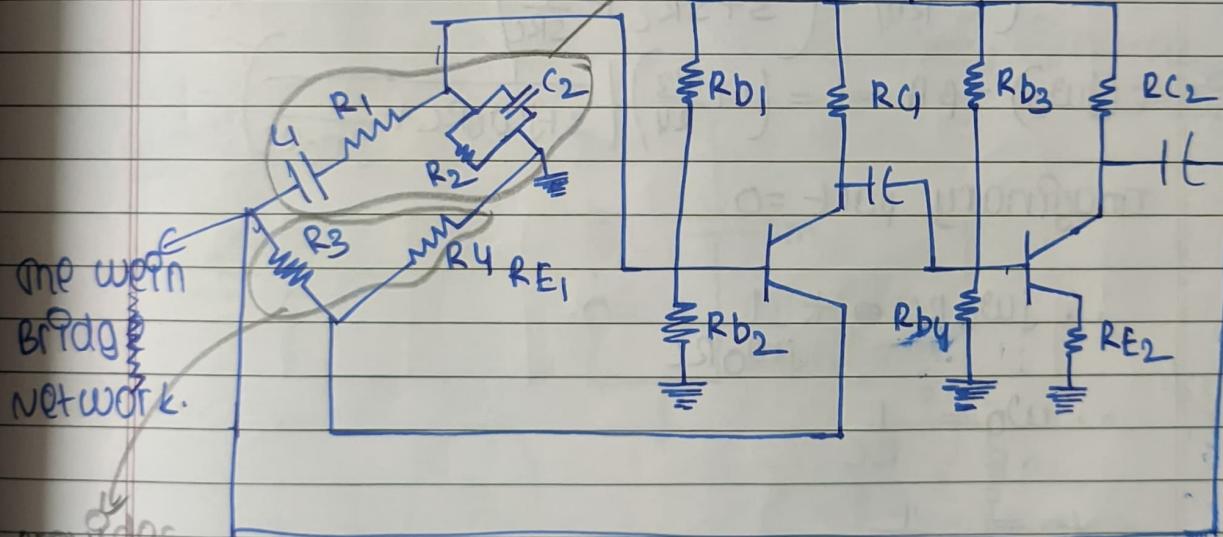(20Hz - 1MHz)
provides true feedback
@ Vcc



~~provides~~

-ve feedback.

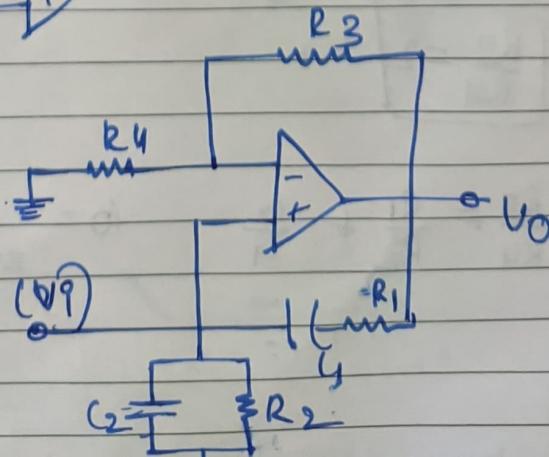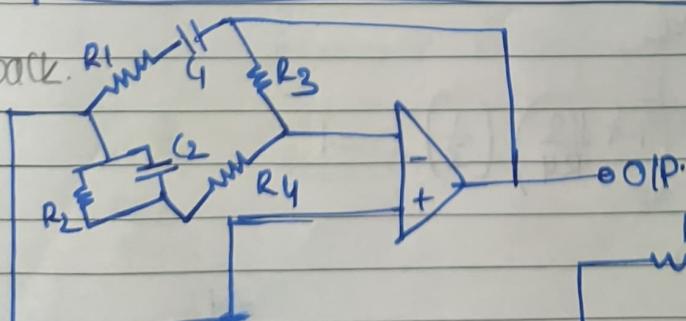

$$A = 1 + \frac{R_3}{R_4}$$

$$\beta = \frac{Z_P}{Z_P + Z_S} \quad Z_P = \frac{R_2 \times \frac{1}{SC_2}}{R_2 + \frac{1}{SC_2}} = \frac{R_2}{SR_2 C_2 + 1}$$

$$Z_S = R_1 + \frac{1}{SC_1} = \frac{1 + SR_1 C_1}{SC_1}$$

$$T(s) = \beta A = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{Z_P}{Z_P + Z_S}\right)$$

$$\text{If } R_1 = R_2 = R \quad C_1 = C_2 = C$$

$$T(s) = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{1}{3 + SRC + \frac{1}{SRC}}\right)$$

$$T(j\omega_0) = \beta A = 1 = \left(1 + \frac{R_3}{R_4}\right) \left| \frac{1}{3 + j\omega_0 RC + \frac{1}{j\omega_0 RC}} \right| = 1$$

Imaginary part = 0

$$\therefore j\omega_0 RC + \frac{1}{j\omega_0 RC} = 0.$$

$$\therefore \omega_0 = \frac{1}{RC}$$

$$\omega_0 = \frac{1}{2\pi RC}$$

REAL PART,

$$\left(1 + \frac{R_3}{R_4}\right) \left(\frac{1}{3}\right) = 1$$

$$\boxed{\frac{R_3}{R_4} = 2}$$

$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$

$$\omega_0 = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

- * Wein Bridge network is only for frequency determination.

Advantages:

good temp & freq stability
produces pure sine wave.





X CT-2 X

Crystal & -ve resistance oscillators are for $\omega_0 t - \frac{1}{4} \Rightarrow \text{ctg}$

B50.

Crystal oscillator (10kHz to 200MHz)


(very high freq stability) se).

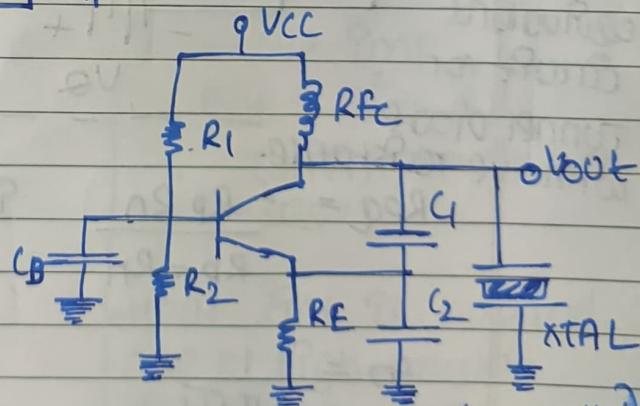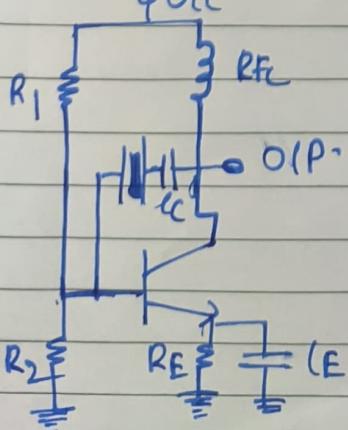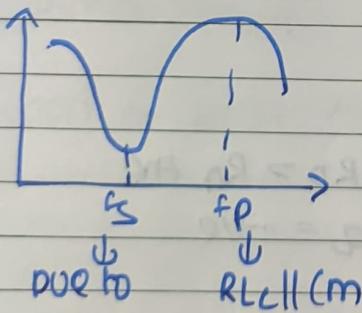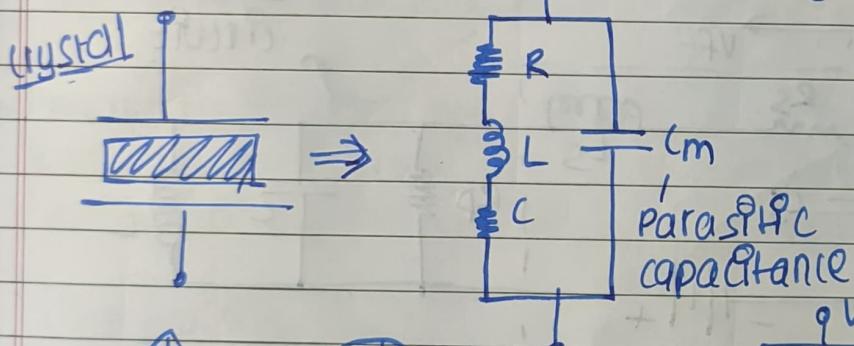


(as parallel resonance)

* It is an RF oscillator.

Negative resistance oscillator

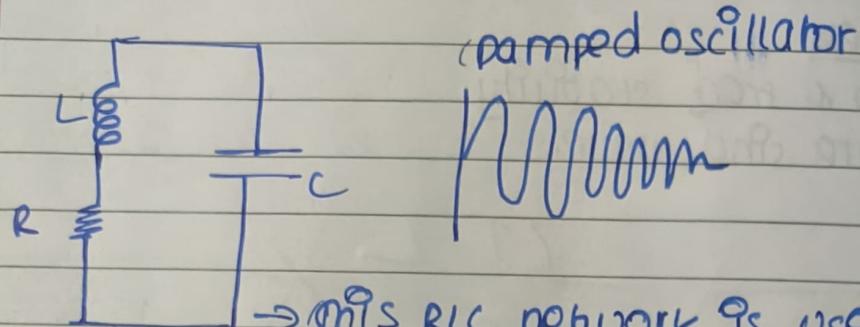

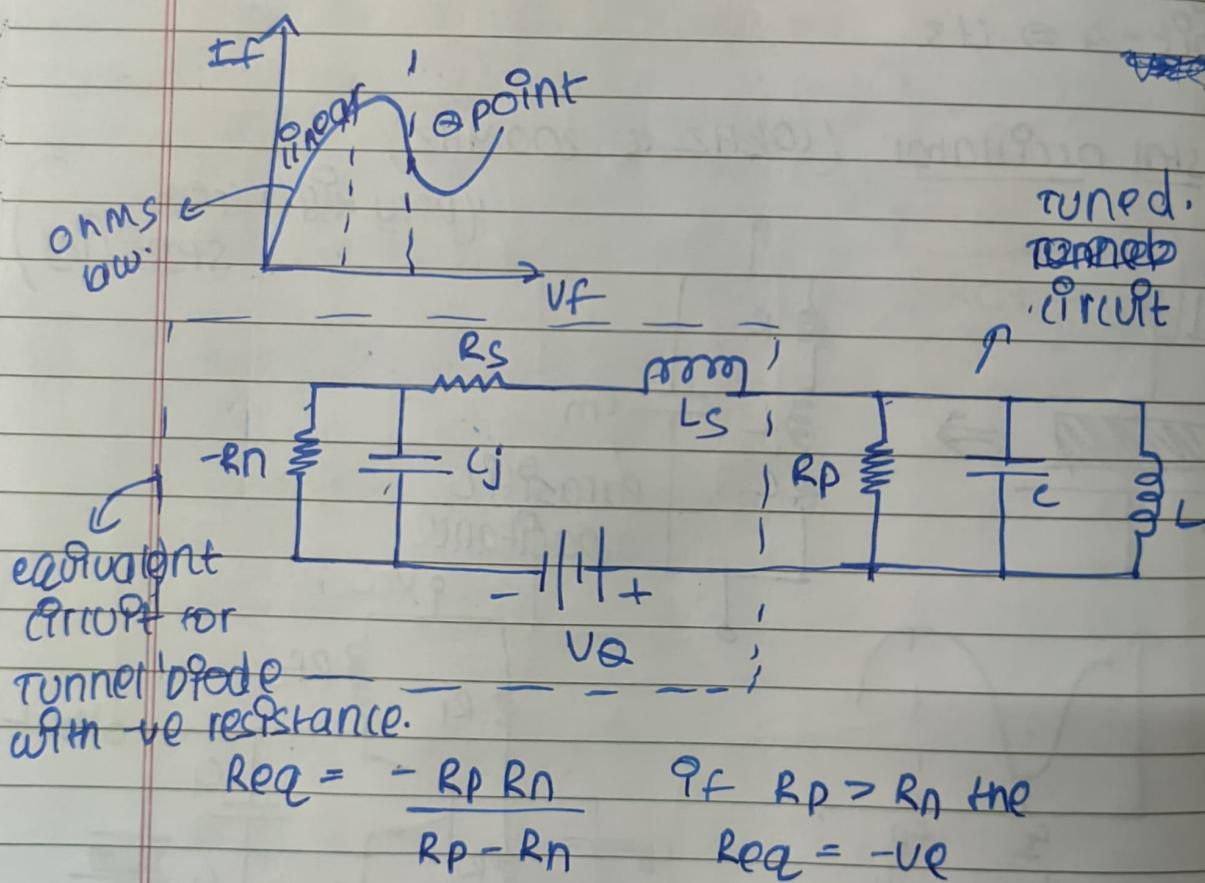→ This RLC network is used in parallel in below circuit.



$$R_{eq} = \frac{-RP R_N}{RP - R_N} \quad \text{If } RP > R_N \text{ then } R_{eq} = -v_Q$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$