


18EECC206J- VLSI DESIGN

UNIT II

MULTIPLEXER


- “Selects” binary information from one of many input lines and directs it to a single output line.
- Also known as the “selector” circuit,
- Selection is controlled by a particular set of input lines whose no. depends on the no. of the data input lines.
- For a 2^n -to-1 multiplexer, there are 2^n data input lines and n selection lines whose bit combination determines which input is selected.

Multiplexer (cont.)

 


2-to-1 Multiplexer

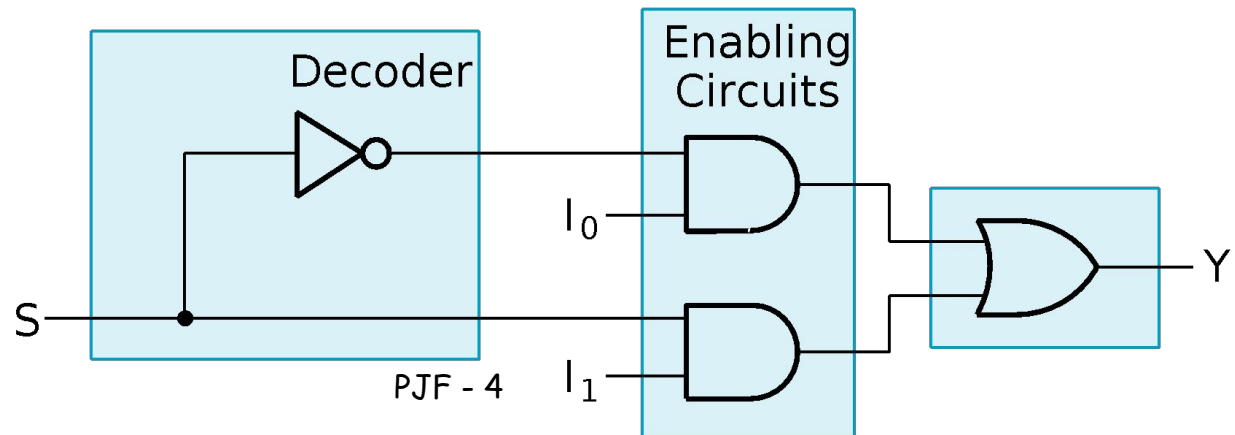- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1
- The equation:
$$Y = S' I_0 + S I_1$$
- The circuit:





4-to-1 MUX

 


MUX as a Universal Gate

  - All basic gates can be designed using 2-to-1 MUXs. Thus, 2-to-1 MUX is a universal gate.



$$z = 0x + 1x' = x'$$

 

$$z = x_1 x_0 + 0x_0' = x_1 x_0$$

Implementing Boolean functions with Multiplexers

- Any Boolean function of n variables can be implemented using a 2^{n-1} -to-1 multiplexer.
- The SELECT signals generate the minterms of the function.
- The data inputs identify which minterms are to be combined with an OR.
- Example


Implement $F(X,Y,Z) = \Sigma m(1,2,6,7)$ using Multiplexers

$$\Sigma m(1,2,6,7) = X'Y'Z + X'YZ' + XYZ' + XYZ$$

- $X'Y'Z + X'YZ' + XYZ' + XYZ$
- There are $n=3$ inputs, thus we need a 4-to-1 MUX
- The first $n-1$ ($=2$) inputs serve as the selection lines

X	Y	Z	F	
0	0	0	0	$F = Z$
0	0	1	1	
0	1	0	1	$F = \bar{Z}$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 

(b) Multiplexer implementation

Efficient Method for implementing Boolean functions

- For an n -variable function (*e.g.*, $f(A,B,C,D)$):
 - Need a 2^{n-1} line MUX with $n-1$ select lines.
 - Enumerate function as a truth table with consistent ordering of variables (*e.g.*, A,B,C,D)
 - Attach the most significant $n-1$ variables to the $n-1$ select lines (*e.g.*, A,B,C)
 - Examine pairs of adjacent rows (only the least significant variable differs, *e.g.*, $D=0$ and $D=1$).
 - Determine whether the function output for the $(A,B,C,0)$ and $(A,B,C,1)$ combination is $(0,0)$, $(0,1)$, $(1,0)$, or $(1,1)$.
 - Attach 0 , D , D' , or 1 to the data input corresponding to (A,B,C) respectively.

Example

- Consider $F(A,B,C) = \sum m(1,3,5,6)$.
- We can implement this function using a 4-to-1 MUX as follows.
- The inputs are A,B,C. Apply A and B to the S_1 and S_0 selection inputs of the MUX
- Enumerate function in a truth table.

When $A=B=0$, $F=C$

When $A=0$, $B=1$, $F=C$

When $A=1$, $B=0$, $F=C$

When $A=B=1$, $F=C'$

— [

— [


— [

— [

A	B	C		F
0	0	0		0
0	0	1		1
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		1
1	1	0		1
1	1	1		0

A larger Example

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

 


DECODERS

- A combinational circuit that converts binary information from n coded inputs to a maximum 2^n coded outputs

n -to- m decoder, $m \leq 2^n$


□ n -to- 2^n decoder

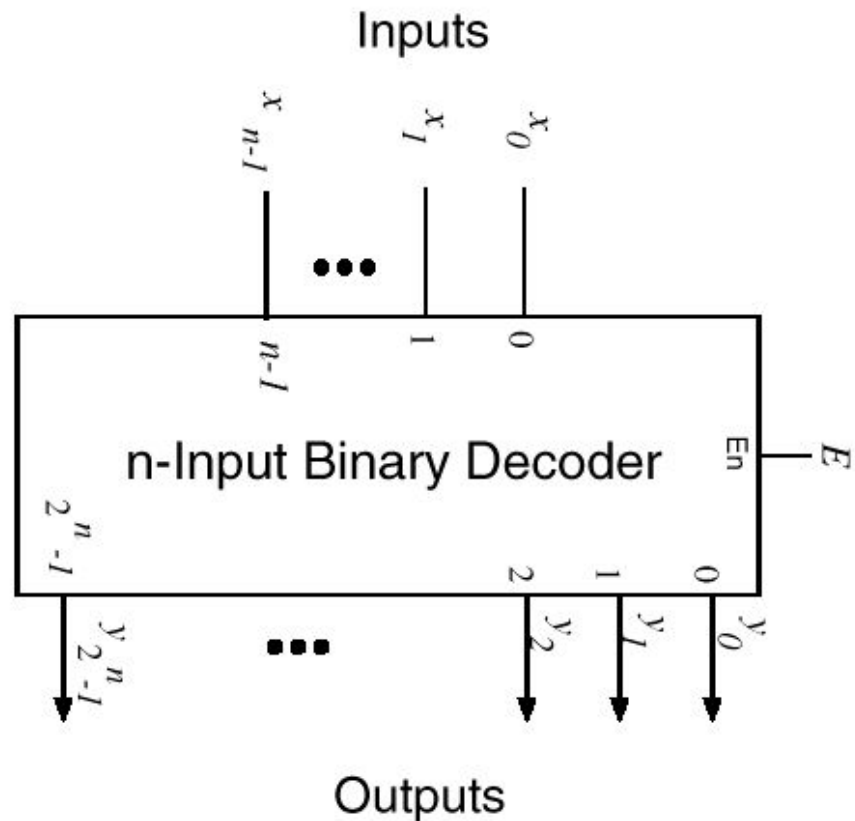

1-2 Decoder

A	D₀	D₁
0	1	0
1	0	1

(a)

 


(b)

2-to-4 Decoder

A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

 


(b)


2-to-4 Active Low Decoder

Figure 4.5 An active low decoder.

<i>a</i>	<i>b</i>	<i>0</i>	<i>1</i>	<i>2</i>	<i>3</i>
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

 

3-to-8 Decoder

 


3-to-8 Decoder (cont.)

- Three inputs, A_0 , A_1 , A_2 , are decoded into eight outputs, D_0 through D_7
- Each output D_i represents one of the minterms of the 3 input variables.
- $D_i = 1$ when the binary number $A_2A_1A_0 = i$
- Shorthand: $D_i = m_i$
- The output variables are mutually exclusive; exactly one output has the value 1 at any time, and the other seven are 0.

Decoder with enable

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

 


(b)

Implementing Boolean functions using decoders

- Any combinational circuit can be constructed using decoders and OR gates!
- Here is an example:
Implement a full adder circuit with a decoder and two OR gates.
- Recall full adder equations, and let X, Y, and Z be the inputs:
 - $S(X,Y,Z) = X+Y+Z = \Sigma m(1,2,4,7)$
 - $C(X,Y,Z) = \Sigma m(3, 5, 6, 7)$.
- Since there are 3 inputs and a total of 8 minterms, we need a 3-to-8 decoder.

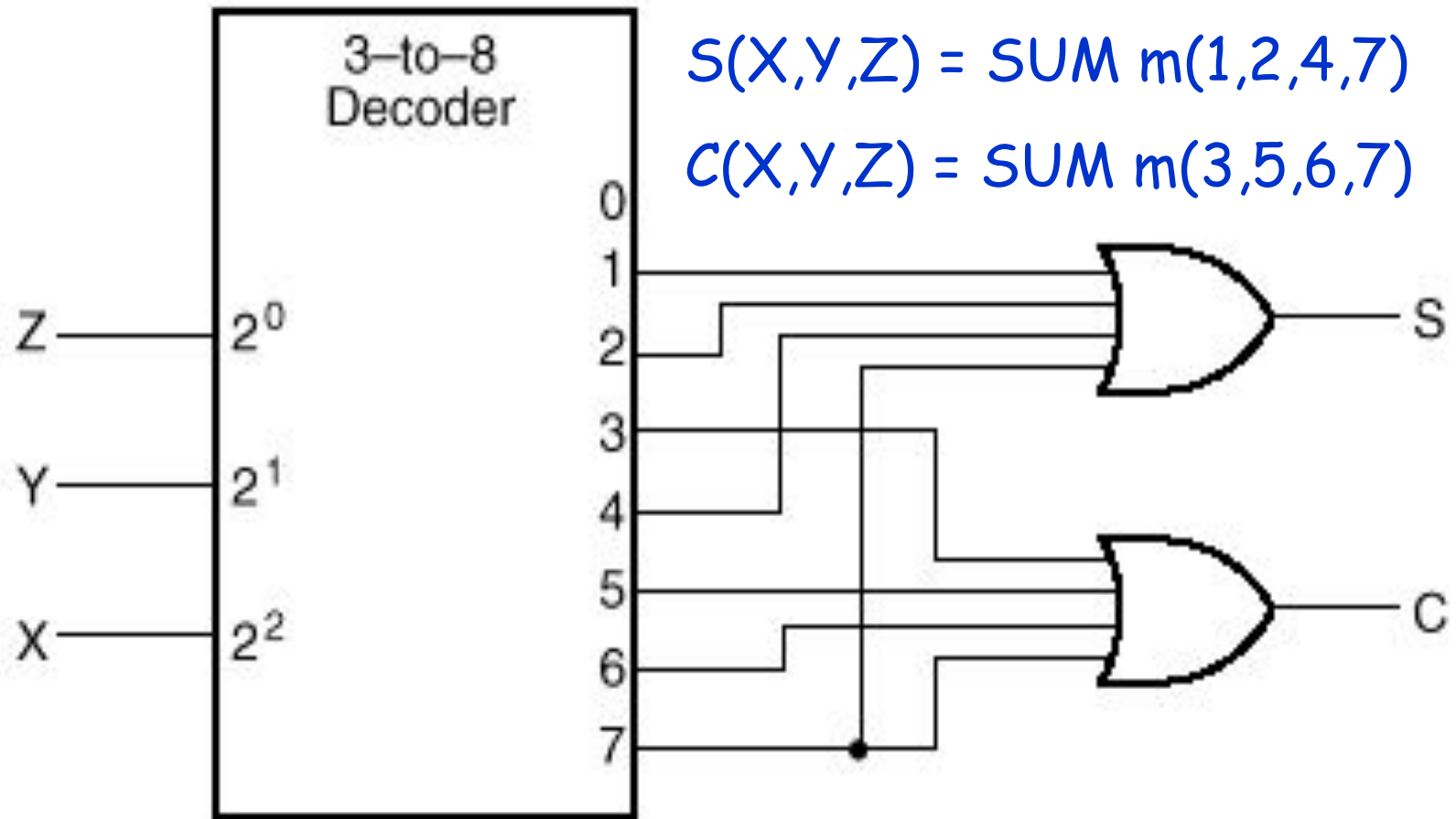Implementing a Binary Adder Using a Decoder



ENCODERS

- An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has 2^n input lines and n output lines.
- The output lines generate the binary equivalent to the input line whose value is 1.

Encoders (cont.)

 


Figure 9.12: 2^n -input binary encoder.

Encoder Example

- Example: 8-to-3 binary encoder (octal-to-binary)

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

 


Figure 9.13: Implementation of an 8-input binary encoder.

Encoder Design Issues

- There are two ambiguities associated with the design of a simple encoder:
 1. Only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination (for example, if D_3 and D_6 are 1 simultaneously, the output of the encoder will be 111).
 2. An output with all 0's can be generated when all the inputs are 0's, or when D_0 is equal to 1.



PRIORITY ENCODERS

- Solves the ambiguities mentioned above.
- Multiple asserted inputs are allowed; one has priority over all others.
- Separate indication of no asserted inputs.


Example: 4-to-2 Priority Encoder

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

  - The operation of the priority encoder is such that:
 - If two or more inputs are equal to 1 at the same time, the input in the highest-numbered position will take precedence.
 - A ***valid output indicator***, designated by V, is set to 1 only when one or more inputs are equal to 1.
 - $V = D_3 + D_2 + D_1 + D_0$ by inspection.



Logic Diagram

 

8-to-3 Priority Encoder

Table 4.6 A priority encoder.

A_0	A_1	A_2	A_3	A_4	A_5	A_6	A_7	Z_0	Z_1	Z_2	NR
0	0	0	0	0	0	0	0	X	X	X	1
X	X	X	X	X	X	X	1	1	1	1	0
X	X	X	X	X	X	1	0	1	1	0	0
X	X	X	X	X	1	0	0	1	0	1	0
X	X	X	X	1	0	0	0	1	0	0	0
X	X	X	1	0	0	0	0	0	1	1	0
X	X	1	0	0	0	0	0	0	1	0	0
X	1	0	0	0	0	0	0	0	0	1	0
1	0	0	0	0	0	0	0	0	0	0	0

Uses of priority encoders

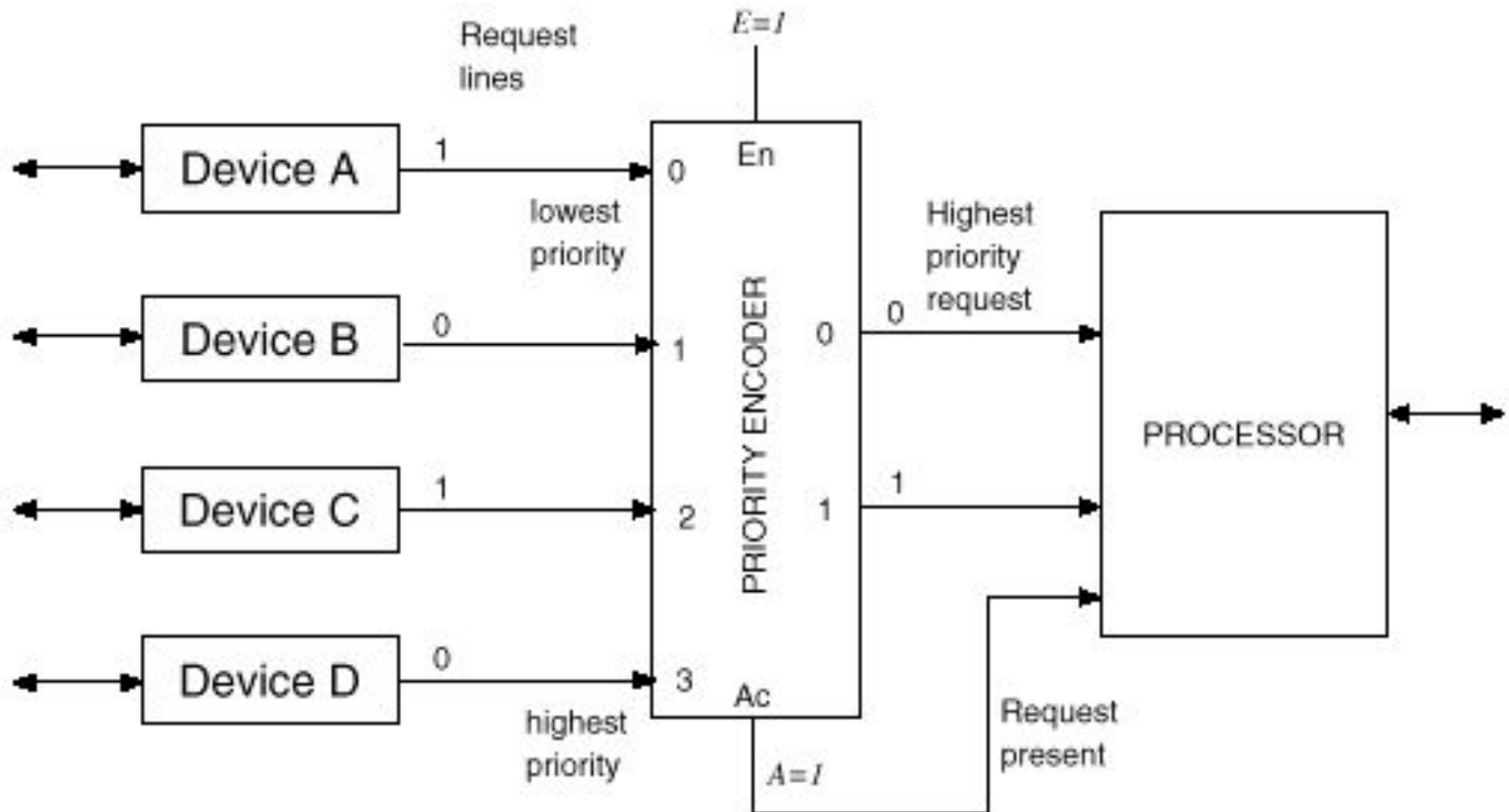



Figure 9.17: Resolving interrupt requests using a priority encoder.

COMPARATOR

MAGNITUDE COMPARATOR

- A magnitude comparator determines the larger of two binary numbers.
- The comparison of two numbers and gives outputs: $A > B$, $A = B$, $A < B$
- Design Approaches
 - the truth table- 2^{2n} entries - too cumbersome for large n
 - use inherent regularity of the problem to reduce design efforts

1 bit comparators

 


(b)

X_i	Y_i	$X > Y$	$X = Y$	$X < Y$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

- $X > Y$ only if $X_i=1, Y_i=0$
- $X < Y$ only if $X_i=0, Y_i=1$
- $X = Y$ only if $X_i=Y_i=0$ or $X_i=Y_i=1$

4 bit Comparator

 - To compare two unsigned numbers A and B, compute $B - A = B + A + 1$.
- If there is a carry-out, $A \leq B$; otherwise, $A > B$.
- The relative magnitude is determined from the carry-out (C) and zero (Z) signals according to Table




4-bit unsigned comparator built from a carry-ripple adder and two's complementer.

Relation	Unsigned Comparison
$A = B$	Z
$A \neq B$	\bar{Z}
$A < B$	$C \cdot \bar{Z}$
$A > B$	C
$A \leq B$	C
$A \geq B$	$\bar{C} + Z$

EQUALITY COMPARATOR

 
- An equality comparator determines if $(A = B)$ with XNOR gates and a ones detector,



ADDITION OF BINARY NUMBERS

Full Adder. The full adder is the fundamental building block of most arithmetic circuits:

 The sum and carry outputs are described as:




$$\text{Sum} = A \oplus B \oplus C_{in}$$

$$C_{out} = A.B + B.C_{in} + A.C_{in}$$

Carry-Ripple Adder

Simplest design: Cascading full adders

 

Critical path goes from C_{in} to C_{out}

Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N-1)t_{\text{carry}} + t_{\text{sum}}$$

Carry Look-ahead Adder

- Try to “predict” C_i earlier than $T_c * n$
- Instead of passing through n stages, compute C_i separately
- A carry-lookahead adder improves speed by reducing the amount of time required to determine carry bits.

<i>Inputs</i>			<i>Outputs</i>	
c_i	a_i	b_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Propagate: $c_i = 0, a_i \oplus b_i = 1 \Rightarrow c_{i+1} = 0$
 Propagate: $c_i = 0, a_i \oplus b_i = 1 \Rightarrow c_{i+1} = 0$
 Generate: $c_i = 0, a_i \wedge b_i = 1 \Rightarrow c_{i+1} = 1$
 Propagate: $c_i = 1, a_i \oplus b_i = 1 \Rightarrow c_{i+1} = 1$
 Propagate: $c_i = 1, a_i \oplus b_i = 1 \Rightarrow c_{i+1} = 1$
 Generate: $c_i = 1, a_i \wedge b_i = 1 \Rightarrow c_{i+1} = 1$

- Carry look-ahead logic uses the concepts of *generating* and *propagating* carries.

$$g_i = a_i \bullet b_i$$

$$p_i = a_i \oplus b_i$$

- The addition of two inputs A and B is said to *generate* if the addition will always carry, regardless of whether there is an input carry

$$s_i = a_i \oplus b_i \oplus c_i = p_i \oplus c_i$$


- The addition of two inputs A and B is said to *propagate* if the addition will carry whenever there is an input carry

$$c_{i+1} = g_i + p_i c_i$$

$$C_{out} = A \bullet B + A \bullet C + B \bullet C$$

$$C_{out} = \underbrace{A \bullet B}_{\text{Carry Generate}} + \underbrace{(A + B) \bullet C}_{\text{Carry Propagate}}$$

CLA: 4-bit adder

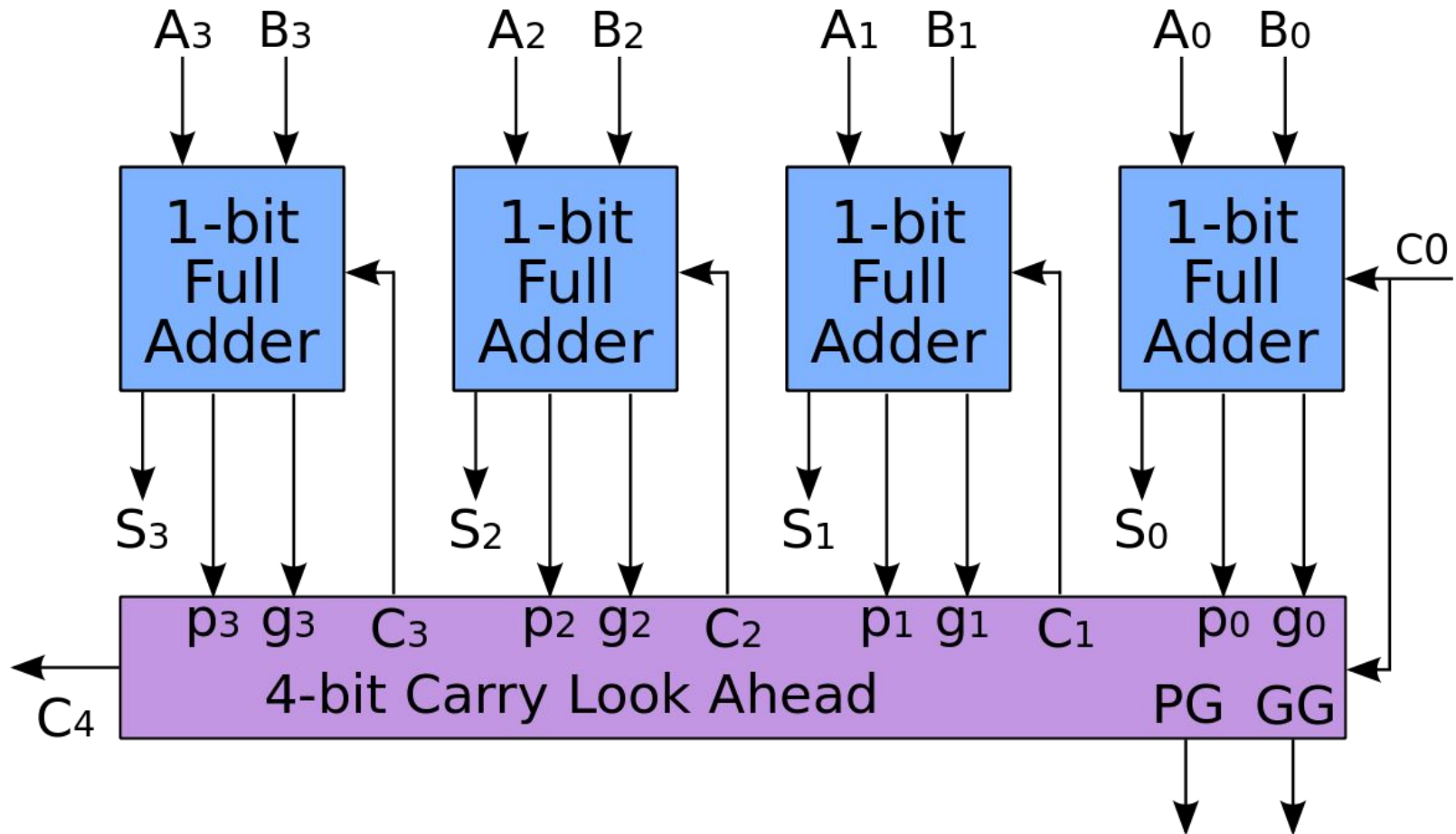


$$\begin{array}{lll}
C_1 = G_0 + P_0 C_0 & C_2 = G_1 + P_1 C_1 & C_3 = G_2 + P_2 C_2 \\
C_2 = G_1 + P_1 (G_0 + P_0 C_0) & C_3 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) & \\
C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0 & C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 &
\end{array}$$

$$C_4 = G_3 + P_3 C_3$$

$$C_4 = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0)$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

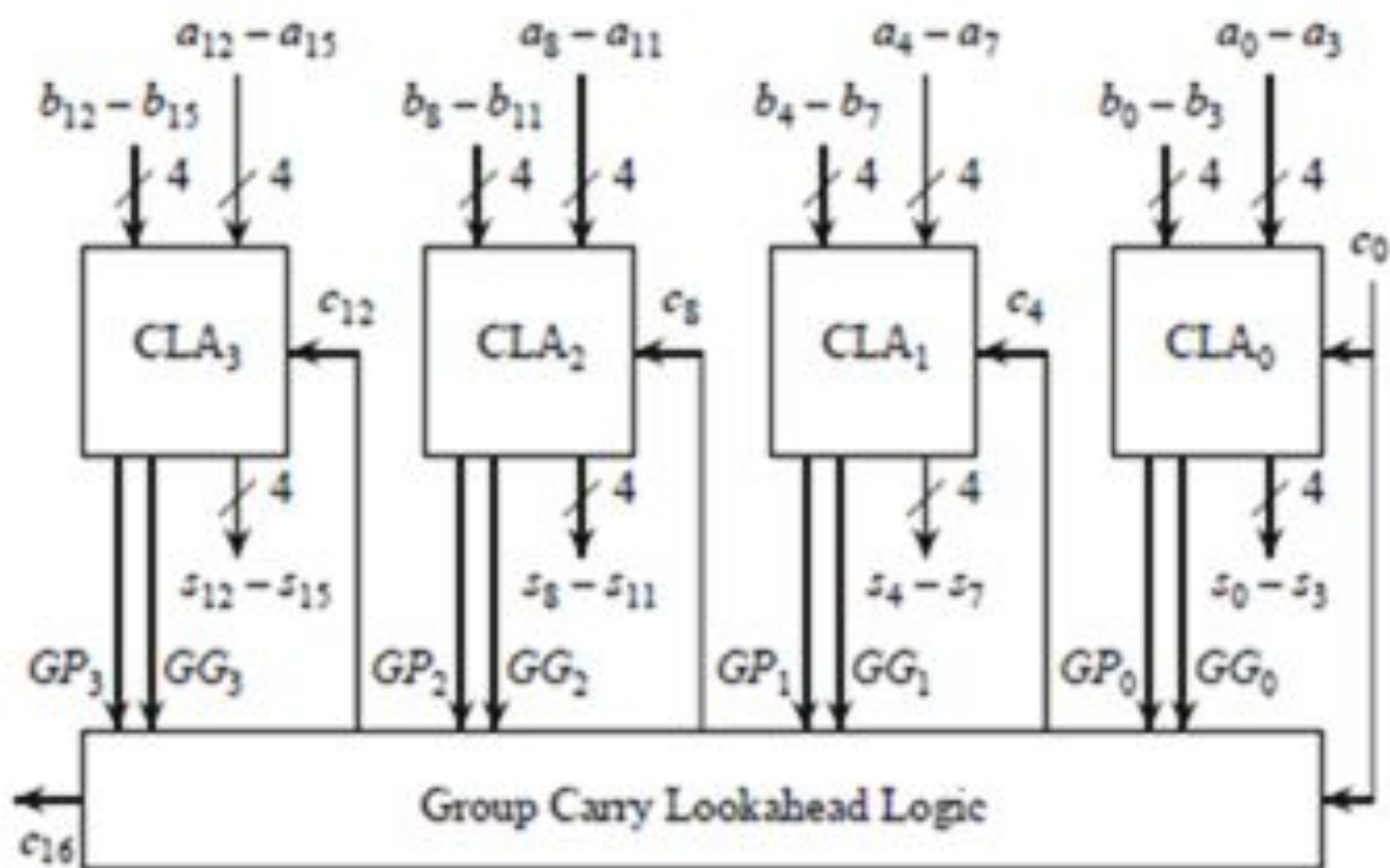- As the number of bit increases length of the expression increases.
- However each expression is only three logic levels deep.
- Logic does rapidly become cumbersome and provides fan-out and fan-in problem.



Carry lookahead depends on two things:

- Calculating, for each digit position, whether that position is going to propagate a carry if one comes in from the right.
- Combining these calculated values to be able to deduce quickly whether, for each group of digits, that group is going to propagate a carry that comes in from the right.

Supposing that groups of four digits are chosen. Then the sequence of events goes something like this:

- All 1-bit adders calculate their results. Simultaneously, the lookahead units perform their calculations.
- Suppose that a carry arises in a particular group. Within at most five gate delays, that carry will emerge at the left-hand end of the group and start propagating through the group to its left.
- If that carry is going to propagate all the way through the next group, the lookahead unit will already have deduced this. Accordingly, *before the carry emerges from the next group*, the lookahead unit is immediately (within one gate delay) able to tell the *next* group to the left that it is going to receive a carry – and, at the same time, to tell the next lookahead unit to the left that a carry is on its way.
- The net effect is that the carries start by propagating slowly through each 4-bit group, just as in a ripple-carry system, but then move four times as fast, leaping from one lookahead carry unit to the next. Finally, within each group that receives a carry, the carry propagates slowly within the digits in that group.

Let Δ be One gate delay

- Delay of one Δ to calculate p, g
- Delay of two Δ to generate C_i
- Delay of two Δ to generate S_i

• Total of five Δ regardless of n.

CLA compared to ripple-carry adder:

- 4 times Faster but delay still linear (w.r.t. # of bits)
- Larger area

P, G signal generation

Carry generation circuits

Carry generation circuit for each bit position (no re-use)

- Limitation: cannot go beyond 4 bits of look-ahead

Large fan-out slows down carry generation


```

module CLA_4bmod(sum,c_4,a,b,c_0);
input [3:0]a,b;
input c_0;
output [3:0]sum;
output c_4;
wire p0,p1,p2,p3,g0,g1,g2,g3;
wire c1,c2,c3,c4;
assign
p0=a[0]^b[0],
p1=a[1]^b[1],
p2=a[2]^b[2],
p3=a[3]^b[3],
g0=a[0]&b[0],
g1=a[1]&b[1],
g2=a[2]&b[2],
g3=a[3]&b[3];
assign
c1=g0|(p0&c_0),
c2=g1|(p1&g0)|(p1&p0&c_0),
c3=g2|(p2&g1)|(p2&p1&g0)|(p2&p1&p0&
c_0),
c4=g3|(p3&g2)|(p3&p2&p1&g1)|(p3&p2&
p1&g0)|(p3&p2&p1&p0&c_0);
assign
sum[0]=p0^c_0,
sum[1]=p1^c1,
sum[2]=p2^c2,
sum[3]=p3^c3,
c_4=c4;
endmodule

```

Carry Skip Adder

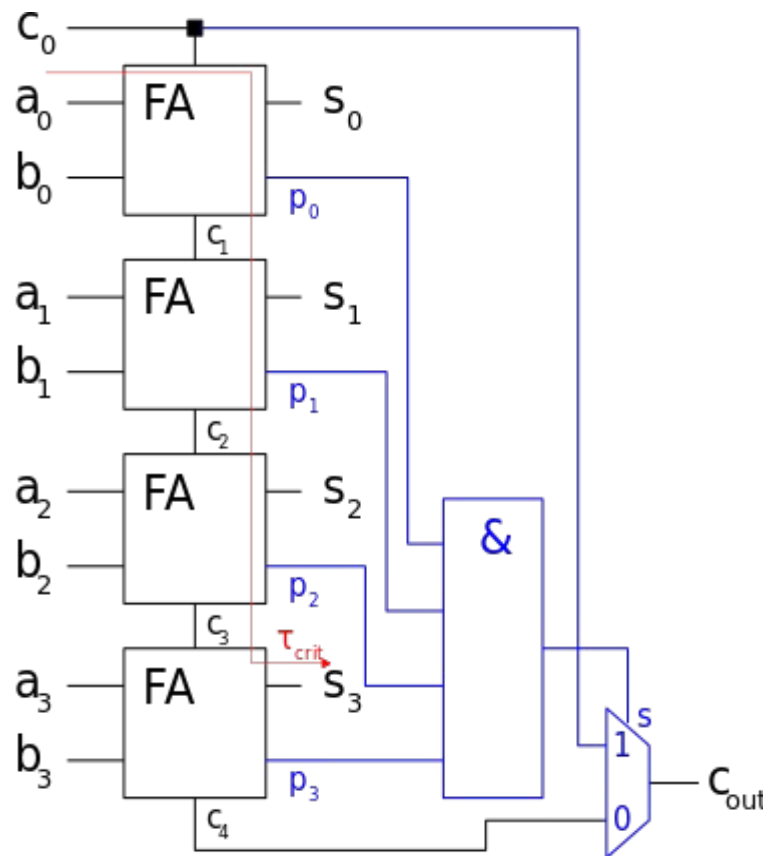- A **carry-skip adder/ carry-bypass adder** improves the delay of a ripple-carry adder.
- A n -bit-carry-skip adder consists of a n -bit-carry-ripple-chain, a n -input AND-gate and one multiplexer.



- For each operand input bit pair (a_i , b_i) the propagate-conditions are determined using an XOR-Gate. $p_i = a_i \oplus b_i$
- Each propagate bit that is provided by the carry-ripple-chain is connected to the n -input AND-gate.
- The resulting bit is used as the select bit of a multiplexer that switches either the last carry-bit or the carry-in to the carry-out signal .
- The carry bit for each block can now "skip" over blocks with a *group* propagate signal set to logic 1 . This greatly reduces the latency of the adder
- The number of inputs of the AND-gate is equal to the width of the adder. For a large width, this becomes impractical and leads to additional delays, because the AND-gate has to be built as a tree.
- A good width is achieved, when the sum-logic has the same depth like the n -input AND-gate and the multiplexer.

```
module carry_skip_4bit(a, b, cin, sum,
cout);
```

```
input [3:0] a,b;
```

```
input cin;
```

```
output [3:0] sum;
```

```
output cout;
```

```
wire [3:0] p;
```

```
wire c0;
```

```
wire bp;
```

```
ripple_carry_4_bit rca1
```

```
(a[3:0],b[3:0],cin,sum[3:0],c0);
```

```
propagate_p p1(a,b,p,bp);
```

```
mux2X1 m0(c0,cin,bp,cout);
```

```
endmodule
```

```
module propagate_p(a,b,p,bp);
```

```
input [3:0] a,b;
```

```
output [3:0] p;
```

```
output bp;
```

```
assign p= a^b;//get all propagate bits
```

```
assign bp= &p;// and p0p1p2p3 bits
```

```
endmodule
```

```
module ripple_carry_4_bit(a, b, cin,
sum, cout);
```

```
input [3:0] a,b;
```

```
input cin;
```

```
wire c1,c2,c3;
```

```
output [3:0] sum;
```

```
output cout;
```

```
full_adder fa0(a[0], b[0],cin,
```

```
sum[0],c1);
```

```
full_adder fa1(a[1], b[1],c1,
```

```
sum[1],c2);
```

```
full_adder fa2(a[2], b[2],c2,
```

```
sum[2],c3);
```

```
full_adder fa3(a[3], b[3],c3,
```

```
sum[3],cout);
```

```
endmodule
```


```
module full_adder(a,b,cin,sum, cout);  
input a,b,cin;  
output sum, cout;  
wire x,y,z;  
half_adder h1(a,b,x,y);  
half_adder h2(x,cin,sum,z);  
or or_1(cout,z,y);  
endmodule
```

```
module half_adder( a,b, sum, cout );  
input a,b;  
output sum, cout;  
xor xor_1 (sum,a,b);  
and and_1 (cout,a,b);  
endmodule
```


```
module mux2X1( in0,in1,sel,out);  
input in0,in1;  
input sel;  
output out;  
assign out=(sel)?in1:in0;  
endmodule
```



Carry Select Adder

- Consists of two ripple carry adders and a multiplexer.
- Adding two n-bit numbers with a carry-select adder is done with two adders (therefore two ripple carry adders).
- The calculation is performed twice,
 - one time with the assumption of the carry-in being zero
 - the other assuming it will be one.
- After the two results are calculated, the correct sum, as well as the correct carry-out, is then selected with the multiplexer once the correct carry-in is known.

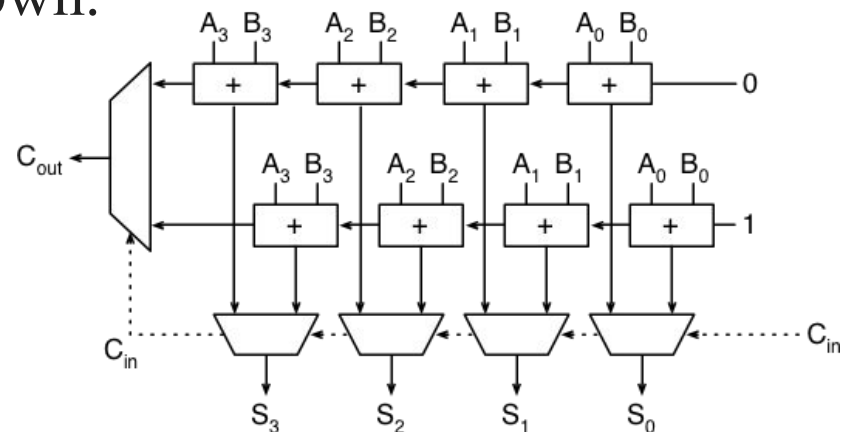

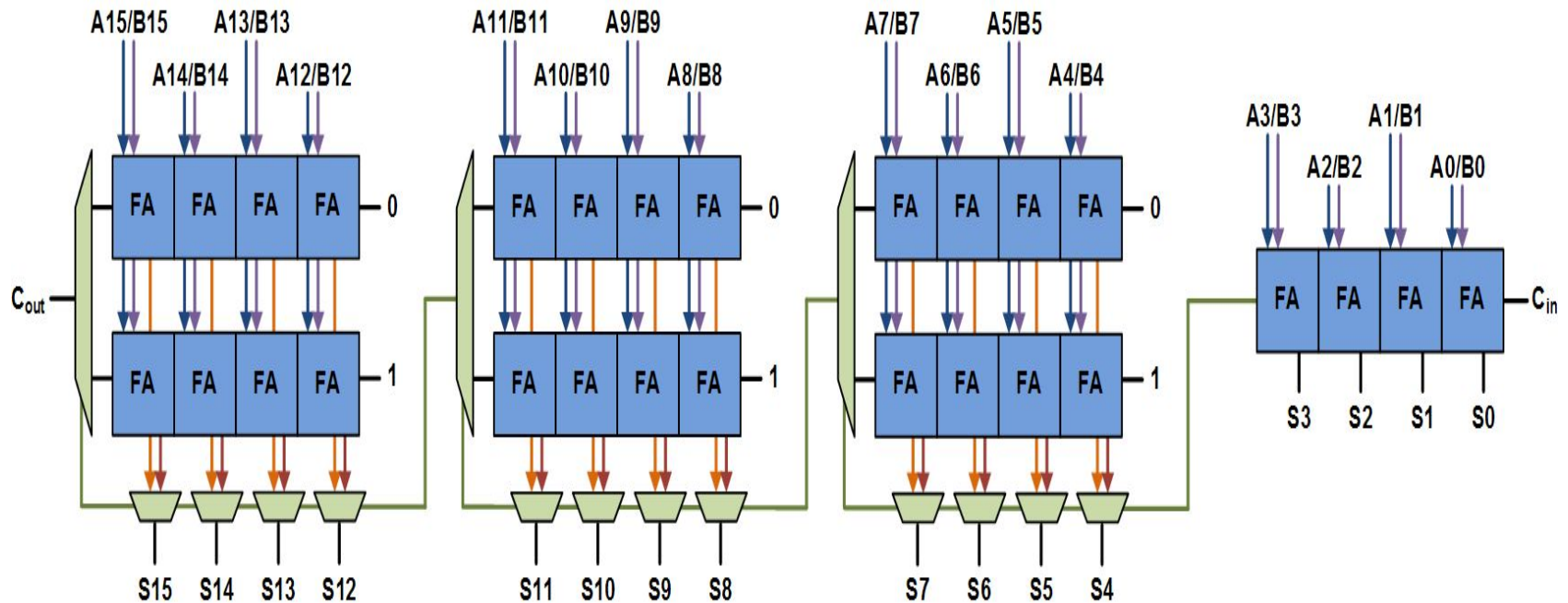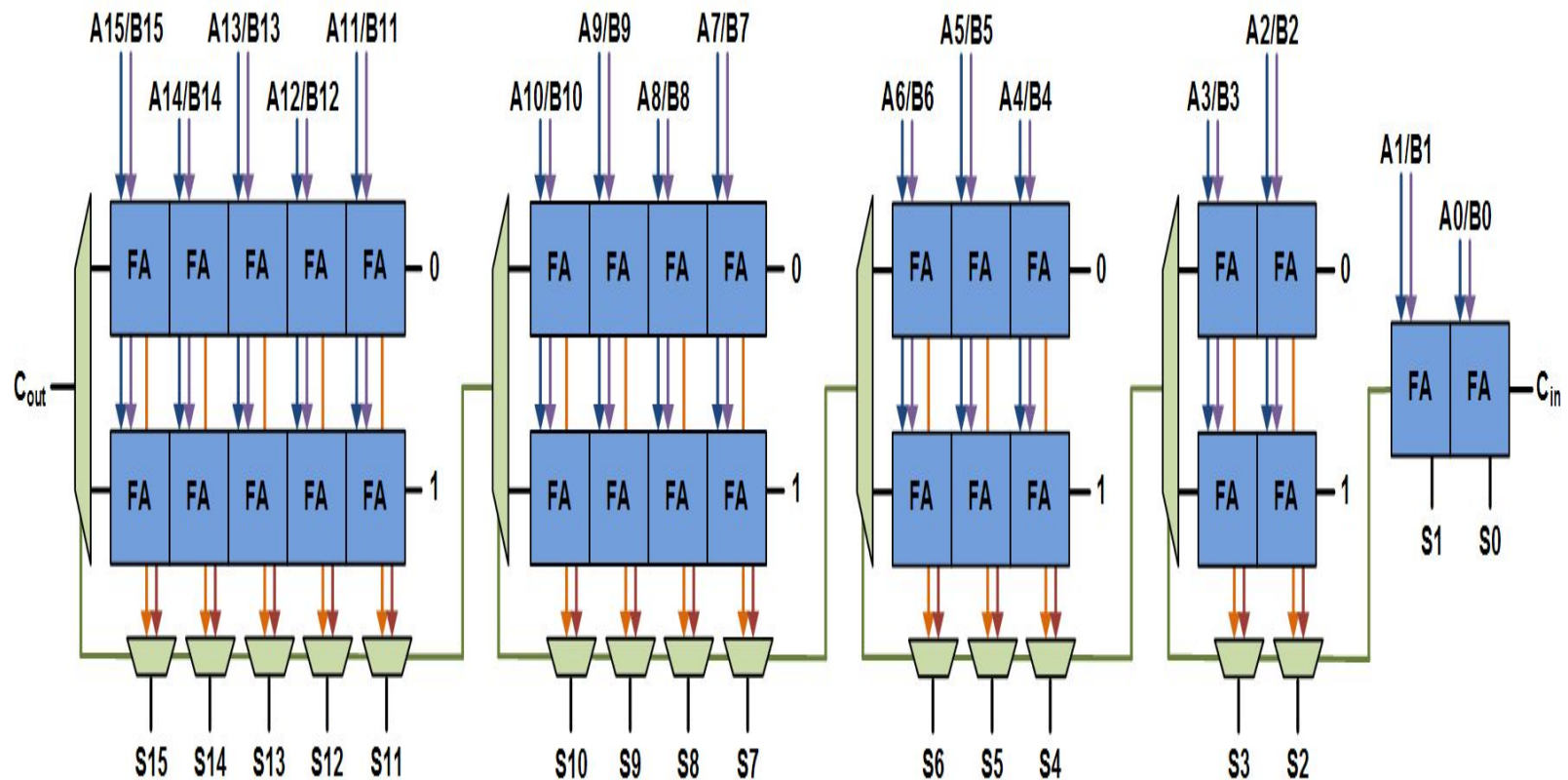- The number of bits in each carry select block can be uniform, or variable. In the uniform case, the optimal delay occurs for a block size of $(O\sqrt{n})$
- When variable, the block size should have a delay, from addition inputs A and B to the carry out, equal to that of the multiplexer chain leading into it






$$T_{add} = T_{setup} + M \cdot t_{carry} + (N/M) \cdot T_{mux} + T_{sum}$$

Carry Save Adder

 
- Set of one-bit full adders, without any carry-chaining.
- n-bit CSA receives three n-bit operands, namely A, B and CIN and generates two n-bit result values SUM, COUT.
- The final stage must be a normal adder because we need to obtain a single output.




$$(C, S) = C + S = A_0 + A_1 + A_2$$


$$2c_{i+1} + s_i = a_{0,i} + a_{1,i} + a_{2,i}$$

$$i = 0, 1, \dots, n-1$$

 

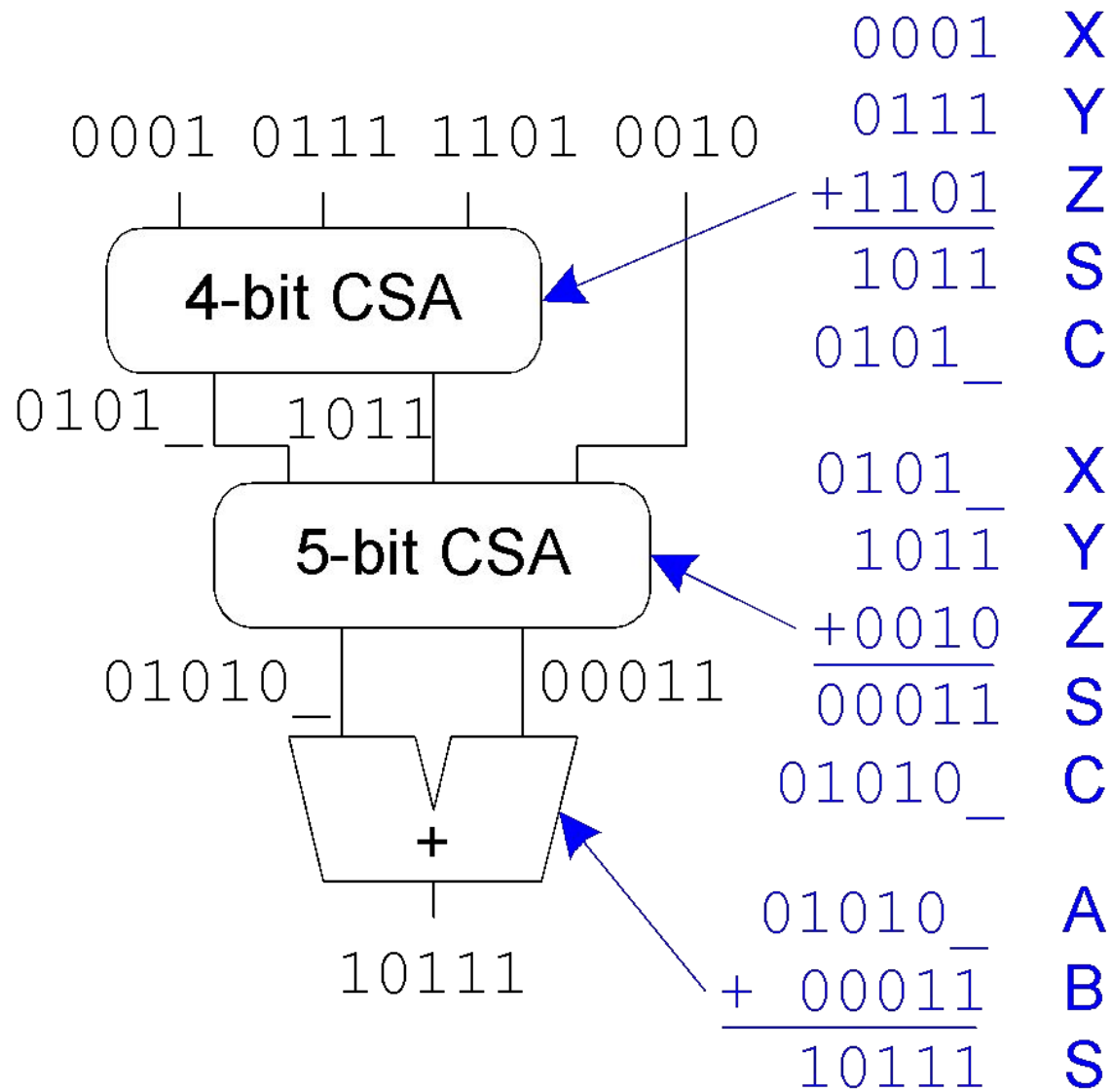

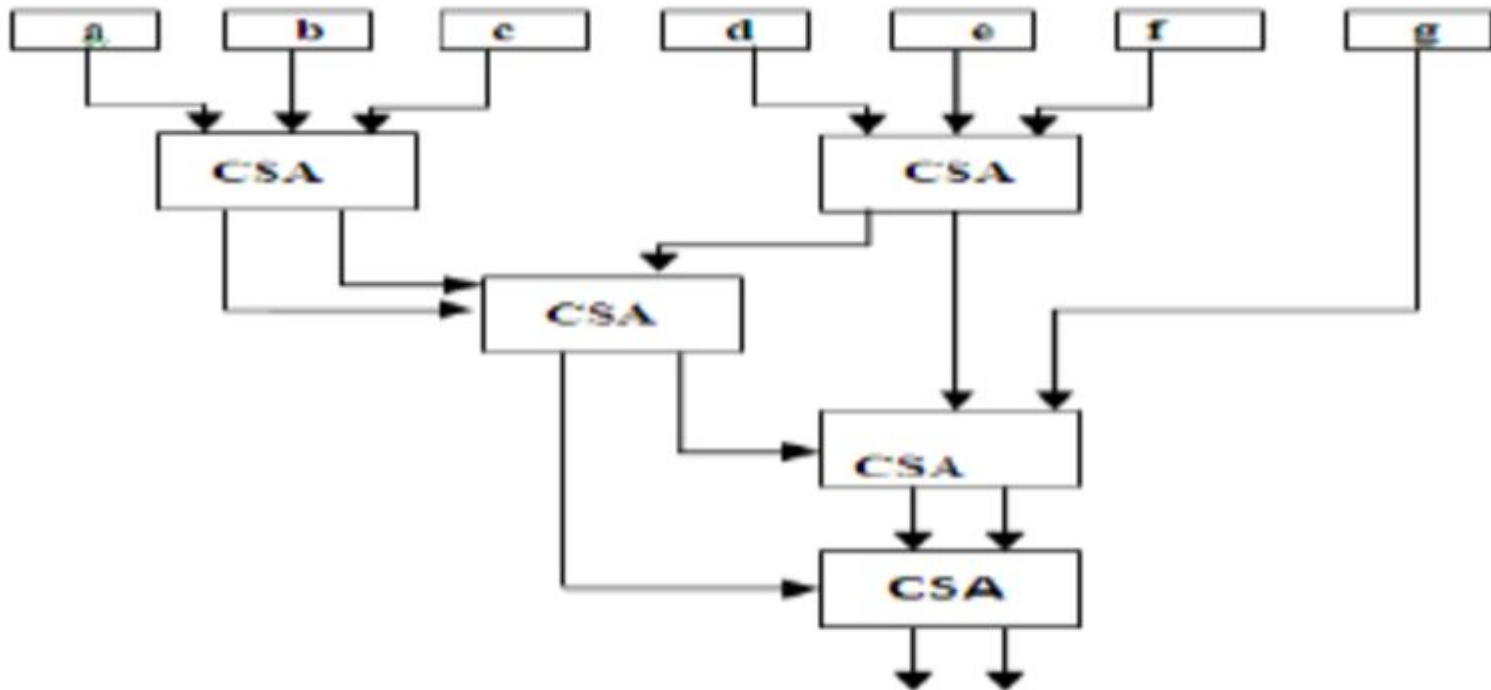- The delay is the same as for a conventional look-ahead adder tree but uses much less circuitry.
- The irregularity of the tree causes a reduction in efficiency but this is relatively small (and becomes even smaller for large K).



Multiplier

- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- Product:
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$

						multiplicand					
						y_5	y_4	y_3	y_2	y_1	y_0
						x_5	x_4	x_3	x_2	x_1	x_0
						<hr/>					
						$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$
					$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$	
				$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$		
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$			
		$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$				
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$					
<hr/>											
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0


]

partial
products


product

				1	0	1	0	1	0		Multiplicand
x					1	0	1	1			Multiplier
<hr/>											
				1	0	1	0	1	0		} Partial products
			1	0	1	0	1	0			
		0	0	0	0	0	0				
	+	1	0	1	0	1	0				
<hr/>											
		1	1	1	0	0	1	1	1	0	Result

Array Multiplier

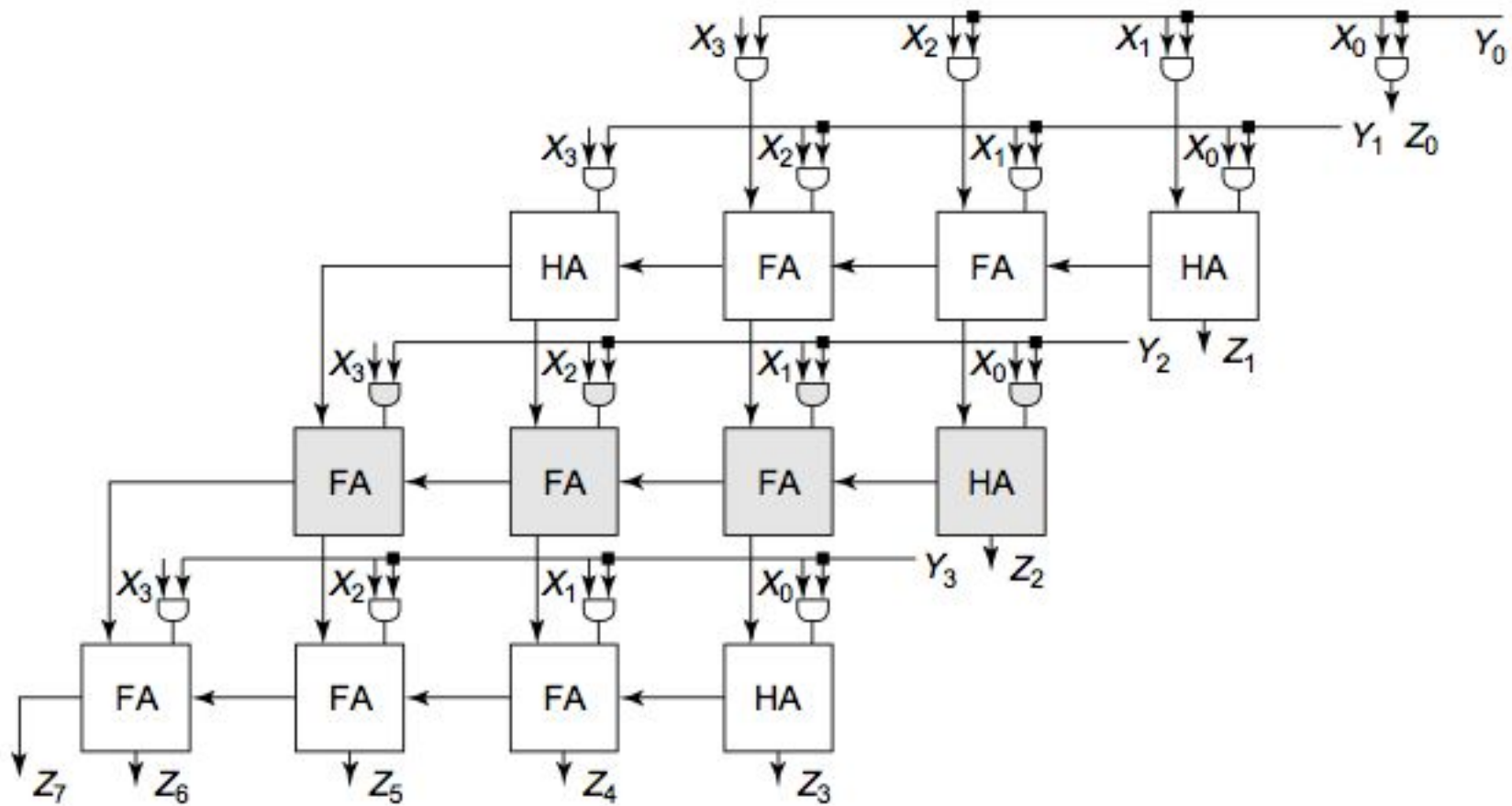

Critical path

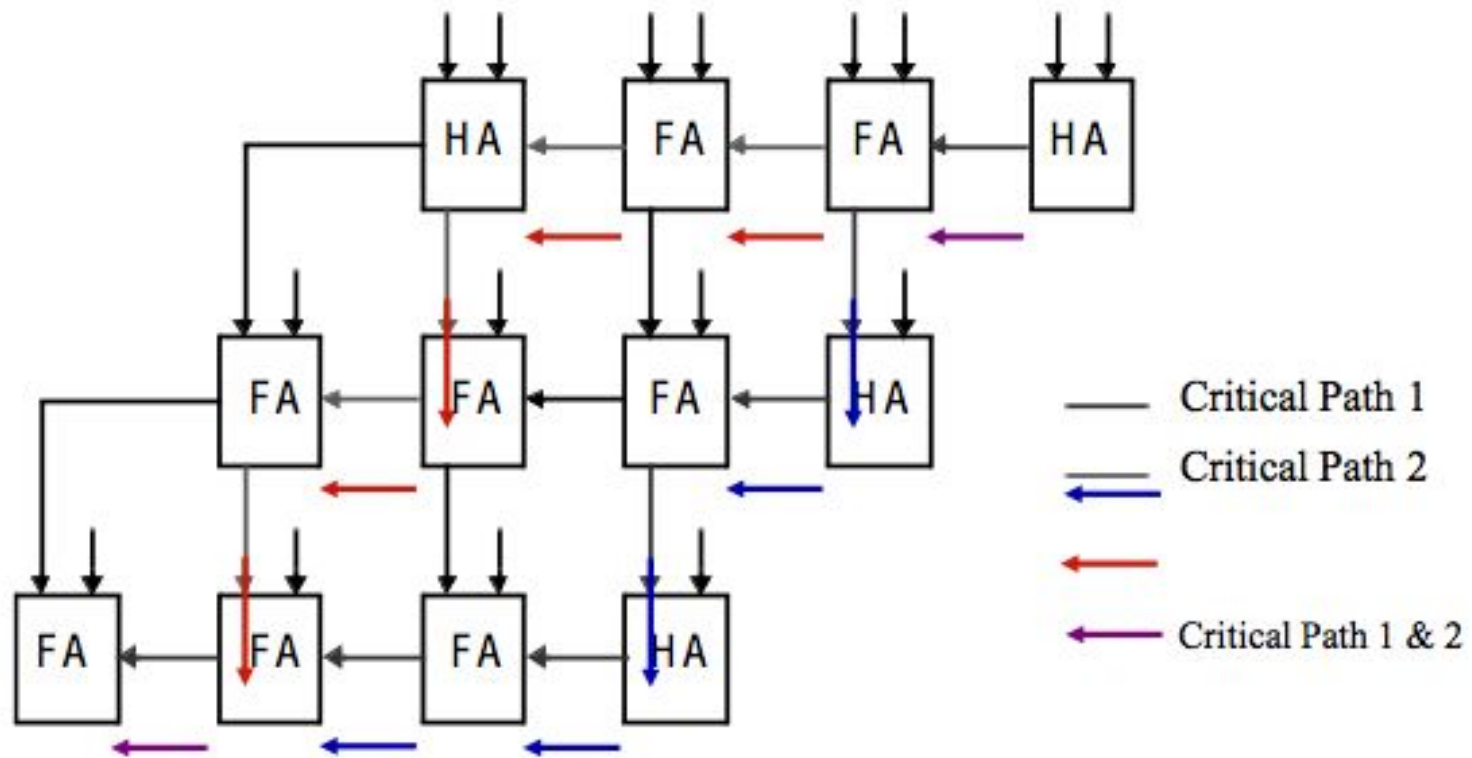


$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$


Multiplication Algorithm

- Generation of partial products
- Adding up partial products
 - Sequentially (sequential shift and add)
 - Serially (combinational shift and add)
 - In parallel
- Speed-up techniques
 - Reduce the number of partial products
 - Accelerate addition of partial products

BRAUN Multiplier

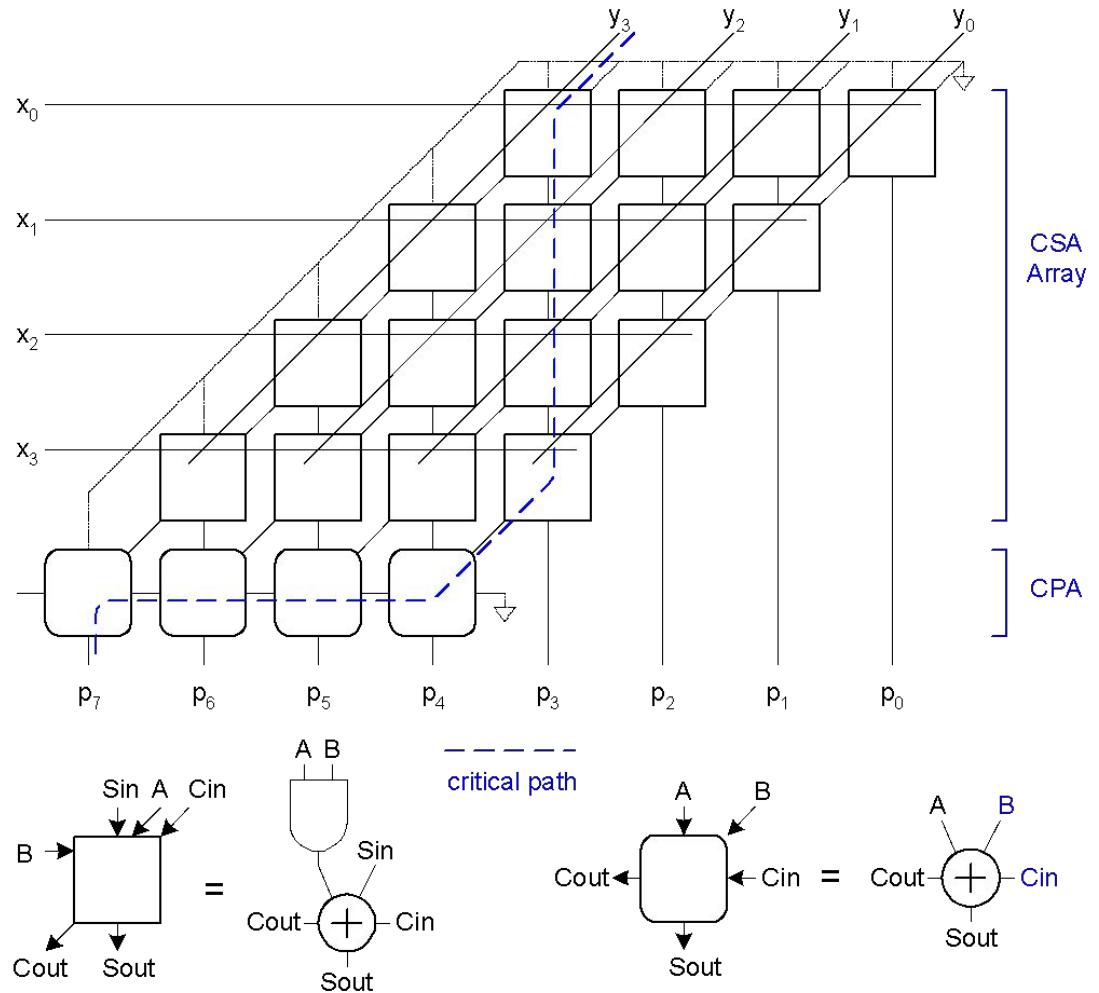- Consists of an array of AND gates and CSA arranged in an iterative structure and a final CPA
- Does not require any logic registers
- Restricted to multiplication of two unsigned numbers



 

- Performs well for unsigned operands that are less than 16 bits in terms of speed, power and area
- Simple and regular structure as compared to the other multipliers
- No. of components required increases quadratically with the no. of bits
- The delay of the multiplier is given by

$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

Booth's Multiplier

- Multiplies two signed binary numbers in two's complement notation.
- Uses shifting than adding to increase their speed.
- Recall grade school trick
When multiplying by 9:
 - Multiply by 10 (easy, just shift digits left)
 - Subtract once
- Booth's algorithm applies same principle

When using Booth's Algorithm:

- You will need twice as many bits in your **product** as you have in your original two **operands**.
- The **leftmost bit** of your operands (both your multiplicand and multiplier) is a SIGN bit, and cannot be used as part of the value.
- Decide which operand will be the **multiplier** and which will be the **multiplicand**
- Convert both operands to **two's complement** representation using X no. of bits

- X must be at least one more bit than is required for the binary representation of the numerically larger operand
- Begin with a product that consists of the multiplier with an additional 'X no. of leading zero bits'.
- For our example, let's multiply **$(-5) \times 2$**
The numerically larger operand (5) would require 3 bits to represent in binary (101). So we must use AT LEAST 4 bits to represent the operands, to allow for the sign bit.
- Let's use 5-bit 2's complement
-5 is **11011** (multiplier)
2 is **00010** (multiplicand)

- The multiplier is:
11011 (-5 in 2's complement)
- Add 5 leading zeros to the **multiplier** to get the **beginning product**:

00000 11011

STEP 1

- Use the **LSB** and the **previous LSB** to determine the arithmetic action.
If it is the **FIRST** pass, use 0 as the previous LSB.
- Possible arithmetic actions:
 - 00 ☐ no arithmetic operation
 - 01 ☐ add multiplicand to left half of product
 - 10 ☐ subtract multiplicand from left half of product
 - 11 ☐ no arithmetic operation

STEP 2

- Perform an **arithmetic right shift (ASR)** on the entire product.
- **NOTE:** For X-bit operands, Booth's algorithm requires X passes.
- Initial Product and **previous LSB**
00000 11011 0
- (Note: Since this is the first pass, we use 0 for the previous LSB)
- **Pass 1, Step 1:** Examine the last 2 bits
00000 1101**1** 0
- The last two bits are **10**, so we need to subtract the **multiplicand** from left half of product

Pass 1, Step 1: Arithmetic action

(1) 00000 (left half of product)
-00010 (multiplicand)
11110 (uses a phantom borrow)

Place result into **left half** of product

11110 11011

Step 2: ASR (arithmetic shift right)

Before ASR

11110 11011

After ASR

11111 01101

(left-most bit was 1, so a 1 was shifted in on the left)

Pass 1 is complete.

- Current Product and previous LSB

11111 01101 1

- Pass 2, Step 1: Examine the last 2 bits

11111 01101 1

- The last two bits are 11, so we do NOT need to perform an arithmetic action just proceed to step 2.
- Step 2: ASR (arithmetic shift right)

Before ASR

11111 01101 1

After ASR

11111 10110 1

(left-most bit was 1, so a 1 was shifted in on the left)

- Pass 2 is complete.

- Current Product and **previous LSB**

11111 10110 1

- **Pass 3**, Step 1: Examine the last 2 bits

11111 10110 1

The last two bits are **01**, so we need to add the **multiplicand** to the left half of the product

Arithmetic action

(1) 11111 (left half of product)
 +00010 (multiplicand)

 00001 (drop the leftmost carry)

Place result into **left half** of product

00001 10110 1

- Step 2: ASR (arithmetic shift right)

Before ASR

00001 10110 1

After ASR

00000 11011 0

(left-most bit was 0, so a 0 was shifted in on the left)

- Pass 3 is complete.

PASS 4

- Current Product and previous LSB

00000 11011 0

- Step 1: Examine the last 2 bits

00000 11011 0

- The last two bits are 10, so we need to subtract the **multiplicand** from the left half of the product

- Step 1: Arithmetic action

$$\begin{array}{r}
 (1) \quad 00000 \quad (\text{left half of product}) \\
 \quad -00010 \quad (\text{multiplicand}) \\
 \hline
 \quad 11110 \quad (\text{uses a phantom borrow})
 \end{array}$$

- Place result into **left half** of product

11110 11011 0

- Step 2: ASR (arithmetic shift right)

Before ASR

11110 11011 0

After ASR

11111 01101 1

(left-most bit was 1, so a 1 was shifted in on the left)

- Pass 4 is complete.

- Current Product and **previous LSB**

11111 01101 1

- **Pass 5**, Step 1: Examine the last 2 bits

11111 0110**1 1**

- The last two bits are **11**, so we do NOT need to perform an arithmetic action just proceed to step 2.
- Step 2: ASR (arithmetic shift right)

Before ASR

11111 01101 1

After ASR

11111 10110 1

(left-most bit was 1, so a 1 was shifted in on the left)

- Pass 5 is complete.

- Dropping the **previous LSB**, the resulting final product is:



11111 10110

- To confirm we have the correct answer, convert the 2's complement **final product** back to decimal.
- Final product: **11111 10110**
- Decimal value: **-10**

which is the **CORRECT** product of:

$$\mathbf{(-5) \times 2}$$

Multiplicand (M)

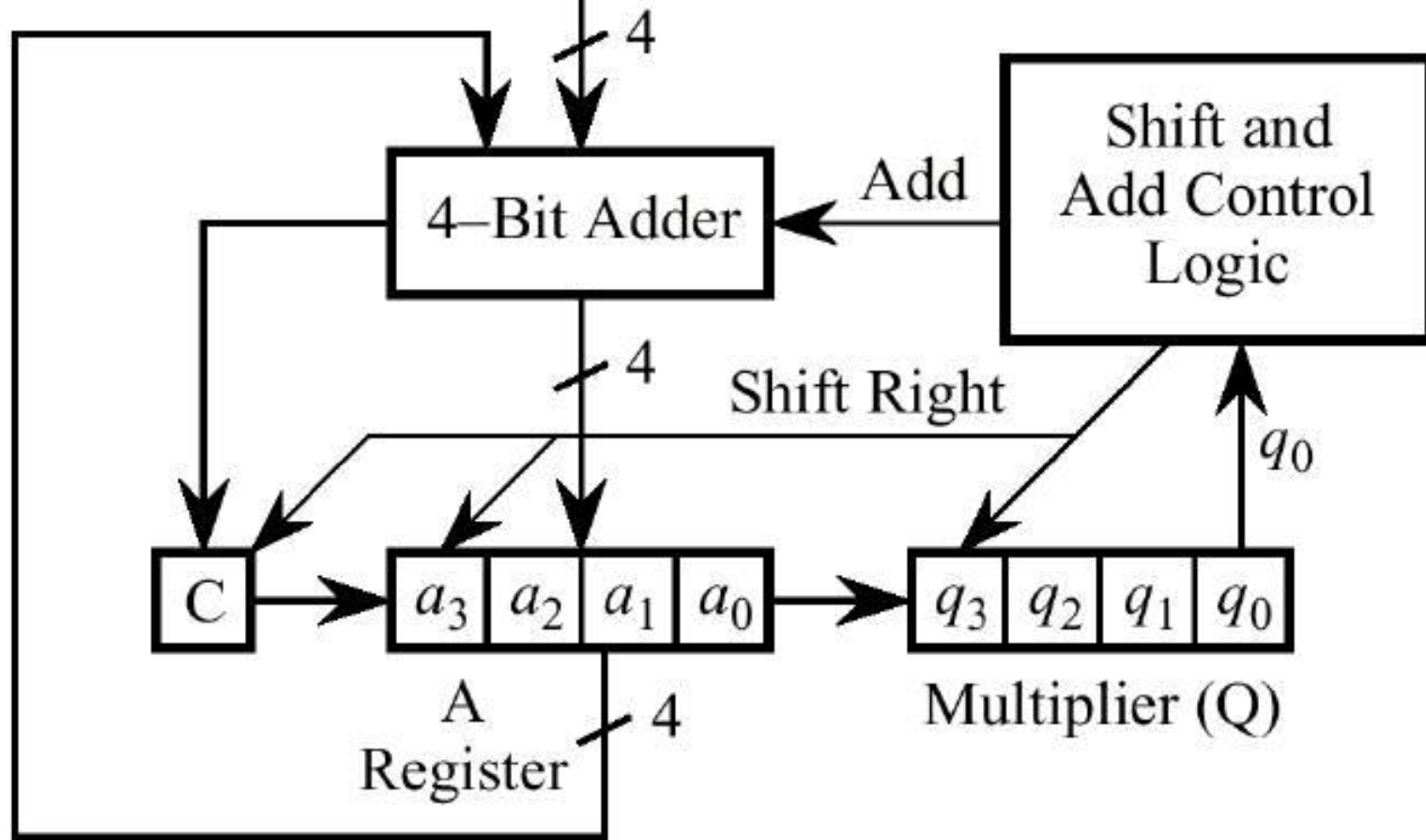 

Modified Booth Multiplier (Booth Encoding)

- Can encode the digits by looking at three bits at a time



- Booth recoding table:

$i+1$	i	$i-1$	add
0	0	0	$0*M$
0	0	1	$1*M$
0	1	0	$1*M$
0	1	1	$2*M$
1	0	0	$-2*M$
1	0	1	$-1*M$
1	1	0	$-1*M$
1	1	1	$0*M$

- Must be able to add *multiplicand* times -2 , -1 , 0 , 1 and 2

Algorithm

  
1. Pad the LSB with one zero.
2. Pad the MSB with 2 zeros if n is even and 1 zero if n is odd.
3. Divide the multiplier into overlapping groups of 3-bits.
4. Determine partial product scale factor from modified booth 2 encoding table.
5. Compute the Multiplicand Multiples
6. Sum Partial Products



ad LSB with 1 zero

is even then pad the MSB with two zeros

Example

 

Groups			Coding
0	1	0	$1 \times Y$
1	0	0	$-2 \times Y$
1	0	1	$-1 \times Y$
0	1	1	$2 \times Y$


[illegible]

Barrel Shifter

- A barrel shifter is a digital circuit that can shift a data word by a specified number of bits in one clock cycle.
- It can be implemented with multiplexers (MUX)

Function Table for 4-Bit Barrel Shifter

Select		Output				Operation
S_1	S_0	Y_3	Y_2	Y_1	Y_0	
0	0	D_3	D_2	D_1	D_0	No rotation
0	1	D_2	D_1	D_0	D_3	Rotate one position
1	0	D_1	D_0	D_3	D_2	Rotate two positions
1	1	D_0	D_3	D_2	D_1	Rotate three positions

 

i positions of left rotation is the same as $2^n - i$ bits of right rotation


implementing a barrel shifter would be to use N (where N is the number of input bits) parallel N -to-1 multiplexers, one multiplexer that multiplexes all inputs into one of the outputs.

This would create an equivalent $N \times N$ to N multiplexer, which would use significant hardware resources (**multiplexer input grows in $O(N^2)$**).

A more efficient implementation is possible by creating a hierarchy of multiplexers.

- 32-bit barrel shifter: can use 32 32-to-1 multiplexers
- However, large fan-in undesirable. So, use layers of multiplexers

 Example:
Use 2 layers of 4
2-to-1 multiplexers
for 4-bit barrel
shifter



For an 8 bit rotate component the multiplexers would be constructed as follows:

- the top level multiplexers rotate the data by 4 bits
- the second level rotates the data by 2 bits
- the third level rotates the data by 1 bit.

The number of multiplexers required is $n * \log_2(n)$, for an n bit word.

Four common word sizes and the number of multiplexers needed are:

$$64\text{-bit} - 64 * \log_2(64) = 64 * 6 = 384$$

$$32\text{-bit} - 32 * \log_2(32) = 32 * 5 = 160$$

$$16\text{-bit} - 16 * \log_2(16) = 16 * 4 = 64$$

$$8\text{-bit} - 8 * \log_2(8) = 8 * 3 = 24$$

```
module barrel_shifter(d,out,q,c); / Main module of 8-Bit Barrel shifter
  input [7:0]d;
  output [7:0]out,q;
  input[2:0]c;
  mux m1(q[0],d,c);
  mux m2(q[1],{d[0],d[7:1]},c);
  mux m3(q[2],{d[1:0],d[7:2]},c);
  mux m4(q[3],{d[2:0],d[7:3]},c);
  mux m5(q[4],{d[3:0],d[7:4]},c);
  mux m6(q[5],{d[4:0],d[7:5]},c);
  mux m7(q[6],{d[5:0],d[7:6]},c);
  mux m8(q[7],{d[6:0],d[7:7]},c);
  assign out=q;
endmodule
```

Baugh-Wooley Multiplier

- Efficient way to handle sign bits
- Regular Multipliers, suited for 2's-complement numbers
- Signed number representation

$$X = -x_{n-1}2^{n-1} + \sum_{i=0}^{n-2} x_i 2^i$$

eg: $(1110)_2$

= (-2)

$$A = -a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$$

$$B = -b_{n-1}2^{n-1} + \sum_{i=0}^{n-2} b_i 2^i$$

$$P = A \times B$$

$$= \left(-a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i \right) \times \left(-b_{n-1}2^{n-1} + \sum_{j=0}^{n-2} b_j 2^j \right)$$

$$= a_{n-1}b_{n-1}2^{2n-2} + \sum_{i=0}^{n-2} \sum_{j=0}^{n-2} a_i b_j 2^{i+j}$$

$$-2^{n-1} \sum_{i=0}^{n-2} a_i b_{n-1} 2^i - 2^{n-1} \sum_{j=0}^{n-2} a_{n-1} b_j 2^j$$

The Baugh-Wooley Method and Its Modified Form

$$\begin{aligned}
 -a_4x_0 &= a_4(1 - x_0) - a_4 \\
 &= a_4x_0' - a_4
 \end{aligned}$$

$$\begin{array}{cc}
 -a_4 & a_4x_0' \\
 \uparrow & \\
 & a_4
 \end{array}$$

In next column



					×	$\frac{a_4}{x_4}$	$\frac{a_3}{x_3}$	$\frac{a_2}{x_2}$	$\frac{a_1}{x_1}$	$\frac{a_0}{x_0}$
						$\overline{a_4x_0}$	a_3x_0	a_2x_0	a_1x_0	a_0x_0
				$\overline{a_4x_1}$		$\overline{a_3x_1}$	a_2x_1	a_1x_1	a_0x_1	
		$\overline{a_4x_2}$		$\overline{a_3x_2}$		$\overline{a_2x_2}$	a_1x_2	a_0x_2		
	$\overline{a_4x_3}$	$\overline{a_3x_3}$		$\overline{a_2x_3}$		$\overline{a_1x_3}$	a_0x_3			
	$\overline{a_4x_4}$	$\overline{a_3x_4}$	$\overline{a_2x_4}$	$\overline{a_1x_4}$		$\overline{a_0x_4}$				
1	$\frac{a_4}{x_4}$					$\overline{a_4}$				
						x_4				
p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

$$\begin{aligned}
 -a_4x_0 &= (1 - a_4x_0) - 1 \\
 &= (a_4x_0)' - 1
 \end{aligned}$$

$$\begin{array}{cc}
 -1 & (a_4x_0)' \\
 \uparrow & \\
 & 1
 \end{array}$$


In next column

					×	$\frac{a_4}{x_4}$	$\frac{a_3}{x_3}$	$\frac{a_2}{x_2}$	$\frac{a_1}{x_1}$	$\frac{a_0}{x_0}$
						$\overline{a_4x_0}$	a_3x_0	a_2x_0	a_1x_0	a_0x_0
				$\overline{a_4x_1}$		$\overline{a_3x_1}$	a_2x_1	a_1x_1	a_0x_1	
		$\overline{a_4x_2}$		$\overline{a_3x_2}$		$\overline{a_2x_2}$	a_1x_2	a_0x_2		
	$\overline{a_4x_3}$	$\overline{a_3x_3}$		$\overline{a_2x_3}$		$\overline{a_1x_3}$	a_0x_3			
	$\overline{a_4x_4}$	$\overline{a_3x_4}$	$\overline{a_2x_4}$	$\overline{a_1x_4}$		$\overline{a_0x_4}$				
1				1						
\bar{p}_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

 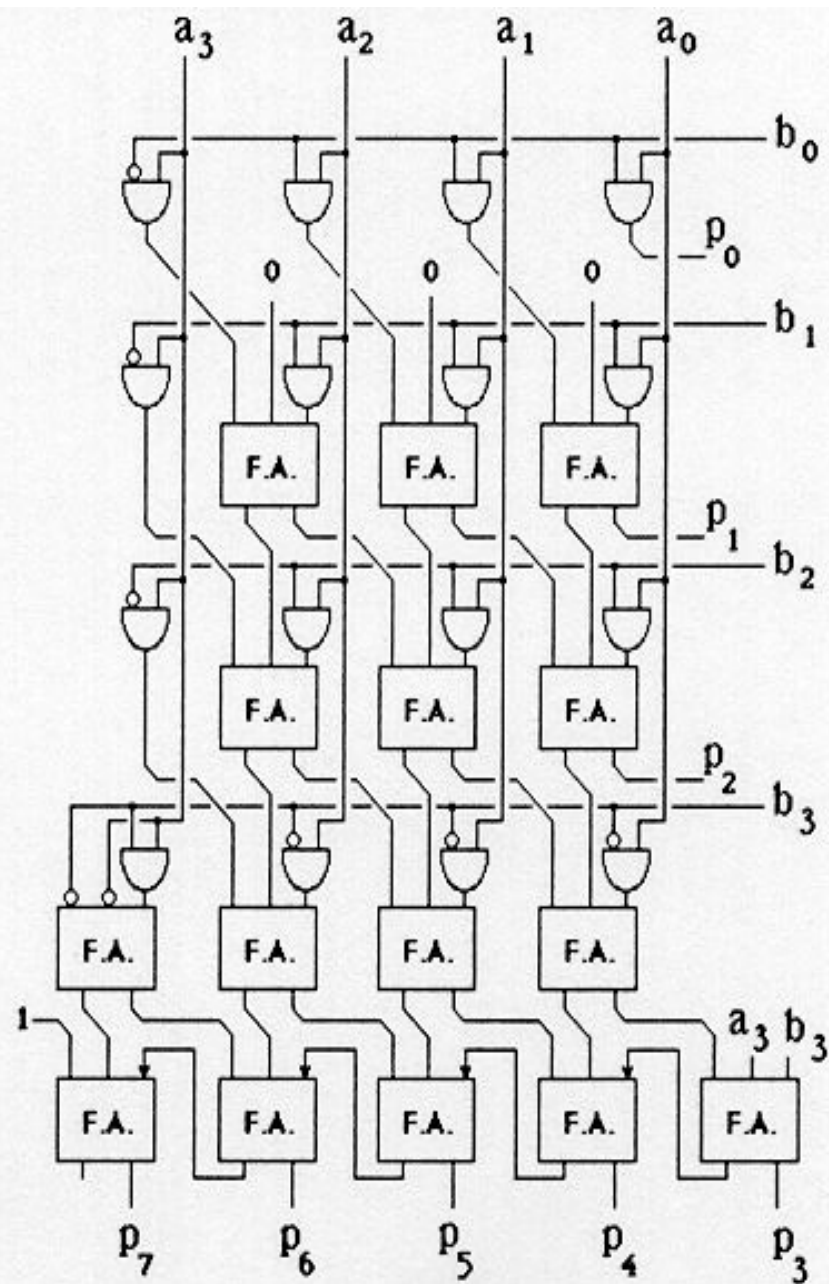


Wallace-Tree Multiplier


Partial products

 


First stage

 


Second stage

 


Final adder

 

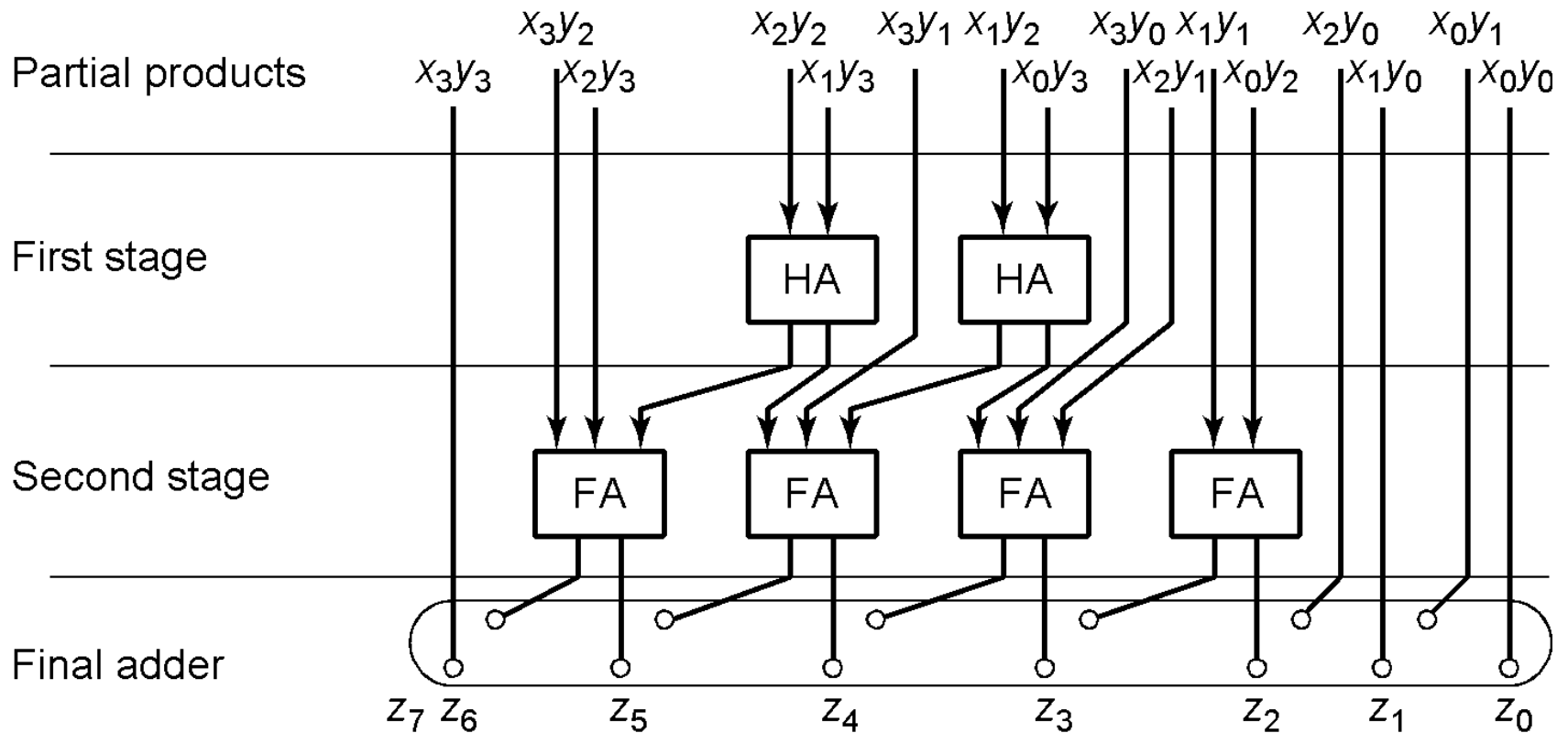


Full adder = (3,2) compressor

(4,2) Counter

 


 - Built out of two (3,2) counters (just FA's!)
 - all of the inputs (4 external plus one internal) have the **same weight** (i.e., are in the **same** bit position)
 - the **internal** carry output is fed to the next higher weight position (indicated by the)




Note: Two carry outs - one “**internal**” and one “**external**”

Tiling (4,2) Counters

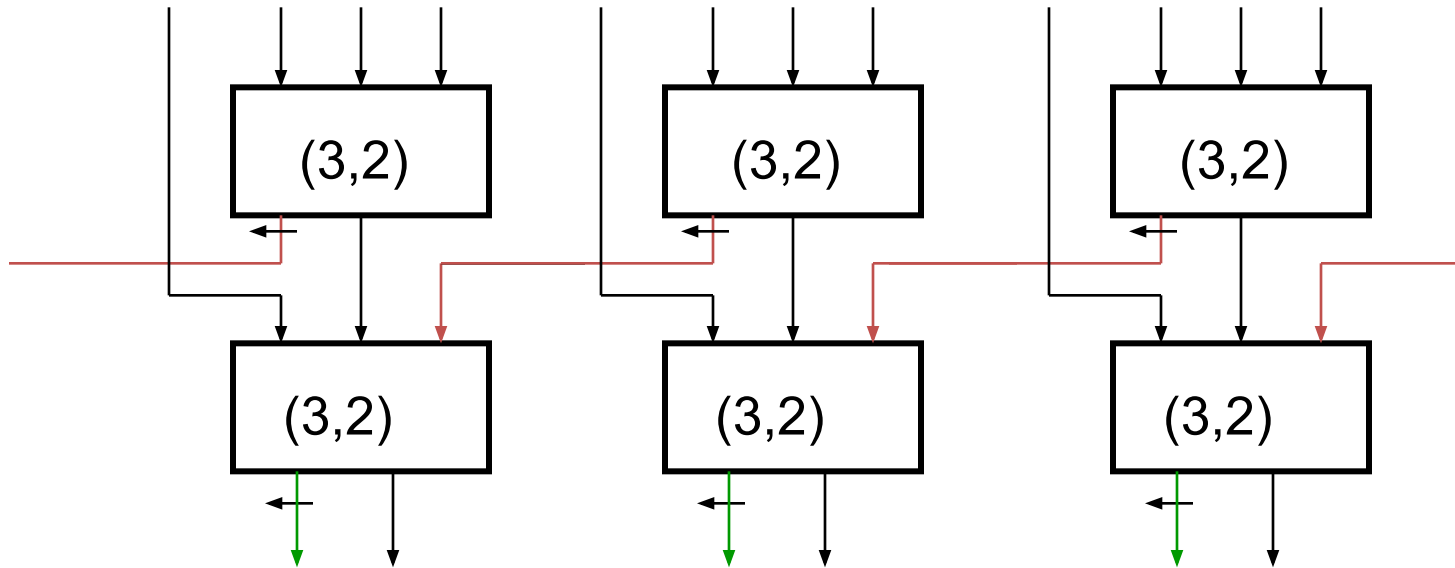


- ❑ Reduces columns **four** high to columns only **two** high
 - Tiles with neighboring (4,2) counters
 - **Internal** carry in at same “level” (i.e., bit position weight) as the **internal** carry out

Tiling (4,2) Counters


 


4x4 Partial Product Array Reduction

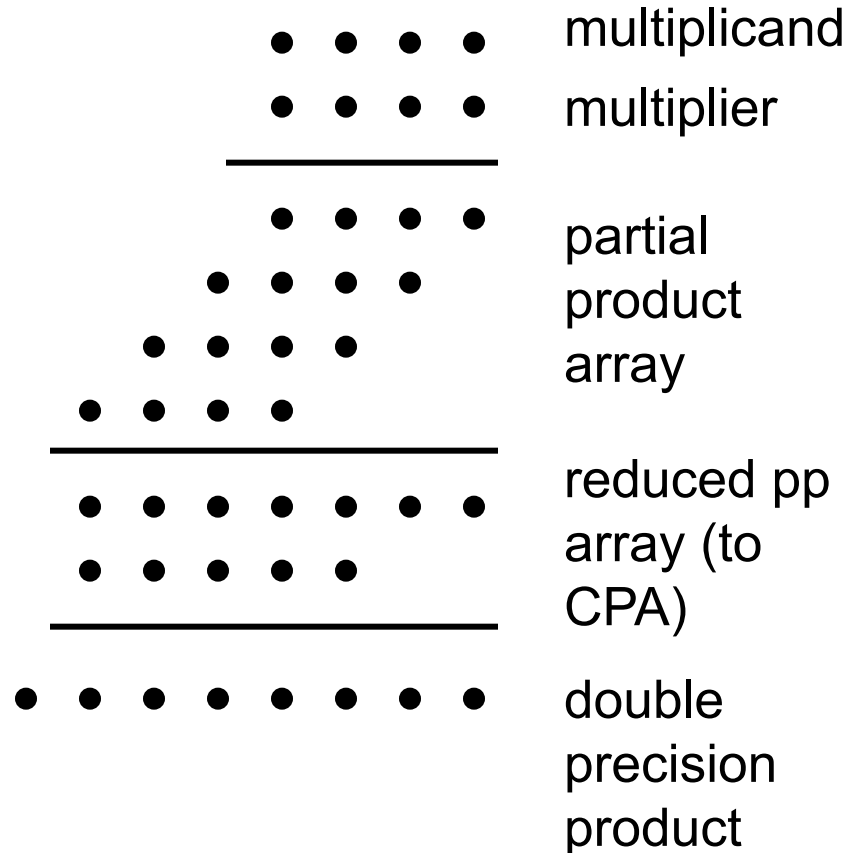- Fast 4x4 multiplication using (4,2) counters



  Fast 4x4 multiplication using (4,2) counters



8x8 Partial Product Array Reduction

□ Wallace tree multiplier

