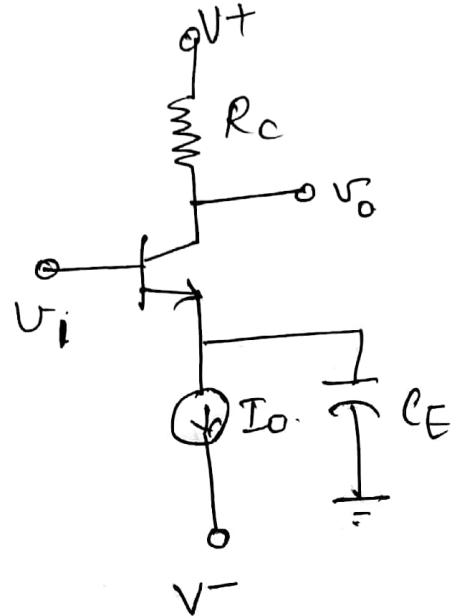


Current Source & Current MirrorIntroduction :-



- \* The biasing techniques for BJT and FET amplifiers for the most part used voltage-divider resistor networks.
- \* For IC, this is not possible.
- \* Resistors require large areas on an IC compared to transistors; therefore a resistor intensive circuit would necessitate a large chip area.  
Also the resistor biasing technique uses coupling & bypass capacitors which is almost impossible to fabricate in  $\mu$ m range.
- \* Biasing IC involves the use of constant current source.
- \* Transistors are also used as load instead of  $R_C$  &  $R_O$ . These are called active loads.

Bipolar Transistor Current Sources

The circuit shown can be designed to establish the bias current  $I_O$ .



Two transistor Current Source :- 2(b)

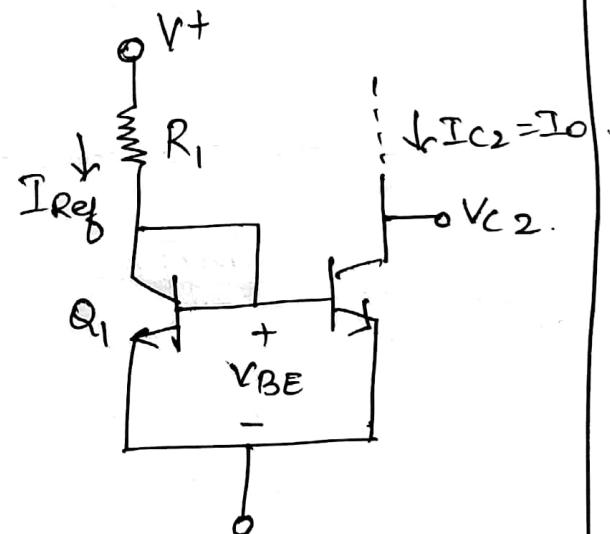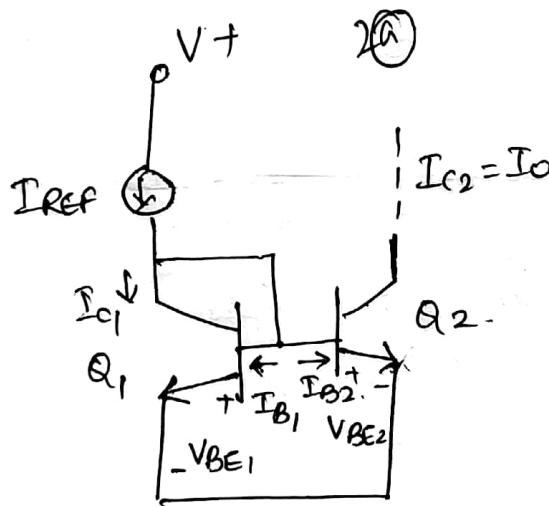

- \* The 2 transistor current source (current mirror), is the basic building block in the design of IC current source.
- \*  $Q_1$  &  $Q_2$  are matched transistors.
- \*  $V_{BE1} = V_{BE2}$ .
- \* base & emitter of two transistors are

connected together.

- \* Q<sub>1</sub> is connected as a diode, when supply voltages are applied, B-E junction of Q<sub>1</sub> is forward biased, I<sub>Ref</sub> is established.
- \* Once V<sub>B E1</sub> is established it is applied to the base of Q<sub>2</sub> & generates I<sub>O</sub> which is used to bias a transistor.

$$I_{Ref} = \frac{V^+ - V_{BE} - V^-}{R_1}$$

- \* Connecting base & collector terminal produces a 2 terminal device with I-V characteristics identical to i<sub>c</sub> vs V<sub>BE</sub> of BJT.

### Current Relationships

$$I_{B1} = I_{B2}$$

$$I_{C1} = I_{C2}$$

Sum of currents at the collector of Q<sub>1</sub>,

$$I_{Ref} = I_{C1} + I_{B1} + I_{B2} = I_c + 2I_{B2}$$

$$I_{B2} = \frac{I_{C2}}{\beta}$$

$$\therefore I_{Ref} = I_c + 2\frac{I_{C2}}{\beta} = I_{C2}\left(1 + \frac{2}{\beta}\right)$$

$$I_{C2} = \frac{I_{Ref}}{1 + \frac{2}{\beta}} = I_0$$


$Q_2$  is biased in the active region &

$$V_A = \infty$$
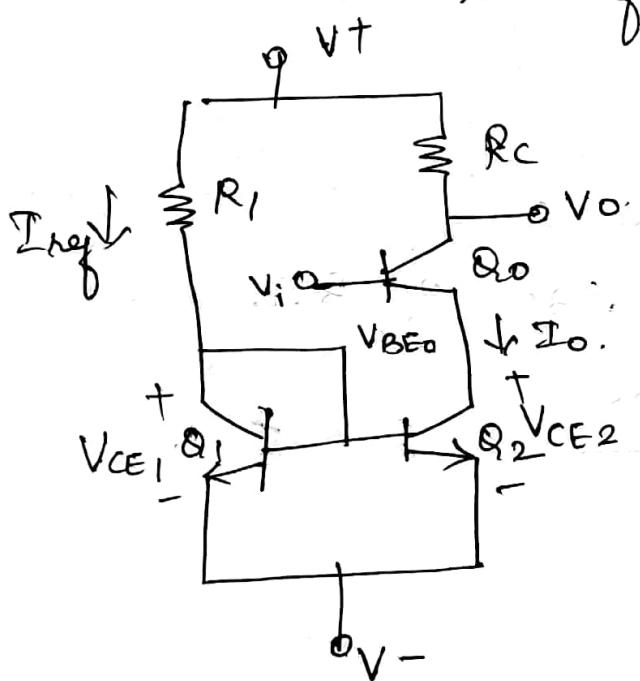
### Output Resistance

\* Early effect is finite

Collector current is a function of  $V_{CE}$ .



$$\frac{I_0}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta}} \left( 1 + \frac{V_{CE2}}{V_A} \right) \quad \left( 1 + \frac{V_{CE1}}{V_A} \right)$$

↑  
ratio of load current  
to reference current  
taking into acc early effect.

$$V_{CE1} = V_{BE} \text{ and } V_{CE2} = V^+ - V_{BE0} - V^-.$$

\* If  $V_i$  changes then  $V_{CE2}$  changes.

\* A change in dc bias conditions in the load circuit affects the collector-emitter voltage of  $Q_2$ .

$$\frac{dI_o}{dV_{CE2}} = \frac{I_{ref}}{1 + \frac{2}{\beta}} \frac{1}{V_A} \frac{1}{1 + \frac{V_{BE}}{V_A}}$$

If  $V_{BE} \ll V_A$

$$\frac{dI_o}{dV_{CE2}} \approx \frac{I_o}{V_A} = \frac{1}{r_o}$$

$r_o$  = small signal opp resistance looking into the collector of  $Q_2$ .

### Mismatched transistors

$Q_1$  &  $Q_2$  may not be exactly identical.

If  $\beta \gg 1$ , we can neglect base currents.

The current-voltage relationship for the circuit in Fig. 2(b).

$$I_{ref} = I_{C1} = I_{S1} e^{\frac{V_{BE}}{V_T}} \rightarrow ①$$

and

$$I_o = I_{C2} = I_{S2} e^{\frac{V_{BE}}{V_T}} \rightarrow ②$$

$I_{S1}$  &  $I_{S2}$  contain both electrical & geometric parameters of  $Q_1$  &  $Q_2$ .

If  $Q_1$  &  $Q_2$  are not identical  $I_{S1} \neq I_{S2}$ ,

$$\frac{I_0}{I_{ref}} = \frac{I_{S2} e^{\frac{V_{BE}}{V_T}}}{I_{S1} e^{\frac{V_{BE}}{V_T}}}$$

$$I_0 = I_{ref} \left[ \frac{I_{S2}}{I_{S1}} \right] \rightarrow \begin{matrix} \text{reverse bias} \\ \text{saturation} \\ \text{current} \end{matrix}$$

Any deviation in bias current from the ideal, as a function of mismatch b/w  $Q_1$  &  $Q_2$ , is directly related to the ratio of  $(I_{S2}/I_{S1})$ .

$I_S \rightarrow$  strong function of temperature.

$Q_1$  &  $Q_2 \rightarrow$  must have the same temperature so should be placed close in the circuit.

### Improved Current Source Circuits

Improved load current stability against changes in  $\beta$  & changes in O/p collector current.

### Basic 3 transistor Current Source


All transistors are identical

$$I_{B1} = I_{B2} \& I_{C1} = I_{C2}$$

$Q_3$  supplies the base current of  $Q_1$  &  $Q_2$ , so their base currents are less dependant on  $I_{ref}$ .

(A)

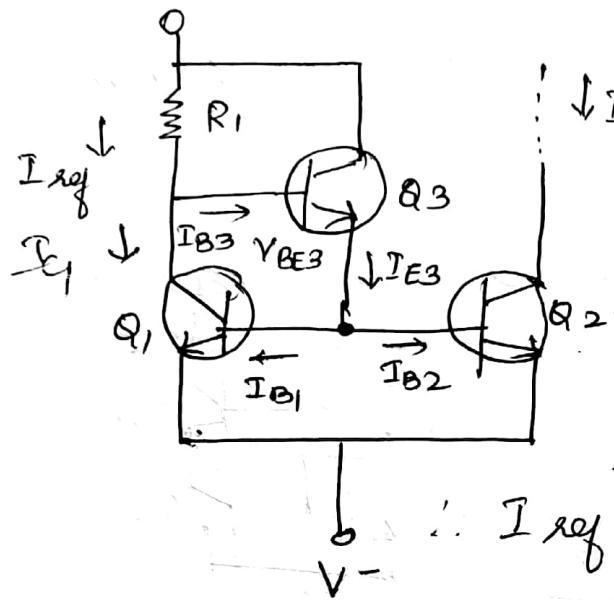Current gain of  $Q_1 = Q_2 = \beta$  & current gain of  $Q_3$  is  $\beta_3$ . Summing the currents at the collector node of  $Q_1$ , we have.



$$I_{\text{Ref}} = I_{C1} + I_{B3}$$

$$I_{B1} + I_{B2} = 2I_{B2} = I_{E3}$$

and

$$I_{E3} = (1 + \beta_3) I_{B3}$$

$$\therefore I_{\text{Ref}} = I_{C1} + \frac{I_{E3}}{1 + \beta_3}$$

(or)

$$I_{\text{Ref}} = I_{C1} + \frac{\alpha I_{B2}}{1 + \beta_3}$$

$$\left[ \begin{array}{l} I_1 = I_{C2} \\ I_{B2} = \frac{\beta I_{C2}}{\beta} \end{array} \right]$$

$$I_{\text{Ref}} = I_{C2} + \frac{2 I_{C2}}{\beta(1 + \beta_3)}$$

$$= I_{C2} \left[ 1 + \frac{2}{\beta(1 + \beta_3)} \right]$$

$$\therefore I_0 = I_{C2} = \frac{I_{\text{Ref}}}{\left[ 1 + \frac{2}{\beta(1 + \beta_3)} \right]}$$

$$\left[ 1 + \frac{2}{\beta(1 + \beta_3)} \right]$$

where

$$I_{ref} = \frac{V^+ - V_{BE3} - V_{BE} - V^-}{R_1} \approx \frac{V^+ - 2V_{BE} - V^-}{R_1}$$


Compared to 2 transistor current source  $I_o \approx I_{ref}$   
is better for 3 transistor current source.

### Off resistance

Same as 2 transistor current source

$$\frac{dI_o}{dV_{CE2}} = \frac{1}{R_{O2}}$$

### Cascode Current source

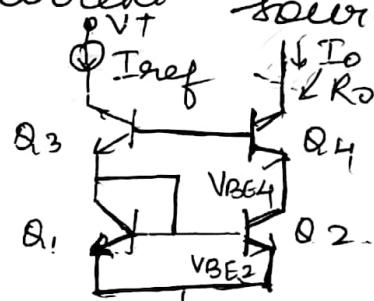

\* Current sources can be designed such that the resistance is much greater than that of 2-transistor current source.

\* In cascode current source if the transistors are matched, then the load & reference currents are essentially equal.

\* We may calculate the off resistance  $R_o$  by considering the small signal equivalent transistor circuits.

\* For a constant reference current  $V_{BE}$  of Q1,

and  $Q_4$  are constant, which implies that these terminals are at signal ground.

$$\text{Since } g_{m2}V_{be2} = 0 \quad V_{be4} = -I_x (\frac{r_{o4}}{r_{o4} + r_{\pi4}})$$

Summing currents at off node yields:-

$$I_x = g_{m4}V_{be4} \left( \frac{-I_x (\frac{r_{o2}}{r_{o2} + r_{\pi4}})}{r_{o4}} \right)$$

$$I_x = -g_{m4}I_x (\frac{r_{o2}}{r_{o2} + r_{\pi4}}) + \frac{V_x - I_x (\frac{r_{o2}}{r_{o2} + r_{\pi4}})}{r_{o4}}$$

$$R_o = \frac{V_x}{I_x}$$



$$I_x + g_{m4}I_x (\frac{r_{o2}}{r_{o2} + r_{\pi4}}) + \frac{I_x (\frac{r_{o2}}{r_{o2} + r_{\pi4}})}{r_{o4}} = \frac{V_x}{r_{o4}}$$

$$I_x \left[ 1 + g_{m4} (\frac{r_{o2}}{r_{o2} + r_{\pi4}}) + \frac{1}{r_{o4}} (\frac{r_{o2}}{r_{o2} + r_{\pi4}}) \right] = \frac{V_x}{r_{o4}}$$

$$\frac{V_x}{I_x} = r_{o4} + g_{m4}r_{o4} (\frac{r_{o2}}{r_{o2} + r_{\pi4}}) + (\frac{r_{o2}}{r_{o2} + r_{\pi4}})$$

$$\approx r_{o4} + g_{m4}r_{o4} r_{\pi4} + r_{\pi4}$$


$$\approx r_{o4}(1 + \beta r_{o4}) + r_{\pi4} \approx \beta r_{o4}$$

$$R_o = \frac{V_x}{I_x} \approx \beta r_{o4}$$

The off resistance has increased by a factor of  $\beta$ .
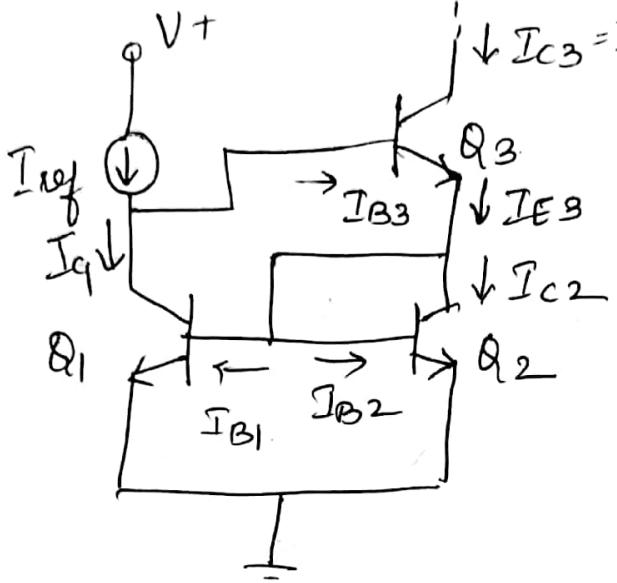
## Wilson Current Source

- \* Has large O/P resistance.
- \*  $I_{B1} = I_{B2}$  &  $I_{C1} = I_{C2}$  & current gains of these transistors are equal.



$$I_{ref} = I_{C1} + I_{B3}$$

$$I_{E3} = I_{C2} + \beta I_{B1} + I_{B2} = I_{C2} + 2\beta I_{B2},$$

$$I_{E3} = I_{C2} + \frac{2I_{C2}}{\beta} = I_{C2} \left(1 + \frac{2}{\beta}\right).$$

$$I_{C2} = \frac{I_{E3}}{1 + \frac{2}{\beta}}$$

$$I_{ref} = I_{C2} + I_{B3} = \frac{I_{E3}}{1 + \frac{2}{\beta}} + \frac{I_{E3}}{1 + \beta} \rightarrow ①$$

$$I_{E3} = (1 + \beta) I_{B3}$$

$$\underline{I_{E3} = \frac{1 + \beta}{\beta} I_{C2}}$$

SRM

(6)

Sub in ①

$$\begin{aligned}
 I_{Ref} &= I_{C3} \frac{1+\beta}{\beta(1+\frac{1}{\beta})} + I_{C3} \frac{1+\beta}{\beta(1+\frac{1}{\beta})} \\
 &= I_{C3} \left[ \frac{1+\beta}{2+\beta} \right] + \frac{I_{C3}}{\beta} \\
 &= I_{C3} \left[ \frac{1+\beta}{2+\beta} + \frac{1}{\beta} \right].
 \end{aligned}$$

$$I_{C3} = \frac{I_{Ref}}{\left( \frac{1+\beta}{2+\beta} + \frac{1}{\beta} \right)} = I_0$$

$$\text{Op resistance } \approx \frac{\beta R_{O3}}{2} \approx \frac{\beta}{2}.$$

### Widlar Current Source

The load & reference currents are <sup>nearly</sup> equal in other current sources. Hence the Resistor value required is large.

To limit the value of  $R'$  we use Widlar Current source.

to

102


SRM

\* A voltage difference is produced across  $R_S$  which means B-E voltage of  $Q_2$  is less than B-E voltage of  $Q_1$ , hence  $I_o$  is smaller than  $I_{ref}$ .
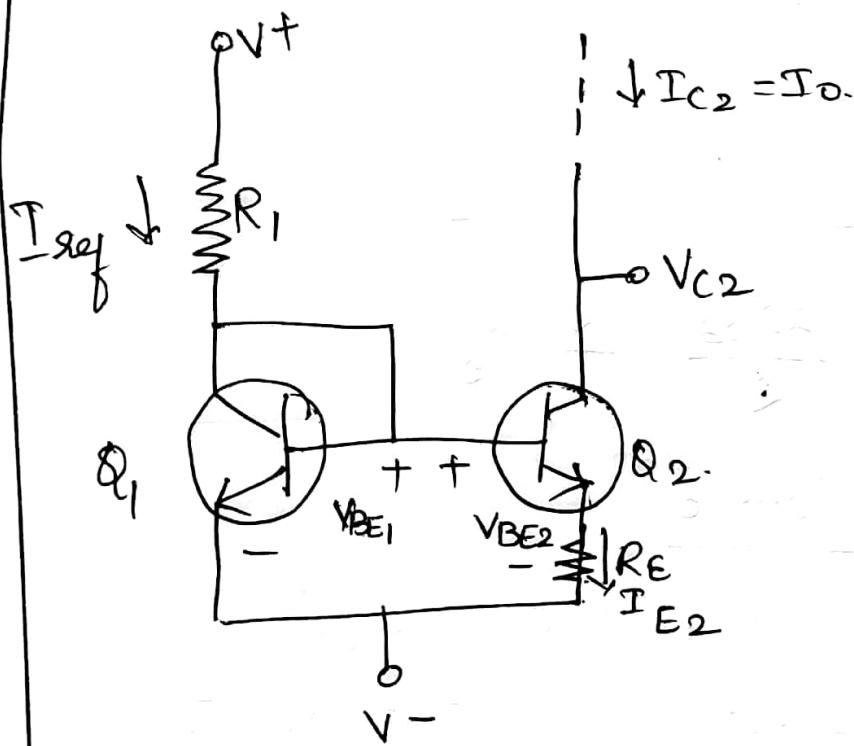
### Current Relationship

$$I_{ref} \approx I_{C1} = I_s e^{V_{BE1}/V_T} \rightarrow \textcircled{1}$$

$$I_o \approx I_{C2} = I_s e^{V_{BE2}/V_T} \rightarrow \textcircled{2}$$



$$\text{From } \textcircled{1} \quad V_{BE1} = V_T \ln \left( \frac{I_{ref}}{I_s} \right) \rightarrow \textcircled{3}$$

$$\text{From } \textcircled{2} \quad V_{BE2} = V_T \ln \left( \frac{I_o}{I_s} \right) \rightarrow \textcircled{4}$$

9

Ans. From ③ & ④

$$V_{BE1} - V_{BE2} = V_T \ln \left( \frac{I_{ref}}{I_0} \right)$$

But from fig

$$V_{BE1} = V_{BE2} + I_E R_E$$


$$\therefore V_{BE1} - V_{BE2} = I_E R_E \approx I_0 R_E$$

$$I_0 R_E = V_T \ln \left( \frac{I_{ref}}{I_0} \right)$$

The above equation gives the relationship between  $I_0$  &  $I_{ref}$ .

With small change in  $V_{BE}$  large change in  $I_c$  occurs. Maintaining equal temperature is important.

### Output Resistance

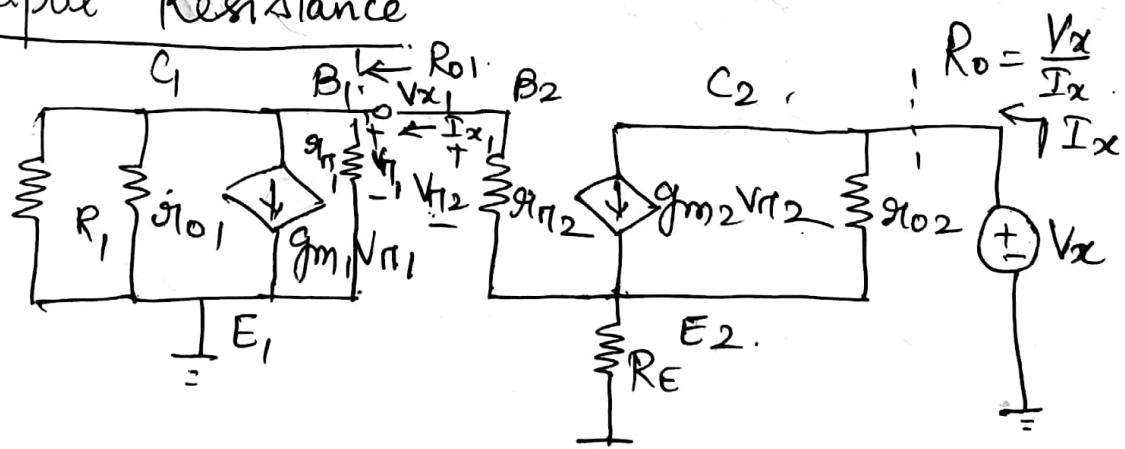

SRM

$$I_x = -g_{m2} I_x \left( \frac{R_E}{g_{m2}} || \frac{V_x}{g_{m2}} \right) + \frac{V_x}{g_{m2}} - \frac{I_x (R_E || \frac{V_x}{g_{m2}})}{g_{m2}}$$

$$I_x + I_x g_{m2} R_E' + \frac{I_x R_E'}{g_{m2}} = \frac{V_x}{g_{m2}}$$

$$I_x \left[ 1 + g_{m2} R_E' + \frac{R_E'}{g_{m2}} \right] = \frac{V_x}{g_{m2}}$$

$$I_x \left[ 1 + \left( g_{m2} + \frac{1}{g_{m2}} \right) R_E' \right] = \frac{V_x}{g_{m2}}$$

$$\frac{V_x}{I_x} = g_{m2} \left[ 1 + R_E' \left( g_{m2} + \frac{1}{g_{m2}} \right) \right]$$

If  $\frac{1}{g_{m2}} \ll g_{m2}$

$$R_o \approx g_{m2} (1 + R_E' g_{m2})$$

The O/P resistance of Widlar current source is larger than other current sources.

### Multibitistor Current Mirrors

B-E voltage of  $Q_1$  can be applied to additional transistors to generate multiple load currents.

$$I_x = -g_{m2} I_x \left( \frac{R_E}{g_{m2}} \| g_{m2} \right) + \frac{V_x}{g_{m2}} - \frac{I_x}{g_{m2}} \left( R_E \| g_{m2} \right)$$

$$I_x + I_x g_{m2} R_E' + \frac{I_x R_E'}{g_{m2}} = \frac{V_x}{g_{m2}}$$

$$I_x \left[ 1 + g_{m2} R_E' + \frac{R_E'}{g_{m2}} \right] = \frac{V_x}{g_{m2}}$$

$$I_x \left[ 1 + \left( g_{m2} + \frac{1}{g_{m2}} \right) R_E' \right] = \frac{V_x}{g_{m2}}$$

$$\frac{V_x}{I_x} = g_{m2} \left[ 1 + R_E' \left( g_{m2} + \frac{1}{g_{m2}} \right) \right]$$


If  $\frac{1}{g_{m2}} \ll g_{m2}$

$$R_o \approx g_{m2} (1 + R_E' g_{m2})$$

The  $O_P$  of Widlar current source is larger than other current sources.

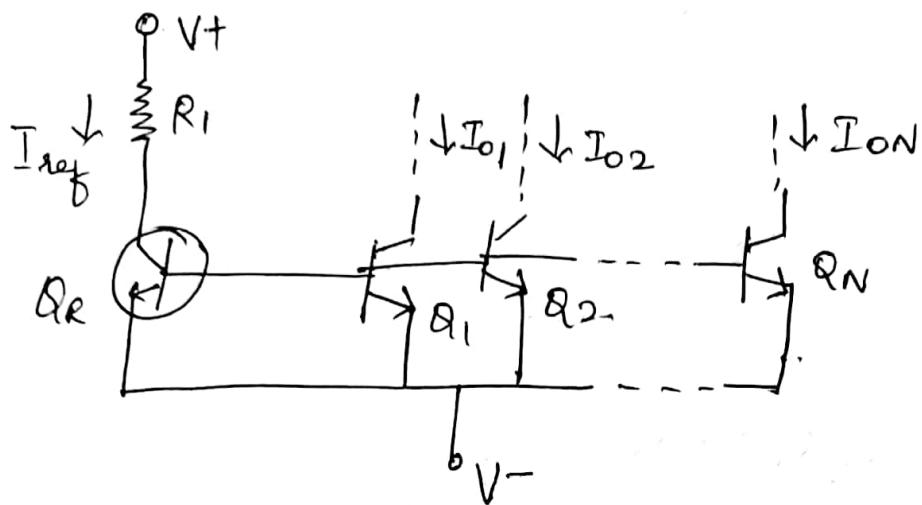
### Multibiasistor Current Mirrors

B-E voltage of  $Q_1$  can be applied to additional transistors to generate multiple load currents.




- \*  $Q_R$  is the reference transistor, connected as a diode.
- \* The Base-Emitter voltage of  $Q_R$  is applied to  $N$   $\text{NPN}$  transistors, creating  $N$  load currents. The transistors are matched.
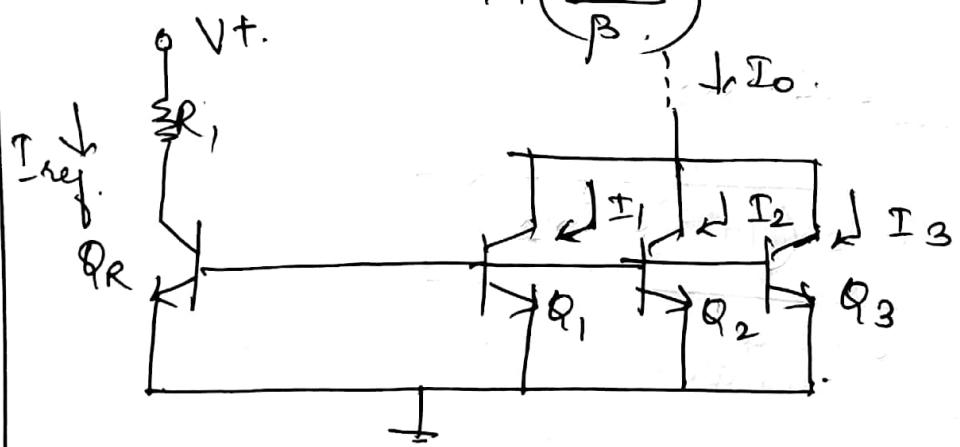
$$I_{O1} = I_{O2} = I_{ON} = \frac{I_{ref}}{1 + \left( \frac{1+N}{\beta} \right)}$$



- \*  $I_O = 3I_{ref}$ .
- \* The collectors of multiple transistors can be connected together.

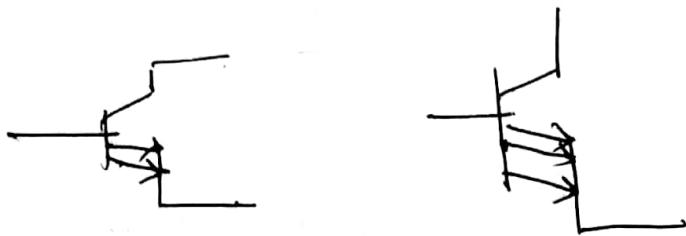\* This increases the B-E area of the device.




Current Mirror Circuit Symbols:

$$I_{ref} = \frac{V^+ - V_{EB}(Q_{R1}) - V_{BE}(Q_{R2}) - V^-}{R_1}$$

$Q_{R1}$  &  $Q_{R2}$  are connected as diodes.

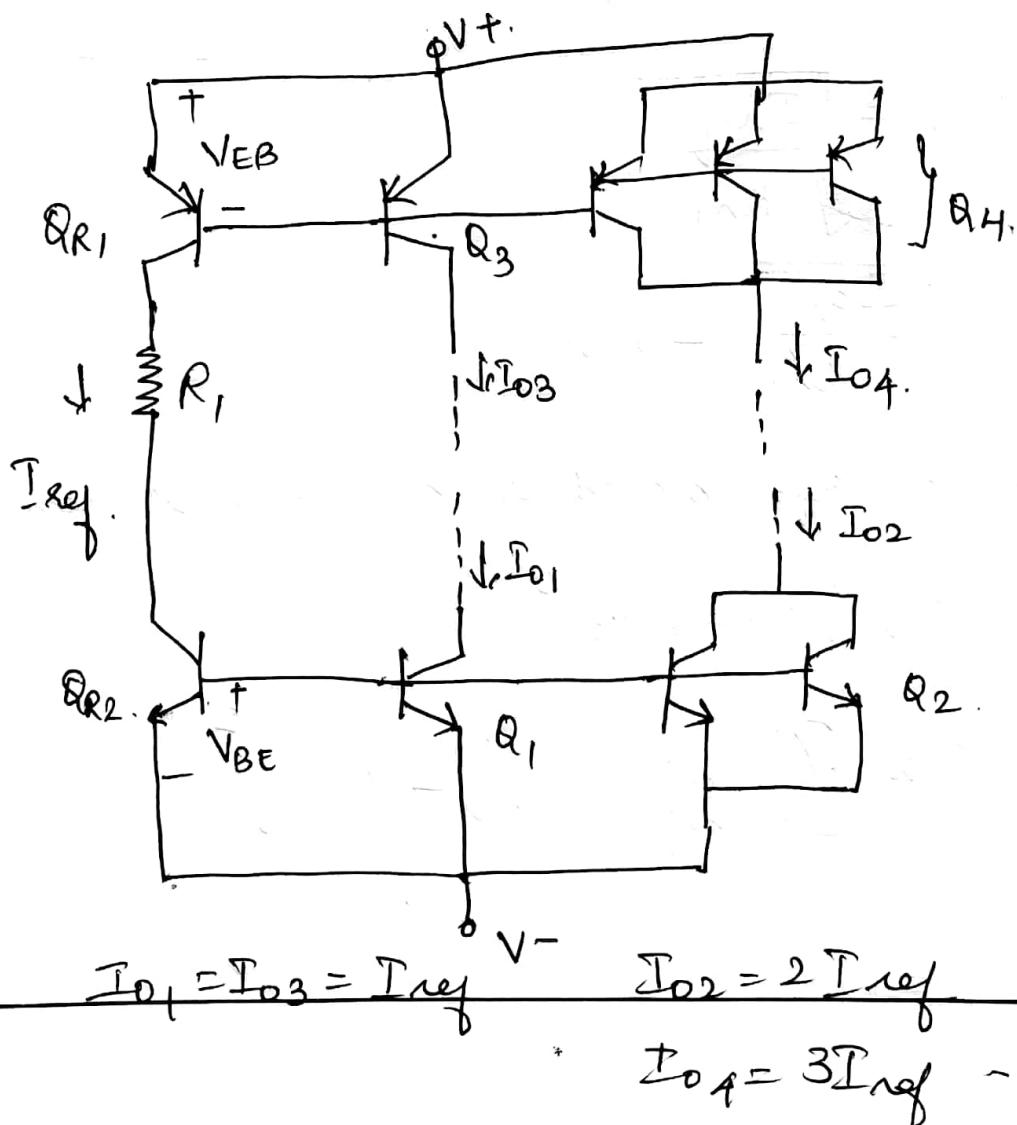The reference current is established by  $Q_R$ , &  $Q_{R2}$ .



If the aspect ratios of 2 transistors are not same then

$$I_o = \frac{(W/L)_2}{(W/L)_1} I_{ref}$$

### Output resistance

Taking into account the finite output resistance of the transistors, we can write the load & difference currents as,

$$I_o = k_{n2} (V_{ds} - V_{TN2})^2 (1 + d_2 V_{DS2}).$$

$$\underline{I}_{ref} = k_{n1} (V_{ds} - V_{TN1})^2 (1 + d_1 V_{DS1})$$

All the physical parameters are same for both the transistors. hence,

$$\frac{I_o}{I_{ref}} = \frac{(W/L)_2 (1 + d V_{DS2})}{(W/L)_1 (1 + d V_{DS1})}$$

$$\frac{1}{R_o} = d \frac{I_{ref}}{R_o}$$

### 3-transistor Current Source

The reference current in bipolar current source circuits is usually established by bias voltage & resistor.

If the aspect ratios of 2 transistors are not same then

$$I_o = \frac{(W/L)_2}{(W/L)_1} I_{ref}$$

### Output resistance

Taking into account the finite output resistance of the transistors, we can write the load & reference currents as,

$$I_o = k_{n2} (V_{ds} - V_{TN2})^2 (1 + \alpha_2 V_{DS2}).$$

$$\underline{I_{ref}} = k_{n1} (V_{ds} - V_{TN1})^2 (1 + \alpha_1 V_{DS1}).$$

All the physical parameters are same for both the transistors. hence,


$$\frac{I_o}{I_{ref}} = \frac{(W/L)_2 (1 + \alpha V_{DS2})}{(W/L)_1 (1 + \alpha V_{DS1})}$$

$$\frac{1}{R_o} = \alpha I_{ref}$$
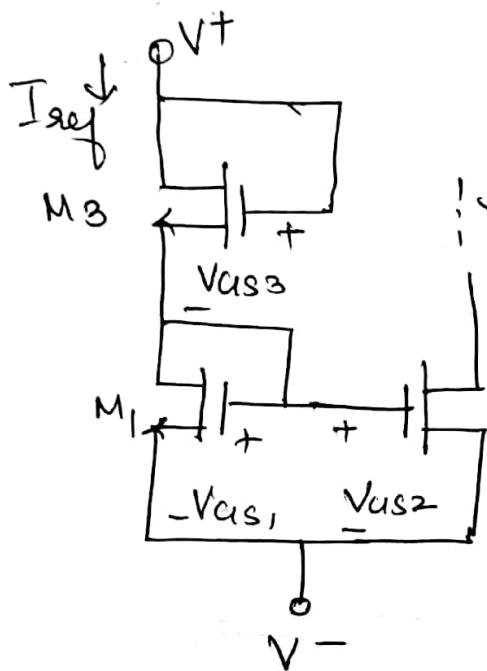
### 3-transistor Current Source

The reference current in bipolar current source circuits is usually established by bias voltage & resistor.

\* Since MOSFET can be configured to act like resistor, the reference current is MOSFET. Current mirror is usually established by using additional transistor.



Since  $M_1$  &  $M_3$  are in Series

$$I_{DQ3} = I_0$$

$$k_{n1}(V_{GS1} - V_{TN1})^2$$

$$= k_{n3}(V_{GS3} - V_{TN3})^2$$

$$V_{GS1} - V_{TN1} = \sqrt{\frac{k_{n3}}{k_{n1}}} (V_{GS3} - V_{TN3})$$

$$V_{GS1} = \sqrt{\frac{k_{n3}}{k_{n1}}} (V_{GS3} - V_{TN3}) + V_{TN1}$$

$$= \sqrt{\frac{k_{n3}}{k_{n1}}} \cdot V_{GS3} - \sqrt{\frac{k_{n3}}{k_{n1}}} V_{TN3} + V_{TN1}$$

Let  $V_{TN3} = V_{TN1} = V_{TN}$  then

$$V_{GS1} = \sqrt{\frac{k_{n3}}{k_{n1}}} V_{GS3} + \left(1 - \sqrt{\frac{k_{n3}}{k_{n1}}}\right) V_{TN} \rightarrow ①$$

also  $V^+ - V^- = V_{GS1} + V_{GS3} \rightarrow ②$

Substituting the eqn for  $V_{GS3}$  from ② in ①

$$V_{GS1} = \sqrt{\frac{(W/L)_3}{(W/L)_1}} (v^+ - v^- - V_{GS1}) + \left(1 - \sqrt{\frac{(W/L)_3}{(W/L)_1}}\right) V_{TN}$$

$$\left[ \frac{(W/L)_3}{(W/L)_1} V_{GS1} + V_{GS1} \right] = \sqrt{\frac{(W/L)_3}{(W/L)_1}} (v^+ - v^-) + \left(1 - \sqrt{\frac{(W/L)_3}{(W/L)_1}}\right) V_{TN}$$

$$V_{GS1} \left[ 1 + \sqrt{\frac{(W/L)_3}{(W/L)_1}} \right] = \sqrt{\frac{(W/L)_3}{(W/L)_1}} (v^+ - v^-) + \left(1 - \sqrt{\frac{(W/L)_3}{(W/L)_1}}\right) V_{TN}$$

$$V_{GS1} = \frac{\sqrt{\frac{(W/L)_3}{(W/L)_1}} (v^+ - v^-) + \left(1 - \sqrt{\frac{(W/L)_3}{(W/L)_1}}\right) V_{TN}}{1 + \sqrt{\frac{(W/L)_3}{(W/L)_1}}} = V_{GS2}$$


The load current

$$I_L = \left(\frac{W}{L}\right)_2 \left(\frac{1}{2} \mu_n C_{ox} \right) (V_{GS2} - V_{TN})^2$$

Since the designer has control over  $W/L$  of the transistors there is considerable flexibility in the design of MOSFET current sources.

SRM

## CASCODE Current Mirror

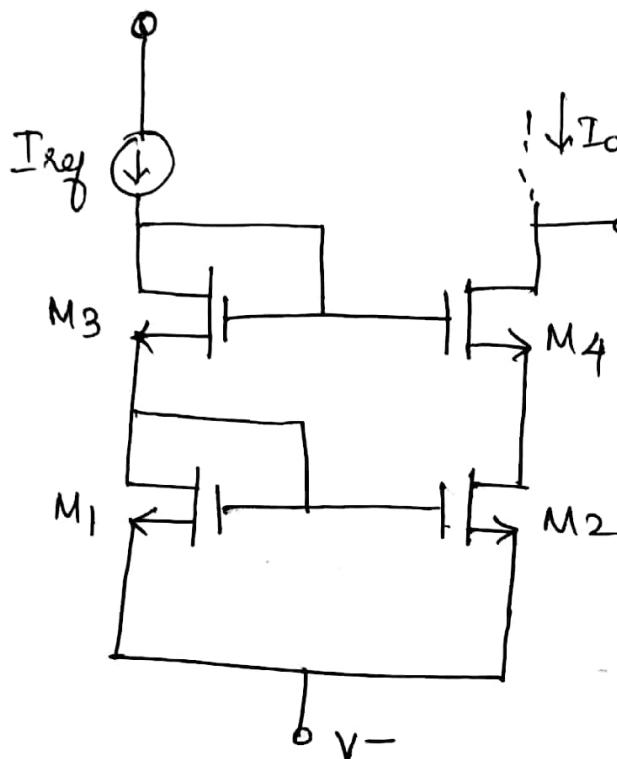


\* O/P resistance is a measure of stability with respect to changes in O/P voltage.

\* O/P resistance can be increased by modifying the circuit.

\*  $I_{ref}$  is established by including another MOSFET in the reference branch.

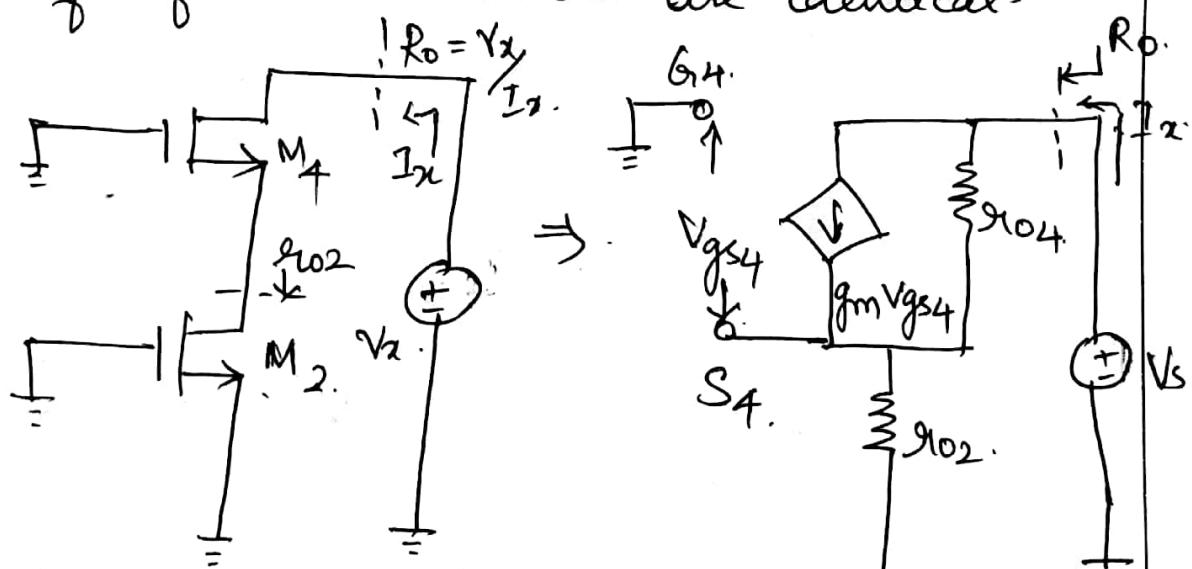\*  $I_o = I_{ref}$  if all transistors are identical.



To determine O/P resistance at the drain of  $M_4$ . Since  $I_{ref}$  is constant, the gate voltage to  $M_1$ ,  $M_3$  &  $M_2$  &  $M_4$  are constant.

SRM

$$I_x = g_m V_{gs4} + \frac{(V_x + V_{gs4})}{r_{o4}}$$

$$V_{gs4} = -I_x r_{o2}$$

$$\therefore I_x = -g_m I_x r_{o2} + \frac{V_x - I_x r_{o2}}{r_{o4}}$$

$$I_x \left[ 1 + g_m r_{o2} + \frac{r_{o2}}{r_{o4}} \right] = \frac{V_x}{r_{o4}}$$

$$\frac{V_x}{I_x} = R_o = r_{o4} + \cancel{r_{o4}} \left( \frac{\cancel{g_m r_{o2} r_{o4} + r_{o2}}}{\cancel{r_{o4}}} \right)$$

$$R_o = r_{o4} + r_{o2} (1 + g_m r_{o4})$$

$$g_m r_{o4} \gg 1$$



$$\therefore R_o = r_{o4} + r_{o2} r_{o4} g_m$$

$R_o$  is much larger than  $\beta$ -transistor current source.


### Wilson Current Source

The primary advantage of these circuits is that it increases the O/P resistance which stabilizes the load current.

## Modified Circuit

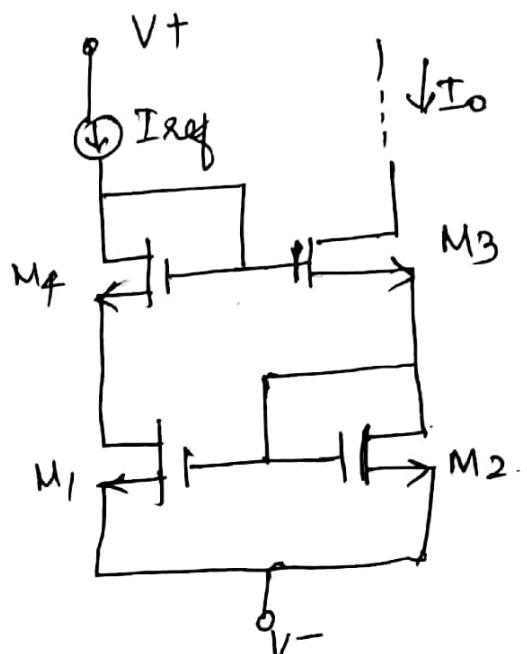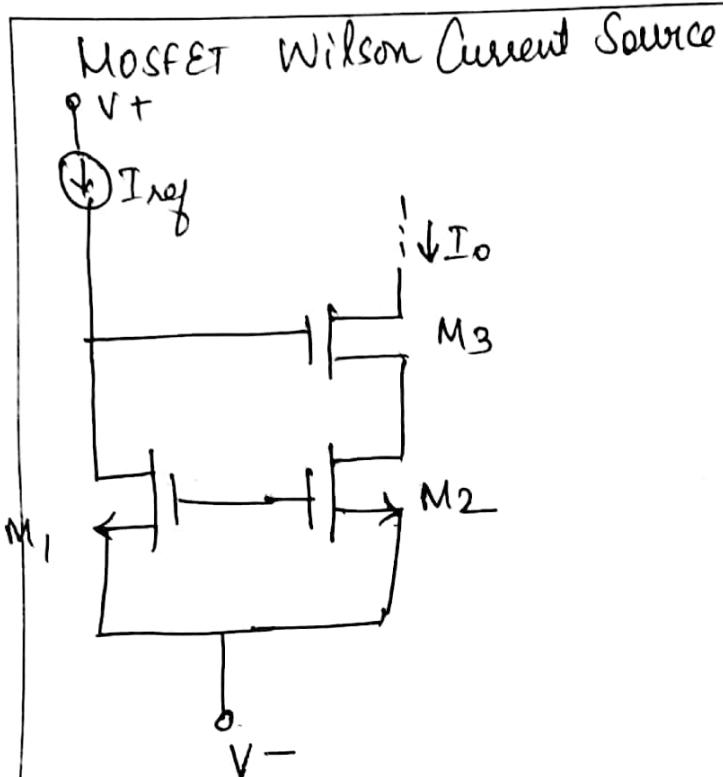

### THE DIFFERENTIAL AMPLIFIER

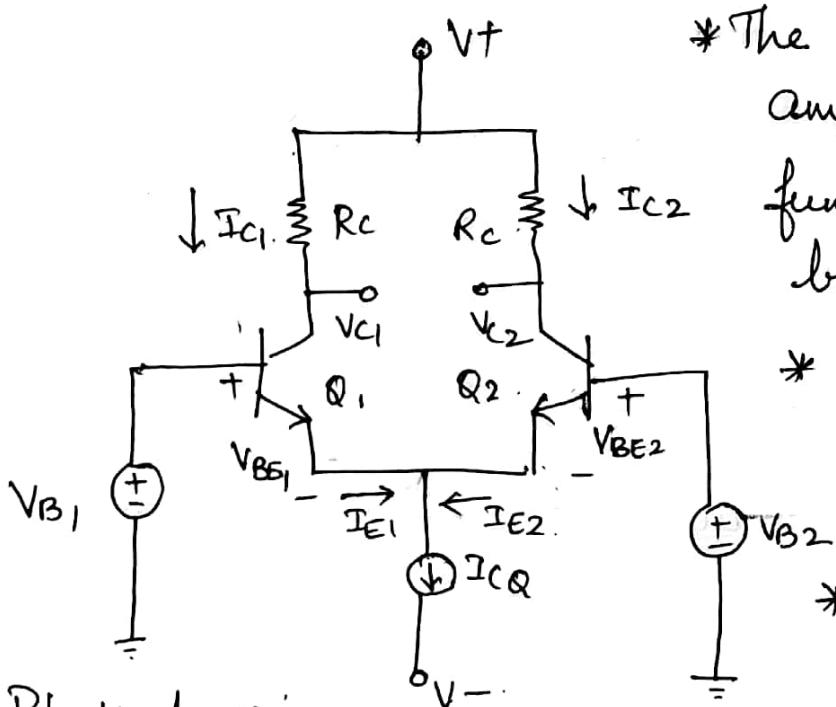


\* The differential amplifier is the fundamental building block of analog circuits.

\* i/p stage in every Op-amp,

\* basis of ECL.

Block diagram

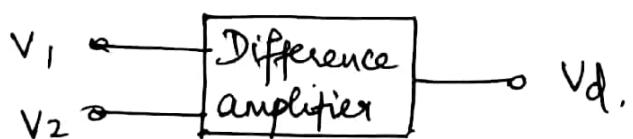

The difference amplifier amplifies the difference b/w 2 i/p signals.

$$V_o = A_d(V_1 - V_2).$$

If  $V_1 = V_2$  o/p voltage = 0

If  $V_1 \neq V_2$  o/p voltage  $\neq 0$ .

Differential mode i/p voltage

$$V_d = V_1 - V_2$$

Common mode i/p voltage

$$V_{cm} = \frac{V_1 + V_2}{2}$$

The o/p voltage due to both differential & common mode i/p is

$$V_o = A_d V_d + A_{cm} V_{cm}$$


↑                              ↑  
differential                  common mode  
mode gain                  gain

CMRR Common Mode rejection ratio

The ability of a diff-amp to reject common mode signal

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| \quad \text{in dB} \quad 20 \log \left| \frac{A_d}{A_{cm}} \right|$$
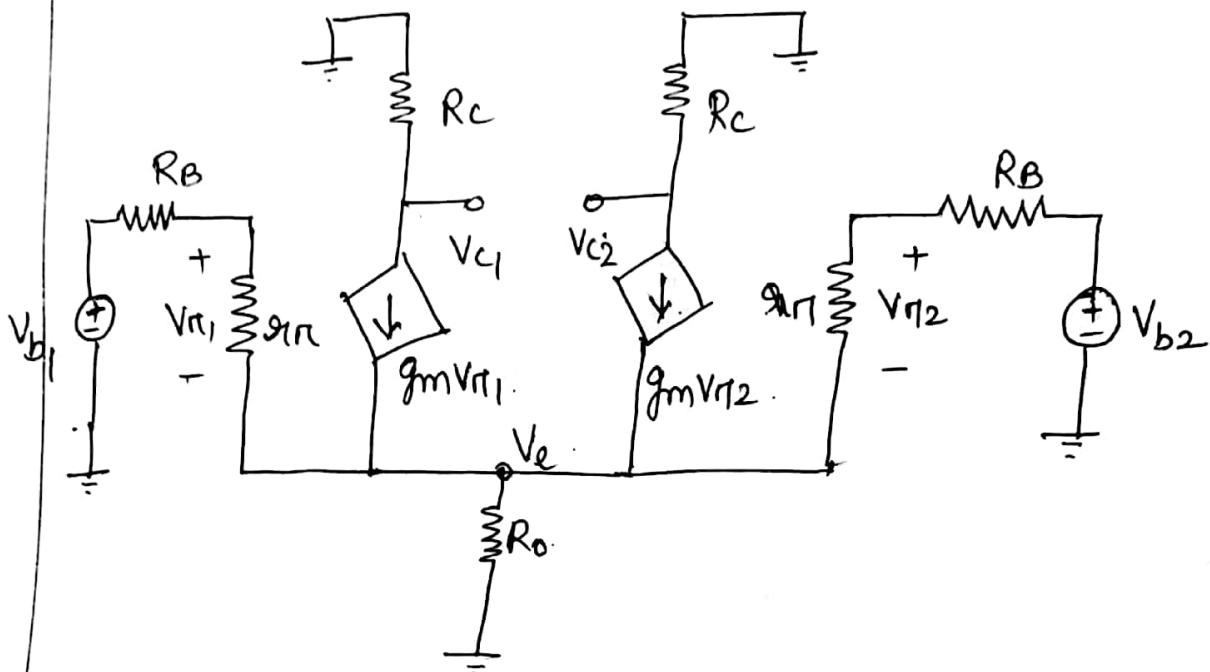
# Small signal Equivalent Circuit analysis



- \* Assume Early effect is infinite.
- \* Constant Current source can be represented by a finite open circuit impedance  $R_o$ . &  $R_B$  is also not neglected.

Since the 2 transistors are biased at the same quiescent current we have,

$$\vartheta_{\pi_1} = \vartheta_{\pi_2} = \vartheta_{\pi} \quad \& \quad g_{m1} = g_{m2} = g_m.$$

Writing a KCL at  $V_e$  :-

$$g_{m1} V_{\pi 1} + \frac{V_{\pi 1}}{\vartheta_{\pi}} + g_m V_{\pi 2} + \frac{V_{\pi 2}}{\vartheta_{\pi}} = \frac{V_e}{R_o}.$$

$$\text{Now } V_{\pi 1} \left( \frac{g_m \vartheta_{\pi} + 1}{\vartheta_{\pi}} \right) + \cancel{g_m} V_{\pi 2} \left( \frac{g_m \vartheta_{\pi} + 1}{\vartheta_{\pi}} \right) = \frac{V_e}{R_o}$$

SRM

$$V_e = \frac{V_{b_1} + V_{b_2}}{2 + \frac{\alpha_n + R_B}{R_o(1+\beta)}} \rightarrow ⑤$$

If we consider one sided QP at the collector of  $Q_2$  Then

$$V_o = V_{c_2} = -g_m v_{\pi 2} R_c \rightarrow ⑥$$

Sub the eqn for  $v_{\pi 2}$  from ③ into ⑥;

$$V_o = V_{c_2} = -g_m \alpha_n \left( \frac{V_{b_2} - V_e}{\alpha_n + R_B} \right) R_c$$

$$V_o = \frac{-\beta R_c}{\alpha_n + R_B} (V_{b_2} - V_e) \rightarrow ⑦$$

Sub the eqn for  $V_e$  from ⑤ in ⑦

$$V_o = -\frac{\beta R_c}{\alpha_n + R_B} \left[ V_{b_2} - \left( \frac{V_{b_1} + V_{b_2}}{2 + \frac{\alpha_n + R_B}{R_o(1+\beta)}} \right) \right]$$

$$= \frac{-\beta R_c}{\alpha_n + R_B} \left[ \frac{V_{b_2} \left( 2 + \frac{\alpha_n + R_B}{R_o(1+\beta)} \right) - V_{b_1} - V_{b_2}}{2 + \frac{\alpha_n + R_B}{R_o(1+\beta)}} \right]$$

$$= \frac{-\beta R_c}{\alpha_n + R_B} \left[ \frac{2V_{b_2} + V_{b_2} \left( \frac{\alpha_n + R_B}{R_o(1+\beta)} \right) - V_{b_1} - V_{b_2}}{2 + \frac{\alpha_n + R_B}{R_o(1+\beta)}} \right]$$

$$V_{\pi_1} \left( \frac{1+\beta}{g_{\pi}} \right) + V_{\pi_2} \left( \frac{1+\beta}{g_{\pi}} \right) = \frac{Ve}{R_o} \rightarrow ①$$

$$V_{\pi_1} = \left[ \frac{V_{b_1} - Ve}{g_{\pi} + R_B} \right] g_{\pi} \rightarrow ②$$

$$V_{\pi_2} = \frac{(V_{b_2} - Ve)}{g_{\pi} + R_B} \rightarrow ③$$

Sub ② & ③ in ①

$$\left( \frac{V_{b_1} - Ve}{g_{\pi} + R_B} \right) g_{\pi} \left( \frac{1+\beta}{g_{\pi}} \right) + \left( \frac{V_{b_2} - Ve}{g_{\pi} + R_B} \right) g_{\pi} \left( \frac{1+\beta}{g_{\pi}} \right) = \frac{Ve}{R_o}$$

$$\frac{(V_{b_1} - Ve)(1+\beta) + (V_{b_2} - Ve)(1+\beta)}{g_{\pi} + R_B} = \frac{Ve}{R_o}$$

$$\frac{(V_{b_1} + V_{b_2} - 2Ve)(1+\beta)}{g_{\pi} + R_B} = \frac{Ve}{R_o} \rightarrow ④$$

Solving for  $Ve$

$$V_{b_1} + V_{b_2} - 2Ve = \frac{Ve(g_{\pi} + R_B)}{R_o(1+\beta)}$$

$$V_{b_1} + V_{b_2} = \frac{Ve(g_{\pi} + R_B)}{R_o(1+\beta)} + 2Ve$$

$$V_{b_1} + V_{b_2} = Ve \left[ 2 + \frac{g_{\pi} + R_B}{R_o(1+\beta)} \right]$$

SRM

(15)

$$V_o = \frac{-\beta R_c}{2 + \frac{g_n + R_B}{R_o(1+\beta)}} \left\{ V_{b_2} \left[ 1 + \frac{g_n + R_B}{R_o(1+\beta)} \right] - V_{b_1} \right\} \rightarrow (8)$$

In an ideal current source  $R_o = \infty$  [in (8)]

$$\therefore V_o = \frac{-\beta R_c}{2 + 0} \left[ \frac{V_{b_2} (1+0) - V_{b_1}}{1+0} \right]$$

$$V_o = \frac{-\beta R_c (V_{b_2} - V_{b_1})}{2(g_n + R_B)} \rightarrow (9)$$

$$\therefore V_{b_2} - V_{b_1} = -V_d \quad (\text{or}) \quad \boxed{V_d = V_{b_1} - V_{b_2}} \rightarrow (10)$$

Sub (10) in (9)

$$V_o = \frac{\beta R_c V_d}{2(g_n + R_B)}$$

$$\frac{V_o}{V_d} = \frac{\beta R_c}{2(g_n + R_B)} = Ad. \rightarrow (11)$$

$$\text{w.r.t. } V_{cm} = \frac{V_{b_1} + V_{b_2}}{2} \quad \& \quad V_d = V_{b_1} - V_{b_2}$$

In terms of  $V_d$

$$\therefore V_{b_1} = V_{cm} + \frac{V_d}{2}. \text{ And} \rightarrow (12)$$

$$V_{b_2} = V_{cm} - \frac{V_d}{2} \rightarrow (13)$$

SRM

The two i/p signals can be written as the sum of differential mode i/p signal component & a common mode i/p signal component.

Sub (12) & (13) into (8)

$$V_o = \frac{-\beta R_c}{2(\gamma_{1\pi} + R_B)} \left[ V_{cm} - \frac{V_d}{2} \left( 1 + \frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)} \right) - \left( V_{cm} + \frac{V_d}{2} \right) \right] \frac{2 + \gamma_{1\pi} + R_B}{(1+\beta)R_o} \rightarrow (14)$$

Solving for  $V_d$  only:

$$\Rightarrow \frac{\beta R_c V_d}{2(\gamma_{1\pi} + R_B)} \left( 1 + \frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)} \right) + \frac{V_d \beta R_c}{2(\gamma_{1\pi} + R_B)}$$

$$\therefore 2 + \frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)}$$

$$\Rightarrow \frac{V_d \beta R_c}{2(\gamma_{1\pi} + R_B)} \left[ \frac{1 + \frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)} + 1}{2 + \frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)}} \right]$$

$$\Rightarrow V_d \frac{\beta R_c}{2(\gamma_{1\pi} + R_B)} \left[ \frac{2 + \cancel{\frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)}}}{\cancel{2 + \frac{\gamma_{1\pi} + R_B}{R_o(1+\beta)}}} \right]$$

$$\Rightarrow V_d \frac{\beta R_c}{2(\gamma_{1\pi} + R_B)} \rightarrow (15)$$

For  $V_{cm}$

$$\Rightarrow V_{cm} \left[ \frac{-\beta R_c}{g_m + R_B} \left( \frac{1 + \frac{g_m + R_B}{R_o(1+\beta)}}{2 + \frac{g_m + R_B}{(1+\beta)R_o}} \right) \right]$$

$$\Rightarrow -\frac{V_{cm} \beta R_c}{g_m + R_B} \left[ \frac{\frac{g_m + R_B}{R_o(1+\beta)}}{\frac{2(1+\beta)R_o + g_m + R_B}{(1+\beta)R_o}} \right]$$

$$\Rightarrow \frac{-\beta R_c V_{cm}}{g_m + R_B} \left[ \frac{g_m + R_B}{2(1+\beta)R_o + g_m + R_B} \right]$$

$$\Rightarrow -\frac{\beta R_c V_{cm}}{g_m} \left[ \frac{1}{1 + \frac{2R_o(1+\beta)}{g_m + R_B}} \right]$$

$$\Rightarrow -\frac{g_m R_c V_{cm}}{1 + \frac{2R_o(1+\beta)}{g_m + R_B}}$$

Combining ⑮ & ⑯

$$V_o = \frac{\beta R_c}{2(g_m + R_B)} V_d - \frac{g_m R_c}{1 + \frac{2R_o(1+\beta)}{g_m + R_B}} V_{cm}$$

$$= A_d V_d + A_{gm} V_{cm}$$

$$Ad = \frac{\beta R_C}{2(R_{IN} + R_B)} \quad & A_{CM} = -\frac{g_m R_C}{1 + 2(1+\beta)R_O} \\ \frac{1}{2(R_{IN} + R_B)} & \frac{g_m R_C}{1 + 2(1+\beta)R_O}$$


If  $R_O = \infty$

then  $A_{CM} = 0$

### Small signal analysis of BJT active load.

\*  $R_L$  represents the small signal i/p resistance of the gain stage.


\* Differential mode i/p is applied.

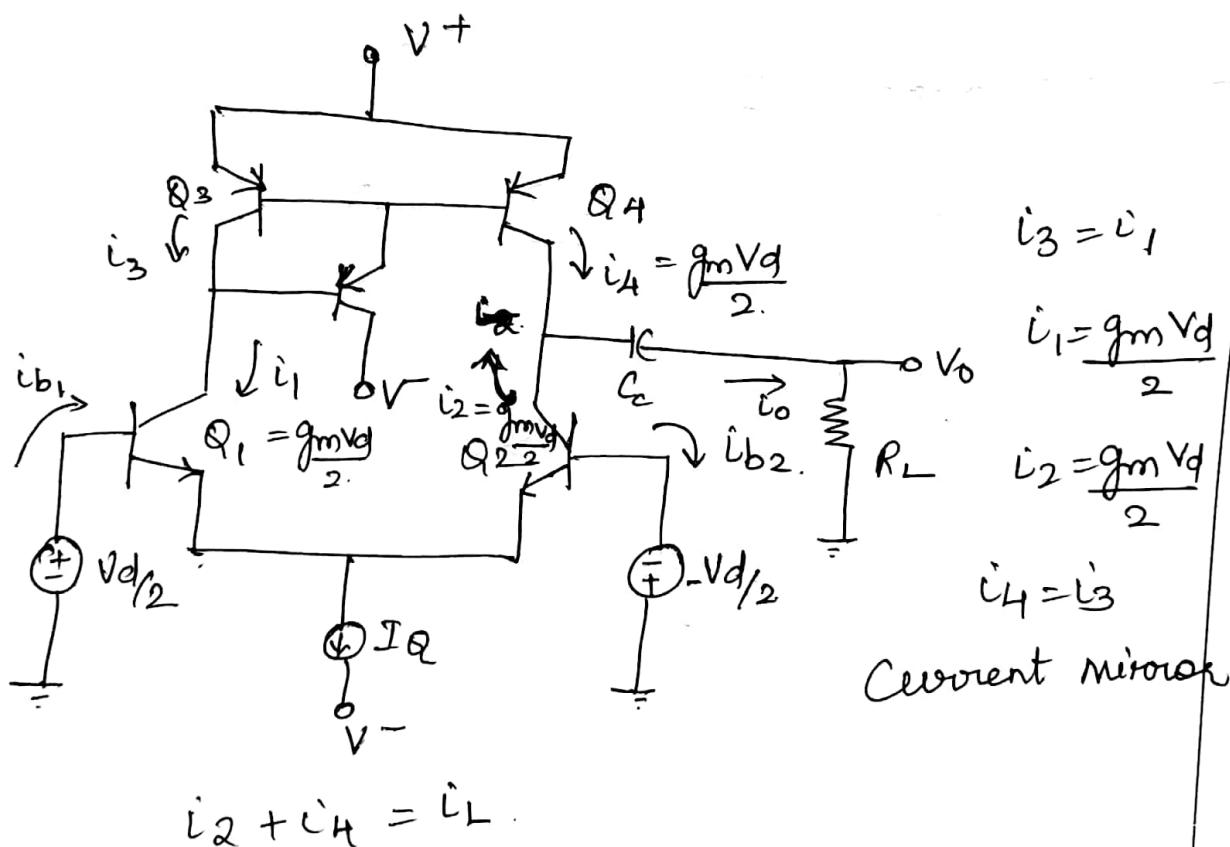


Current mirror

# Small signal Equivalent circuit

(17)

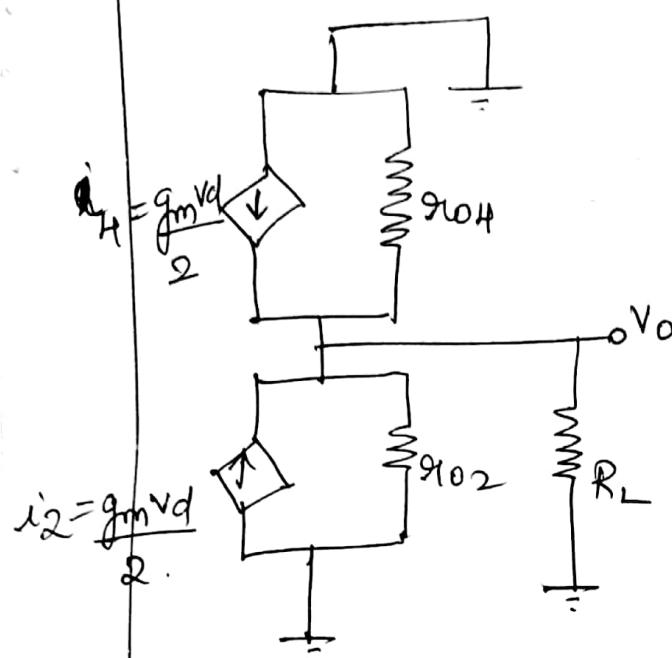

rearranged circuit

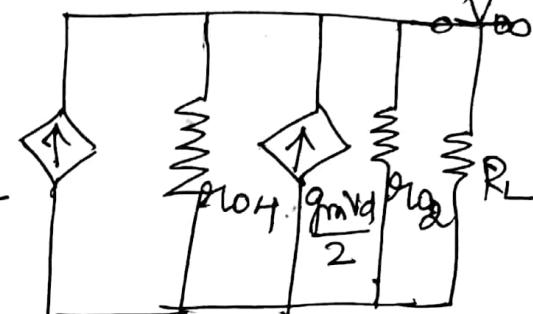

$$\begin{aligned}
 V_o &= \left( \frac{g_m V_d}{2} + \frac{g_m V_d}{2} \right) \left( r_{o4} \parallel r_{o2} \parallel R_L \right) \\
 &= 2 \left( \frac{g_m V_d}{2} \right) \left( r_{o4} \parallel r_{o2} \parallel R_L \right)
 \end{aligned}$$

$$Ad = \frac{V_o}{V_d} = g_m (r_{o4} \parallel r_{o2} \parallel R_L)$$

or  $Ad = \frac{g_m}{\frac{1}{r_{o4}} + \frac{1}{r_{o2}} + \frac{1}{R_L}} = \frac{g_m}{g_{o2} + g_{o4} + G_L}$

w.r.t  $g_m = \frac{I_Q}{2V_T}$ ,  $r_{o2} = \frac{V_{A2}}{I_2}$  and  $r_{o4} = \frac{V_{A4}}{I_4}$


$$I_2 = I_4 = I_Q/2$$

$$Ad = \frac{\frac{I_Q}{2V_T}}{\frac{I_Q}{2V_T} + \frac{I_Q}{2V_{A4}} + \frac{1}{R_L}}$$


SRM

This is similar to that of a single amplifier with an active load.

### Basic FET Differential pair

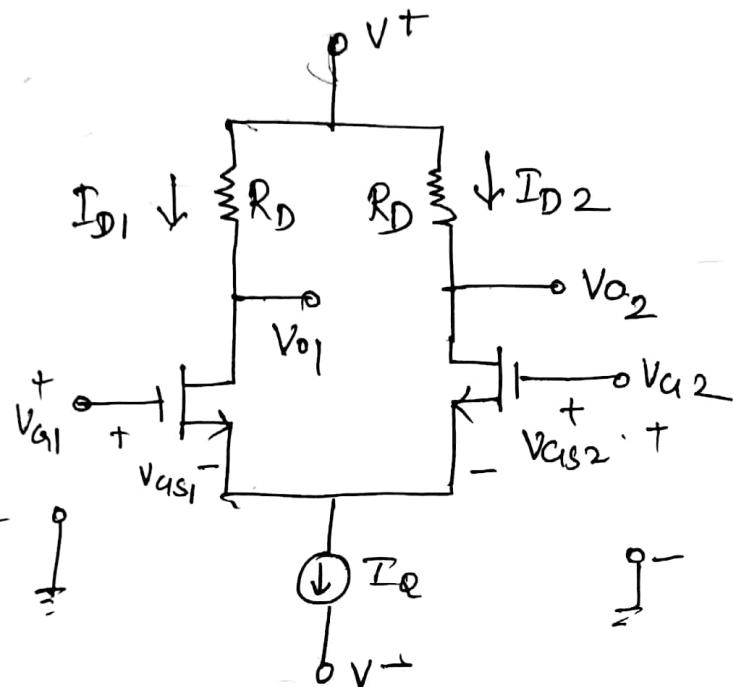
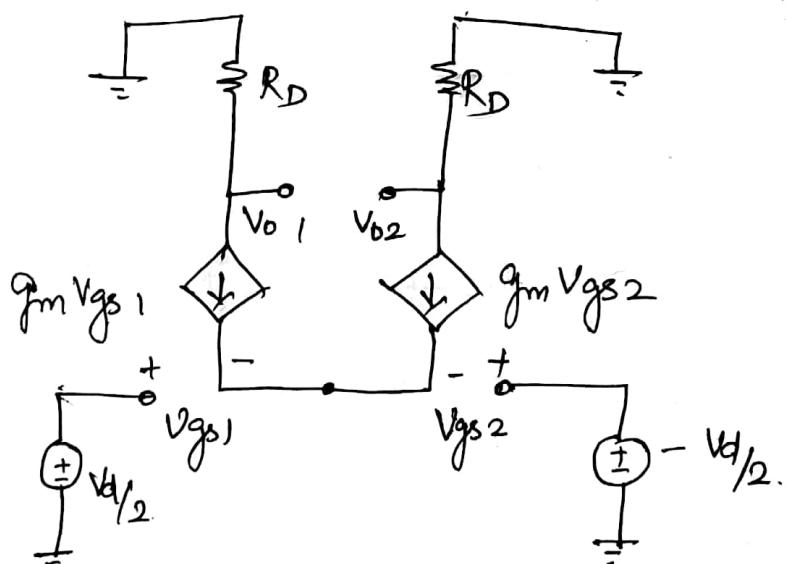
### Small signal Analysis of FET diff-amp



Applying KCL to the common source node:

$$g_m V_{gs1} + g_m V_{gs2} = 0$$

$$g_m V_{gs1} = -g_m V_{gs2} \Rightarrow V_{gs1} = -V_{gs2} \rightarrow ①$$

The differential mode o/p voltage is

$$V_d = V_1 - V_2 = V_{gs1} - V_{gs2} \rightarrow ②$$

① in ②

$$\therefore V_d = -V_{gs2} - V_{gs2} = -2V_{gs2}$$

& one sided o/p at  $V_{o2}$  is given by

$$V_{o2} = -g_m V_{gs2} R_D = -g_m \left(\frac{V_d}{2}\right) R_D$$

$$A_d = \frac{V_{o2}}{V_d} = +\frac{g_m R_D}{2}$$

$A_d = \frac{g_m R_D}{2}$

If constant current source & o/p resistance is finite, then the JFET amplifier will have a non zero common mode gain.

### MOSFET Differential Amplifier with Active Load

$M_1$  &  $M_2$  are n-channel devices and form differential pair biased with  $I_Q$ . The load

Circuit consists of  $M_3$  &  $M_4$ , both p-channel devices.

$$i_{D1} = i_{D2} = \frac{I_Q}{2}$$

There are no gate currents therefore


$$i_{D3} = i_{D1} \quad \& \quad i_{D4} = i_{D2}$$


If

$V_d = V_1 - V_2$  is applied, then ~~from~~


$$i_{D1} = \frac{I_Q}{2} + i_d \quad \& \quad i_{D2} = \frac{I_Q}{2} - i_d$$
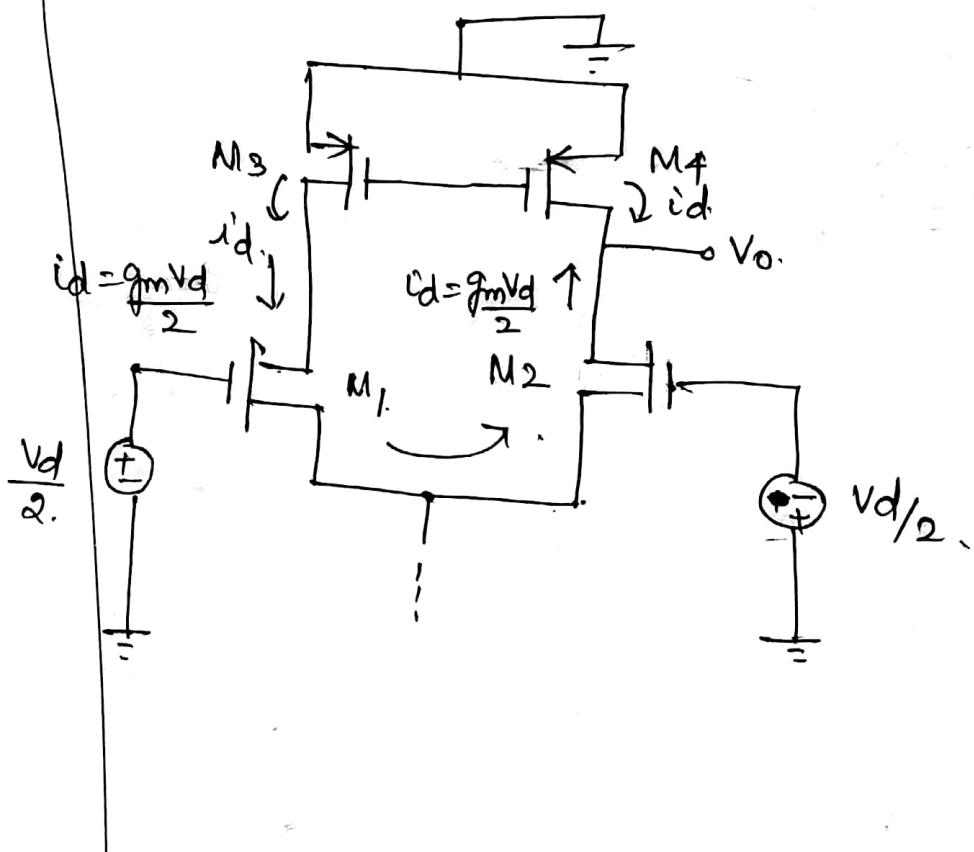
$$i_{D1} = i_{D3} = \frac{I_Q}{2} + i_d \quad \& \quad i_{D4} = i_{D2} = \frac{I_Q}{2} - i_d$$



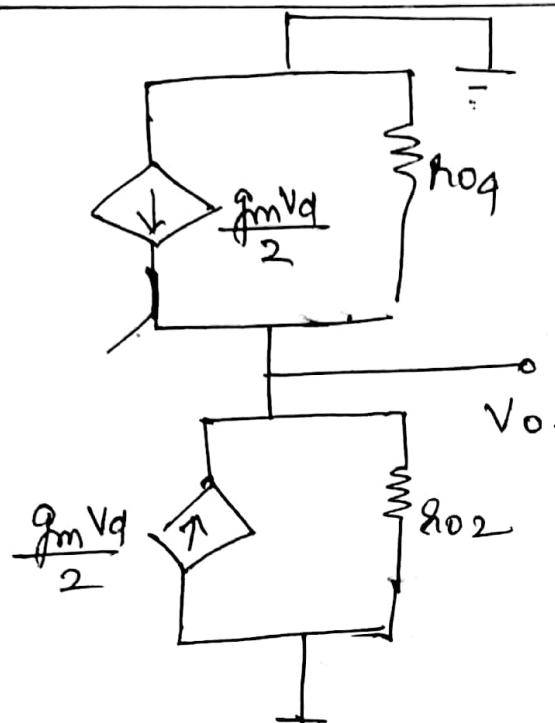

The small signal equivalent circuit:

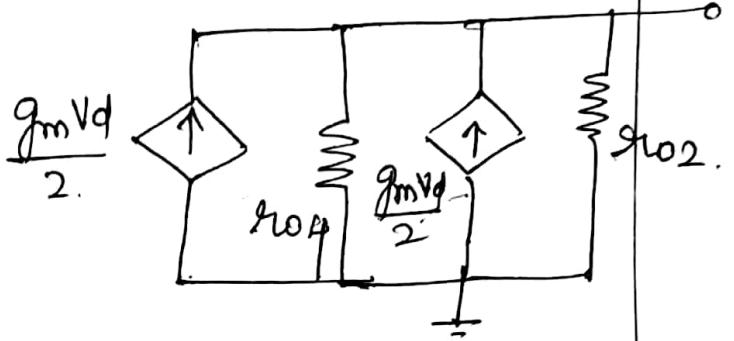

$$V_o = 2 \left( \frac{g_m V_d}{2} \right) (r_{02} \| r_{04})$$

$$\frac{V_o}{V_d} = Ad = g_m (r_{02} \| r_{04}).$$

$$Ad = \frac{g_m}{\frac{1}{r_{02}} + \frac{1}{r_{04}}} = \frac{g_m}{g_{02} + g_{04}}$$

$$g_m = 2 \sqrt{k_n I_D} = \sqrt{2 k_n I_Q}$$

$$g_{02} = d_2 I_{DQ2} = (d_2 I_Q / 2)$$

$$g_{04} = d_4 I_{DQ4} = (d_4 I_Q / 2) \text{ then}$$


$$Ad = \frac{2 \sqrt{2 k_n I_Q}}{I_Q (d_2 + d_4)} = 2 \sqrt{\frac{2 k_n}{I_Q}} \cdot \frac{1}{d_2 + d_4}$$

## Circuits with active load:-

In bipolar amplifiers, the small signal voltage gain is directly proportional to the collector resistor  $R_C$ . To increase the gain, we need to increase  $R_C$  value, and hence  $V_{CC}$  has to be increased. In practice, there is a limited range of values of  $R_C$  &  $V_{CC}$  that are ~~not~~ reasonable.

- \* We use a load device that is a transistor.
- \* Active loads produce much larger small signal gain than discrete resistors.


### DC Analysis : BJT active Load

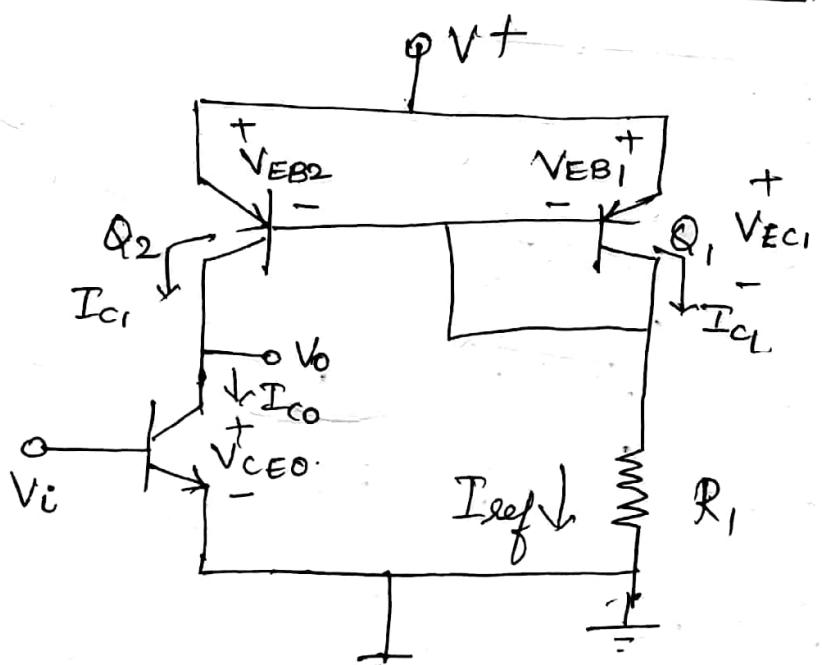

The elements  $R_1$ ,  $Q_1$ , and  $Q_2$  form the active load &  $Q_2$  is referred as the active load device for  $Q_1$ .
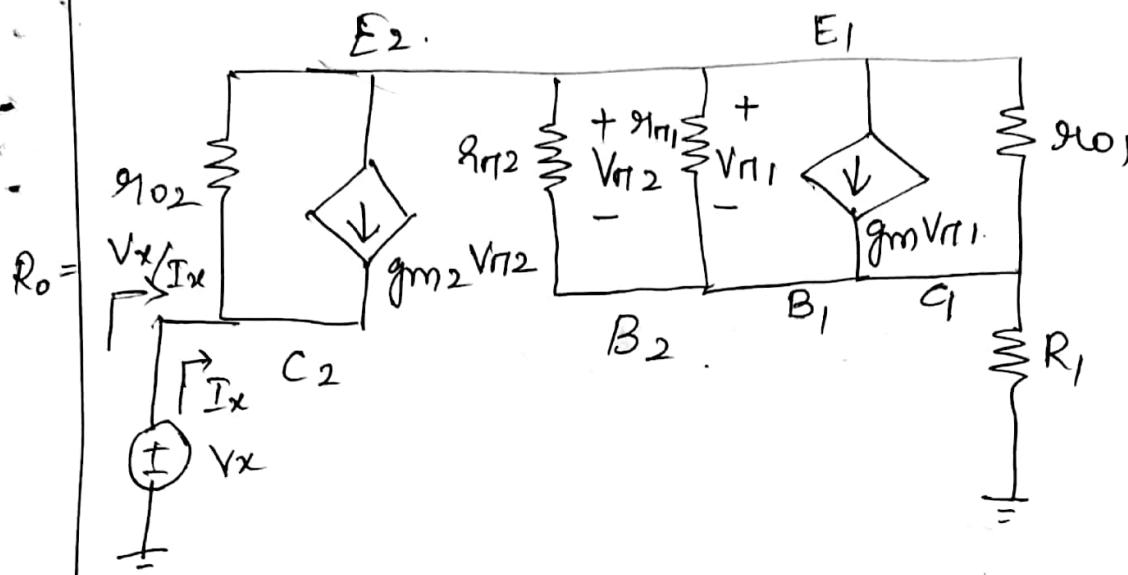
### Small signal analysis

We must determine the resistor looking into the collector of the active load.




In the  $Q_1$  portion of equivalent circuit, there are no independent ac sources to excite any currents or voltages.  $\therefore V_{r1} = V_{r2} = 0$

$$g_m V_{r2} = 0$$

$R_o = r_{\pi 2}$  resistance looking into the collector of  $Q_2$

We will use this equivalent resistance to calculate the small signal voltage gain of the amplifier.

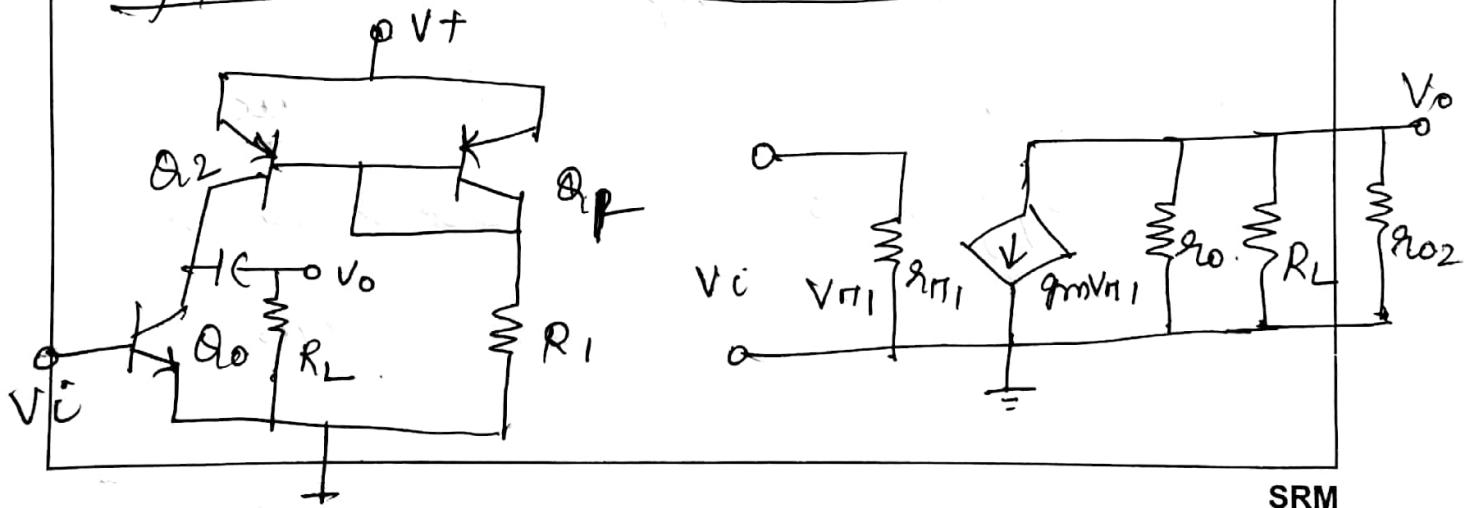Simple BJT with active load & load resistance.



The off voltage is

$$V_o = -g_m V_{T1} (r_0 || R_L || r_{02})$$

$$V_{T1} = V_i$$

$$\therefore \frac{V_o}{V_i} = A_v = -g_m (r_0 || R_L || r_{02})$$

$$A_v = \frac{-g_m}{\frac{1}{r_0} + \frac{1}{R_L} + \frac{1}{r_{02}}}$$

$$A_v = \frac{-g_m}{g_0 + g_L + g_{02}}$$

or


$$A_v = - \left( \frac{\frac{I_{CO}}{V_T}}{\frac{I_{CO}}{V_{AN}} + \frac{1}{R_L} + \frac{I_{CO}}{V_{AP}}} \right)$$

$$\frac{I_{CO}}{V_{AN}} + \frac{1}{R_L} + \frac{I_{CO}}{V_{AP}}$$


Small Signal Analysis of CS with Active load

M<sub>1</sub> & M<sub>2</sub> form a PMOS active load circuit

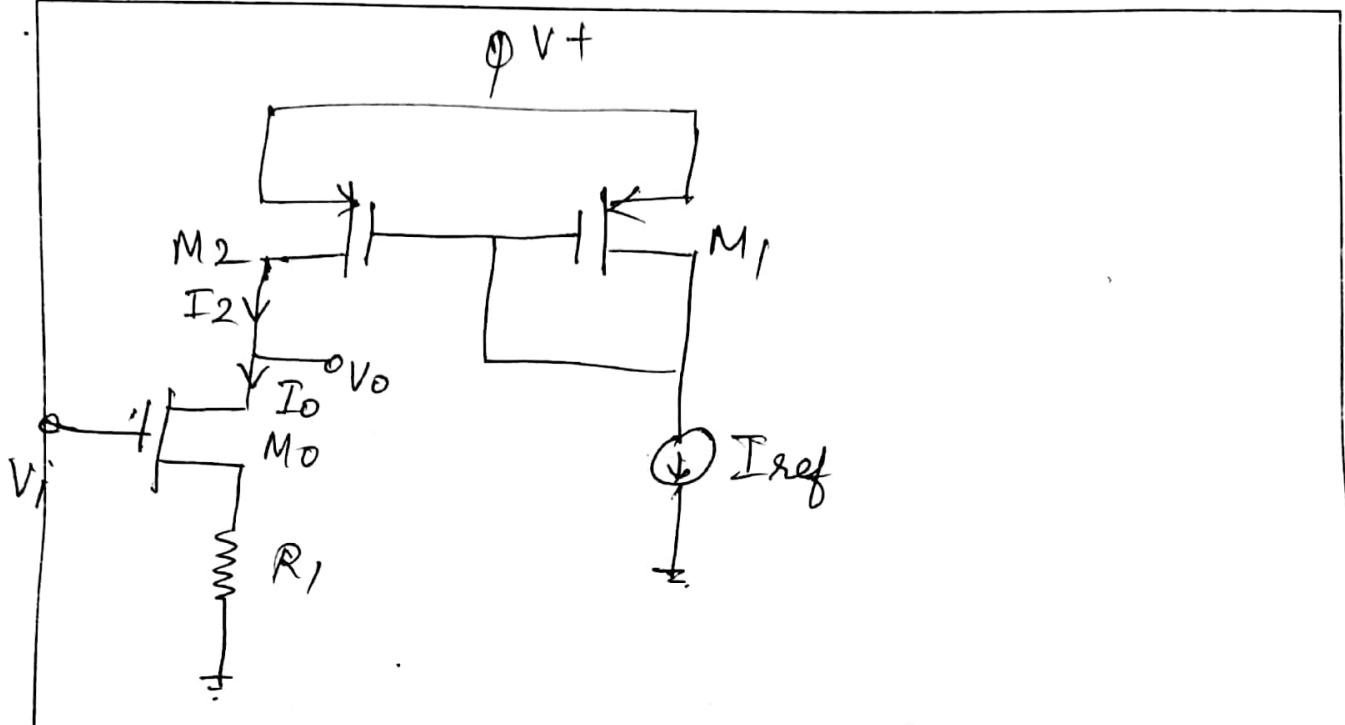& M<sub>2</sub> is the active load device.



Small signal equivalent

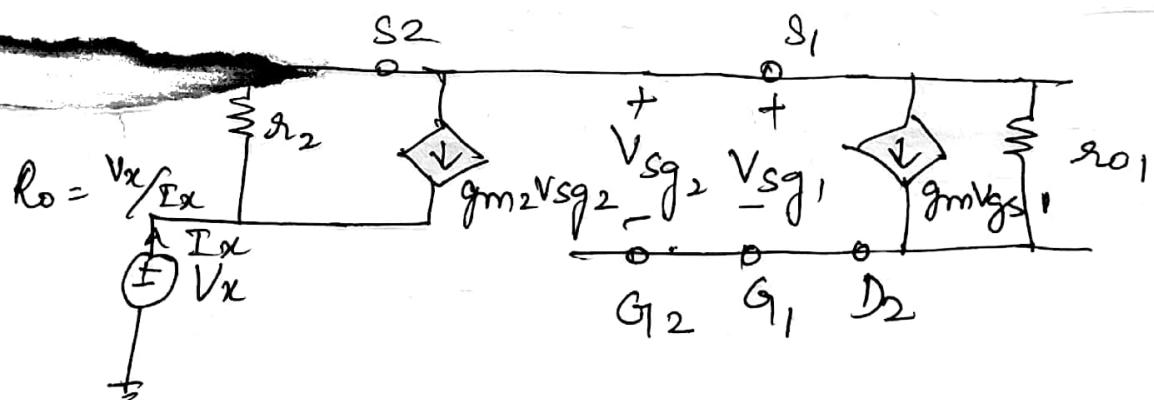

To find  $R_o$ :


No independent ac source is supplied for  $M_2 \therefore V_{gs1} = V_{gs2} = 0$

$$g_m V_{gs1} = g_m V_{gs2} = 0$$

$$R_o = r_{D2}$$

A simple MOSFET CS with an active load &  $R_o$

# Small signal equivalent ckt

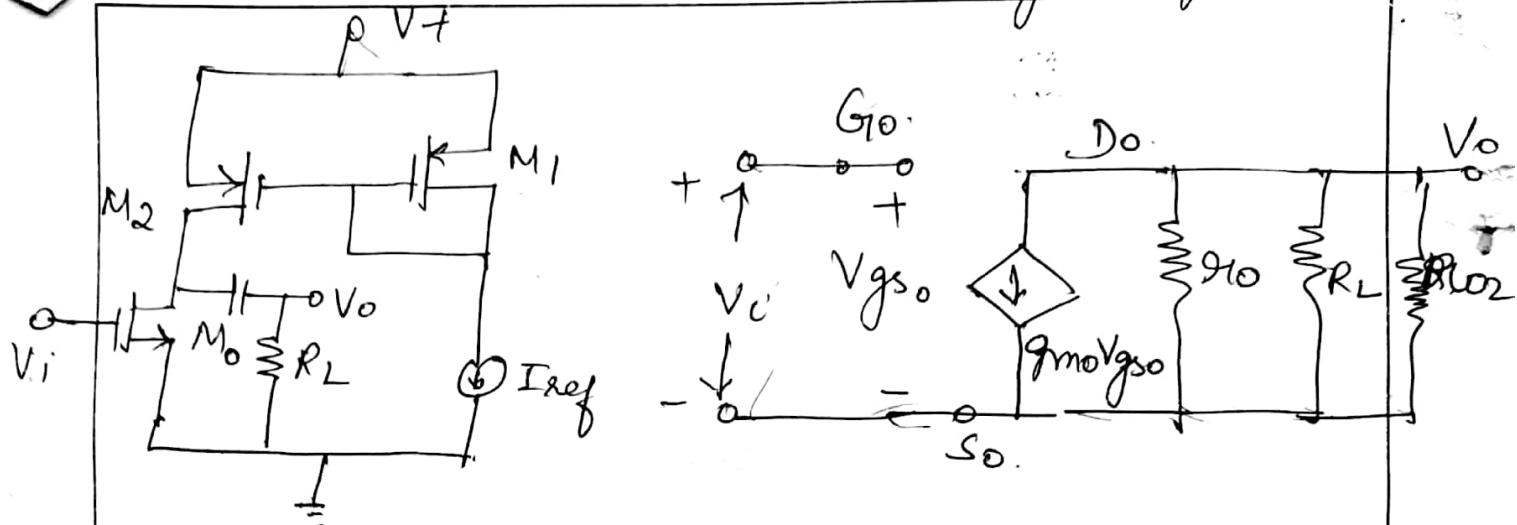

To find  $A_v$  :-

$$V_o = -g_m v_{gs0} (r_{o1} \parallel R_L \parallel r_{o2}) \quad v_{gs0} = V_i$$

$$\frac{V_o}{V_i} = -g_m (r_{o1} \parallel R_L \parallel r_{o2})$$

$$A_v = \frac{-g_m}{\frac{1}{r_{o1}} + \frac{1}{R_L} + \frac{1}{r_{o2}}} = \frac{-g_m}{g_o + g_L + g_{o2}}$$