

Unit-3 (Feedback Amplifier)

$$A_V = -g_m \left(\frac{R_i}{R_i + R_s} \right) R_o$$

$$= - \frac{I_o}{V_{in}} \left(\frac{R_i}{R_i + R_s} \right) R_o$$

$$= - \frac{I_o}{V_{in}} \cdot \frac{1}{R_i} R_o \quad [\text{if } R_s = 0]$$

$$A_V = - A_I \frac{R_o}{R_i}$$

If $A_I = 100$, $R_i = 1.1 \text{ k}\Omega$, $R_o = 2.2 \text{ k}\Omega$.

$$A_V = -200$$

If $V_i = 1 \text{ mV}$

$$\begin{aligned} \therefore V_o &= |A_V| V_i \\ &= 200 \times 1 \text{ mV} \\ &= 200 \text{ mV} \end{aligned}$$


If Temp \uparrow , $A_I \uparrow$, to 110.

Then

$$A_V = 110 \cdot \frac{2.2 \text{ k}}{1.1 \text{ k}} = 220$$

$$\begin{aligned} \therefore V_o &= 220 \cdot 1 \text{ mV} \\ &= 220 \text{ mV} \end{aligned}$$

Feedback Amp. Block Diagram :-

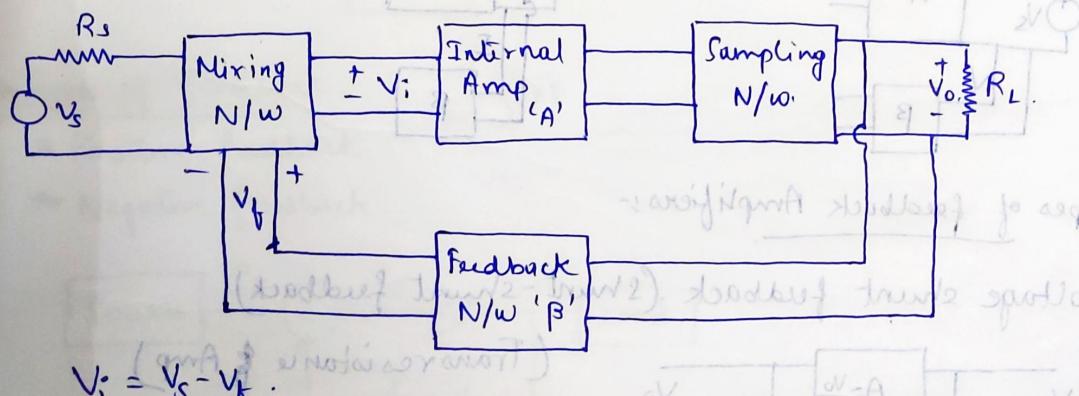


∴ If $V_o \uparrow$ due to any fluctuations,

$V_f \uparrow \therefore V_i \downarrow \Rightarrow$ Brought down V_o to constant.

∴ If $V_o \downarrow$, $V_f \downarrow$, $V_i \uparrow \Rightarrow$ Brought down V_o to constant.


► Sampling N/W :-

i)

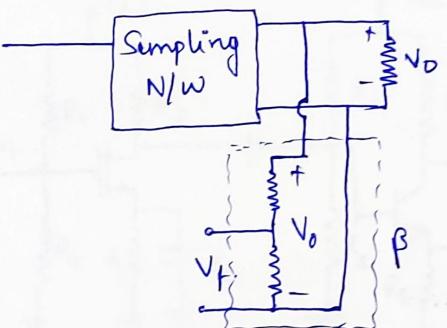


$$\text{Voltage Sampling} := \frac{V_o}{V_{in}} = \frac{\beta}{\beta + 1}$$

ii) Current Sampling :-

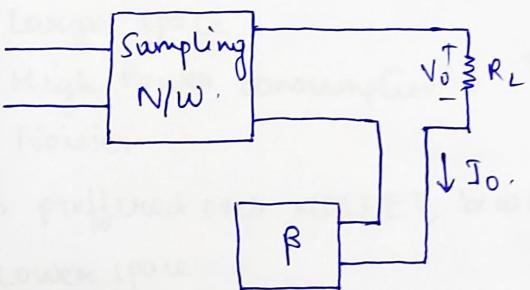


► Mixing N/W :-

i) Series mixing

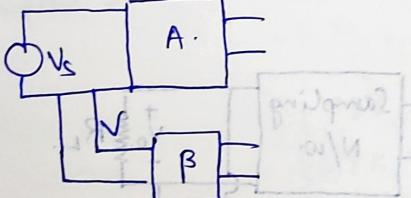


ii) Shunt mixing

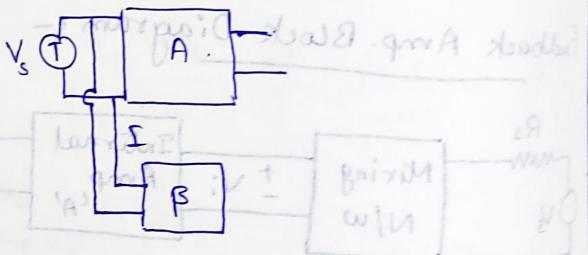


► Types of feedback Amplifiers :-

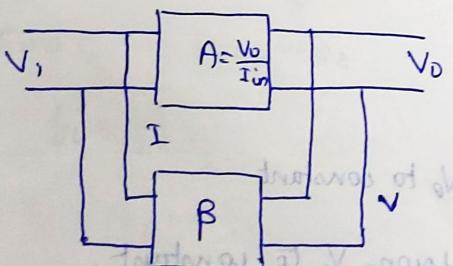i) Voltage shunt feedback (Shunt-shunt feedback),




(Transresistance Amp)

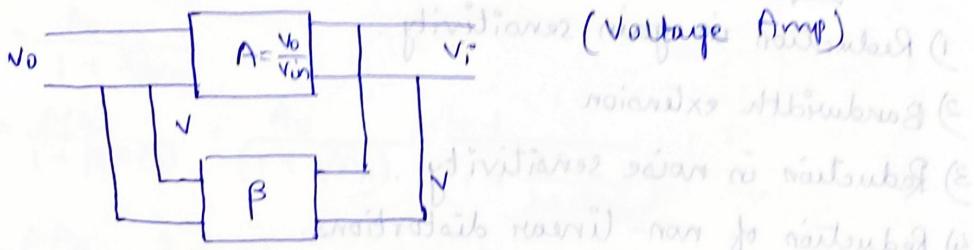
2) Voltage Series Feedback (Series shunt feedback).



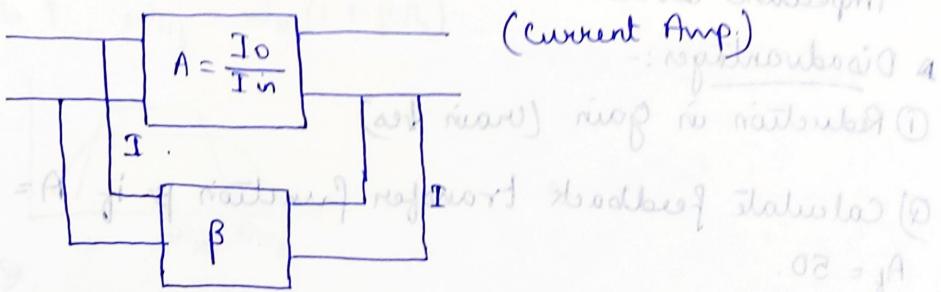3) Current Shunt Feedback (Shunt - series feedback).



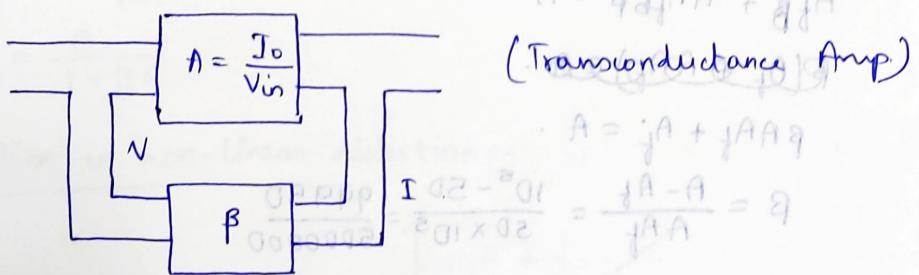
4) Current Series Feedback (Series - series feedback).



► Types of Feedback :

► Positive feedback.

► Negative feedback.

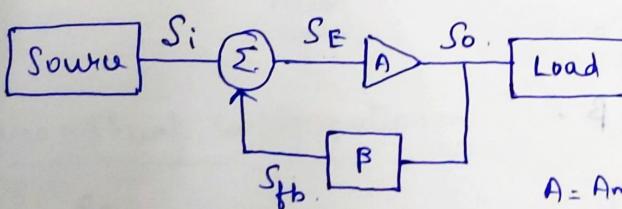

$$S_o = A \cdot S_E.$$

$$S_{fb} = \beta S_o.$$

$$S_E = S_i - S_{fb}.$$

$$S_o = A(S_i - S_{fb}) = AS_i - A\beta S_o \Rightarrow AS_i = S_o + A\beta S_o \Rightarrow A_{fb} = \frac{S_o/S_i}{1 + A\beta} = \frac{A}{1 + A\beta}.$$

A = Amplification factor / open loop gain

β = feedback transfer function
OR

$A\beta > 1$

$$\therefore A_{fb} = \frac{A}{A\beta} = \frac{1}{\beta}.$$

feedback factor.

Advantages of Negative feedback :-

- 1) Reduction in gain sensitivity.
 - 2) Bandwidth extension.
 - 3) Reduction in noise sensitivity.
 - 4) Reduction of non-linear distortions.
- (*) -ve feedback has good control over input & output impedance levels.

Disadvantages :-

- 1) Reduction in gain (gain loss)

- 2) Calculate feedback transfer function β if $A = 10^5$,

$$A_f = 50.$$

$$A_{fb} = \frac{A}{1 + AB}$$

$$A_f B + A A_{fb} \beta = A$$

$$(A_f + A A_{fb}) \beta = 0$$

$$\beta A A_f + A_f = A$$

$$\beta = \frac{A - A_f}{A A_f} = \frac{10^5 - 50}{50 \times 10^5} = \frac{99950}{5000000} = 0.0199.$$

Advantages of Negative Feedback:

- i) Reduction in gain sensitivity :-


$$A_f = \frac{A}{1 + AB}$$

$$\frac{dA_f}{dA} = \frac{1}{1 + AB} - \frac{A}{(1 + AB)^2} \cdot B$$

$$\frac{dA_f}{dA} = \frac{1}{(1 + BA)^2} = \frac{1}{B^2} = \frac{1}{9A^2} = \frac{1}{81A^2}$$

$$dA_f = \frac{dA}{(1 + BA)^2}$$
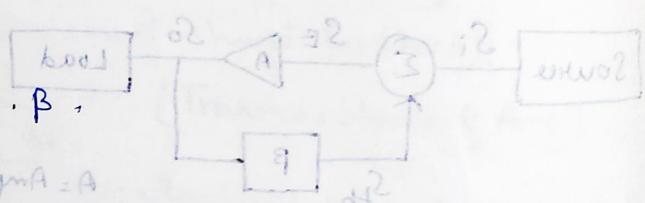
$$\frac{dA_f}{A_f} = \frac{dA / (1 + BA)^2}{A / (1 + AB)} = \frac{1}{1 + AB} \cdot \frac{dA}{A}$$



$$\frac{1}{9} = \frac{A}{9A} = dA/A$$

$$dA = 1/9A = 1/81A^2$$


$$dA = 1/81A^2 = 1/81 \cdot 1/81 = 1/6561$$

ii) Bandwidth extension:-

$$A(s) = \frac{A_0}{1 + s/\omega_H}$$

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)} = \frac{A_0}{(1 + s/\omega_H)} \cdot \frac{1}{\left(1 + \frac{\beta A_0}{1 + s/\omega_H}\right)} \\ = \left(\frac{A_0}{1 + \beta A_0}\right) \left(\frac{1}{1 + s/\omega_H(1 + \beta A_0)}\right)$$

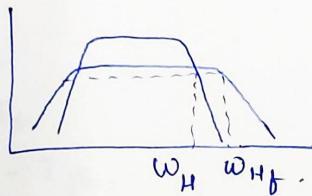i.e. ω_H is ↑, $\omega_{H_f} = \omega_H (1 + \beta A_0)$





iii) Noise & distortion Reduction:-



$$N_f = \frac{N}{1 + \beta A}$$

$$D_f = \frac{D}{1 + \beta A}$$

iv) Reduction in non-linear distortion:-

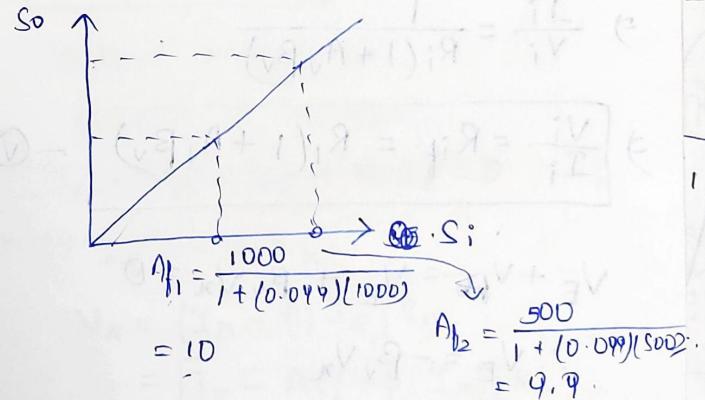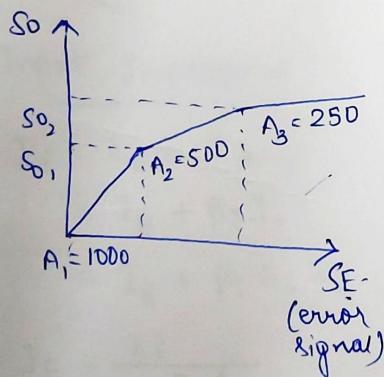

► Series-Shunt Configuration:-

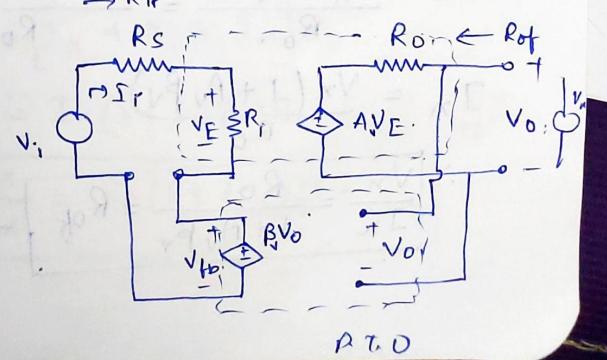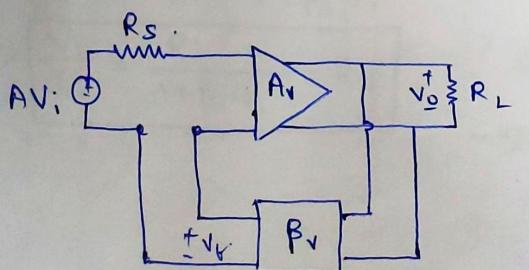

$$V_o = A_v V_E \quad \text{--- (1)}$$

$$\& V_{fb} = \beta_v V_o \quad \text{--- (2)}$$

$$V_E = V_i - V_{fb}$$

$$\therefore V_o = A_v (V_i - V_{fb}) \quad \text{--- (3)}$$

$$\therefore V_o = A_v (V_i - \beta_v V_o)$$

$$\Rightarrow V_o = A_v V_i - \beta_v V_o A_v$$

$$\Rightarrow V_o (1 + A_v \beta_v) = A_v V_i$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} = \frac{A_v}{1 + A_v \beta_v} = A_v f_v} \quad \text{--- (4)}$$

$$V_i = V_E + V_{fb} = V_E + \beta_v V_o$$

$$V_i = V_E + \beta_v (A_v V_E)$$

$$\Rightarrow V_i = V_E (1 + A_v \beta_v)$$

$$\Rightarrow V_E = \frac{V_i}{1 + A_v \beta_v}$$

$$I_i = \frac{V_E}{R_i} = \frac{V_i}{R_i (1 + A_v \beta_v)}$$

$$\Rightarrow \frac{I_i}{V_i} = \frac{1}{R_i (1 + A_v \beta_v)}$$

$$\Rightarrow \boxed{\frac{V_i}{I_i} = R_{if} = R_i (1 + A_v \beta_v)} \quad \text{--- (5)}$$

$$V_E + V_{fb} = V_E + \beta_v V_n = 0$$


$$\therefore V_E = -\beta_v V_n$$

$$I_n = \frac{V_n - A_v V_E}{R_o} = \frac{V_n + A_v \beta_v V_n}{R_o}$$

$$I_n = \frac{V_n (1 + A_v \beta_v)}{R_o}$$

$$\Rightarrow \boxed{\frac{V_n}{I_n} = \frac{R_o}{1 + A_v \beta_v} = R_{of}} \quad \text{--- (6)}$$

Shunt-Series Configuration :-

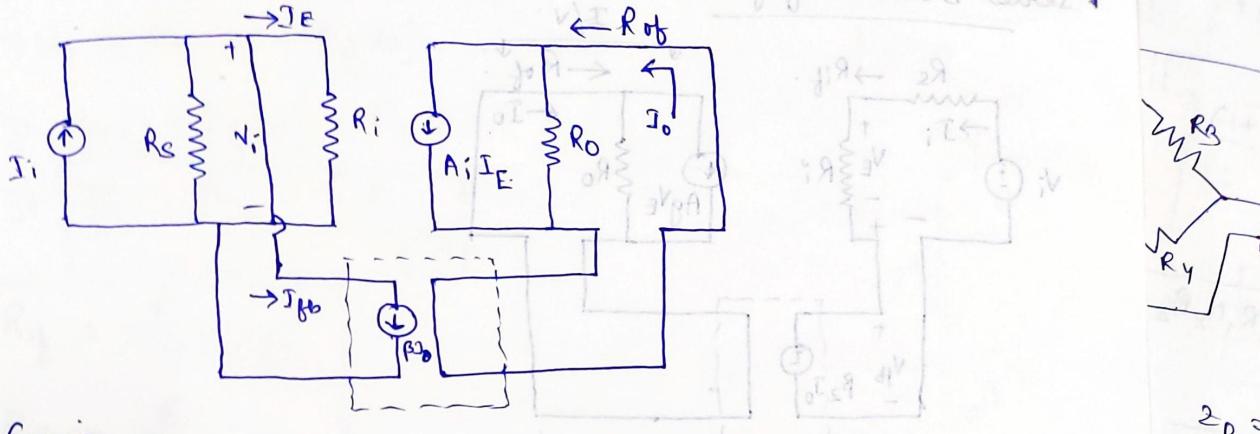

Gain

$$I_o = A_i I_E$$

$$I_{fb} = \beta_i I_o$$

$$I_E = I_i - I_{fb}$$

$$I_i = I_E + I_{fb}$$

$$= I_E + \beta_i I_o$$

$$= \frac{I_o}{A_i} + \beta_i I_o$$

$$\Rightarrow I_i = \frac{I_o + \beta_i A_i I_o}{A_i}$$

~~$$\frac{I_o}{I_i} = \frac{A_i I_E}{I}$$~~

Input Impedance

$$I_i = I_E + I_{fb}$$

$$= I_E + \beta_i I_o$$

$$= I_E + \beta_i A_i I_E$$

$$\Rightarrow I_E = \frac{I_i}{1 + \beta_i A_i}$$

$$V_i = I_E R_i = \frac{I_i R_i}{1 + \beta_i A_i}$$

$$\Rightarrow \frac{V_i}{I_i} = \frac{R_i}{1 + \beta_i A_i} = R_{ip}$$

$$\Rightarrow I_i = \frac{I_o (1 + \beta_i A_i)}{A_i (1 + \beta_i A_i) - \beta_i I_o} = \frac{I_o}{A_i}$$

$$\Rightarrow \frac{I_o}{I_i} = \frac{A_i}{1 + \beta_i A_i}$$

Output Impedance

Connect V_x at O/P

$$I_E + I_{fb} = I_E + \beta_i I_x = 0$$

$$I_E = -\beta_i I_x = f \Omega$$

$$V_x = (I_x - A_i I_E) R_o$$

$$= [I_x - A_i (-\beta_i I_x)] R_o$$

$$V_x = [I_x + A_i \beta_i I_x] R_o$$

$$\Rightarrow V_x = I_x (1 + A_i \beta_i) R_o = f I$$

$$\Rightarrow \frac{V_x}{I_x} = R_o (1 + A_i \beta_i) = R_{of}$$

$$V_o = A_2 (I_i - I_{fb})$$



$$\Rightarrow V_o = A_2 (I_i - \beta_g V_o)$$

$$\Rightarrow V_o (1 + \beta_g A_2) = A_2 I_i$$

$$\Rightarrow \frac{V_o}{I_i} = A_{2f} = \frac{A_2}{1 + \beta_g A_2}$$

$$R_{if} = \frac{R_i}{1 + A_2 \beta_g}$$

$$R_{of} = \frac{R_o}{1 + A_2 \beta_g}$$

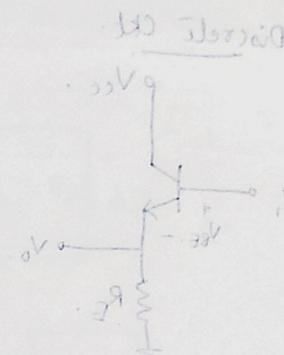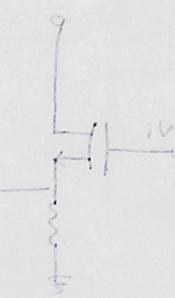



$$Z_p = R$$

$$Z_s = R$$

Configuration	Type of Amp	Chain with feedback	$(I/P \text{ Imp})$	$O/P \text{ Imp}$
Series-Shunt	I/P = V O/P = V Voltage Amp	$\frac{A_v g_i}{1 + \beta_v A_v}$	$R_{if} = \frac{R_i}{1 + \beta_v A_v}$	$R_{of} = \frac{R_o}{1 + \beta_v A_v}$
Shunt-Series	I/P = I O/P = I Current Amp	$\frac{A_i}{1 + \beta_i A_i}$	$R_{if} = \frac{R_i}{1 + \beta_i A_i}$	$R_{of} = R_o (1 + \beta_i A_i)$
Series-Series	I/P = I O/P = I Transconductance	$\frac{A_g}{1 + A_g \beta_2}$	$R_{if} = \frac{R_i}{1 + A_g \beta_2}$	$R_{of} = R_o (1 + \beta_2 A_g)$
Shunt-shunt	I/P = I O/P = V	$\frac{A_2}{1 + \beta_g A_2}$	$R_{if} = \frac{R_i}{1 + A_2 \beta_g}$	$R_{of} = \frac{R_o}{1 + A_2 \beta_g}$

Practical feedback ckt: $V_o = (v_A v_g + 1) I_i = (v_A v_g + 1) R_f = j R_f$

Voltage Amp:

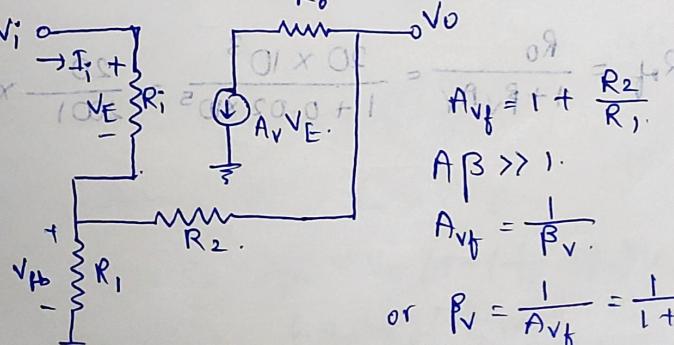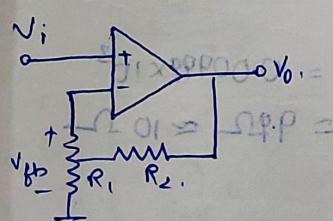




$$A_{vf} = \frac{A_v}{1 + \beta_v A_v} = \frac{A_v}{1 + \frac{A_v}{1 + R_2/R_1}}$$

$$\text{or } P_v = \frac{1}{A_{vf}} = \frac{1}{1 + R_2/R_1}$$

$$A_{vf} \gg 1$$

$$A_{vf} = \frac{1}{\beta_v}$$

Discrete Ckt.

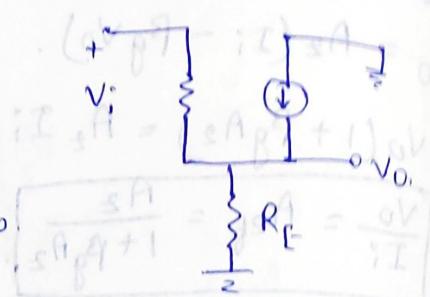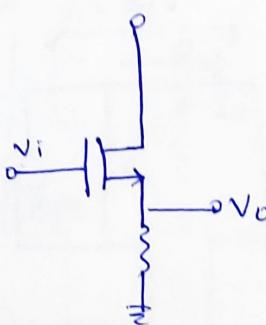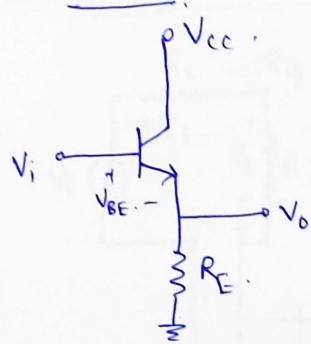

$$A_v = \left(\frac{1}{r_n} + g_m \right) R_E = \frac{R_E}{r_n}$$

$$R_{if} = r_n + (1 + h_{fe}) R_E$$

$$R_{of} = R_E \parallel \frac{r_n}{1 + h_{fe}} = R_E \parallel r_{oE}$$

Q) Determine i/p imp of series i/p connection and o/p imp of a shunt o/p connection for an ideal voltage amp. if $A_v = 10^5$,

$$A_{vf} = 50, R_i = 10 \text{ k}\Omega, R_o = 20 \text{ k}\Omega$$

$$A_{vf} = \frac{A_v}{1 + \beta_v A_v}$$

$$1 + \beta_v A_v = \frac{A_v}{A_{vf}}$$

$$\beta_v = \left(\frac{A_v}{A_{vf}} - 1 \right) \frac{1}{A_{vf}} = \frac{1}{A_{vf}} - \frac{1}{A_v}$$

$$\beta_v = \frac{1}{50} - \frac{1}{10^5} = 0.019$$

$$R_{if} = R_i (1 + \beta_v A_v) = 10 (1 + 0.019 \times 10^5) \times 10^3$$

$$= 19010 \text{ k}\Omega \approx 20 \text{ M}\Omega$$


$$R_{of} = \frac{R_o}{1 + \beta_v A_v} = \frac{20 \times 10^3}{1 + 0.019 \times 10^5} = \frac{20}{2001} \times 10^3 = 0.00999 \times 10^3$$

$$= 9.99 \approx 10 \text{ M}\Omega$$

$$\frac{1}{\beta_v + 1} = \frac{1}{\beta_v A} = \frac{1}{10^5} = 10^{-5}$$

$$\frac{1}{\beta_v + 1} = \frac{1}{\beta_v A} = \frac{1}{10^5} = 10^{-5}$$

Current Amp (Shunt Series)

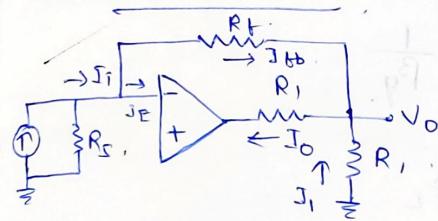

$$V_o = -I_f R_f \\ = -I_i R_f$$

$$I_i = -\frac{V_o}{R_1}$$

$$I_o = I_{fb} + I_i$$

$$I_o = I_i + (-k_t)(-I_i R_f)$$



$$\Rightarrow I_o = I_i \left(1 + \frac{R_f}{R_1}\right)$$

$$\boxed{\frac{I_o}{I_i} = 1 + \frac{R_f}{R_1}}$$

$$A_{if} \approx \frac{1}{\beta_i} = \frac{I_o}{I_i}$$

$$\therefore \beta_i = \frac{1}{1 + \frac{R_f}{R_1}}$$


CB Circuit

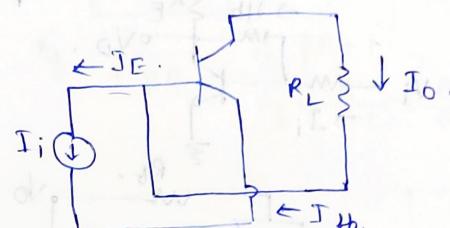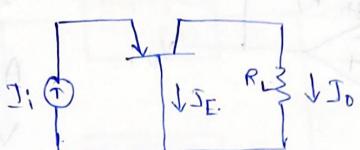


$$A_i = \frac{I_o}{I_i} = h_{fe}$$

$$A_{if} = \frac{h_{fe}}{1 + h_{fe}} = \frac{A_i}{1 + A_i}$$

β_i = unity.

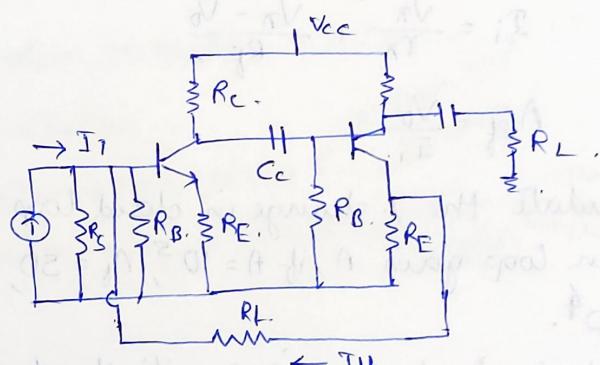

Transconductance Amp :-

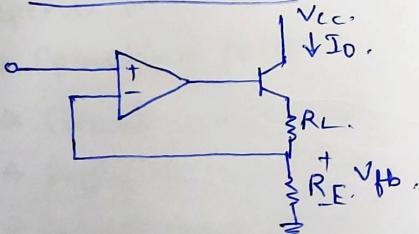

$$A_{gf} = \frac{I_o}{V_i} = \frac{1}{\beta_2}$$

$$V_i = V_{fb} = I_o R_E$$

$$A_{gf} = \frac{I_o}{V_i} = \frac{1}{R_E}$$


$$\beta_2 = R_E$$

$$I_o = (-g_m V_\pi) \left(\frac{R_L}{R_C + R_L} \right)$$


$$V_{fb} = \left(\frac{V_\pi}{R_\pi} + g_m V_\pi \right) R_E$$

$$V_i = V_\pi + V_{fb} = V_\pi \left(1 + \left(\frac{1}{R_\pi} + g_m \right) R_E \right)$$
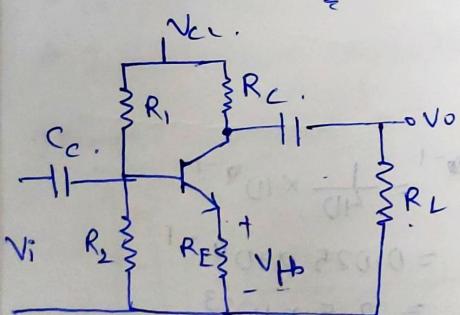
$$A_{gf} = \frac{I_o}{V_i} = \frac{(-g_m V_\pi) \left(\frac{R_L}{R_C + R_L} \right)}{V_\pi \left(1 + \left(\frac{1}{R_\pi} + g_m \right) R_E \right)}$$



Transresistance Amp.


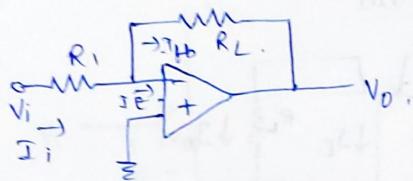


$$A_{2f} = \frac{V_D}{I_i} = \frac{1}{\beta g}$$

$$A_{2f} = -R_L$$

$$V_D = -I_H R_L$$

$$\beta g = -\frac{1}{R_L}$$

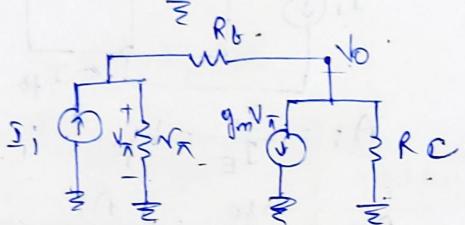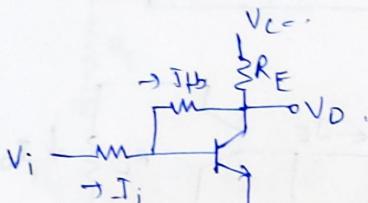

$$\frac{V_D}{R_C} + g_m V_{pi} + \frac{(V_D - V_{pi})}{R_f} = D$$

$$I_i = \frac{V_{pi}}{r_{pi}} + \frac{V_{pi} - V_D}{R_f}$$

$$A_{2f} = \frac{V_D}{I_i}$$

Q) Calculate the % change in closed loop gain A_f , given a change in open loop gain A , if $A = 10^5$, $A_f = 50$, $\beta = 0.01999$, $\alpha = 10^4$, $dA = 10^4$.

Reduction of change in sensitivity of gain

$$\frac{dA_f}{A_f} = ?$$

$$dA_f = A_f \cdot \frac{dA}{A}$$




$$dA_f = \frac{50}{1 + 0.01999 \times 10^5} \cdot \frac{10^4}{10^5}$$

$$dA_f = \frac{50}{1 + 1999} \times 10^{-1} = \frac{50}{2000} \times 10^{-1} = \frac{1}{40} \times 10^{-1} = 0.025 \times 10^{-1} = 2.5 \times 10^{-3}$$

$$\Rightarrow dA_f = 2.5 \times 10^{-3}$$

$$\frac{dA_f}{A_f} = \frac{\left(\frac{1}{40} \times 10^{-1}\right) \left(1 + 1999\right)}{50} = \frac{0.025 \times 10^{-1} \times 2000}{50} = 10^{-4}$$

Oscillators :-

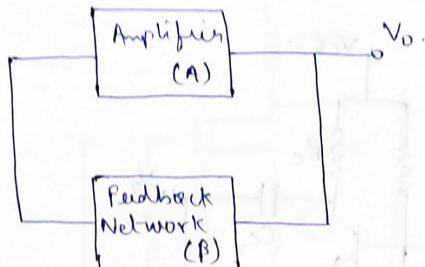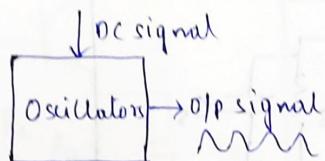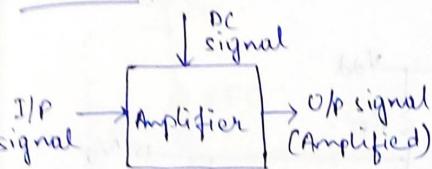

$$\alpha_B = \frac{A}{1 - BA}, \text{ if } BA = 1$$

$$\alpha_B = \frac{A}{1 - 1} = \frac{A}{0} = \infty$$

Condition for oscillation:-

$$BA = 1 \text{ LO}^{\circ}$$

- i) $|BA| \geq 1$
 - ii) $|BA| = 0^{\circ} \text{ or } 360^{\circ}$
- Barkhausen criteria.


Types:-

- i) Sinusoidal or harmonic oscillator.
- ii) Non-sinusoidal or Relaxation oscillator.

According to freq. of oscillation:-

i) Audio frequency oscillator $\rightarrow 20 \text{ Hz} - 20 \text{ KHz}$

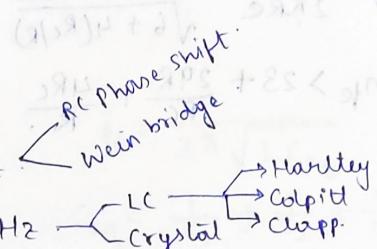ii) Radio frequency oscillator \rightarrow Beyond 20 KHz





Frequency stability :-

Depends on:-


- ★ Operating point.
- ★ Circuit components.
- ★ Supply voltage
- ★ Output load
- ★ Inter-element capacitance and stray capacitance.

ii) Sustained oscillation

→ const amplitude
→ const frequency

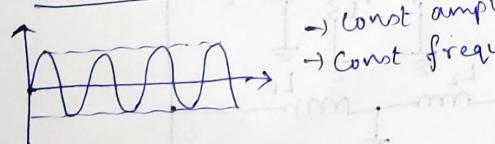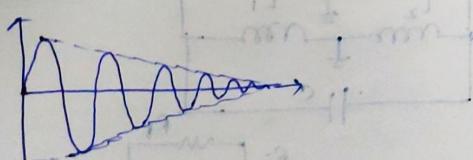

RC Phase Shift Oscillator :-

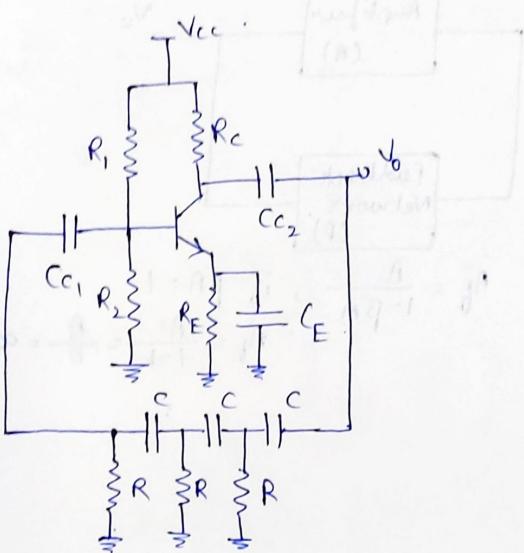


$$\beta = \frac{1}{29}$$

$$A > 29$$

$$f = \frac{1}{2\pi RC} \cdot \frac{1}{\sqrt{6 + 4(R_C/R)}}$$

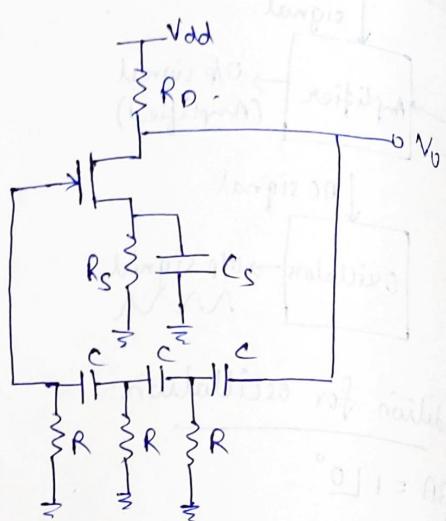
$$h_{fe} > 23 + \frac{29R}{RC} + \frac{4R_C}{R}$$




$$|A| = g_m R_L$$

$$R_L = \frac{R_D r_d}{R_D + r_d}$$

$$f = \frac{1}{2\pi RC \sqrt{6}}$$

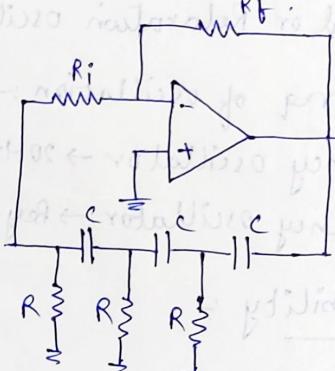

Hartley oscillator :-

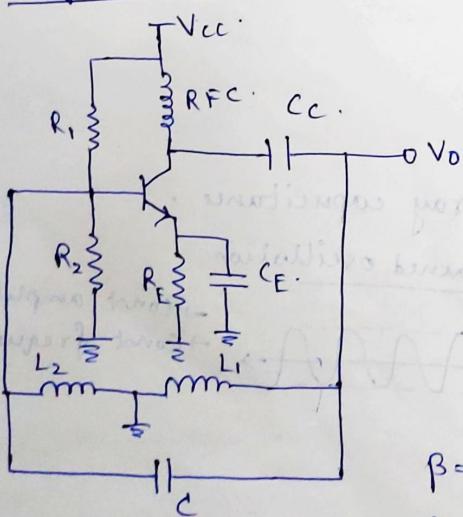



$$L_{eq} = L_1 + L_2 + 2M$$

$$f_0 = \frac{1}{2\pi \sqrt{L_{eq} C}}$$


$$\beta = \frac{L_2}{L_1}$$

$$A = L_1/L_2$$

(M = mutual inductance)

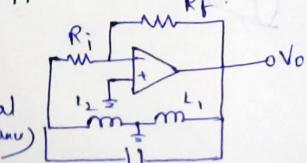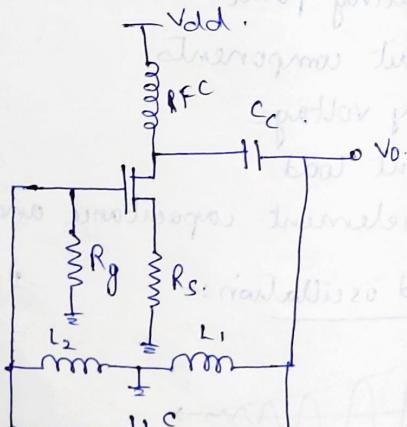



Colpitt oscillator :-

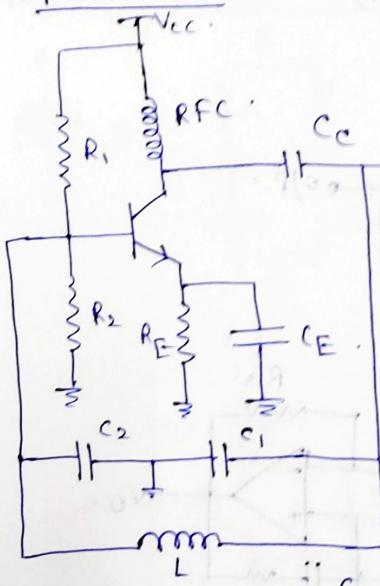


$$\beta = \frac{C_2}{C_1}$$

$$A = \frac{C_1}{C_2}$$

resonant frequency

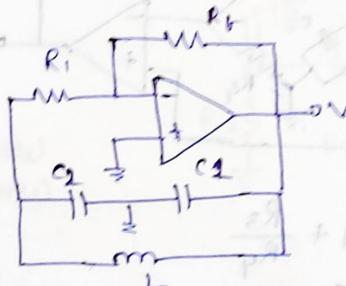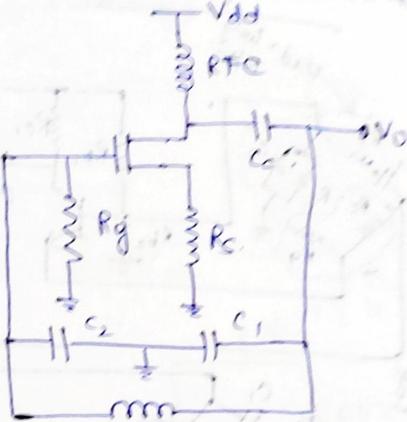

Clapp oscillator

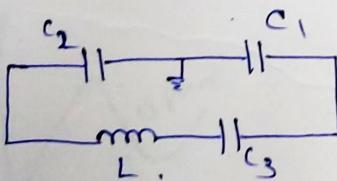

$$\omega_0 = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$\frac{\omega_0^2 + 1}{\omega_0} \cdot C_{eq} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\left(\frac{\omega_0}{2\pi + \omega_0}\right) \left(\frac{\omega_0}{\omega_0}\right) C_3 = \text{small}$$

$$\omega_0 \approx \frac{1}{(\sqrt{LC_3})^{2\pi}}$$

$$\left(\frac{1}{2\pi + \omega_0} + \frac{1}{\omega_0}\right) \left(\frac{\omega_0}{\omega_0} + 1\right) = 1$$

$$\omega_0 = \omega_0 = (2\pi)^2$$

$$1 = \left(\frac{1}{2\pi + \omega_0} + \frac{1}{\omega_0} \right) \left(\frac{\omega_0}{\omega_0} + 1 \right)$$

freq term

$$1 = \left(\frac{1}{2\pi} \right) \left(\frac{\omega_0}{\omega_0} + 1 \right)$$




$$\omega_0 = \frac{\omega_0}{2\pi}$$

$$0 = \frac{1}{2\pi} + 2\pi f_0 \omega_0$$

$$\frac{1}{2\pi} = 2\pi f_0 \omega_0$$

$$f_0 = \frac{1}{2\pi} \cdot \frac{1}{2\pi} = 0.01$$

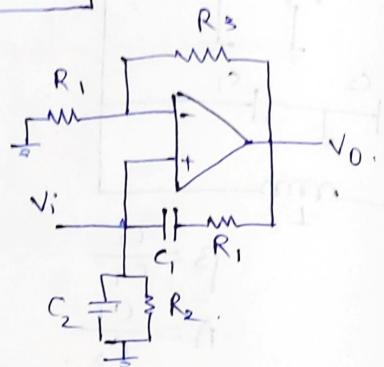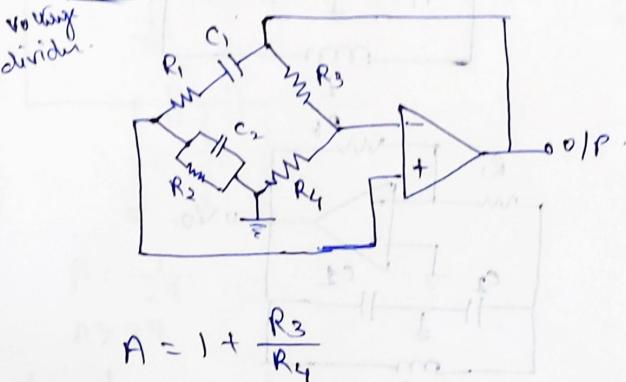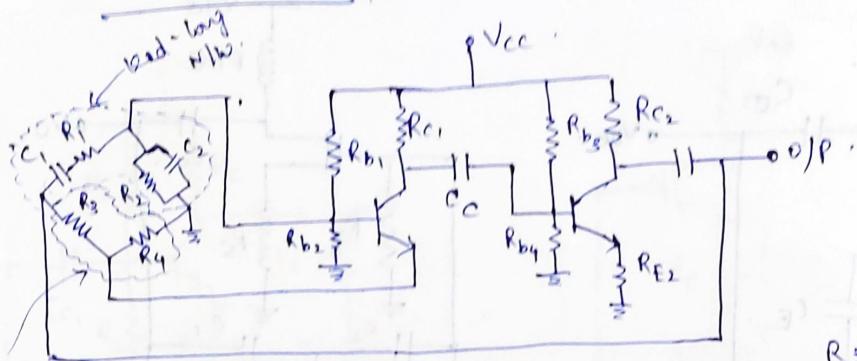Wien Bridge Oscillator :- (20 Hz to 1 MHz)



$$A = 1 + \frac{R_3}{R_4}$$

$$\beta = \frac{2p}{2p + Z_s}$$

$$Z_p = \frac{R_2 \times \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{sR_2C_2 + 1}$$

$$Z_s = R_1 + \frac{1}{sC_1} = \frac{1 + sR_1C_1}{sC_1}$$

$$T(s) = \beta A = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{2p}{2p + Z_s}\right)$$

If $R_1 = R_2 = R$ and $C_1 = C_2 = C$.

$$T(s) = \left(1 + \frac{R_3}{R_4}\right) \left(\frac{1}{3 + sRC + \frac{1}{sRC}}\right)$$

$$T(j\omega_0) = \beta A = 1 \text{ (at resonance)}$$

$$= \left(1 + \frac{R_3}{R_4}\right) \left(\frac{1}{3 + j\omega_0 RC + \frac{1}{j\omega_0 RC}}\right) = 1$$

Imaginary part = 0

$$\therefore j\omega_0 RC + \frac{1}{j\omega_0 RC} = 0$$

$$\therefore \omega_0 = \frac{1}{RC}$$

$$\therefore f_0 = \frac{1}{2\pi RC}$$

Voltage divider





$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$

$$f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$


Real part,
 $\left(1 + \frac{R_3}{R_4}\right)\left(\frac{1}{3}\right) = 1$
 $\therefore \frac{R_3}{R_4} = 2$.

Crystal oscillator (10 KHz to 200 MHz)


(Very high freq. stability)

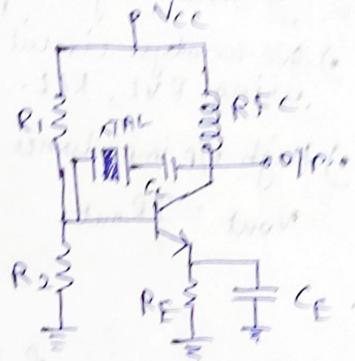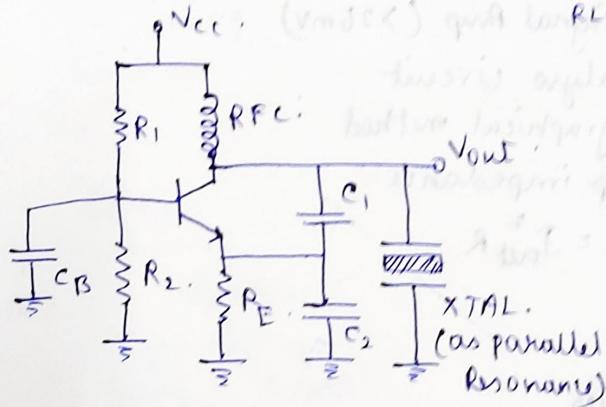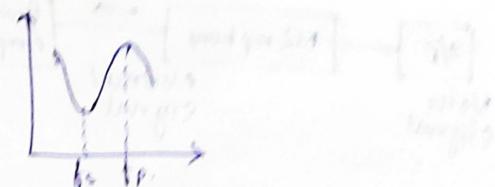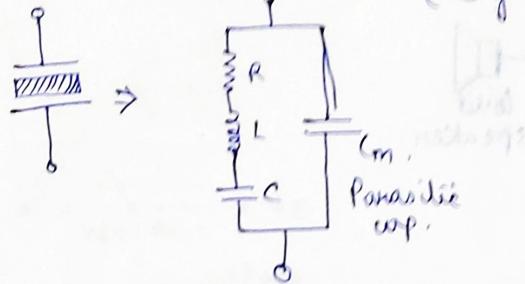

Negative Resistance Oscillator

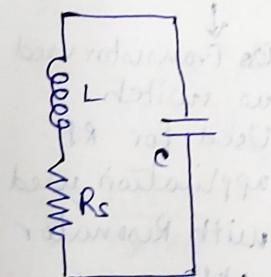


Tunnel diode :

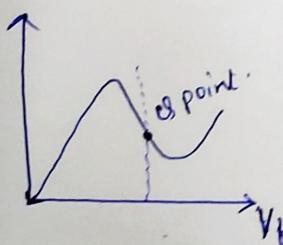

Damped oscillations



Tunnel diode

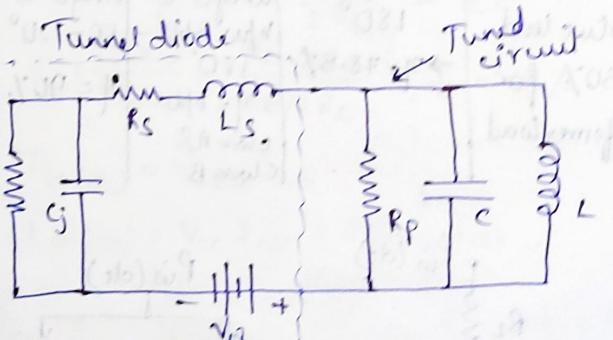

$$R_{eq} = \frac{R_p R_n}{R_p + R_n}$$

if $R_p > R_n$ then, $R_{eq} = -ve$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\frac{(3a)^2}{(3b)^2} = \frac{1}{3}$$