

Output Stages & Power Amplifiers

Power amplifiers :- provide sufficient power to an off load to drive a speaker or other power device.

Features of power amplifiers

- 1) Power efficiency
- 2) Maximum amount of power that the circuit is capable of handling
- 3) Impedance matching to the off device.

* Amplifier classes represent the amount of the off signal varies over one cycle of operation for a full cycle of off voltage.

Class A Power Amplifier

The off signal varies for a full 360° of the cycle. The Q point should be placed such that at least half the signal swing of the off may vary up & down without going to a high voltage enough to be limited by the supply voltage.

Class B Power Amplifier

provides an o/p signal varying over one half the i/p signal cycle or for 180° of the signal.

dc bias point is at 0V.

Class AB

The o/p swing occurs between 180° & 360° , and is neither class A nor class B operation. bias level is above the zero base current level of class B and above one half the supply voltage level of class A.

Class C

biased for operation at less than 180° of the cycle & will operate only with a tuned circuit, which provides a full cycle of operation for the tuned frequency.

Class D :

form of amplifier operation using pulse signals.

Series Fed Class A Amplifier

Fixed bias connection

* I_P is of volts range.



* $\beta = 100$

DC Bias Operation

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

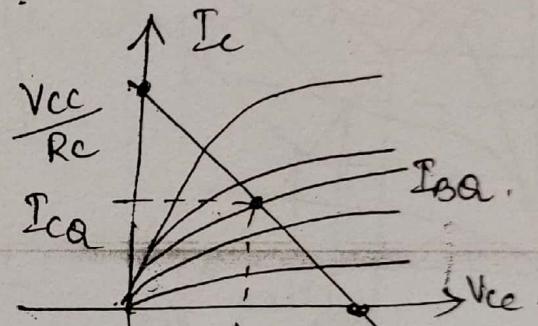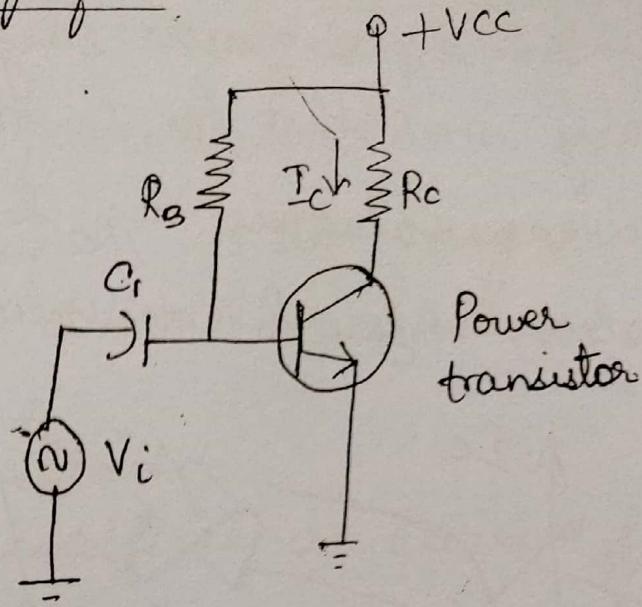

* If I_{cq} is set exactly as half, the maximum O/P swing will be 0 to V_{ce}/R_C , the largest collector current is possible.


* If V_{ce} is also exactly half, the largest voltage swing is possible.

* Q point is set based on this consideration.

AC operation

A small i/p signal will cause the base current to vary above and below the dc bias point, which will cause I_C & V_{CE} to vary around its dc bias value.

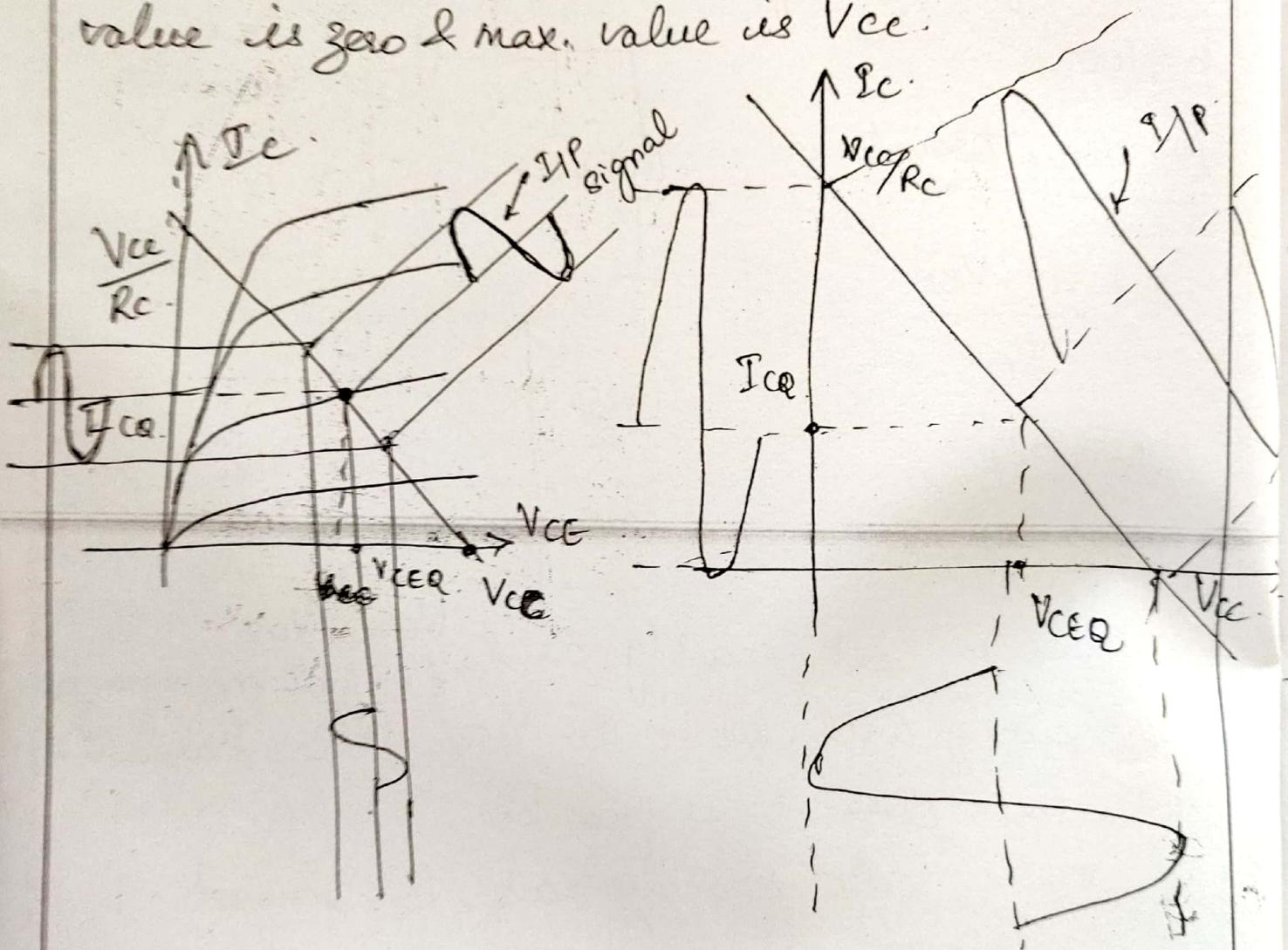As the i_{IP} is made larger, the off well will vary such that for I_C the min value is zero & max value is V_{CC}/R_C & for V_{CE} the minimum value is zero & max. value is V_{CC} .



Power Considerations

DC IP power.

With no i_{IP} signal, the dc current drawn is the collector current I_{CQ} .

$$P_i(\text{dc}) = V_{CC} \times I_{CQ}$$

AC Operation

- * The op voltage & current varying around the bias point provide ac power to load.
- * The ac signal V_i causes I_B to vary around the dc bias current & collector current around I_{CQ} .
- * The ac i/p signal results in ac current & ac voltage signals. The larger the i/p, the larger the op.

AC op power

$$P_{oac} = V_m (\text{rms}) I_m (\text{rms})$$

$$V_m = V_{CE}$$

$$I_m = I_c$$

$$P_{oac} = \frac{V_m}{R_2} \times \frac{I_m}{R_2} = \frac{V_m I_m}{2} = \frac{V_m^2}{2R_c} \text{ or } \frac{I_m^2}{2} R_c$$

$$= \underbrace{\left(\frac{V_{max} - V_{min}}{2} \right)}_{\Delta V} \underbrace{\left(\frac{I_{max} - I_{min}}{2} \right)}_{\Delta I}$$

$$P_{oac} = \frac{V_{pp}}{8} I_{pp}$$

$$P_{oac} = \frac{V_{pp}^2}{8} \left(\frac{V_{pp}}{R_c} \right) = \frac{V_{pp}^2}{8R_c} \text{ or } \frac{I_{pp}^2}{8} R_c$$

$$P_{o(ac)} = \frac{V_m^2}{2R_c} = \frac{V_{pp}^2}{8R_c}$$

Efficiency

$$\% \eta = \frac{P_o(ac)}{P_i(dc)} \times 100 \%$$

Maximum Efficiency

$$P_{o(ac) \text{ Max}} = \frac{V_{cc}^2}{8R_c}$$

$$P_{i(de) \text{ max}} = V_{cc} \times I_{cq} = V_{cc} \times \frac{V_{cc}}{2R_c}$$


$$\therefore \% \eta_{\text{max}} = \frac{\frac{V_{cc}^2}{8R_c} \times 100\%}{\frac{V_{cc}^2}{2R_c}} = \frac{25}{84} \times 100\% = 25\%$$

Transformer Coupled class A Amplifier

4

Transformer action

$N_1 : N_2$

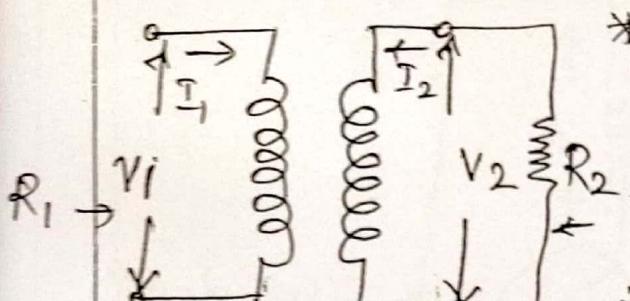

* A transformer can increase or decrease voltage or current levels according to the turns ratio.

* The impedance connected to one side of transformer can be made to appear larger or smaller at the other side of the transformer, depending on the square of the transformer winding turns ratio.

Voltage Transformation

The transformer can step up or down a voltage applied to one side directly as the ratio of the turns on each side. The voltage transformation is given by:

$$\boxed{\frac{V_2}{V_1} = \frac{N_2}{N_1}}$$

$$V_2 = V_1 \times \left(\frac{N_2}{N_1} \right)$$

If $N_2 > N_1$, then $V_2 > V_1$.

Current Transformation

The current transformation ratio:

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$I_2 = I_1 \left(\frac{N_1}{N_2} \right)$$

The current in the secondary ~~side~~ is ^{winding} larger than inversely proportional to the number of turns in the windings.

Impedance Transformation

$$\frac{R_2}{R_1} = \frac{V_2/I_2}{V_1/I_1} = \frac{V_2}{V_1} \times \frac{I_1}{I_2} = \frac{N_2}{N_1} \times \frac{N_2}{N_1}$$


$$\frac{R_2}{R_1} = \frac{N_2^2}{N_1^2} \Rightarrow R_1 = \left(\frac{N_1}{N_2} \right)^2 R_2$$

$$R_2 = \left(\frac{N_2}{N_1} \right)^2 R_1 = \alpha^2 R_1$$

The reflected impedance is related directly to the square of turns ratio.

If $N_2 > N_1$ then $R_2 > R_1$

Transformer Coupled class A Amplifier

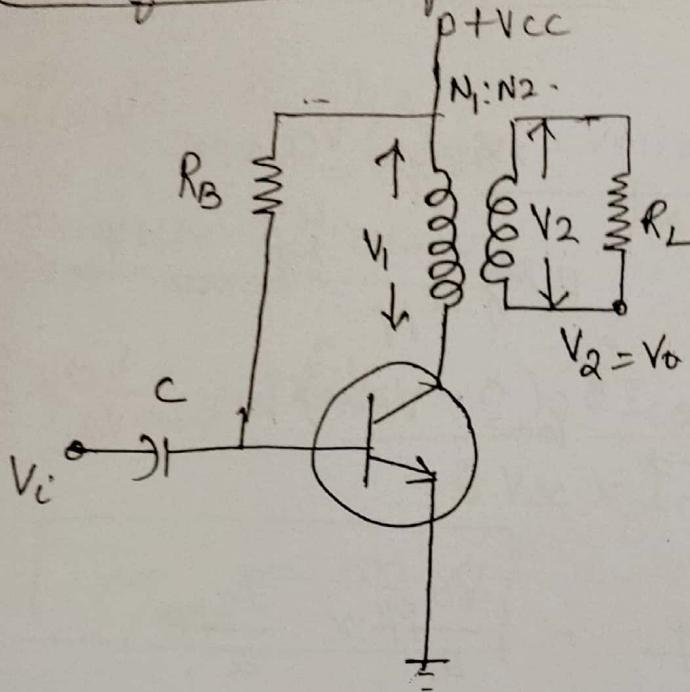

dc load line


Transformer dc

winding determines
the dc load line.

$$V_{CEQ} = V_{CC}$$

Q-point

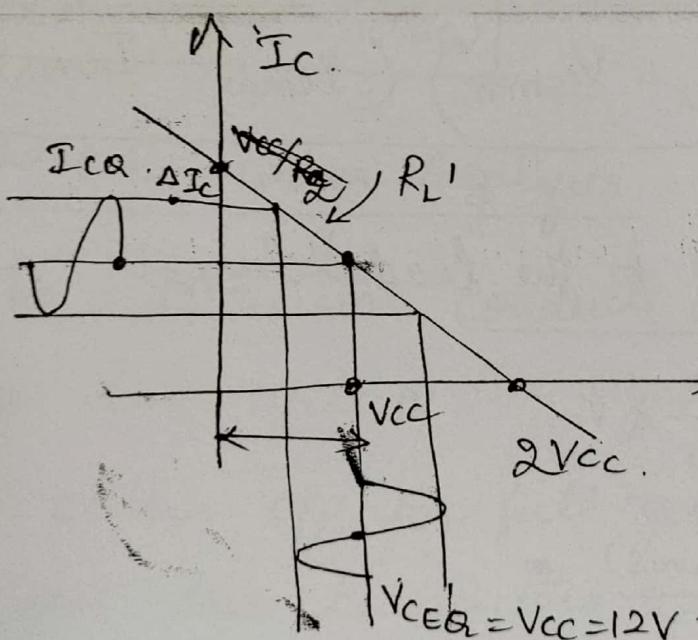
Intersection of
dc load line
with \$I_B\$.



Ac load line

Draw the ac load line on O/P characteristics.
The slope is $-\frac{1}{R_L}$. The O/P swing can exceed
 V_{CC} .

Signal swing & O/P AC power.

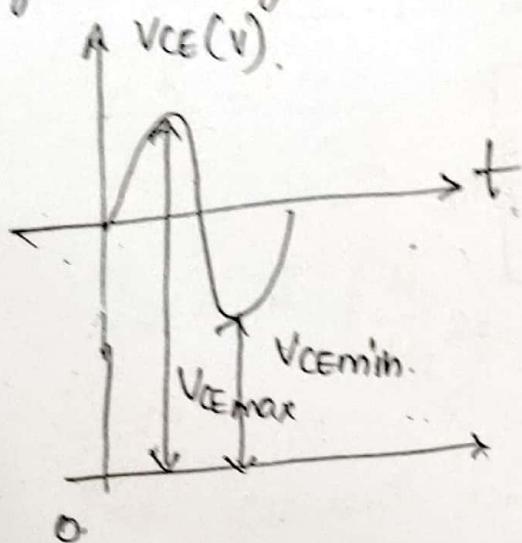

$$V_{CEpp} = V_{CEmax} - V_{CEmin}$$

$$\text{Similarly } I_{Cpp} = I_{Cmax} - I_{Cmin}$$

$$P_{ac} = V_{rms} \times I_{rms} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$

$$P_{oac} = \frac{\frac{V_{CEpp} I_{Cpp}}{2}}{2} = \frac{\frac{V_{CEpp}}{2} \times \frac{I_{Cpp}}{2}}{2}$$

$$= \frac{(V_{CEmax} - V_{CEmin})(I_{Cmax} - I_{Cmin})}{8}$$

Voltage delivered to the load. & Current

$$V_L = V_2 = \frac{N_2}{N_1} \times V_1$$

$$P_L = \frac{V_L^2 (\text{rms})}{R_L}$$

$$I_L = \frac{\cancel{V_L (\text{rms})^2}}{R_L} \left(\frac{N_1}{N_2} \right) I_1$$

$$\therefore P_L = I_L^2 (\text{rms}) \times R_L$$

Efficiency

$$P_{dc} = V_{cc} \times I_{cq}$$

$$\therefore \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8 V_{cc} I_{cq}}$$

Maximum Efficiency

$$\eta_{max} = \frac{(2V_{cc} - 0)(2I_{cq} - 0)}{8 V_{cc} \times I_{cq}} = \frac{(2 \times 15)(2 \times 15)}{8 \times 15}$$

$$\boxed{\eta_{max} = 50\%}$$

$$\boxed{P_o = P_{dc(d)} - P_{o(ac)}}$$

Class B Power Amplifier


- * The transistor conducts current only for one half cycle of the signal cycle.
- * To obtain OIP for full cycle, it is necessary to use two transistors & have each conduct on opposite half cycles, the combined operation providing a full cycle of OIP signal.

Push-pull circuit: one part of circuit pushes high & other part pulls low.

Block Representation of push pull circuit

Operation

Connection of push p
to load

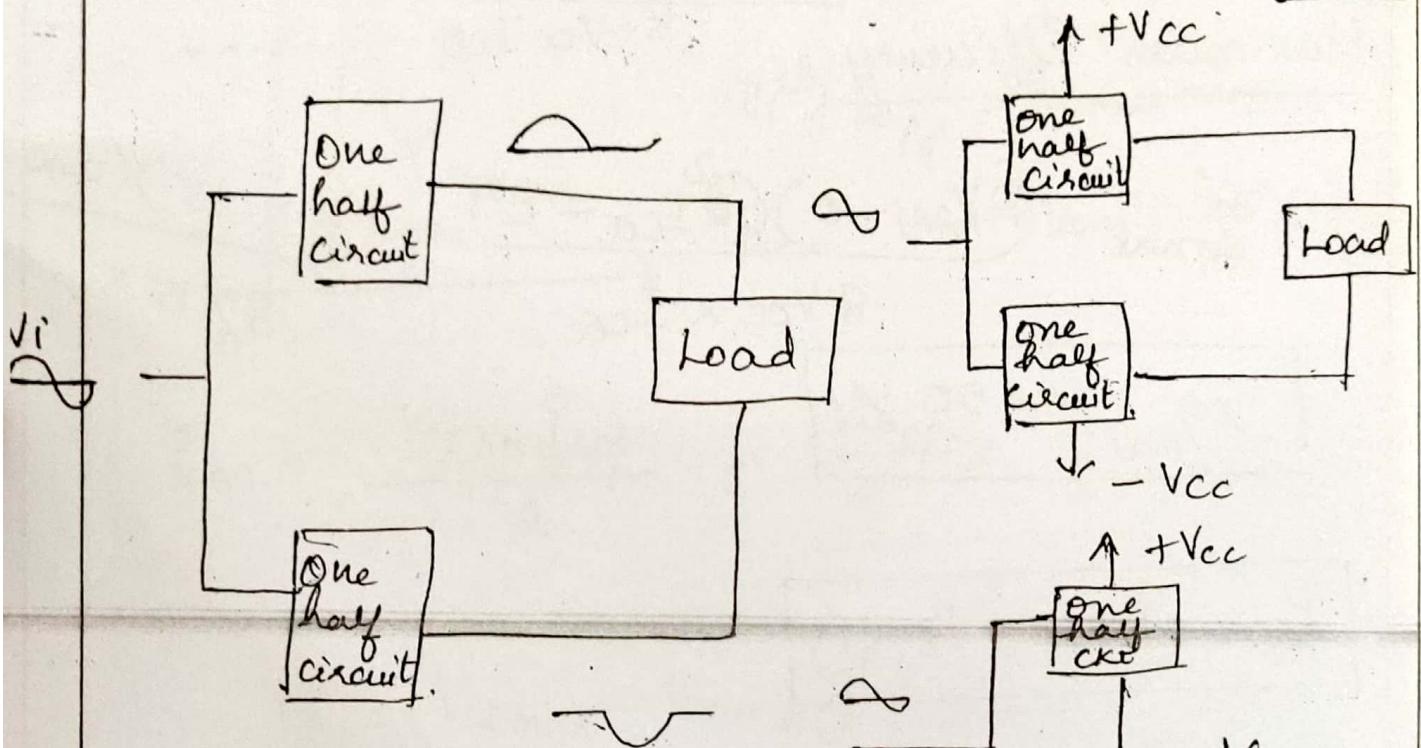

- * Class B Operation provides greater efficiency than was possible using a single transistor + class A operation

Input (DC) power

$$P_{i(de)} = V_{cc} I_{dc}$$

$I_{dc} \rightarrow$ average DC current drawn from the power supplies.

- * Current drawn from single power supply is in the form of a full wave rectified signal

whereas that drawn from two power supplies has the form of a half wave rectified signal from each supply.

$$I_{dc} = \frac{I_m}{\pi} + \frac{I_m}{\pi} = \frac{2I_m}{\pi}$$

$I_m \rightarrow$ peak value of O/p current.

$$P_{dc} = V_{cc} \left(\frac{2I_m}{\pi} \right)$$

O/p AC Power

The power delivered to the load can be calculated by using an rms meter to measure the voltage across the load

$$P_o(ac) = \frac{V_L^2(\text{rms})}{R_L}$$

$$V_L(\text{rms}) = \frac{V_L}{\sqrt{2}}$$

$$V_L = \frac{V_{pp}}{2}$$

$$\therefore P_o(ac) = \frac{V_L^2}{2R_L}$$

$$V_L \text{rms} = \frac{V_{pp}}{2\sqrt{2}}$$

$$V_L^2 \text{rms} = \frac{V_{pp}^2}{8}$$

Efficiency

$$\% \eta = \frac{P_o(ac)}{P_{dc}} \times 100 = \frac{V_L^2 / 2R_L}{V_{cc} \left(\frac{2I_m}{\pi} \right)} = \frac{V_L^2 / 2R_L}{V_{cc} \left(\frac{2}{\pi} \times \frac{V_L}{\sqrt{2}} \right)}$$

$$I_m = \frac{V_L}{\sqrt{2}}$$

SRM

$$\times \eta = \frac{\pi}{4} \times \frac{V_L}{V_{CC}} \times 100\%$$

Maximum Efficiency $V_L = V_{CC}$

$$\text{Maximum Efficiency} = \frac{\pi}{2} \times \frac{V_{CC}}{V_{CC}} \times 100\%$$

$$\times \eta_{max} = \frac{\pi}{4} \times 100\% = 78.5\%$$


Power dissipated by Q1P Transistors

$$P_{2Q} = P_i(dc) - P_o(ac)$$


$$P_Q = \frac{P_{2Q}}{2}$$

Class B Amplifier Circuits

Transformer Coupled Push Pull Circuit

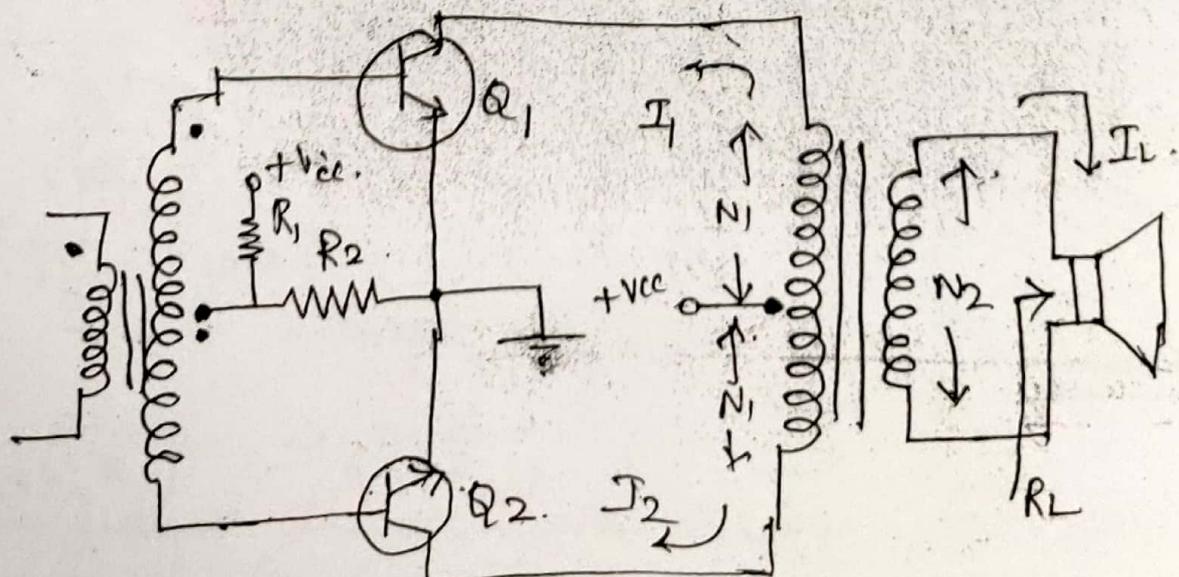

Circuit Diagram:

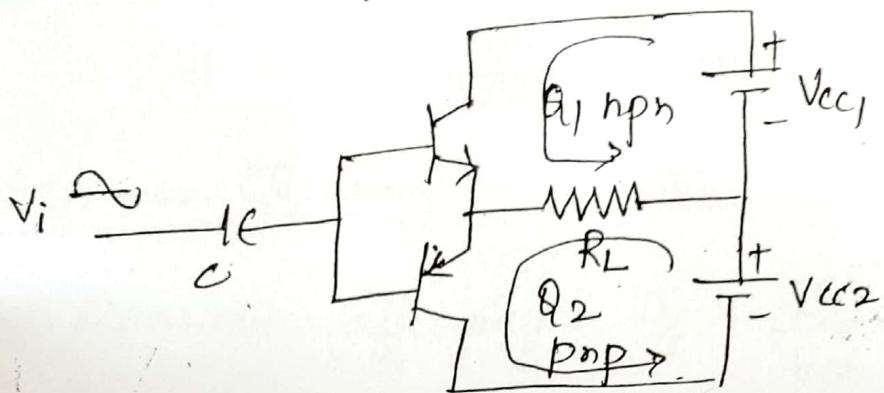

* The n-p-n (Q_1) will be biased into conduction during the positive half cycle of the i/p resulting in a half cycle of signal across the load.

* During negative half cycle of signal, the p-n-p transistor is biased into conduction.


During a complete i/p cycle, a complete off cycle appears across the load.

Disadvantage:

need for two power supply.

Crossover distortion :-

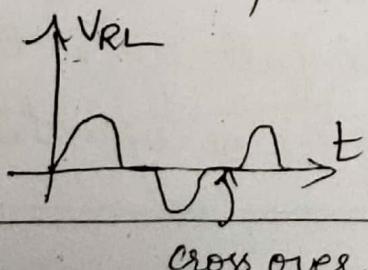During the signal cross over from positive to negative there is some non-linearity in the o/p signal. This is because the circuit does not provide exact switching.



Class AB will eliminate this distortion.

Amplifier Distortion

* A pure sinusoidal signal has a single frequency at which the voltage varies positive & negative by equal amounts. Any signal varying over less than 360° cycle is considered to have distortion.

Reasons for distortion

- * Device characteristics not linear \rightarrow amplitude distortion
- * Circuit elements & devices respond to the input signal differently at various frequencies \rightarrow frequency distortion

Fourier Analysis

- * Technique for describing distortion.
- * Any periodic waveform is described in terms of fundamental frequencies & higher frequency components at integer multiples.
 - 1kHz signal \rightarrow OIP 1kHz \rightarrow fundamental frequency
 - 2kHz \rightarrow 2nd harmonic
 - 3kHz \rightarrow 3rd harmonic.

Harmonic Distortion

A signal is considered to have harmonic distortion if there are harmonic frequency components.

$$\% \text{ nth harmonic distortion} = \% D_n = \frac{|A_n|}{|A_1|} \times 100\%$$

$A_1 \rightarrow$ amplitude of fundamental frequency

$A_n \rightarrow$ amplitude of n^{th} frequency component.


$$A_1 > A_n.$$

Second Harmonic Distortion

Consider a distorted signal waveform

$$i_c \approx I_{CQ} + I_0 + I_1 \cos \omega t + I_2 \cos 2\omega t.$$

At 1 :- $\omega t = 0$.

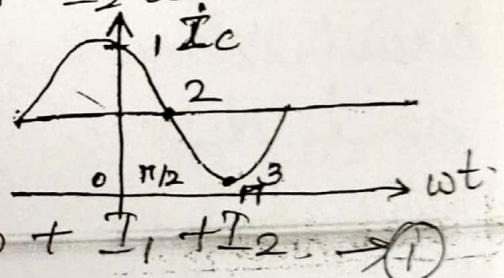

∴ $i_c = I_{C\max} = I_{CQ} + I_0 + I_1 + I_2 \rightarrow ①$

At 2 $\omega t = \pi/2$.

$$i_c = I_{CQ} = I_{CQ} + I_0 + I_1 \cos \pi/2 + I_2 \cos 2\pi/2$$

$$I_{CQ} = I_{CQ} + I_0 - I_2. \rightarrow ②$$

At 3 $\omega t = \pi$.

$$i_c = I_{C\min} = I_{CQ} + I_0 - I_1 + I_2. \rightarrow ③$$

Solving ①, ② & ③.

$$I_0 = I_2 = \frac{I_{C\max} + I_{C\min} - 2I_{CQ}}{2}$$

4.

$$I_1 = \frac{I_{C\max} - I_{C\min}}{2}$$

2nd Harmonic Distortion :-

40

$$D_2 = \left| \frac{\frac{I_2}{I_1}}{\frac{\frac{1}{2}(I_{C\max} + I_{C\min}) - I_{CQ}}{I_{C\max} - I_{C\min}}} \right| \times 100\%$$

Similarly D_2 in terms of voltage

$$D_2 = \left| \frac{\frac{1}{2}(V_{CE\max} + V_{CE\min}) - V_{CEQ}}{V_{CE\max} - V_{CE\min}} \right| \times 100\%$$

Power of a signal having distortion

$$P_1 = \frac{I_1^2 R_C}{2} \quad \therefore THD = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$$


$$P = \left(I_1^2 + I_2^2 + I_3^2 + \dots \right) \frac{R_C}{2}$$

$$P = (1 + D_2^2 + D_3^2 + \dots) I_1^2 \frac{R_C}{2} = (1 + THD^2) P_1$$


Class-C Amplifier

total harmonic distortion.

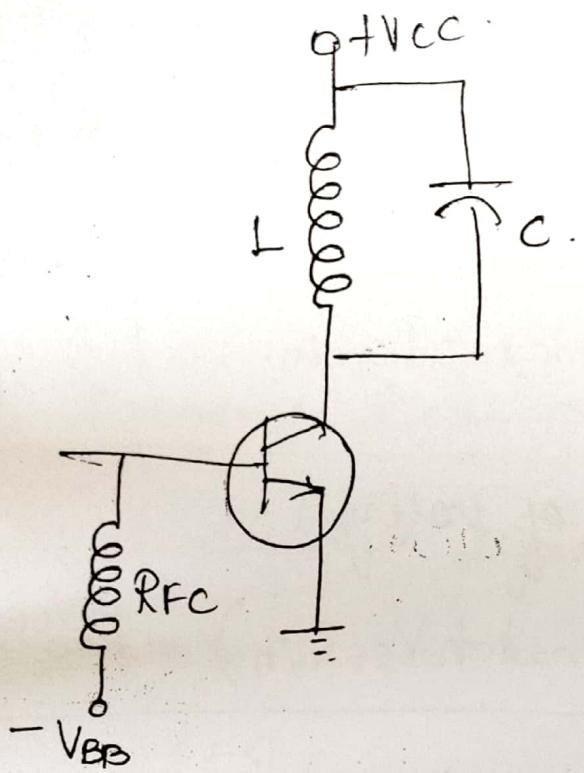- * biased to operate for less than 180° but LC provides full Q.F.



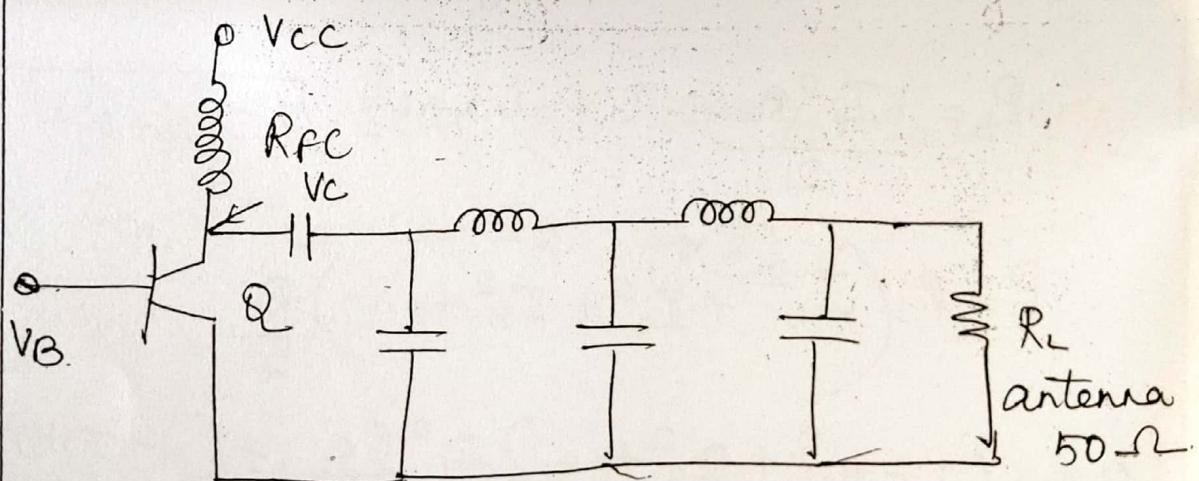Class D Amplifier - Schematic diagram of
Class C Amplifier



Operation : When the i/p voltage is positive and above the cut-in voltage of the transistor, the transistor operates in the saturation region.

In this region, the o/p is proportional to the saturation voltage of Q. ~~and remains~~

When $\theta_{\text{Q2}} \rightarrow \text{off}$ $V_c(t) = V_{cc}$.

\therefore From ① $\Rightarrow V_{cc} = V_{cesat} + V_{dc}$ of $V_m \cos \omega t$.

$$V_{dc} = V_{cesat} + \frac{V_m}{\pi}$$

$$\therefore V_m = \pi (V_{cc} - V_{cesat}).$$

DC Power

$$P_{dc} = V_{cc} \times I_{dc}.$$

$I_{dc} \rightarrow$ average value of supply current.

The same average current flows through the transistor when it is in saturation region.

$$P_d = V_{cesat} I_{dc}.$$

\uparrow
Power dissipated

The remaining power must appear as useful ac power across load


$$\therefore P_{ac} = P_{dc} - P_d = V_{cc} I_{dc} - V_{cesat} I_{dc} = I_{dc} (V_{cc} - V_{cesat})$$

$$\therefore \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{I_{dc} (V_{cc} - V_{cesat})}{V_{cc} I_{dc}} \times 100 =$$

$$\therefore \eta = \left(1 - \frac{V_{cesat}}{V_{cc}}\right) \times 100 \quad \underline{\text{Note}} \quad V_{cesat} \ll V_{cc}$$



$$\therefore \eta > 90\%$$

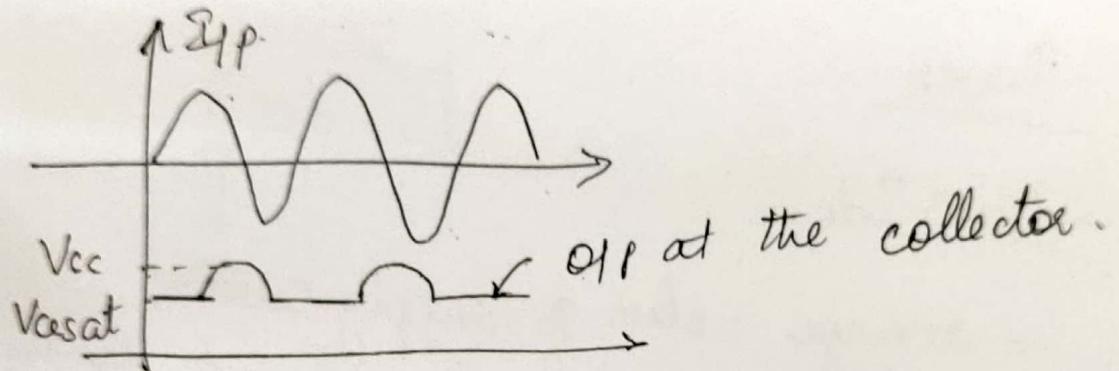constant. As long as the i/p voltage is ~~more~~
less than the cut-in voltage, the transistor
remains off, while the induced emf in
the inductor provides the collector current
as shown below



Efficiency of class-C Amplifier

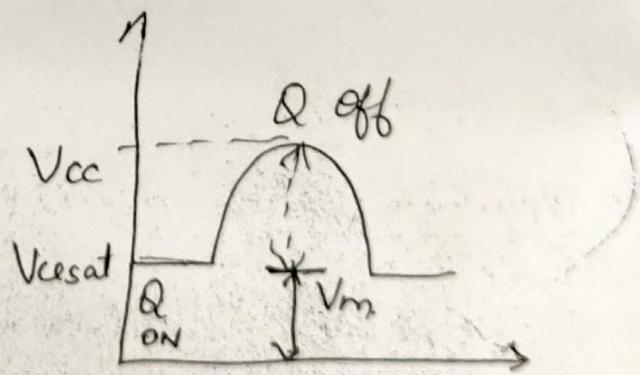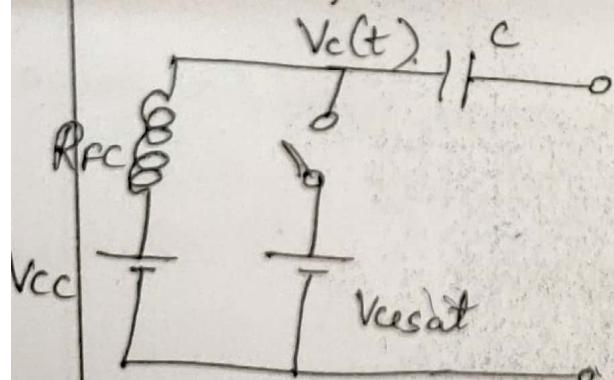The class-C amplifier can be modeled as
shown below.



Collector voltage when α is off

$$V_c(t) = V_{cesat} + V_m \cos \omega t \rightarrow ①$$


When transistor is ON

$$V_c(t) = V_{cesat}$$

The dc resistance of the coil is zero

& the time average value of $V_c(t)$ is zero.

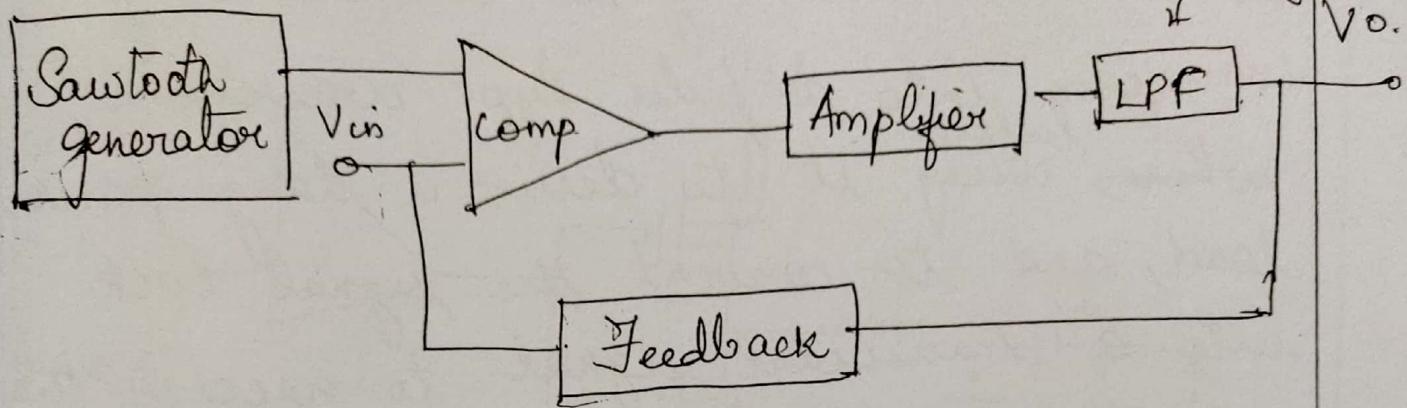amplifier (i.e.) the unit required to amplify the digital signal & then convert it back into a sinusoidal signal using a LPF.



operation of class - D amplifier

There are 3 stages of operation:

- ① Generation of pulses
- ② Modulation
- ③ Filtering

Generation of pulses:


The first stage has a comparator which has 2 i/p's.

- ① triangular wave signal
- ② audio sinusoidal i/p signal

The O/P of comparator is rectangular pulses with duty cycle according to the input sinusoidal signal.

Class D Power Amplifier

- * Class D power amplifier is designed to operate with digital or pulse type signal.
- * It becomes necessary to convert any waveform into a pulse type waveform ^{before} using it to derive a large power load, and to convert the signal back into a sinusoidal signal to recover the original signal.
- * Following figure shows a sinusoidal signal that is to be converted into a pulse type signal using some form of sawtooth or Chopping waveform.

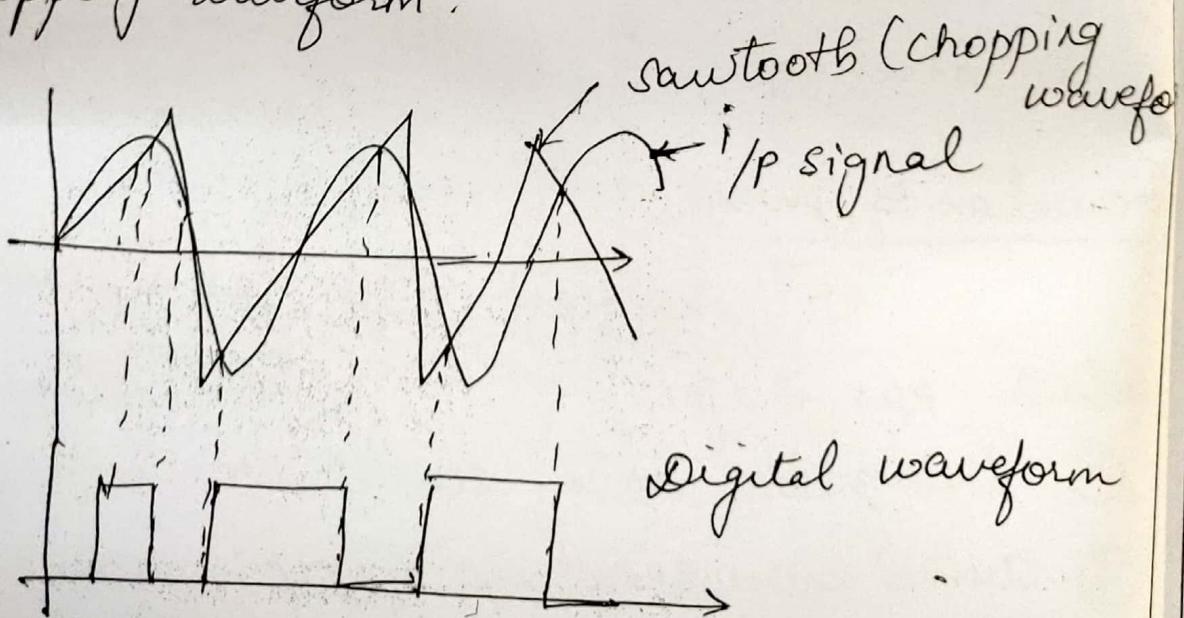


Block diagram of class D amplifier

Following shows the block diagram of class D

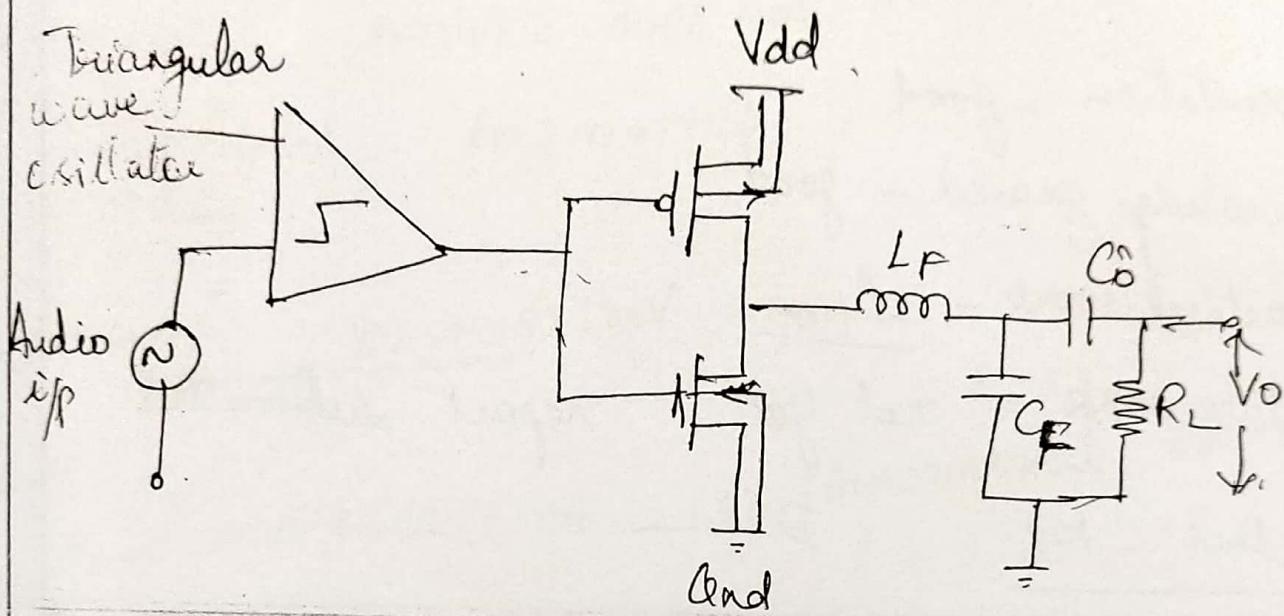(13).

The comparator should be fast so that it can respond to high frequency triangular waves.



Modulation :-

Second stage consists of a complementary pair of a p-channel & an n-channel device in push pull configuration.

Filtering

Since the harmonics have a frequency higher than the fundamental frequency, it is easy to remove these by passing this off to a low pass filter.

Industrial training BSNL

① 206 - Syed Imran Hazuri

presentation - good

knowledge gained - good

practical work - l/w

future work - not yet report submitted

② Pundhri - 198 BSNL

presentation - slide preparation - poor

↪ okay → reading from slide

knowledge gained - nothing okay

future work → nothing

report - submitted

③ 186 - P. C. Pawan - BHEL - Electronic Components

presentation - good.

knowledge gained - good

practical work - okay

future work - nothing

report - submitted

some

project related

some

Q1 & Q2

to do

Coffee break

SR

Note:

1. Fundamental Frequency is not considered a harmonic
2. Fourier Analysis does not allow for fractional harmonics.

HARMONIC DISTORTION

Let $A_1 \rightarrow$ Amplitude of fundamental frequency

$A_n \rightarrow$ Amp. of n^{th} harmonic

then a harmonic distortion can be defined

$$\% \text{ } n^{\text{th}} \text{ harmonic distortion} = \% D_n = \frac{|A_n|}{|A_1|} \times 100\%$$

PROBLEMS

calculate the harmonic distortion components for an output signal having fundamental amplitude of 2.5V, second harmonic amp. of 0.25V, third har. amp. of 0.1V and fourth harmonic amp. of 0.05V.

AMPLIFIER DISTORTION

- * Any signal varying over less than the full cycle (360°) is considered to have distortion.
- * Distortion can occur because the device characteristic is not linear.
- * One technique for describing distortion period waveforms uses Fourier Analysis.

FOURIER ANALYSIS:

- * A method that describes any periodic waveform in terms of its fundamental frequency component and harmonics (freq. components at integer multiples)

* For example,

$$f_0 = 1\text{ KHz}$$

Let,

then

2 KHz = second harmonic

3 KHz = third harmonic

... and so on.

SOLUTION

given $A_1 = 2.5V$ $A_2 = 0.25V$ $A_3 = 0.1V$ $A_4 = 0.05V$

$$\% D_2 = \frac{|A_2|}{|A_1|} \times 100\% = \frac{0.25}{2.5} \times 100\% = 10\%$$

$$\% D_3 = \frac{|A_3|}{|A_1|} \times 100\% = \frac{0.1}{2.5} \times 100\% = 4\%$$

$$\% D_4 = \frac{|A_4|}{|A_1|} \times 100\% = \frac{0.05}{2.5} \times 100\% = 2\%$$

Total Harmonic Distortion (THD)


$$\% THD = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$$

calculate THD for the above problem.

$$\begin{aligned} \% THD &= \sqrt{D_2^2 + D_3^2 + D_4^2} \times 100\% \\ &= \sqrt{(0.1)^2 + (0.04)^2 + (0.02)^2} \times 100\% \end{aligned}$$

$$\left\{ \% THD = 10.95\% \right\}$$

Second Harmonic Distortion

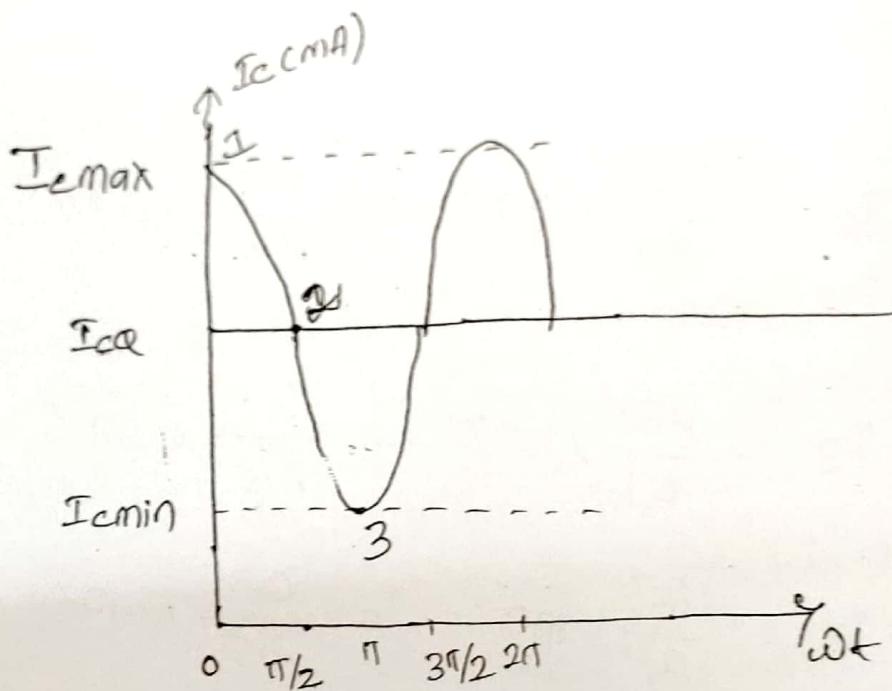

* Above figure is used to obtain second harmonic distortion. A collector current waveform is shown with the quiescent, minimum and maximum signal levels.

An equation that approximately describes the distorted signal waveform is

$$i_c \approx I_{cq} + I_0 + I_1 \cos \omega t + I_2 \cos 2\omega t$$

where

I_{cq} - original quiescent current

I_0 - additional dc current

I_1 - fundamental component of the distortion signal

I_2 - second harmonic component at twice the fundamental freq

At Point 1; $\omega t = 0$, $i_c = I_{c\max}$

$$\therefore \textcircled{1} \Rightarrow I_{c\max} = I_{c\emptyset} + I_0 + I_1 \cos 0 + I_2 \cos 0$$

$$I_{c\max} = I_{c\emptyset} + I_0 + I_1 + I_2 \dots \textcircled{2}$$

At Point 2: $\omega t = \pi/2$, $i_c = I_{c\emptyset}$

$$\textcircled{1} \Rightarrow I_{c\emptyset} = I_{c\emptyset} + I_0 + I_1 \cos \pi/2 + I_2 \cos \pi$$

$$I_{c\emptyset} = I_{c\emptyset} + I_0 - I_2 \dots \textcircled{3}$$

At Point 3: $\omega t = \pi$, $i_c = I_{c\min}$

$$\textcircled{1} \Rightarrow I_{c\min} = I_{c\emptyset} + I_0 + I_1 \cos \pi + I_2 \cos 2\pi$$

$$I_{c\min} = I_{c\emptyset} + I_0 - I_1 + I_2 \dots \textcircled{4}$$

To find I_1 and I_2

$$\textcircled{3} \Rightarrow I_{c\emptyset} = I_{c\emptyset} + I_0 - I_2$$

$$\therefore I_0 = I_2 \dots \textcircled{5}$$

$$\text{Sub } \textcircled{5} \text{ in } \textcircled{2} \Rightarrow I_{c\max} = I_{c\emptyset} + I_1 + 2I_2 \dots \textcircled{6}$$

$$\text{Sub } \textcircled{5} \text{ in } \textcircled{4} \Rightarrow I_{c\min} = I_{c\emptyset} - I_1 + 2I_2 \dots \textcircled{7}$$

$$\textcircled{6} + \textcircled{7} \Rightarrow I_{c\max} + I_{c\min} = 2I_{c\emptyset} + 4I_2$$

$$\therefore I_0 = I_2 = \frac{I_{C\max} + I_{C\min} - 2I_{C\alpha}}{4} \quad \text{--- (8)}$$

$$6 - 7 \Rightarrow I_1 = \frac{I_{C\max} + I_{C\min}}{2} \quad \text{--- (9)}$$

w.k.t $\Rightarrow D_2 = \frac{|I_2|}{|I_1|} \times 100\%$

$$D_2 = \left| \frac{\frac{I_{C\max} + I_{C\min} - 2I_{C\alpha}}{4}}{\frac{I_{C\max} + I_{C\min}}{2}} \right| \times 100\%$$

In a similar manner the second harmonic distortion can be expressed ^{intern} of collector-emitter voltages:

$$D_2 = \left| \frac{\frac{V_{CE\max} + V_{CE\min} - 2V_{CE\alpha}}{4}}{\frac{V_{CE\max} + V_{CE\min}}{2}} \right| \times 100\%$$

PROBLEMS

An output waveform displayed on CRO provides the following measurements:

$$① V_{CE\min} = 1V \quad V_{CE\max} = 22V, \quad V_{CEO} = 12V$$

$$② V_{CE\min} = 4V \quad V_{CE\max} = 20V \quad V_{CEO} = 12V$$

Solution

$$① D_2 = \left| \frac{\frac{(1+22)-24}{4}}{\frac{1+22}{2}} \right| \times 100\%$$

$$= \left| \frac{-1/4}{23/2} \right| \times 100\%$$

$$\left\{ \begin{array}{l} D_2 = 2.17\% \end{array} \right.$$

$$② D_2 = \left| \frac{\frac{(4+20)-24}{4}}{\frac{4+20}{2}} \right| \times 100\%$$

$$= \left| \frac{0}{12} \right| \times 100\%$$

$$\left\{ \begin{array}{l} D_2 = 0\% \end{array} \right. \text{ (No Distortion)}$$

Power of Signal Having Distortion

When distortion is present, the output power delivered to the load resistor R_C due to the fundamental component of the distorted signal is

$$P_1 = \frac{I_1^2 R_C}{2} \quad \left(\begin{array}{l} \text{fund. current} = I_1 \\ \therefore \text{RMS} = (I_1) \end{array} \right)$$

The total power due to all the harmonic components of the distorted signal is,

$$P = \left(I_1^2 + I_2^2 + I_3^2 + \dots \right) \frac{R_C}{2}$$

$$P = I_1^2 \left(1 + \frac{I_2^2}{I_1^2} + \frac{I_3^2}{I_1^2} + \dots \right) \frac{R_C}{2}$$

$$P = I_1^2 \left(1 + D_2^2 + D_3^2 + \dots \right) \frac{R_C}{2}$$

$$= (1 + \tau_{HD}^2) \frac{I_1^2 R_C}{2} \quad \left(\because \tau_{HD} = \sqrt{D_2^2 + D_3^2 + \dots} \right)$$

$$\left\{ P = (1 + \tau_{HD}^2) P_1 \right\} \quad \left(\because \frac{I_1^2 R_C}{2} = P_1 \right)$$

PROBLEM 8

① For harmonic distortion reading of
 $D_2 = 0.1$ $D_3 = 0.02$ $D_4 = 0.01$ with $I_f = 4A$ and
 $R_c = 8\Omega$. calculate the total harmonic distortion, fundamental power component and total power.

SOLUTION

$$\begin{aligned} \text{Y.THD} &= \sqrt{D_2^2 + D_3^2 + D_4^2} \times 100\% \\ &= \sqrt{0.1^2 + 0.02^2 + 0.01^2} \times 100\% \\ \left\{ \text{Y.THD} &= 10.2\% \right\} \end{aligned}$$

To find P_f





$$\begin{aligned} \text{Fundamental Power Component} &= \frac{I_f^2 R_c}{2} \\ &= \frac{4^2 \times 8}{2} \\ \left\{ P_f &= 64W \right\} \end{aligned}$$

To find Total Power


$$\begin{aligned} P &= (1 + THD^2) P_f \\ &= (1 + 0.1^2) 64W \\ \left\{ P &= 64.64W \right\} \end{aligned}$$

Graphical Description of Harmonic Components of

Distorted signal

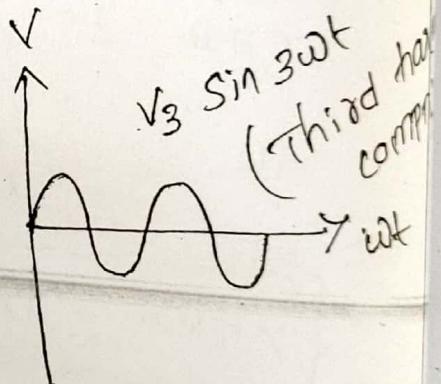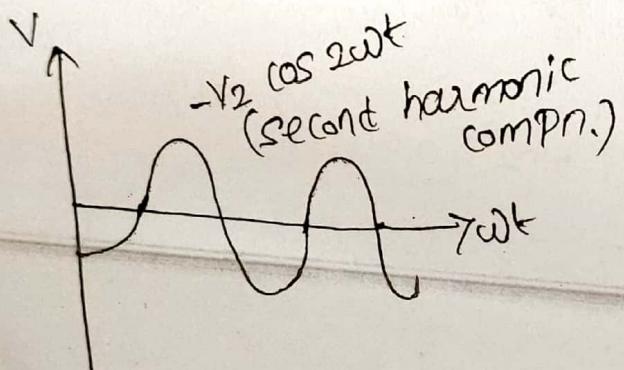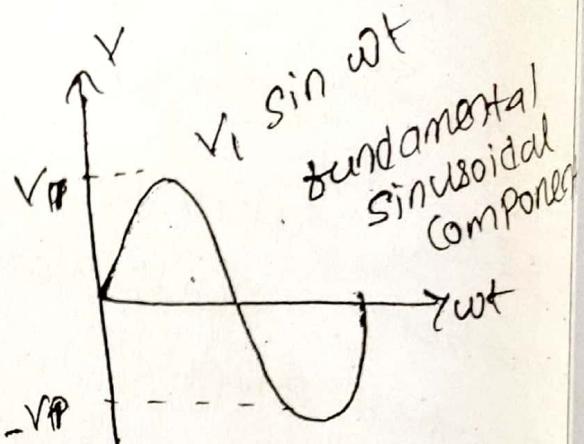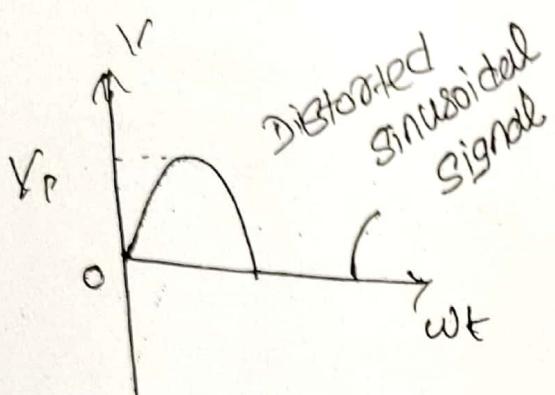

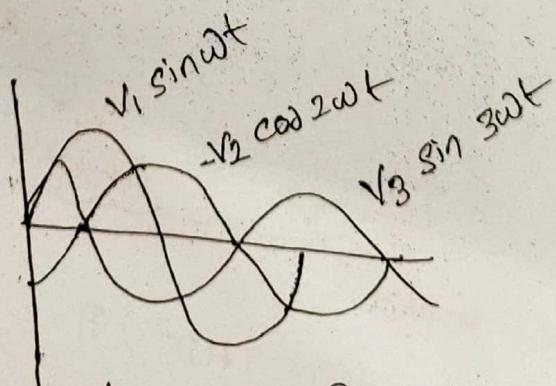Using Fourier technique, the distorted waveform can be made by adding the fundamental and harmonic components as shown below:



Note: In general, any periodic distorted wave can be represented by adding a fundamental component and all harmonic components, each of varying amplitude and at various phase angles.