

# Analog Electronics

## ① DC Analysis of BJT Amplifiers:-

Bjt  $\rightarrow$  current-controlled device.

CE = Emitter Common (Amplifiers).

CB = Base Common.

CC = Collector Common.

Inverse Active

-  $V_{BE}$

No current

(cut off)


$V_{BC}$

Saturation  
(More I)

$V_{BE}$

Active  
(forward)

-  $V_{BC}$

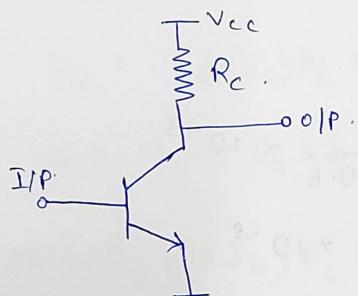


At Cut off


$$I_C = 0, V_{CE} = V_{CC}$$

At Saturation.

$$V_{CE} = 0, I_C = \frac{V_{CC}}{R_C}$$

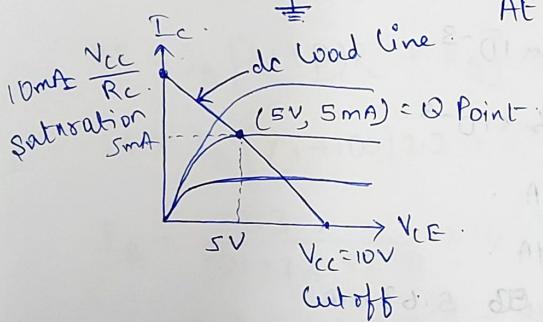

Q)

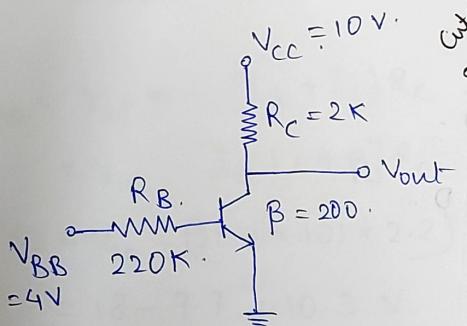

$$(o/p) V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$(i/p) V_{BB} - I_B R_B - V_{BE} = 0$$

$$= 10 - 6 = 4V$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{4 - 0.7}{220 \text{ k}} = \frac{3.3}{220} \text{ mA} = 0.015 \text{ mA}$$

$$V_{CE} = 10 \text{ V (cut off)}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$V_{CC} = I_C R_C$$


$$= 6 \text{ V (saturation)}$$

$$\beta = \frac{I_C}{I_B} \Rightarrow I_C = \beta I_B = 3 \text{ mA}$$


$$I_C = \frac{V_{CC}}{R_C} = \frac{10}{2 \text{ k}}$$

$$I_E = I_C + I_B = 3.015 \text{ mA} = 3.015 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_C Q R_C$$

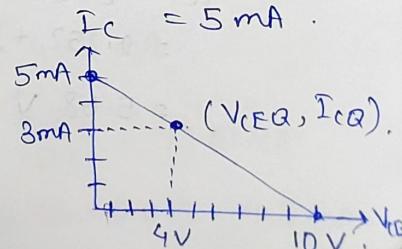

(2)

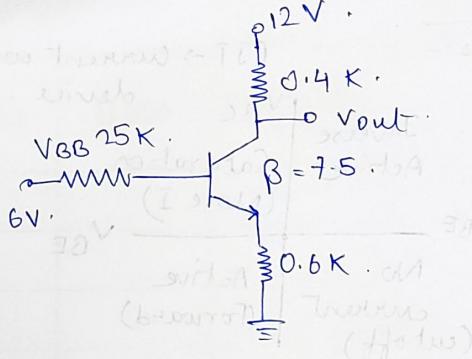

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (1+\beta)R_E} = \frac{6 - 0.7}{25 + (1+7.5)0.6} \times 10^{-3}$$

$$\frac{5.3}{25 + 5.1} \times 10^3$$

$$= \frac{5.3}{30.1} \times 10^{-3}$$

$$= 0.176 \times 10^{-3} \text{ (Am)}$$

$$= 75 \text{ mA}$$

$$I_c = \beta I_B = 7.5(75) = 562.5 \text{ mA}$$

20.5 mA .56 5.63 mA

$$I_E = I_C + I_B = 5.71 \text{ mA}$$

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CC} - I_r R_c - V_{CE} - (1+\beta)R_E =$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E.$$

$$V_{CEQ} = 12 - (5.63 \times 0.4) - (5.71 \times 0.6) \\ = 12 - 2.252 - 3.426 \\ = 6.322 \text{ V}$$

At cutoff:  $I_c = 0$

$$V_{CE} = V_c - E = 12 \text{ V}$$

At saturation ✓

$$V_{CC} = I_C R_C + I_E R_E$$

$$= 2.252 + 3.441$$

$$= 5.68 \checkmark$$


$$= 5.68 \text{ V}$$

$$V_{CC} = I_c R_C + I_c (1 + \frac{1}{B}) R_E$$

$$I_C = \frac{12}{R_s + (1 + \frac{1}{2F}) R_P}$$

$$= \frac{12}{0.4 + \frac{76}{75} \times 0.6} \times 10$$
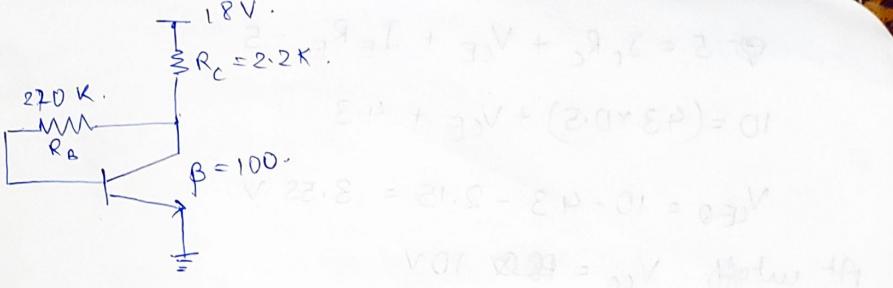
$$= \frac{12}{1.128} \times 10^{-3} = 12 \text{ mA}$$



$$V_{CC} = (I_B + I_C)R_C + I_B R_B + V_{BE}$$

$$18 = (I_B + I_C)R_C + I_B R_B + 0.7$$

$$18 = (I_B + \beta I_B)R_C + I_B R_B + 0.7$$

$$18 = I_B [(1 + \beta)R_C + R_B] + 0.7$$

$$18 = I_B [(1 + 100)2.2 + 270] \times 10^{-3} + 0.7$$

$$I_B = \frac{17.3}{101 \times 2.2 + 270} \times 10^{-3} = \frac{17.3}{492.2} \times 10^{-3}$$

$$= 0.0351 \times 10^{-3} = 35.1 \mu A$$

$$I_{CQ} = \beta I_B$$

$$= 3.51 \text{ mA}$$

$$V_{CEQ} = V_{CC} - (I_B + I_C)R_C$$

$$= V_{CC} - I_B [1 + \beta] R_C$$

$$= V_{CC} - (35.1 \times 10^{-3}) \times 2.2 \times 10^3$$



$$= 18 - 7.7 = 10.3 \text{ V}$$

$$\text{At cut-off } V_{CE} = 18 \text{ V}$$

$$\text{At sat. } V_{CC} = I_C (1 + \frac{1}{\beta}) R_C$$

$$18 = I_C \left( 1 + \frac{101}{100} \right) 2.2 \times 10^{-3}$$
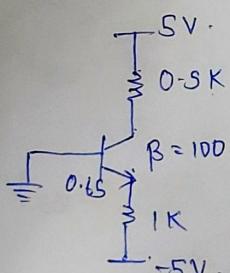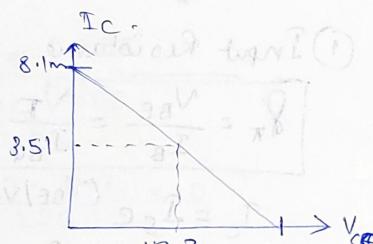
$$I_C = \frac{18}{2.22} \times 10^{-3} = 8.1 \text{ mA}$$



$$0 = 0.65 + I_E R_E - 5$$

$$I_E = \frac{5 - 0.65}{R_E} = 4.35 \text{ mA}$$

$$I_B = \frac{I_E}{1 + \beta} = \frac{4.35}{101} = 43.51 \mu A$$

$$I_E - I_B = I_{CQ} \Rightarrow I_{CQ} = 4.35 - 0.043 = 4.3 \text{ mA}$$

$$V_{CE} = I_C R_C + V_{CE} + I_E R_E - 5$$

$$10 = (4.3 \times 0.5) + V_{CE} + 4.3$$

$$V_{CEQ} = 10 - 4.3 - 2.15 = 3.55 \text{ V}$$

At cutoff:  $V_{CE} = 10 \text{ V}$

$$\text{At sat. } I_D = I_C R_C + I_C (1 + \frac{1}{\beta}) R_E$$


$$I_D = I_C [R_C + (1 + \frac{1}{\beta}) R_E]$$

$$I_D = I_C [2.2 + \frac{101}{100}]$$

$$I_C = \frac{10}{1.5} = 6.6$$

• Small Signal Equivalent ckt :-

Hybrid π Model :-

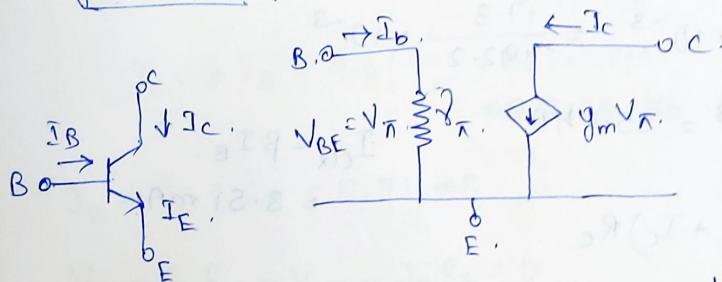

① Input Resistance.

$$R_{in} = \frac{V_{BE}}{I_B} = \frac{V_T}{I_{BQ}} = \frac{\beta_F V_T}{I_{CQ}}$$

$$I_C = I_S e^{(V_{BE}/V_T)}$$

$$I_B = \frac{I_C}{\beta_F} = \frac{I_S}{\beta_F} e^{(V_{BE}/V_T)}$$

$$\frac{1}{R_{in}} = \frac{\partial I_B}{\partial V_{BE}}$$

$$= \frac{\partial}{\partial V_{BE}} \left[ \frac{I_S}{\beta_F} e^{(V_{BE}/V_T)} \right]$$

$$\Rightarrow \frac{1}{R_{in}} = \frac{1}{V_T} \left[ \frac{I_S}{\beta_F} e^{(V_{BE}/V_T)} \right]$$

$$\Rightarrow \frac{1}{R_{in}} = \frac{I_{BQ}}{V_T}$$


$$\Rightarrow R_{in} = \frac{V_T}{I_{BQ}} = \frac{\beta_F V_T}{I_{CQ}}$$

② Transconductance

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_{CQ}}{V_T}$$

$$\beta_F = \frac{\partial I_C}{\partial I_B}$$

$$\beta_F = g_m \frac{1}{\beta}$$

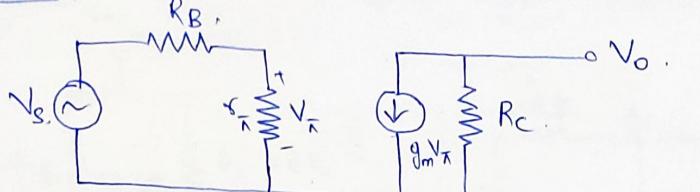


$$A_V = \frac{V_O}{V_S}, \quad V_O = V_{CE} = (-g_m V_{BE}) R_C \\ = -g_m V_\pi R_C.$$

$$\textcircled{3} \quad V_\pi = V_{BE} = \left( \frac{r_\pi}{r_\pi + R_B} \right) V_S.$$

$$\therefore A_V = \frac{V_O}{V_S} = -g_m R_C \frac{r_\pi}{r_\pi + R_B}.$$


\textcircled{4} Output Resistance  $r_o$ .
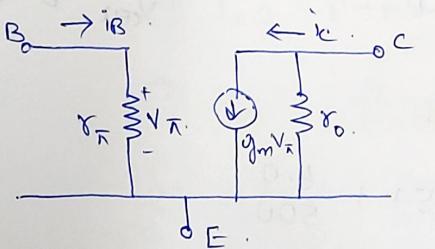
$$r_o = \frac{\partial I_C}{\partial V_{CE}} = \frac{V_A}{I_{CQ}} \quad V_A = \text{Early voltage}.$$



Hybrid  $\pi$  Model

► To determine AC & DC Load Line:

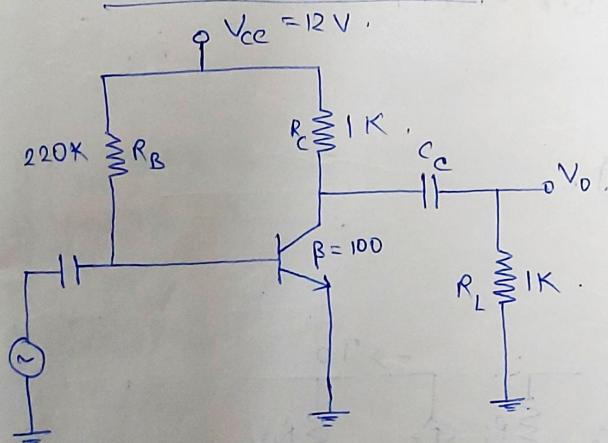

$$V_{CE} = I_C R_C + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$= \frac{12 - 0.7}{220} \times 10^{-3}.$$

$$= 0.051 \text{ mA}.$$

$$= 51 \text{ mA}.$$

$$I_{CQ} = \beta I_B = 100 \times 51 \times 10^{-6} \\ = 51 \times 10^{-4}.$$

$$I_{CQ} = 5.1 \text{ mA}.$$

\textcircled{5} DC Load Line.

Cutoff point:  $V_{CC} = V_{CE} = 12 \text{ V}$ .

Saturation pt:  $V_{CC} = I_C R_C$ .

$$I_C = \frac{V_{CC}}{R_C} = 12 \text{ mA}.$$

$$V_{CEQ} = I_C R_C + V_{CE}.$$

$$V_{CEQ} = 12 - (5.1 \times 1)$$

$$V_{CEQ} = 12 - 5.1 = 6.9 \text{ V}.$$

## AC Load Line

$$R_{ac} = R_C \parallel R_L$$


$$R_{ac} = \frac{1}{\frac{1}{R_C} + \frac{1}{R_L}}$$

$$R_{ac} = \frac{R_C + R_L}{R_C \cdot R_L} = \frac{1}{2 \times 10^{-3}} = 0.5 \times 10^3 \Omega = \frac{2 \times 10^3}{10^{-3}} = 2 \text{ k}\Omega$$

$$\frac{1}{R_{ac}} = \frac{1}{R_C} + \frac{1}{R_L}$$

$$R_{ac} = \frac{R_C R_L}{R_C + R_L} = 0.5 \times 10^3 \Omega$$
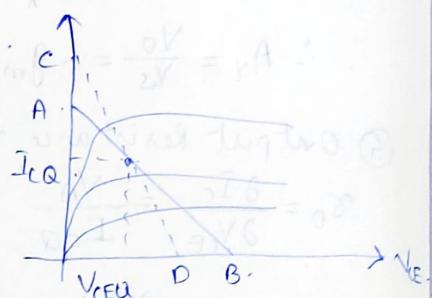
$$\begin{aligned} V_{CE(\max)} &= V_{CEO} + I_{CQ} R_{ac} \\ &= 6.9 + 5.1 \times 500 \times 10^{-3} \\ &= 6.9 + 5.1 \times 5 \times 10^{-1} \\ &= 6.9 + 2.55 \\ &= 9.45 \text{ V} \end{aligned}$$



$$\begin{aligned} i_c(\max) &= I_{CQ} + \frac{V_{CEO}}{R_{ac}} = 5.1 + \frac{6.9}{500} \\ &= 5.1 + (0.0138) \text{ A} \\ &= 5.1 + 13.8 = 18.9 \text{ mA} \end{aligned}$$





More symmetrical swing

$$\Delta i_c = 2 I_{CQ}$$

$$\Delta V_{CE} = \Delta i_c (R_C \parallel R_L)$$

## Common Emitter Amplifier:

### Two port Network

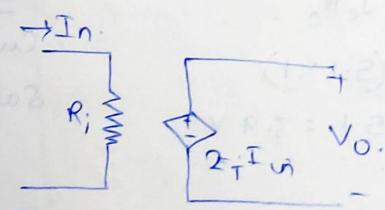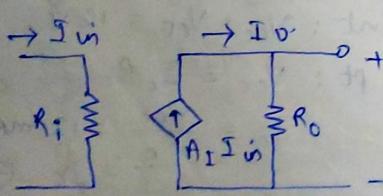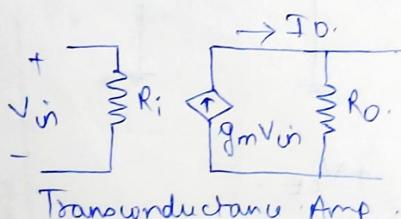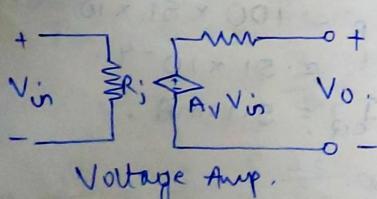


Current Amp.


Transimpedance Amp.

# CE Amplifier

with bypass cap

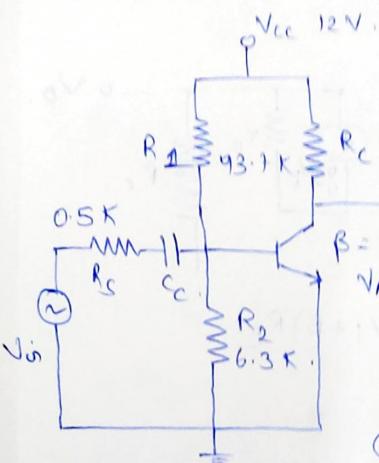
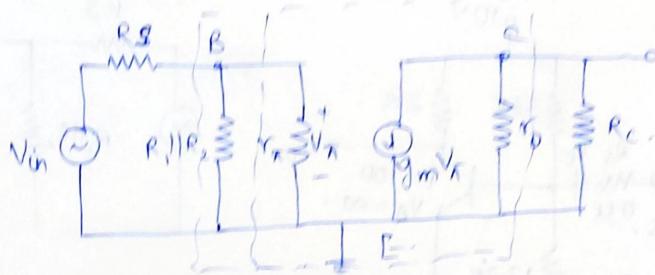
$$R_1 = 43.7 \text{ k}\Omega, R_C = 6 \text{ k}\Omega, \beta = 100, N_A = 1000.$$



STEPS:

$$\textcircled{1} \quad R_{TH} (\text{Find}) = R_1 \parallel R_2$$

$$\textcircled{2} \quad V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$\textcircled{3} \quad I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH}}$$

$$\textcircled{4} \quad I_{CQ} = \beta I_{BQ}$$

$$\textcircled{5} \quad g_m = \frac{I_{CQ}}{V_T}$$

$$\textcircled{6} \quad V_\pi = \frac{V_S (r_\pi \parallel R_1 \parallel R_2)}{(R_1 \parallel R_2 \parallel r_\pi) + R_S}$$

$$\textcircled{7} \quad R_i = R_1 \parallel R_2 \parallel r_\pi$$

$$\textcircled{8} \quad R_o = r_\pi \parallel R_C$$

$$1) \quad R_{TH} = 5.9 \text{ k}\Omega$$

$$2) \quad V_{TH} = 0.756$$

$$3) \quad I_{BQ}$$

$$4) \quad I_{CQ} = 0.9 \text{ mA}$$

$$5) \quad V_{CEQ} = 6.3 \text{ V}$$

$$6) \quad r_\pi = 2.79 \text{ }\Omega$$

$$7) \quad g_m = 36.5 \text{ mA/V}$$

$$8) \quad r_o = 105 \text{ k}\Omega$$

$$9) \quad A_V = -163$$

$$10) \quad R_i = 1.87 \text{ k}\Omega$$

$$11) \quad R_o = 5.67 \text{ k}\Omega$$

$$\textcircled{5} \quad V_{CEQ} = V_{CC} - I_{CQ} R_C \quad (\text{without } R_E)$$

$$= V_{CC} - I_{CQ} R_C - I_{EQ} R_E \quad (\text{with } R_E)$$

$$\textcircled{6} \quad r_\pi = \frac{V_T \beta}{I_{CQ}}$$

$$\textcircled{8} \quad r_o = \frac{V_A}{I_{CQ}}$$



$$\textcircled{9} \quad V_0 = (-g_m V_\pi)(r_o \parallel R_C)$$

$$\textcircled{11} \quad A_V = \frac{V_0}{V_S} \\ = \frac{-g_m V_\pi (r_o \parallel R_C)}{V_S}$$

Substitute for  $V_\pi$ .

$$\therefore A_V = \frac{-g_m (r_\pi \parallel R_1 \parallel R_2) R_C}{(r_\pi \parallel R_1 \parallel R_2) + R_S}$$


## CE Amplifier without bypass:

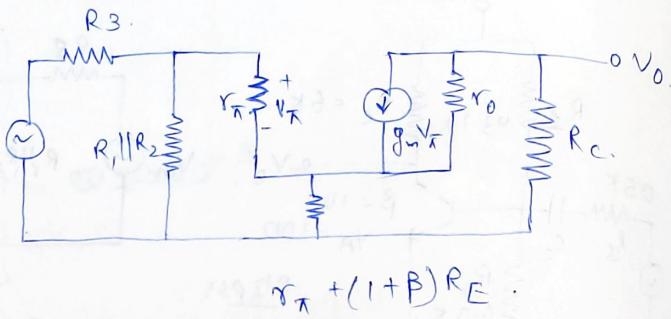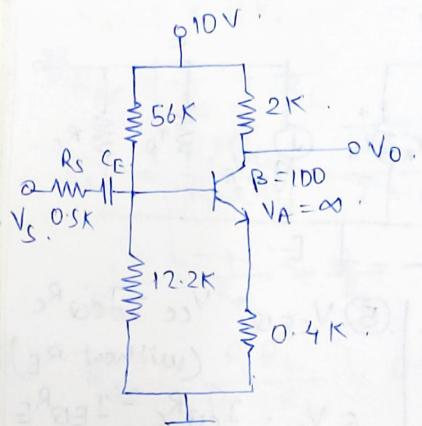

## Features of CE Amplifier ..


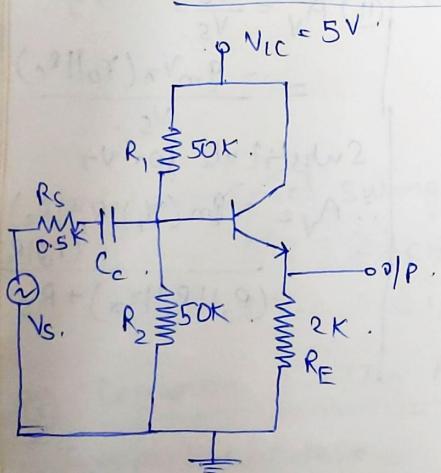
- 1) Phase shift =  $180^\circ$
- 2) Voltage gain is high (without emitter)
- 3) Input & Output impedance are moderate

► Common collector BJT Configuration (Emitter Follower) (Used for impedance matching)



$$g_m V_{be} = \frac{I_c}{V_{be}} V_{BE}$$

$$I_c = \beta I_b$$

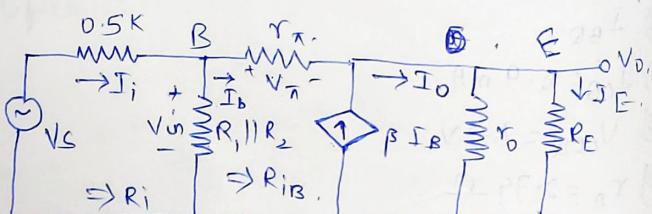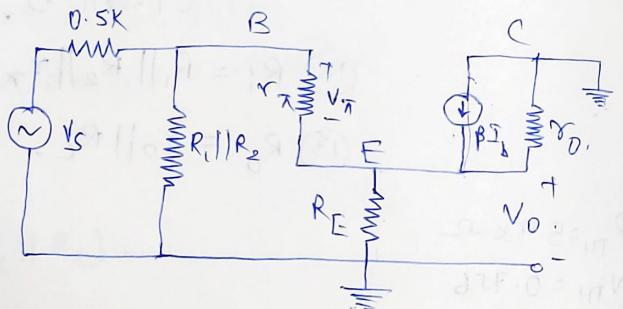

$$V_{in} = \frac{R_i V_S}{R_i + R_S}$$

$$R_i = R_1 || R_2 || R_{iB}$$

$$AV = \frac{V_O}{V_S} = \frac{(1+\beta)R_L}{V_{in}(R_i + R_S)}$$

$$\therefore A_V = \frac{R_i [(1+\beta)I_B] (r_o || R_E)}{V_{in}(R_i + R_S)}$$

$$I_o = I_B + \beta I_B = (1+\beta) I_B \quad \text{--- (1)}$$

$$V_o = [(1+\beta) I_B] (r_o || R_E) \quad \text{--- (2)}$$

$$V_{in} = I_B r_{\pi} + \{(1+\beta) I_B\} (r_o || R_E)$$

$$V_{in} = I_B [r_{\pi} + (1+\beta)(r_o || R_E)]$$

$$\frac{V_{in}}{I_B} = R_{iB} = r_{\pi} + (1+\beta)(r_o || R_E) \quad \text{--- (3)}$$

$$\therefore A_V = \frac{R_i[(1+\beta)I_B](r_o || R_E)}{r_\pi + (1+\beta)(r_o || R_E)(R_i + R_S)}$$

$$\therefore A_V = \frac{(1+\beta)(r_o || R_E)}{r_\pi + (1+\beta)(r_o || R_E)} \frac{R_i}{R_i + R_S} \rightarrow \textcircled{IV}$$

$$r_\pi \ll (1+\beta)(r_o || R_E)$$

$$R_i \gg R_S$$

$$\therefore A_V = \frac{(1+\beta)(r_o || R_E)}{(1+\beta)(r_o || R_E)} \frac{R_i}{R_i} \approx 1$$

$$A_I = \frac{I_E}{I_i} - \textcircled{V}$$

$$I_B = I_i \frac{R_1 || R_2}{(R_1 || R_2) + R_{iB}} - \textcircled{VI}$$

$$I_o = (1+\beta)I_B$$

$$I_E = \frac{I_o r_o}{r_o + R_E} = \frac{(1+\beta)I_B r_o}{r_o + R_E} - \textcircled{VII}$$

$$\therefore A_I = \frac{(1+\beta)I_B r_o}{r_o + R_E} \frac{R_1 || R_2}{I_B [(R_1 || R_2) + R_{iB}]}$$

$$\Rightarrow A_I = \frac{(1+\beta)r_o}{r_o + R_E} \cdot \frac{R_1 || R_2}{R_1 || R_2 + R_{iB}}$$

$$\Rightarrow A_I = \frac{r_o}{r_o + R_E} \frac{(1+\beta)(R_1 || R_2)}{(R_1 || R_2 + R_{iB})} - \textcircled{VIII}$$


$$R_1 || R_2 \gg R_{iB}; r_o \gg R_E$$

$$\therefore A_I = 1 + \beta - \textcircled{IX}$$

To find o/p Imp.

$$V_\pi = -V_n$$

Apply KCL at o/p node.


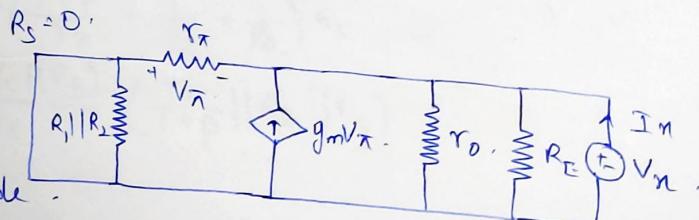


$$g_m V_\pi + I_x = \frac{V_x}{R_E} + \frac{V_x}{r_o} + \frac{V_x}{r_\pi}$$

$$\Rightarrow I_x = V_n \left[ \frac{1}{R_E} + \frac{1}{r_o} + \frac{1}{r_\pi} + g_m \right] \quad [\because g_m = \frac{\beta}{r_\pi}]$$

$$\Rightarrow \frac{V_n}{I_x} = R_D = \frac{r_\pi}{1+\beta} || R_E || r_o \approx \frac{1}{1+\beta} \downarrow -\textcircled{X}$$

### Common Base Amp.

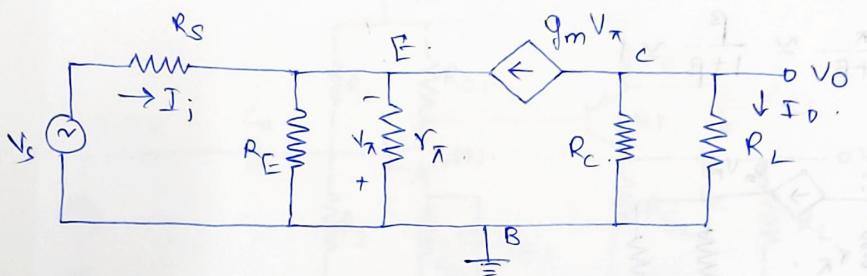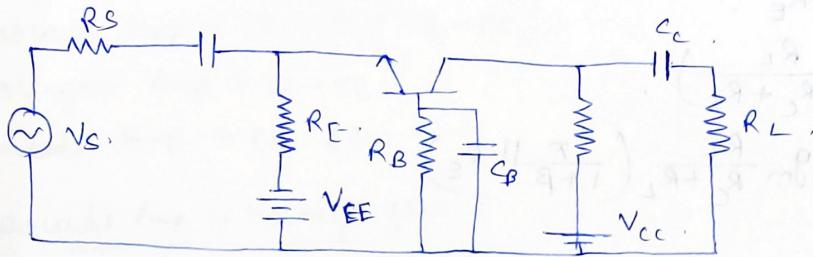

### Voltage Gain:

$$V_O = -g_m V_{\pi} (R_C \parallel R_L) \quad \text{--- (1)}$$

Apply KCL at E:

$$g_m V_{\pi} + \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_E} + \left( \frac{V_S - (-V_{\pi})}{R_S} \right) = 0 \quad \text{--- (2)}$$

$$\beta = g_m r_{\pi}$$

(1) can be:

$$V_{\pi} \left[ \frac{1+\beta}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S} \right] = -\frac{V_S}{R_S}$$

$$V_{\pi} = -\frac{V_S}{R_S} \left[ \left( \frac{r_{\pi}}{1+\beta} \right) \parallel R_E \parallel R_S \right]$$

$$A_V = \frac{V_O}{V_S} = \frac{-g_m V_{\pi} (R_C \parallel R_L)}{-V_{\pi} \left( \frac{r_{\pi}}{1+\beta} + \frac{1}{R_E} + \frac{1}{R_S} \right) R_C}$$

$$A_V = \frac{g_m (R_C \parallel R_L)}{R_S} \left( \frac{r_{\pi}}{1+\beta} \parallel R_E \parallel R_S \right)$$

### Current Gain

KCL at E:

$$I_i + \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} + \frac{V_{\pi}}{R_E} = 0$$

$$\Rightarrow I_i + \frac{V_{\pi}}{r_{\pi}} + \frac{\beta}{r_{\pi}} V_{\pi} + \frac{V_{\pi}}{R_E} = 0$$

$$\Rightarrow I_i = -V_{\pi} \left[ \frac{1+\beta}{r_{\pi}} + \frac{1}{R_E} \right]$$

$$V_{\pi} = \frac{I_i}{1+\beta} + \frac{1}{R_E}.$$


$$I_o = -g_m V_{\pi} \left( \frac{R_L}{R_C + R_L} \right).$$

$$A_i = \frac{I_o}{I_i} = g_m \frac{R_L}{R_C + R_L} \left( \frac{r_{\pi}}{1+\beta} || R_E \right)$$

$R_E \approx \text{infinity}$

$$A_i = g_m \frac{r_{\pi}}{1+\beta} \approx \frac{\beta}{1+\beta} \approx 1$$


I/O Imp.

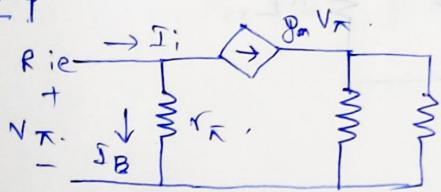

$$R_{ie} = \frac{V_{\pi}}{I_i}$$

$$I_i = I_b + g_m V_{\pi} = \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} = V_{\pi} \left( \frac{1}{r_{\pi}} + g_m \right)$$
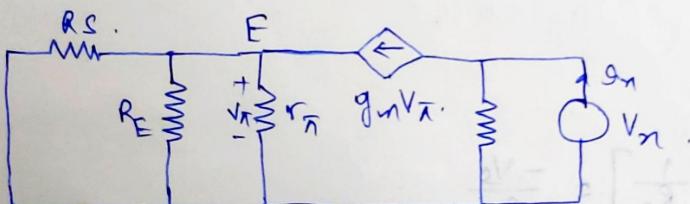
$$\therefore R_{ie} = \frac{V_{\pi}}{I_i} = \frac{r_{\pi}}{1+\beta}$$



KCL at E.

$$g_m V_{\pi} + \frac{V_{\pi}}{r_{\pi}} + \frac{V_{\pi}}{R_E} + \frac{V_{\pi}}{R_S} = 0.$$

$$V_{\pi} = 0 \quad \therefore \frac{V_{\pi}}{I_i} = R_E = R_D \uparrow$$



## Multistage Amp:

Cascade Amp  $\rightarrow$  CE - CE / CE - CC.

Darlington Amp  $\rightarrow$  CC - CC.

Cascade Amp  $\rightarrow$  CE - CB

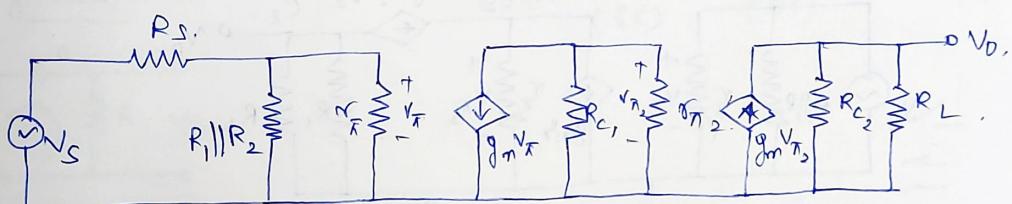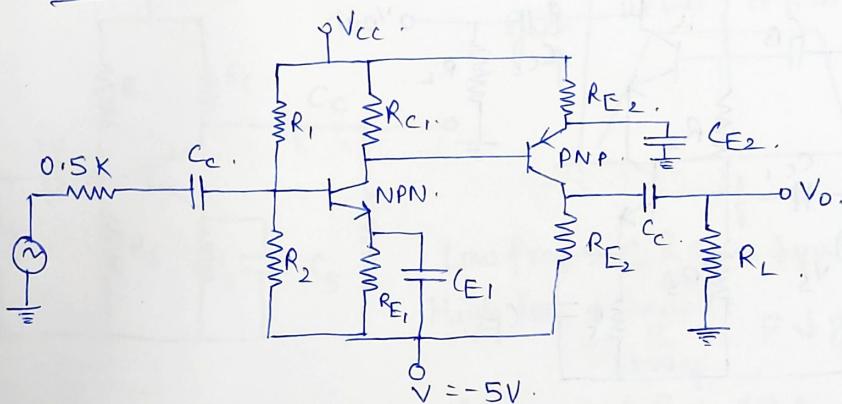Cascade Amp  $\Rightarrow$  Voltage gain  $\uparrow$



$$A_{V1} = \frac{V_{O1}}{V_s} = -g_m (R_C || r_{\pi2}) \frac{R_i}{R_i + R_s}$$

$$A_{V2} = \frac{V_{O2}}{V_{\pi2}} = -g_{m2} (R_C || R_L)$$

$$A_V = \frac{V_o}{V_s} = A_{V1} \cdot A_{V2}$$

$$A_V = g_m, g_{m2} (R_C1 || r_{\pi2}) \frac{R_i}{R_i + R_s} (R_C2 || R_L)$$

$$V_{O1} = -g_{m1} V_{\pi1} (R_C1 || r_{\pi2}).$$

$$V_{O2} = +g_{m2} V_{\pi2} (R_C2 || R_L).$$

$$V_{in} = \frac{R_i}{R_i + R_s} V_s.$$

Q) Determine  $g_m$ ,  $r_{\pi}$ ,  $R_D$ ,  $A_I$ ,  $A_V$ ,  $R_i$ ,  $r_o$  for CB circuit which has



$R_B = 100K\Omega$ ,  $R_E = 10K\Omega$ ,  $R_C = 10K\Omega$ ,  $V_{CC} = V_{EE} = 10V$ .

$R_L = 1K\Omega$ ,  $R_S = 1K\Omega$ ,  $V_{BE} = 0.7V$ ,  $\beta = 100$ ,  $V_A = \infty$ .

$R_{E2} = 1.5K\Omega$ ,  $R_L = 10K\Omega$ ,  $V_T = 5V$ ,  $V_- = 5V$ ,  $r_o = 0.2K\Omega$

Q) Find  $A_V$  (overall),  $R_1 = 70K\Omega$ ,  $R_2 = 6K\Omega$ ,  $R_C = 5K\Omega$ ,  $R_{E1} = 0.2K\Omega$ ,  $\beta = 125$ .  $R_{E2} = 1.5K\Omega$ ,  $R_L = 10K\Omega$ ,  $V_T = 5V$ ,  $V_- = 5V$ ,  $r_o = 0.2K\Omega$

## Cathode Amplifier:

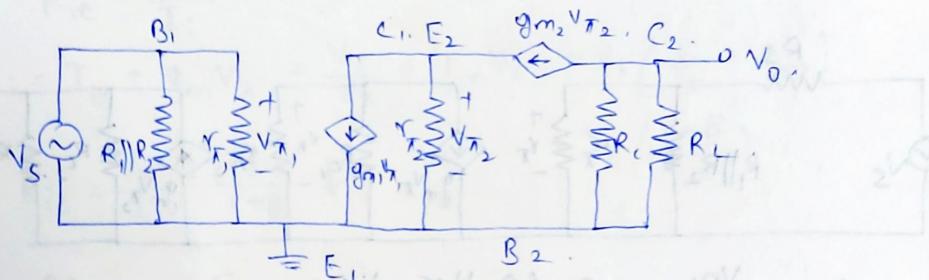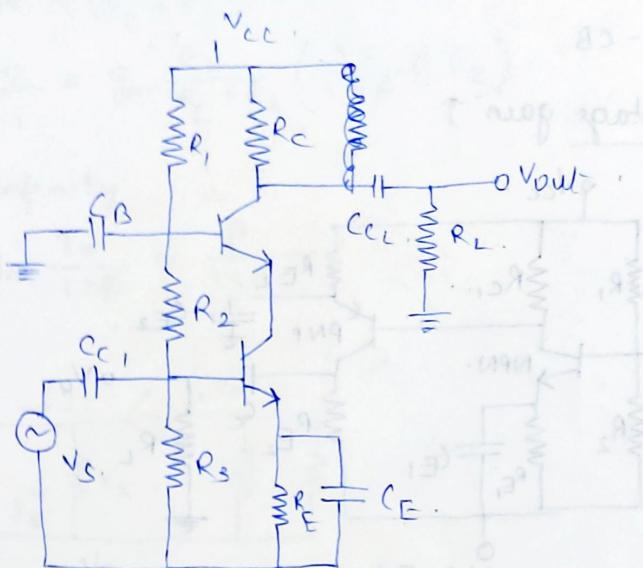

I/P Impedance  $\Rightarrow$  (E  $\Rightarrow$  moderate)

O/P Impedance  $\Rightarrow$  (B  $\Rightarrow$  high)

KCL at E<sub>2</sub>:

$$g_{m1}V_{\pi_1} = \frac{V_{\pi_2}}{r_{\pi_2}} + g_{m2}V_{\pi_2}$$

$$= \frac{V_{\pi_2}}{r_{\pi_2}} + \frac{\beta_2}{r_{\pi_2}}V_{\pi_2}$$

$$g_{m1}V_{\pi_1} = V_{\pi_2} \left( \frac{1 + \beta_2}{r_{\pi_2}} \right)$$

$$V_o = -g_{m2}V_{\pi_2}(R_c || R_L)$$

$$V_o = -g_{m1}g_{m2}V_{\pi_1} \left( \frac{r_{\pi_2}}{1 + \beta_2} \right) (R_c || R_L)$$



$$\therefore A_v = \frac{V_o}{V_s}$$

$$= -g_{m1}g_{m2} \left( \frac{r_{\pi_2}}{1 + \beta_2} \right) (R_c || R_L)$$

$$g_m r_{\pi_2} = \beta_2 ; \quad \frac{g_m r_{\pi_2}}{1 + \beta_2} = \frac{\beta_2}{1 + \beta_2} \approx 1$$

$$\therefore A_v = -g_m (R_C || R_L) \cdot (A_v \text{ of } (E_1))$$

frequency Response of an Amp :-

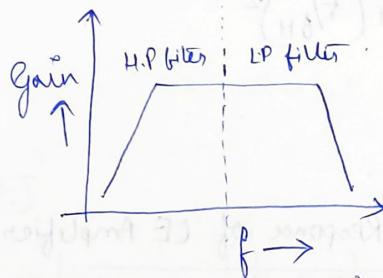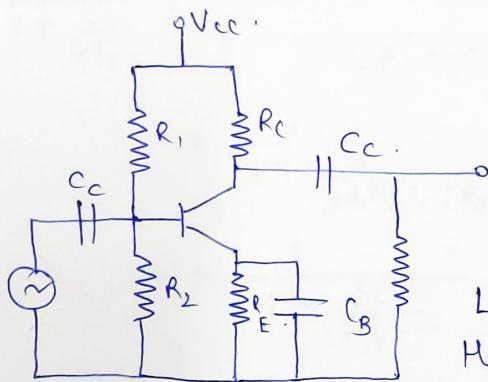


Low freq  $\Rightarrow C_c \text{ & } C_B \Rightarrow \downarrow \text{gain}$   
 High freq  $\Rightarrow \text{Parasitic } (SC) \text{ & } \text{stray} \Rightarrow \downarrow \text{gain}$



E || E/C  
 E || S

Mid freq  $\Rightarrow C_c \text{ & } C_B \text{ & Internal } (SC) \Rightarrow \text{Const. } (OC)$

High Pass Filter

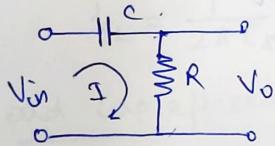

$$V_{in} = IR + IX_C \\ = IR + \frac{I}{2\pi f C}$$

$$V_{out} = IR$$

$$A_v = \frac{R}{R + \frac{1}{2\pi f C}} = \frac{RSC}{RSC + 1} = \frac{1}{1 + \frac{1}{RSC}} = \frac{1}{1 + \frac{1}{j2\pi f RC}} = 1 - j\frac{f}{2\pi f RC}$$


$$= \frac{1}{1 - j\frac{f}{2\pi f RC}} \quad [f_L = \frac{1}{2\pi f RC}]$$

$$|A_v| = \frac{1}{\sqrt{1 + (\frac{f}{f_L})^2}}$$

$$\text{At } f = f_L$$

$$|A_v| = \frac{1}{\sqrt{2}}$$

Low Pass Filter

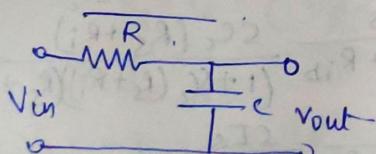

$$V_{out} = IX_C = \frac{I}{SC}$$

$$V_{in} = IR + \frac{I}{SC}$$

$$A_v = \frac{I/SC}{IR + I/SC} = \frac{\frac{1}{SC}}{R + \frac{1}{SC}} = \frac{1}{RSC + 1}$$

$$= \frac{1}{1 + jR_2 R_f C}$$

$$= \frac{1}{1 + j(b/f_H)}$$




$$|Av| = \sqrt{1 + (b/f_H)^2}$$

At  $b = f_H$ ,

$$|Av| = \frac{1}{\sqrt{2}}$$

### Frequency Response of CE Amplifier :-

Coupling capacitor effects:

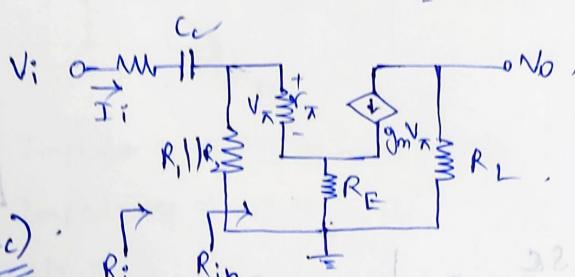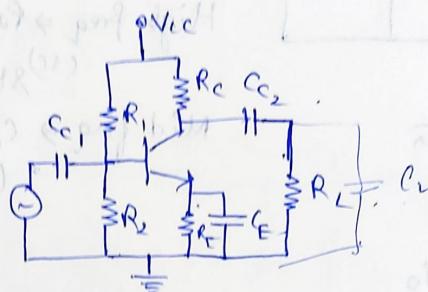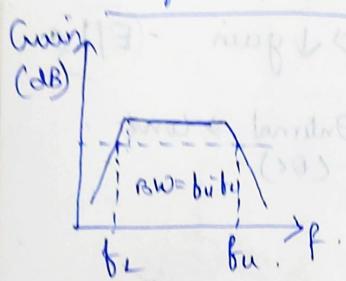

$$I_i = \frac{V_i}{R_s + \frac{1}{SC_c} + R_i}$$

$$I_b = \frac{R_B}{R_B + R_{ib}} I_i$$

$$V_\pi = I_b r_\pi$$

$$R_i = R_B || r_\pi + (1 + \beta) R_E$$

$$R_B = R_1 || R_2$$

Resistance Reflection Rule

$$R_{ib} = \frac{V_\pi}{I_b} = r_\pi + (1 + \beta) R_E$$

$$V_o = -g_m V_\pi R_C$$

$$V_o = -g_m R_C (I_b r_\pi)$$

$$= -g_m R_C r_\pi \frac{R_B}{R_B + R_{ib}} I_i$$

$$= -g_m R_C r_\pi \frac{R_B}{R_B + R_{ib}} \cdot \frac{V_i}{R_s + \frac{1}{SC_c} + R_i}$$

$$A_v = \frac{V_o}{V_i} = -g_m R_C r_\pi \frac{R_B}{R_B + R_{ib}} \frac{SC_c (R_s + R_i)}{(1 + SC_c (R_s + R_i)) (R_s + R_i)}$$

$$= -\frac{g_m R_C r_\pi}{R_s + R_i} \cdot \frac{R_B}{R_B + R_{ib}} \frac{SC_s}{1 + SC_s}$$

$$A_V(s) = \frac{-g_m R_c}{R_i + R_s} r_\pi \frac{R_B}{R_B + R_{ib}} \frac{1}{1 + \frac{1}{sC_s}}$$

$$|A_V(s)| = 20 \log \left( \frac{g_m R_s}{R_i + R_s} r_\pi \frac{R_B}{R_B + R_{ib}} \right)$$

$$\frac{1}{1 + \frac{1}{sC_s}} = \frac{1}{1 + \frac{1}{j\omega C_s (R_s + R_i)}} = \frac{1}{1 + \frac{1}{j2\pi f_c (R_s + R_i)}} = \frac{1}{1 + \frac{jL}{\omega_b}} = \frac{1}{1 + j\frac{f_L}{f_b}} \quad [f_L = \frac{1}{2\pi C_s (R_s + R_i)}]$$

O/P coupling capacitance effect

$$T_s = (R_s + R_L) C_{c_2}$$

$$f_L = \frac{1}{2\pi T_s}$$

Load cap effect


$$T_p = (R_c || R_L)$$

$$A_V = \frac{g_m (R_c || R_L)}{1 + g_m R_s} \left( \frac{1}{1 + \frac{1}{sC_s}} \right)$$

$$A_{V(\text{max})} = \frac{g_m (R_c || R_L)}{1 + g_m R_s}$$

► Effect in Frequency Response :-

Bypass capacitor:

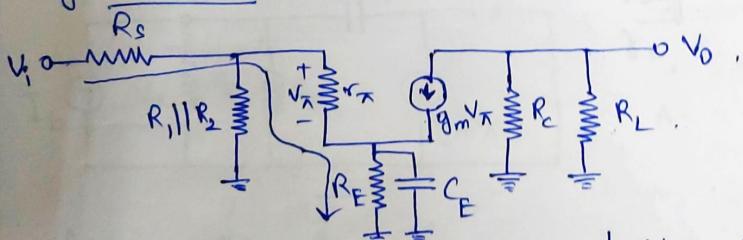

$$I_b = \frac{V_i}{R_s + r_\pi + (1+\beta)(R_E || \frac{1}{sC_E})}$$

$$V_\pi = I_b r_\pi$$

$$V_o = -g_m V_\pi (R_c || R_L)$$

$$\therefore V_o = -g_m I_b r_\pi (R_c || R_L)$$

$$V_o = -g_m r_\pi (R_c || R_L) \frac{V_i}{R_s + r_\pi + (1+\beta)(R_E || \frac{1}{sC_E})}$$

$$A_V = \frac{V_o}{V_i} = \frac{-g_m r_\pi (R_c || R_L)}{R_s + r_\pi + (1+\beta)(\frac{R_E \cdot 1/sC_E}{R_E + 1/sC_E})}$$

$$\begin{aligned}
 &= \frac{-g_m r_\pi (R_c || R_L)}{R_s + r_\pi + (1+\beta) \frac{R_E}{1+sR_E C_E}} \\
 &\Rightarrow \frac{-g_m r_\pi (R_c || R_L) (1 + sR_E C_E)}{(R_s + r_\pi) (1 + sR_E C_E) + (1+\beta) R_E} \\
 &= \frac{-g_m r_\pi (R_c || R_L) (1 + sR_E C_E)}{R_s + r_\pi + (1+\beta) R_E + (R_s + r_\pi) sR_E C_E} \\
 &= \frac{-g_m r_\pi (R_c || R_L) (1 + sR_E C_E)}{R_s + r_\pi + (1+\beta) R_E \left( 1 + \frac{sR_E (R_s + r_\pi) C_E}{R_s + r_\pi + (1+\beta) R_E} \right)}
 \end{aligned}$$



$$= \frac{-g_m r_\pi (R_c || R_L)}{R_s + r_\pi + (1+\beta) R_E} \frac{1 + sT_A}{1 + sT_B}$$

when  $\omega \rightarrow 0$  CE is open circuit.


$$\therefore A_v(s) = \frac{g_m r_\pi (R_c || R_L)}{R_s + r_\pi + (1+\beta) R_E}$$

$\omega \rightarrow \infty$

$$A_v(s) = \frac{g_m r_\pi (R_c || R_L)}{R_s + r_\pi}$$

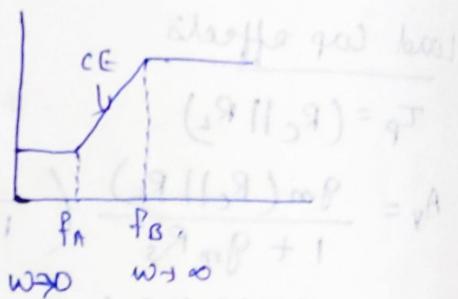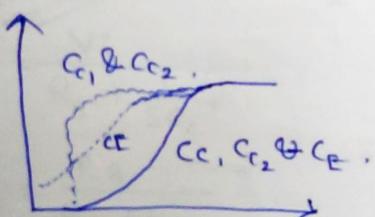

## Nidband Gain:-

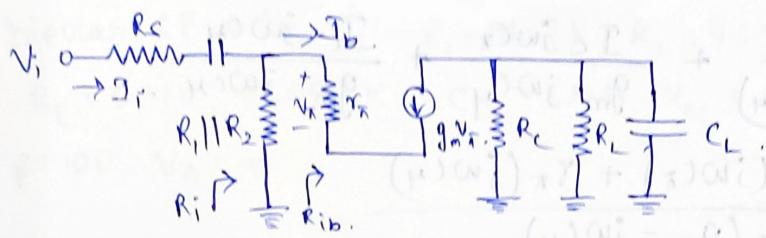

$$I_i = \frac{V_i}{R_s + R_1 || R_2 || R_{ib}}$$

$$I_b = \frac{R_1 || R_2 \cdot I_i}{(R_1 || R_2) + R_{ib}}$$


$$V_\pi = I_b \cdot r_\pi$$

$$V_D = -g_m V_\pi (R_C || R_L)$$


$$V_o = -g_m r_\pi \frac{(R_1 || R_2)}{(R_1 || R_2) + R_i} \frac{V_i}{(R_s + R_1 || R_2 || R_{ib})}$$

$$A_v = \frac{V_o}{V_i} = -g_m r_\pi \frac{(R_1 || R_2)}{(R_1 || R_2) + R_i} \frac{1}{(R_s + R_1 || R_2 || R_{ib})}$$

## Expanded hybrid $\pi$ Model :-

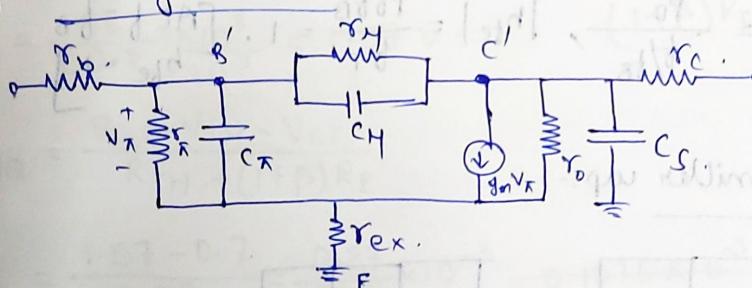

## Short circuit I gain:-

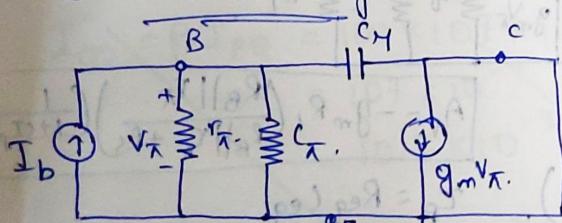

Applying KCL at C.

$$\frac{V_\pi}{j\omega C_H} + I_c = g_m V_\pi$$

$$\therefore V_\pi = \frac{I_c}{g_m - j\omega C_H} \quad \text{--- (1)}$$

## Neglecting :-

$r_b$ ,  $r_c$ ,  $r_{ex}$ ,  $r_h$  &  $C_S$ ,  $V_D$ .

$$A_i = \frac{I_c}{I_b}$$

Apply KCL at B.

$$I_b = \frac{V_\pi}{r_\pi} + \frac{V_\pi}{j\omega C_H} + \frac{V_\pi}{j\omega C_H}$$

--- (1)

Substituting  $\Delta R$  &  $V_n$  in  $I_b$ .

$$I_b = \frac{I_c}{r_\pi(g_m - j\omega C_4)} + \frac{I_c j\omega C_\pi}{g_m + j\omega C_4} + \frac{I_c j\omega C_4}{g_m - j\omega C_4}$$

$$\Rightarrow \frac{I_b}{I_c} = \frac{1 + r_\pi(j\omega C_\pi) + r_\pi(j\omega C_4)}{r_\pi(g_m - j\omega C_4)}$$

$$\Rightarrow \frac{I_c}{I_b} = \frac{r_\pi(g_m - j\omega C_4)}{1 + r_\pi(j\omega C_\pi) + r_\pi(j\omega C_4)}$$

$$\Rightarrow A_i = \frac{g_m - j\omega C_4}{\frac{1}{r_\pi} + j\omega(C_\pi + C_4)}$$


$$\Rightarrow A_i = \frac{g_m - j\omega C_4}{1 + j\omega r_\pi(C_\pi + C_4)}$$

$$= \frac{\beta_0}{1 + j\omega r_\pi(C_\pi + C_4)}$$

$$= \frac{\beta_0}{1 + b/b_B}$$

$$|h_{fe}| = \frac{\beta_0}{\sqrt{1 + (b/b_B)^2}} = \frac{\beta_0}{b/b_B}, \quad |h_{te}| = \frac{\beta_0 b_B}{b_T} = 1. \quad [AT f = f_B, h_{fe} = 1]$$


Miller effect and Miller cap:-

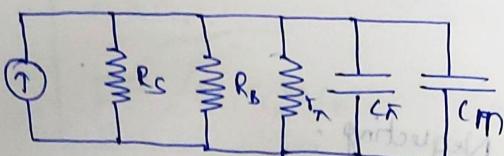

$$C_m = C_4(1 + A_v)$$

$$C_m = C_4(1 + (-g_m(R_C) || R_L)).$$
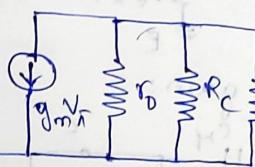
$$\text{Total i/p capacitance} = C_\pi + C_m$$



$$A_V = -g_m R_L \left( \frac{R_B || r_\pi}{R_B || r_\pi + R_S} \right) \left( \frac{1}{1 + s C_P} \right)$$

$$C_P = \text{Req Cap.}$$

$$\text{Req} = r_\pi || R_B || R_S.$$

$$C_{eq} = C_m + C_\pi.$$

$$\therefore f_H = \frac{1}{2\pi \text{Req} C_{eq}}$$

Q) Calculate the corner frequency and max gain of bipolar CE with  $C_C$ .  $R_1 = 51.2 \text{ k}\Omega$ ,  $R_2 = 9.6 \text{ k}\Omega$ ,  $R_C = 2 \text{ k}\Omega$ ,  $R_E = 0.4 \text{ k}\Omega$ ,  $R_S = 0.1 \text{ k}\Omega$ ,  $C_C = 1 \text{ pF}$ ,  $V_{CC} = 10 \text{ V}$ ,  $V_{BE} = 0.9 \text{ V}$ ,  $\beta = 100$ ,  $N_A = \infty$

$$I_{CQ}, g_m, r_\pi, R_i = R_1 || R_2 || r_\pi + (1+\beta)R_E, I_S = (R_S + R_i)C_C,$$

$$f_L = \frac{1}{2\pi C_S}, |A_v| = \frac{g_m r_\pi R_C}{R_S + R_i} \cdot \frac{R_B}{R_B + R_i B}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{(51.2 \times 9.6) \times 10^6}{51.2 + 9.6}$$

$$= 8.08 \text{ k}\Omega$$

$$V_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$= \frac{9.6 \times 10 \times 10^3}{(51.2 + 9.6) \times 10^3}$$

$$= \frac{96}{60.8} \times 10^3 = 1.57 \text{ V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (1+\beta)R_E}$$

$$= \frac{1.57 - 0.7}{8.08 + 40.4} = \frac{0.87}{48.48} \times 10^{-3} = 0.018 \times 10^{-3} = 18 \mu\text{A}$$

$$(1+\beta)R_E = 0.4 \times 10^3$$

$$= 40.4 \text{ k}\Omega$$

$$I_{CQ} = \beta I_{BQ} = 100 \times 18 \times 10^{-6}$$

$$= 1.8 \times 10^{-4}$$


$$= 1.8 \times 10^{-3} = 1.8 \text{ mA}$$

$$\frac{1}{g_m} = \frac{V_T}{I_{CQ}} = \frac{I_{CQ}}{V_T} = \frac{1.8 \times 10^{-3}}{0.026} = 69.23 \times 10^{-3}$$

$$= 0.41$$

~~$$R_Q \approx R_1 || R_2 = 8.08 \text{ k}\Omega$$~~

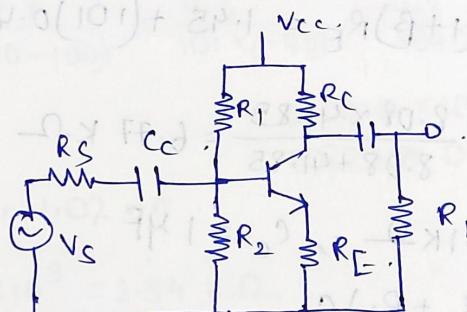~~$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 0.026}{1.8} \times 10^3 = \frac{2.6}{1.8} \text{ k}\Omega = 0.24 \text{ k}\Omega$$~~



$$r_\pi + (1+\beta)R_E = 0.24 + (101)0.4$$

$$I_{CQ} = \beta I_{BQ} = 100 (17.9) \times 10^{-6}$$

$$= 17.9 \times 10^{-4}$$

$$= 1.79 \text{ mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.79 \times 10^{-3}}{0.026} = 68.84 \times 10^{-3} = 0.068$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 0.026 \times 10^3}{1.79} = 1.45 \text{ k}\Omega$$

$$r_\pi + (1+\beta)R_E = 1.45 + (101)0.4 = 41.85 \text{ k}\Omega$$

$$R_i = \frac{8.08 \times 41.85}{8.08 + 41.85} = 6.77 \text{ k}\Omega$$

$$R_S = 0.1 \text{ k}\Omega, C_C = 1 \mu\text{F}$$

$$T_S = (R_S + R_i) C_C$$


$$= (0.1 + 6.77) \times 1 \times 10^{-3}$$

$$= 6.87 \times 10^{-3}$$

$$f_L = \frac{1}{2\pi T_S} = \frac{10^3}{2 \times 3.14 \times 6.87} = \frac{1}{43.14} \times 10^3 = 0.0231 \times 10^3 = 23 \text{ Hz}$$

$$|A_V| = \frac{0.068 \times 1.45 \times 2 \times 10^6}{6.87 \times 10^3} = \frac{8.08 \times 10^3}{(8.08 + 41.85) \times 10^3} = 0.028 \times 10^3 \times 0.162 = 0.0045 \times 10^3 = 4.5$$

$$\text{Amplifier gain} = 4.5$$

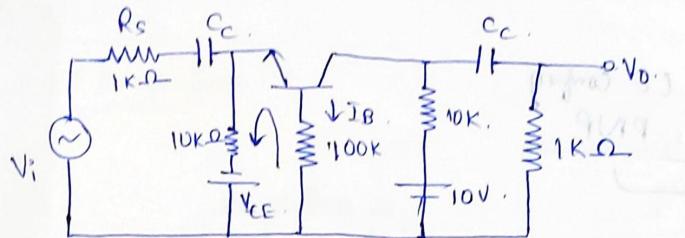

$$I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0.$$

$$\Rightarrow V_{EE} - V_{BE} = I_E R_E - I_B R_B \\ = I_B (1 + \beta) (R_E - R_B).$$

$$I_B = \frac{V_{EE} - V_{BE}}{(1 + \beta)(R_E - R_B)} = \frac{10 - 0.7}{101(10 - 100)} = \frac{9.3}{101 \times (-90)} = \frac{9.3}{9090} \times 10^{-3} \\ = 0.0010 \times 10^{-3} \\ = 0.00204 \text{ mA}$$

$$I_{CQ} = \beta I_{BQ} = 100(0.0010) = 1.02 \text{ mA}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 0.026}{1.02} \times 10^3 = 2.54 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.02 \times 10^{-3}}{0.026} = 39 \text{ mho}$$


$$A_I = \frac{g_m R_L}{R_C + R_L} \left( \frac{r_\pi}{1 + \beta} \parallel R_E \right)$$

$$\frac{r_\pi}{1 + \beta} = \frac{2.54 \times 10^3}{101} = 0.025 \times 10^3$$

$$\frac{r_\pi}{1 + \beta} \parallel R_E = \frac{0.025 \times 10^3 \times 10 \times 10^3}{10 \cdot 0.025 \times 10^3} = 0.0249 \times 10^3$$

$$A_I = \frac{39 \times 10^{-3} \times 1 \times 10^3}{(10 + 1) \times 10^3} \times 0.0249 \times 10^3 = 0.089$$
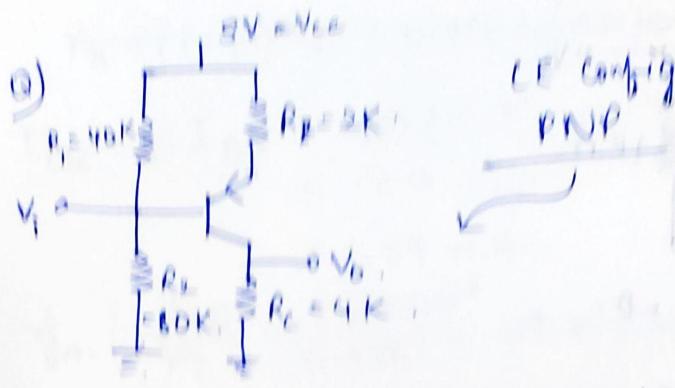
$$= \frac{39 \times 10^{-3} \times 1 \times 10^3}{(10 + 1) \times 10^3} \cdot \frac{3.54 \times 10^{-3}}{(2.54 + 1) \times 10^{-3}} = 0.089$$



Quivalent parameters, small signal voltage gain,  $\beta = 37$   
 Transistor parameters, are  $V_{BE} = 0.7 \text{ V}$ ,  $\beta = 37$ ,  $V_A = \infty$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = 2.4 \text{ k}\Omega = \frac{(1.0 - 0.7)(1.0)}{(0.1 - 0.1)(1.0)} = \frac{30\text{V} - 37\text{V}}{(37 - 37)(9+1)} = 8\Omega$$

$$V_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2} = 8 \text{ V}$$

$$\text{At } Q, V_T = (1 + \beta) I_B R_E + V_{BE} + I_B R_{TH} + V_{TH}$$

$$\frac{V_T - V_{BE} - V_{TH}}{R_{TH} + (1 + \beta) R_E} = I_B \text{ where } \beta = \frac{0.1 \times 2.0 \cdot 1}{0.1 \times 0.1} = \frac{0.1 \times 20}{0.1} = 20 = \beta$$

$$\Rightarrow I_{BO} = \frac{V_T - V_{BE} - V_{TH}}{R_{TH} + (1 + \beta) R_E} = \frac{37 \text{ mV}}{(37 - 37) + 20 \times 0.1} = 1.87 \text{ mA}$$

$$I_{CO} = \beta I_{BO}$$

$$r_n = \frac{\beta n}{I_{CO}} = \frac{\beta n V_T}{I_{CO}}$$

$$g_m = \frac{I_{CO}}{V_T} = \frac{0.1 \times 20 \cdot 0.1}{0.1 \times 37 \text{ mV}} = \frac{20 \times 1 \times 0.1}{0.1 \times (1 + 0.1)} = 18 \text{ A/V}$$

$$r_{FO} = \frac{0.1 \times 10 \cdot 0.1}{0.1 \times 37 \text{ mV}} = \frac{10 \times 1 \times 0.1}{0.1 \times (1 + 0.1)} = \frac{10 \times 10^{-3}}{0.1 \times \left(\frac{1}{37} + \frac{1}{37} \times \frac{1}{1.01}\right)}$$