

## BJT Amplifiers.

Overview of DC analysis of BJT circuits & Models.

Introduction to BJT circuits & models.

# Transistors are 3 terminal device, namely


1. Emitter - heavily doped
2. Base - thin + lightly doped
3. collector - large + moderately doped.

# Two types



1. unipolar - 'I' conduction - one type of charge
2. Bipolar - 'T' " - both the charge carriers

# BJT -

n-p-n

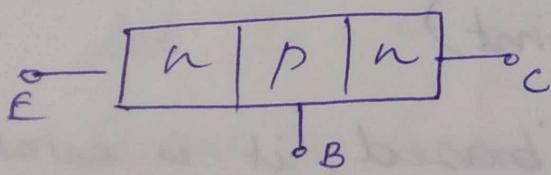

p-n-p

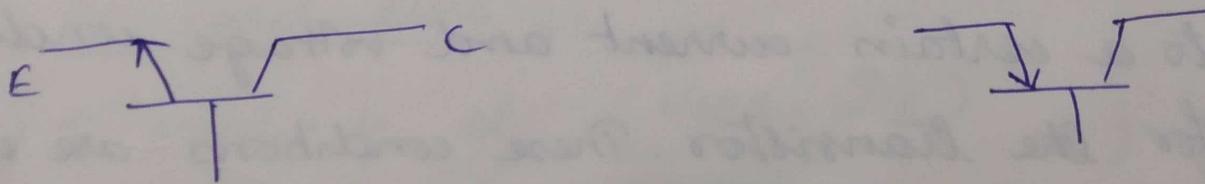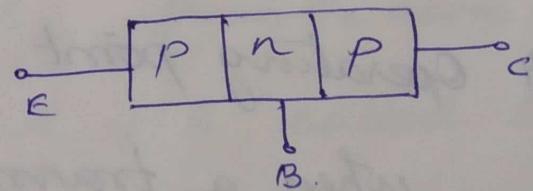


$$\left. \begin{aligned} I_E &= (1 + \beta) I_B \\ I_C &= \beta I_B \\ I_E &\approx I_C \end{aligned} \right\}$$

→ magnitude of  
collector current


## BJT configurations.

CE

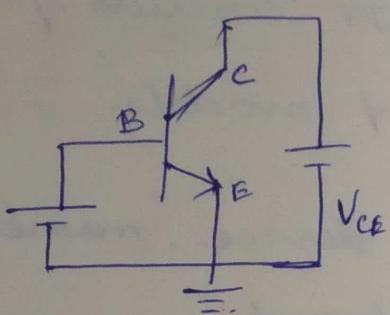


Emitter grounded

CB

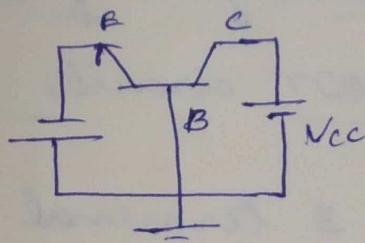

Base ground

CC

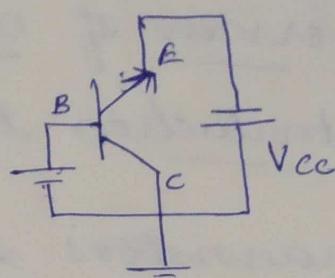

Collector ground.

# CE is the most popular configuration, because of its high voltage and current gain.


# Need for biasing.

- to establish a fixed level of current and voltages.


# Operating point ( $\alpha$ -point)

when a transistor is biased, it is established to a certain current and voltage condition for the transistor. These conditions are called dc operating point.

## DC load line :-

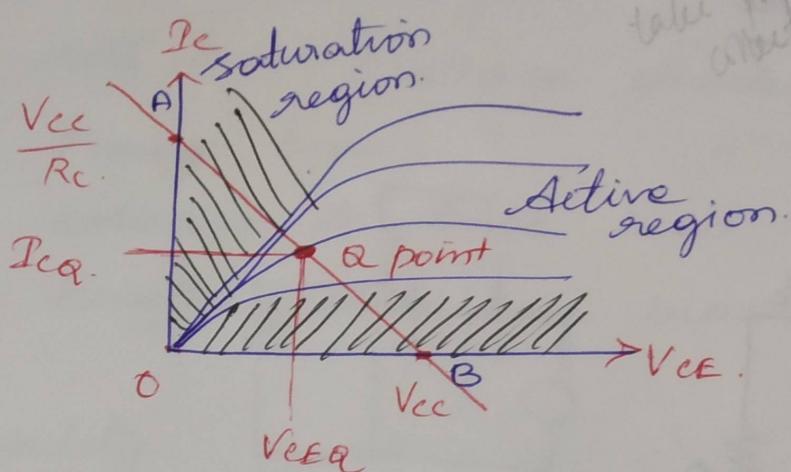

load well  
take from  
other side

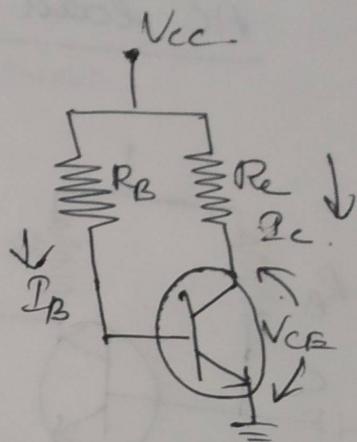

$$V_{EE} - I_C R_C - V_{CE} = 0.$$

To find A + B from the above. (gpm) + (egn)

$$V_{EE} - I_C R_C = V_{EE}.$$

$$y = mx + c$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$V_{CE} \quad I_C R_C \quad V_{EE}$$

. to determine

one component, the other is kept zero.

$$\therefore \text{let } V_{CE} = 0; V_{EE} = I_C R_C$$



$$\therefore I_C = V_{CC} / R_C.$$

let  $I_C = 0; V_{EE} = V_{CE}$ . from the above eq

Draw a line between A + B, called the DC load line,


# Q point is at  $(V_{CEQ}, I_Q)$

## AC load line

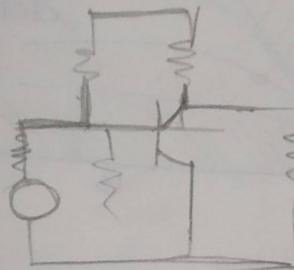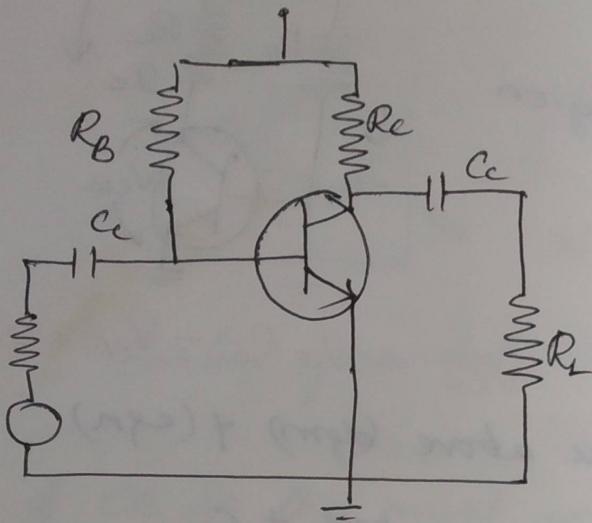


# for AC analysis coupling and bypass capacitors acts as short circuit.
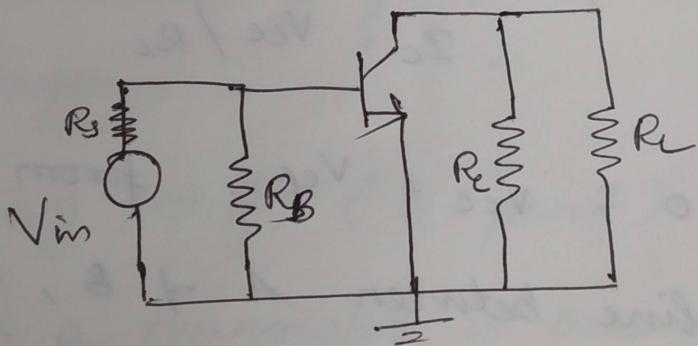
# DC supply also replaced by short circuit



$$\therefore V_{CE\max} = V_{CE\alpha} + I_{C\alpha} \cdot R_{ac}$$
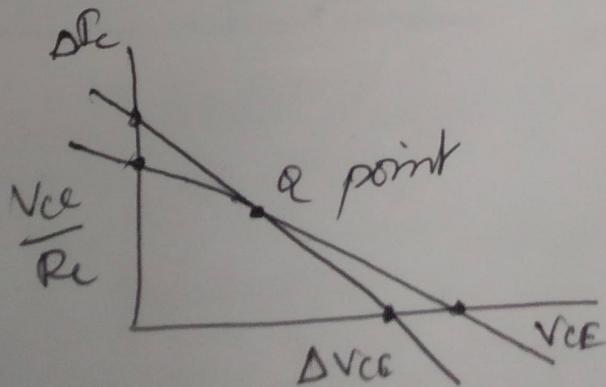
$$I_{C\max} = \frac{V_{CE\alpha}}{R_{ac}} + I_{ea}$$



## Types of biasing.

1. self bias / voltage divider bias.
2. Fixed bias.
3. collector to base bias.
4. Emitter stabilized bias.

## Stability

- measure of sensitivity of a network to variations in its parameters.



$I_c$  is sensitive.

(i)  $\beta$ ;  $s(\beta) = \frac{\Delta I_c}{\Delta \beta}$ .  
phase constant

(ii)  $V_{BE}$ ;  $s(V_{BE}) = \frac{\Delta I_c}{\Delta V_{BE}}$

(iii)  $I_{CO}$ ;  $s(I_{CO}) = \frac{\Delta I_c}{\Delta I_{CO}}$ .  
saturation current  
collector current

## fixed Bias

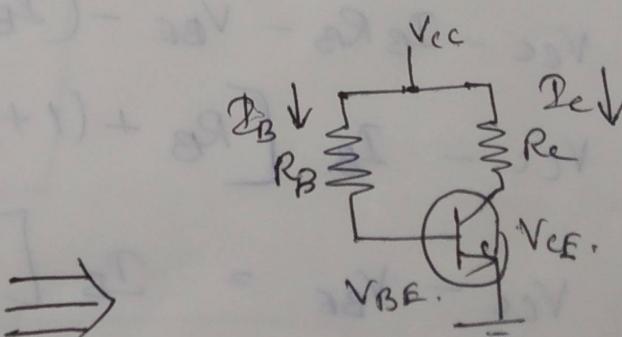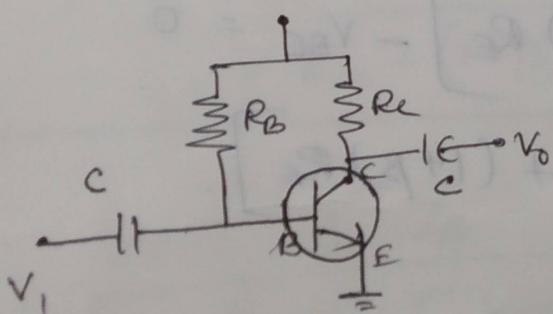

To find Q point.

$$V_{CC} - I_C R_E - V_{CE} = 0 \quad | \quad V_{CC} - I_B R_B - V_{BE} = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_E \quad | \quad \Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B}$$



$$\Rightarrow P_c = \beta I_B$$

$$= \beta \left[ \frac{V_{cc} - V_{BE}}{R_B} \right]$$

$$s(P_{co}) = \beta + 1$$

yawa

# Emitter Bias configurations.

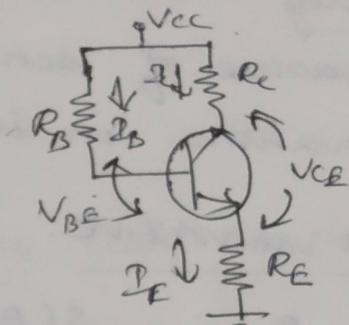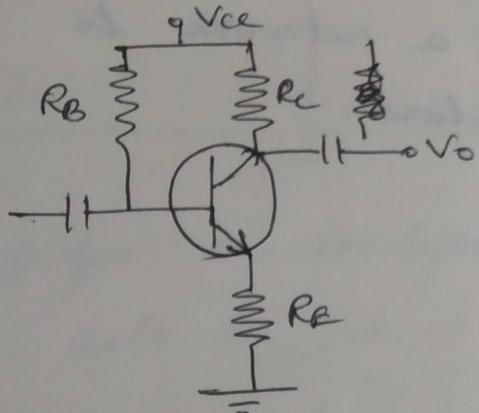

a point

$$V_{cc} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$= V_{cc} - I_B R_B - V_{BE} - (1 + \beta) I_B \cdot R_E = 0$$

$$= V_{cc} - I_B R_B - V_{BE} - (I_B + \beta I_B) \cdot R_E$$

$$= V_{cc} - I_B [R_B + (1 + \beta) R_E] - V_{BE} = 0$$


$$= V_{cc} - V_{BE} = I_B [R_B + (1 + \beta) R_E]$$

$$\boxed{I_B = \frac{V_{cc} - V_{BE}}{R_B + (1 + \beta) R_E}}$$

$$\boxed{P_c = \beta \cdot I_B = \beta \cdot \frac{V_{cc} - V_{BE}}{R_B + (1 + \beta) R_E}}$$

$$\boxed{P_c = \beta \cdot I_B = \beta \cdot \frac{V_{cc} - V_{BE}}{R_B + (1 + \beta) R_E}}$$

## Voltage divider Bias

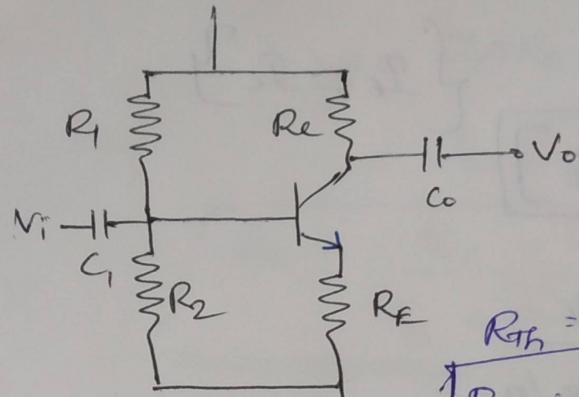


$$R_{TH} = R_1 \parallel R_2$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{TH} = V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$$


yf war

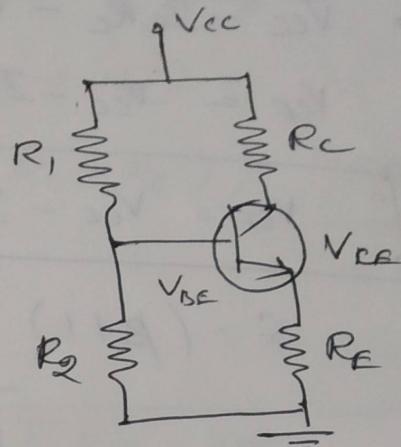

To find Q point.

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$
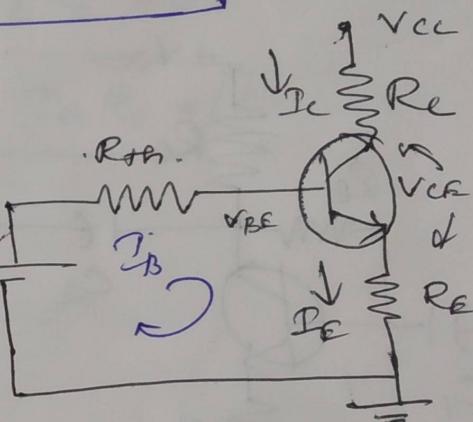
$$= V_{TH} - I_B R_{TH} - V_{BE} - (1+B) I_B R_E = 0$$



$$\Rightarrow I_B (R_{TH} + (1+B) R_E) = V_{TH} - V_{BE}$$

$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1+B) R_E}$$

$$I_C = B \cdot I_B$$

$$I_C = B \cdot \left[ \frac{V_{TH} - V_{BE}}{R_{TH} + (1+B) R_E} \right]$$



$$\Rightarrow V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0.$$

$$V_{CE} = V_{CC} - I_C R_E - I_E R_E \quad \left\{ \begin{array}{l} I_C \approx I_E \\ \end{array} \right\}$$

$$\therefore V_{CE} = V_{CC} - I_C [R_C + R_E]$$

$$S = \frac{(B+1) 1 + R_m/R_E}{(1+B) + R_m/R_E}.$$

### # Collector Feedback Bias.

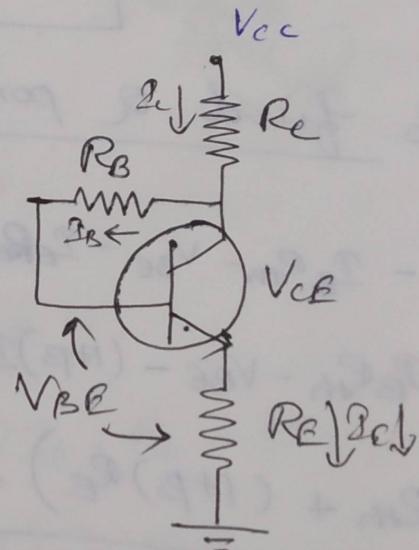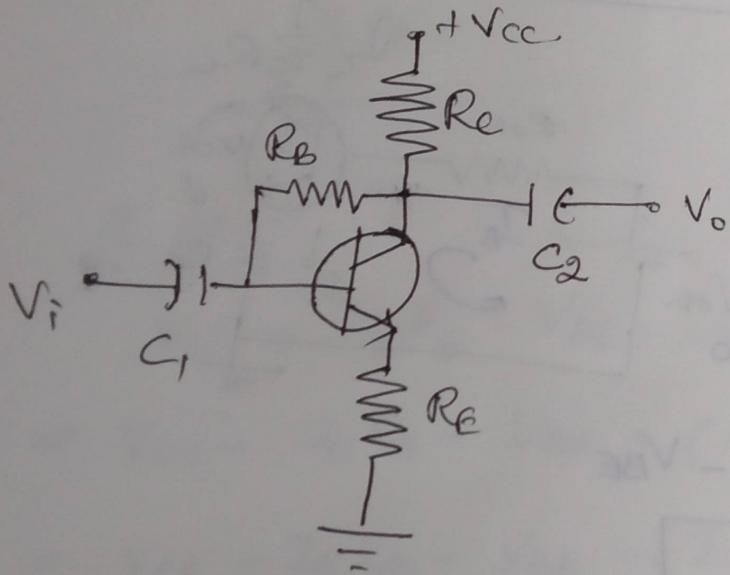

A point :-

$$\Rightarrow V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E = 0.$$

$$\therefore I_E \approx I_C \quad +$$

$$I_C = \beta I_B.$$

$$\Rightarrow V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - I_C R_E = 0$$

$$\Rightarrow V_{CC} - V_{BE} = I_B R_B + \beta I_B R_C + \beta I_B R_E =$$

$$= I_B R_B + \beta I_B (R_C + R_E)$$

$$= I_B (R_B + \beta) (R_C + R_E) \quad (1+\beta)$$

only  $\beta$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \underline{\beta} (R_C + R_E)}$$

$$\therefore I_C = \beta I_B = \beta \left[ \frac{V_{CC} - V_{BE}}{R_B + \beta (R_C + R_E)} \right]$$

$$\Rightarrow V_{CC} - I_C R_E - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_E - I_E R_E =$$


$$= I_B (\underline{\beta + \beta}) (R_C + R_E)$$

$$= I_B (R_B \cdot R_C + \beta R_E + R_B \cdot R_E + \beta R_E)$$

$$= I_B (R_B \cdot R_C + \beta R_E + R_B \cdot R_E + \beta R_E)$$

$$= I_B (R_B \cdot R_C + \beta R_E + R_B \cdot R_E + \beta R_E)$$

## # AC Analysis

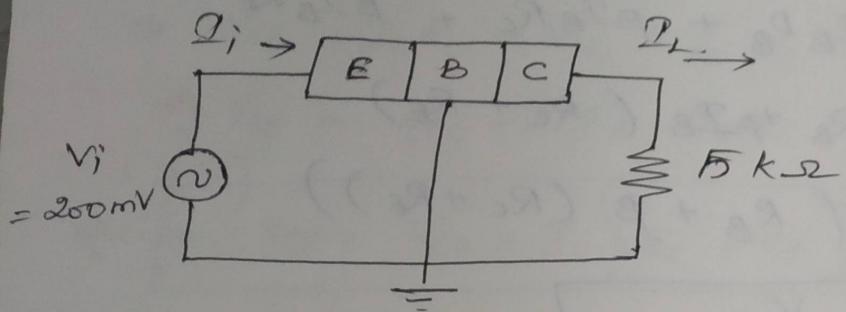

$$\text{Let } R_i = 20 \Omega \quad I_i = V_i / R_i = 10 \text{ mA.}$$

$$I_L = 10 \text{ mA} \quad = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA.}$$

$$V_o = R_L \times I_L$$

$$= 10 \text{ mA} \times 5 \text{ k}\Omega$$

$$= 50 \text{ V.}$$

- An ac signal changes the i/p current (i.e.,)  
If 'I<sub>b</sub>', 'I<sub>c</sub>' changes.
- If 'I<sub>c</sub>' changes Q point shifts.  
 $\therefore$  Therefore ac analysis is necessary.
- AC analysis of a transistor network depends on the magnitude of the i/p signal.

1) small signal analysis

2) large signal analysis

→ # SSA - re-model


- hybrid equivalent model (h-parameter)

- hybrid  $\Pi$  model.

## Model

- A model is a combination of circuit elements that best approximates the actual behavior of a semi-conductor device under specific operating conditions.

Hybrid (approx)

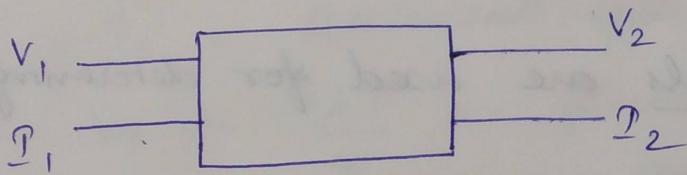

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2.$$


$$h_{11} = \frac{V_1}{I_1} \quad / \quad V_2 = 0 \Rightarrow \text{f/p impedance } (h_f) \rightarrow$$

$$h_{12} = \frac{V_1}{V_2} \quad / \quad I_1 = 0 \Rightarrow \text{Reverse transfer voltage gain } (h_o)$$

$$h_{21} = \frac{I_2}{I_1} \quad / \quad V_2 = 0 \Rightarrow \text{forward transfer current gain } (h_f)$$

$$h_{22} = \frac{I_2}{V_2} \quad / \quad I_1 = 0 \Rightarrow \text{o/p admittance } (h_o) \rightarrow$$

## # Approximate Model (hybrid)

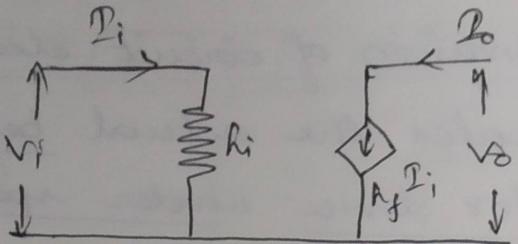


AC analysis of Basic BJT amplifier configurations using classical discrete circuit bias arrangement small scale AC model

- Linear DC models are used for determining the a point,
- AC model is used for determining the voltage or power gain when the transistor is operated as an amplifier in the active region.

## Hybrid $\pi$ model.

- Popular circuit model used for analysing small signal behavior of BJT & FET

These are quite accurate.

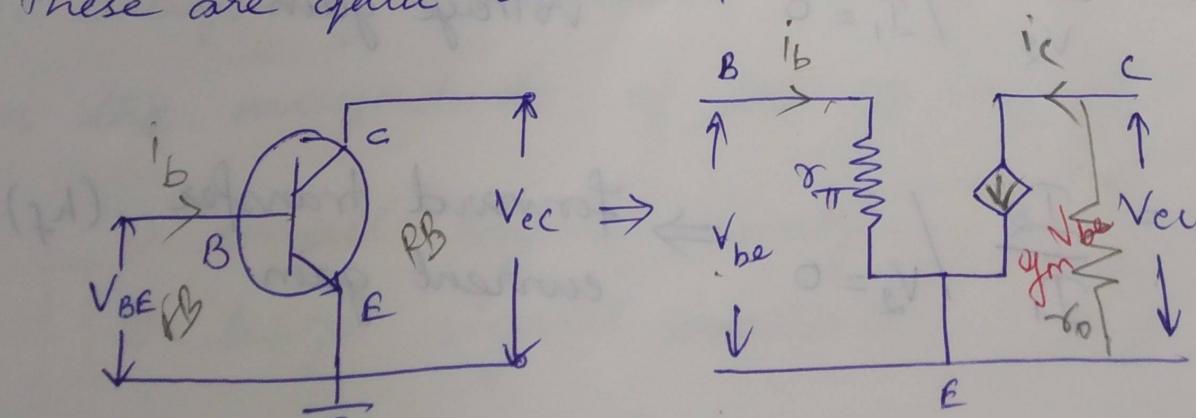

The hybrid  $\Pi$  is a linearised 2 port network approximation to BJT using small signal base emitter voltage (as independent variables)  $V_{be}$ , and  $i_b + i_c$  as dependent variables.

The various parameters are :

$$g_m = \frac{i_c}{V_{be}} \Big|_{V_{ce}=0} = \frac{\mathcal{I}_c}{V_T} \xrightarrow[\text{temp } \uparrow]{\text{charge in } \mathcal{I}_c @ 0^\circ\text{C}}$$

*i.e. voltage  
in active device*

$\mathcal{I}_c$  = Quiescent collector current

$$V_T = \frac{kT}{q} = \text{thermal voltage}$$

$\left\{ \begin{array}{l} k - \text{Boltzman constant} \\ T - \text{temperature in kelvin} \\ q - \text{charge of electron} \end{array} \right.$

$$V_T = 26 \text{ mV} @ \text{room temperature.}$$

$$\left. \begin{array}{l} \text{diffusion resistance} \\ \text{base emitter resistor} \end{array} \right\} r_{\Pi} = \frac{V_{be}}{\mathcal{I}_b} \Big|_{V_{ce}=0}$$

$\mathcal{I}_b$  = DC bias base current.

$\beta_0 = \frac{\mathcal{I}_c}{\mathcal{I}_b}$  is current gain.

$r_o = \frac{V_{ce}}{i_c} \Big|_{V_{be}=0} \simeq \frac{V_A}{\mathcal{I}_c}$  is the output resistance due to Early effect.

$\beta = \frac{\mathcal{I}_c}{\mathcal{I}_b}$   
 $\beta = g_m \beta_0$   
 $\beta = g_m \beta_0 \left( \frac{\mathcal{I}_c}{\mathcal{I}_b} \right)$

Note :- Instead of  $g_m V_{be}$  we can use  $\beta I_B$  also for derivations.


$$g_m = \frac{\beta}{8\pi}$$

$$V_{be} = 8\pi \times I_B.$$

$$\therefore g_m V_{be} = \frac{\beta}{8\pi} \times 8\pi \times I_B.$$

$$\boxed{g_m V_{be} = \beta I_B.}$$

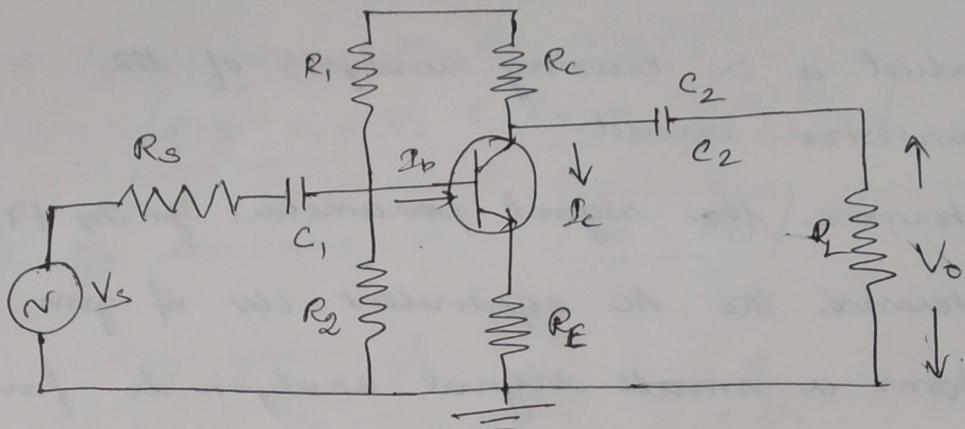
## Common Emitter Amplifier (AC analysis)



- # figure shows CE circuit with voltage divider bias. Emitter is at ground potential.
- # s/g from source is coupled to the base of the transistor through the coupling capacitor.  
↳ this provides DC isolation between the amplifier and signal source.
- #  $R_1 + R_2 \rightarrow$  establish dc transistor biasing & is not disturbed when the current source is capacitively coupled to the amplifier
- # At high frequencies  
 $|Z_C| = \frac{1}{2\pi f_C C}$ , which is very less  
 $\therefore$  capacitor is considered as SC.
- # signal frequency is high enough to consider any coupling capacitor as short circuit and transistor capacitance as OC. open circuit

## Steps involved in analysing an amplifier ckt.

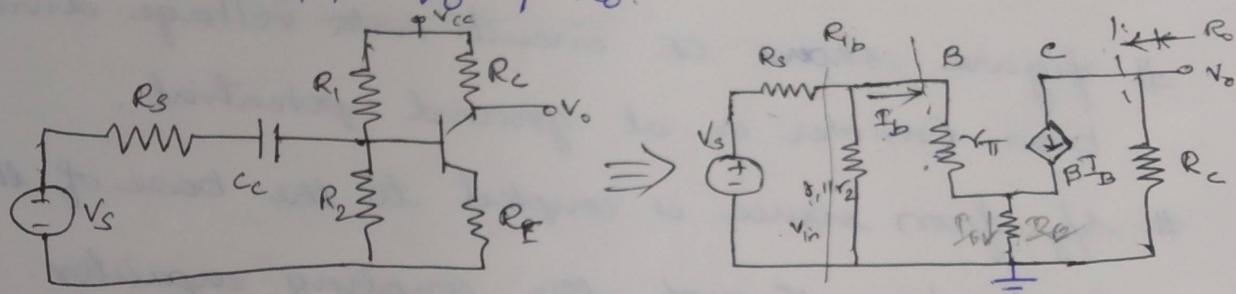1. conduct a DC biasing analysis of the transistor circuit.
2. Determine the signal parameters  $g_m, r_o + r_s$ .
3. Determine the AC equivalent ckt of  $g_m$ .
4. Perform a small signal analysis to find  $R_i, A_{vo}$  &  $R_o$ .



- current gain parameter  $\beta$  is used.
- $r_o \rightarrow$  is neglected since early effect voltage is  $\infty$

$$r_o = \frac{V_A}{I_c} \approx \infty$$

1)  $\text{I/P Resistance } R_i$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$R_{ib} = \frac{V_i}{I_b} = \text{I/P resistance looking into the base of transistor.}$

Applying loop equation :-

$$V_{in} = I_b r_\pi + (I_b + \beta I_b) R_E$$

$$\frac{V_{in}}{I_b} = R_{ib} = r_\pi + (1 + \beta) R_E$$

This is called resistance reflection rule.

\* I/P resistance to the amplifier is

$$R_i = R_1 \parallel R_2 \parallel r_{\pi} + (1+\beta) R_E$$

2) O/p resistance is ,  $R_o = R_C$

3) Voltage gain ,  $A_v$ .

$$A V_o = \frac{V_o}{V_{in}}$$

$$; V_o = - \beta I_b R_C$$

$$; V_{in} = I_b r_{\pi} + (I_b + \beta I_b) R_E$$

$$; V_{in} = I_b [r_{\pi} + (1+\beta) R_E]$$


$$\therefore \frac{V_o}{V_{in}} = \frac{-\beta I_b R_C}{I_b [r_{\pi} + (1+\beta) R_E]}$$

$r_{\pi} \ll (1+\beta) R_E$ , then

$$A V_o = - \frac{\beta R_C}{(1+\beta) R_E}$$

voltage gain including source resistance &  $V_s$
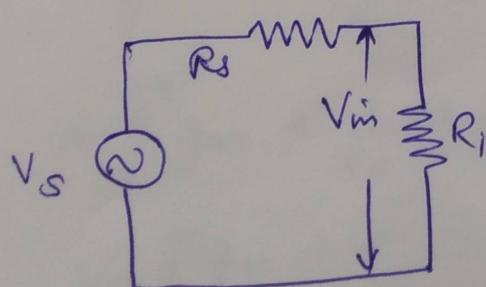
$$A_{vs} = \frac{V_o/V_s}{V_{in}/V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s}$$



using voltage divided rule

$$V_{in} = \frac{V_s \times R_i}{R_s + R_i}$$

$$\frac{V_{in}}{V_s} = \frac{R_i}{R_s + R_i}$$

$$\therefore A_{vs} = \frac{-\beta R_C}{r_{\pi} + (1+\beta) R_E} \cdot \frac{R_i}{R_s + R_i}$$

$A_{v0}$  can be made high by

- choosing large value of  $\beta_f$
- choosing large value of  $R_C$
- choosing low value of  $R_E$  &  $R_E \approx 0$ .

$$A_{v0} = -\frac{\beta_f R_C}{r_\pi} = -\frac{g_m r_\pi R_C}{r_\pi} = -g_m R_C.$$

$$\boxed{\frac{2q}{2(q+1) + \frac{1}{r_\pi}} = \frac{V_o}{V_i}}$$


W.L.O.G consider small signals in loop equation

$$\frac{mV}{2V} \times \frac{0V}{mV} = \frac{0V}{2V} = 0A$$

the loop equation gives



$$\frac{2 + 2}{2 + 2} = \frac{mV}{2V}$$

$$\frac{2A}{2mA} = \frac{mV}{2V}$$

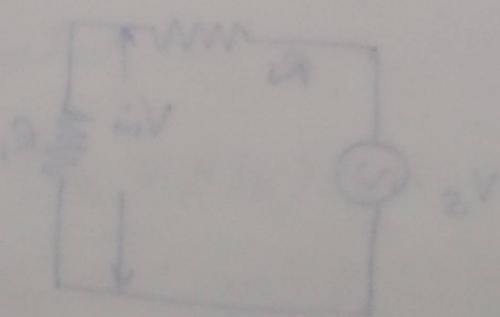
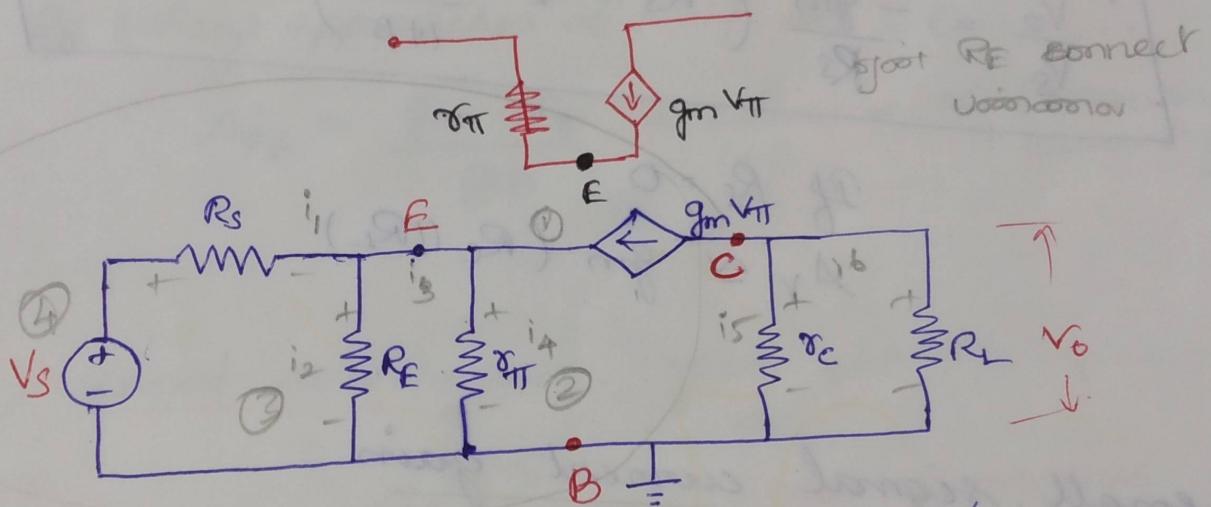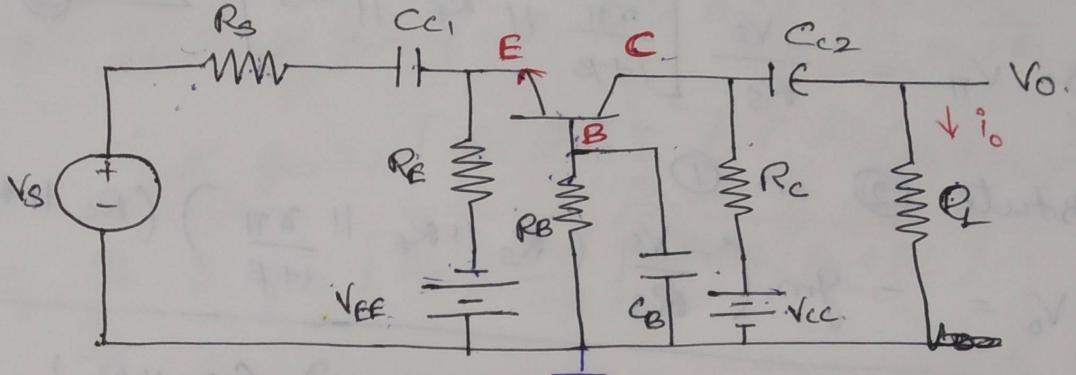
## Common Base Amplifier.

- # Base is at signal ground and i<sub>P</sub> is applied to emitter.
- #  $\infty$  → assumed to be infinite.



# small signal voltage gain  $A_v = \frac{V_o}{V_s}$  as per ckt. + logic.

$$\rightarrow V_o = -gmV_T \times (r_c \parallel r_L) \quad \text{--- (1)}$$

→ KCL @ emitter node.

$$gmV_T + \frac{V_T}{r_T} + \frac{V_s + V_T}{R_s} + \frac{V_T}{R_E} = 0.$$

$$= V_T \left[ gm + \frac{1}{r_T} + \frac{1}{R_E} + \frac{V_s}{R_s} + \frac{1}{R_s} \right] = 0$$

$$= V_T \left[ gm + \frac{1}{r_T} + \frac{1}{r_E} + \frac{1}{R_s} \right] = -\frac{V_s}{R_s}$$

$$\Rightarrow V_{\pi} \left[ \frac{g_m r_{\pi}}{r_{\pi}} + 1 + \frac{1}{R_E} + \frac{1}{R_S} \right] = - \frac{V_S}{R_S}$$

$$\Rightarrow V_{\pi} \left[ \frac{1+\beta}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S} \right] = - \frac{V_S}{R_S}$$

$$\Rightarrow V_{\pi} = - \frac{V_S}{R_S} \left[ \frac{r_{\pi}}{1+\beta} \parallel R_E \parallel R_S \right] \quad \text{--- (2)}$$

Substitute (2) in (1)

$$V_o = - g_m \left( - \frac{V_S}{R_S} \left( R_S \parallel R_E \parallel \frac{r_{\pi}}{1+\beta} \right) (R_C \parallel R_L) \right)$$

$$\boxed{\therefore \frac{V_o}{V_S} = - \frac{g_m}{R_S} \left( R_S \parallel R_E \parallel \frac{r_{\pi}}{1+\beta} \right) (R_C \parallel R_L)}$$

$$\text{If } R_S = 0$$

$$A_v \approx g_m (R_C \parallel R_L)$$

small signal current gain

$$A_i = \frac{I_o}{I_i} \quad \because I_o = - g_m V_{\pi} \cdot \frac{R_C}{R_E + R_L}$$

③

KCL @ i/P.

$$I_i + \frac{V_{\pi}}{R_E} + \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} = 0$$

$$\Rightarrow V_{\pi} \left( \frac{1}{R_E} + \frac{1}{r_{\pi}} + g_m \right) = - \frac{I_i}{R_E}$$

$$\Rightarrow V_{\pi} \left( \frac{1}{R_E} + \frac{1+g_m r_{\pi}}{r_{\pi}} \right) = - \frac{I_i}{R_E}$$

$$\Rightarrow V_{\pi} \left( \frac{1}{R_E} + \frac{1+\beta}{r_{\pi}} \right) = -I_i$$

$$\Rightarrow V_{\pi} = -I_i \left( R_E \parallel \frac{r_{\pi}}{1+\beta} \right) \quad \text{--- (4)}$$

Substitute  $V_{\pi}$  from (4) in (3)

$$\Rightarrow I_o = -g_m \left( -I_i \left( R_E \parallel \frac{r_{\pi}}{1+\beta} \right) \right) \left( \frac{R_C}{R_C + R_L} \right)$$

$$= g_m I_i \left[ R_E \parallel \frac{r_{\pi}}{1+\beta} \right] \left( \frac{R_C}{R_C + R_L} \right)$$


$$\boxed{\therefore A_v = \frac{I_o}{I_i} = g_m \left[ R_E \parallel \frac{r_{\pi}}{1+\beta} \right] \left( \frac{R_C}{R_C + R_L} \right)}$$

$R_E$  (when) approaches  $\infty$ , if  $R_L = 0$ .

$$\therefore A_v = \frac{g_m r_{\pi}}{1+\beta} = \frac{\beta}{1+\beta} = \infty \text{ (common base current gain)}$$

$R_i$ : Input resistance

open ckt top side.  
so

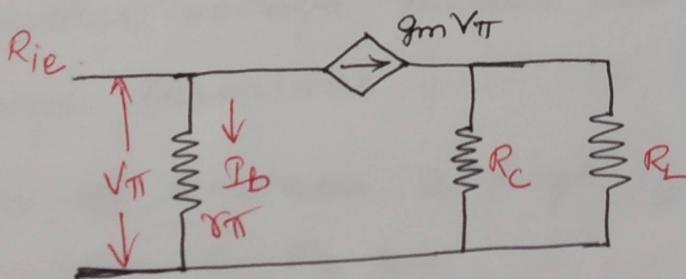

for convenience  
directions reversed.

$$R_{ie} = \frac{V_{\pi}}{I_i}$$

$$I_i = I_b + g_m V_{\pi}$$

$$= \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi}$$

$$= V_{\pi} \left[ \frac{1}{r_{\pi}} + g_m \right]$$

$$= V_{\pi} \left[ \frac{g_m r_{\pi}}{r_{\pi}} \right]$$

$$= V_{\pi} \left[ \frac{1+\beta}{r_{\pi}} \right]$$

$$V_{\pi} = ? \left[ \frac{r_{\pi}}{1+\beta} \right]$$

$$\frac{V_{\pi}}{I_i} = \frac{1}{1+\beta}$$

$$\therefore D_i = \sqrt{\pi} \left[ \frac{1 + \beta}{\gamma \pi} \right]$$

$$\therefore \frac{V_i}{D_i} = \cancel{\frac{\beta}{\gamma}}$$


$$\boxed{\therefore \frac{V_i}{D_i} = \frac{\gamma \pi}{1 + \beta}} \simeq \gamma \pi$$

$R_o$ : op resis.


$$\boxed{R_o \simeq R_c}$$



## Common Collector Amplifier.

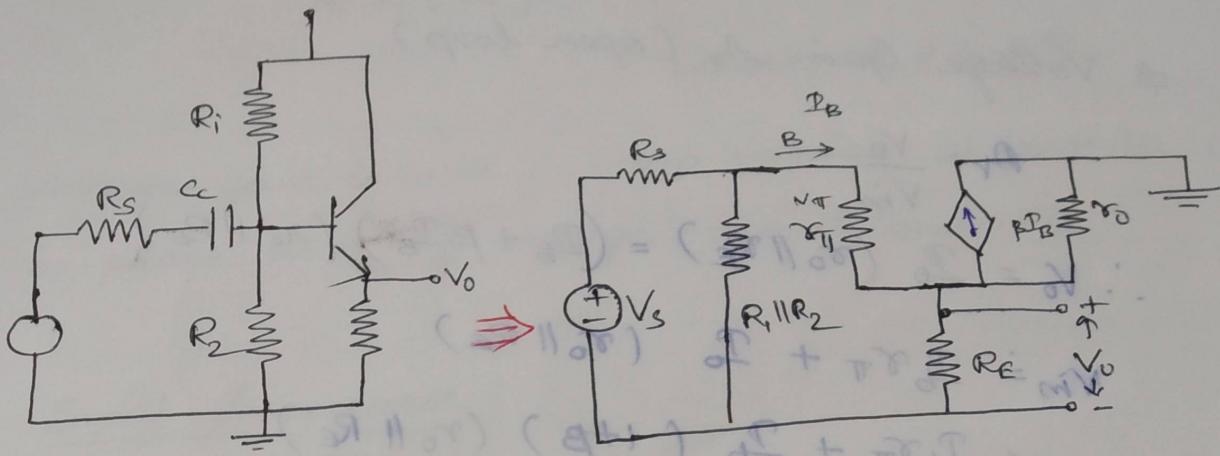

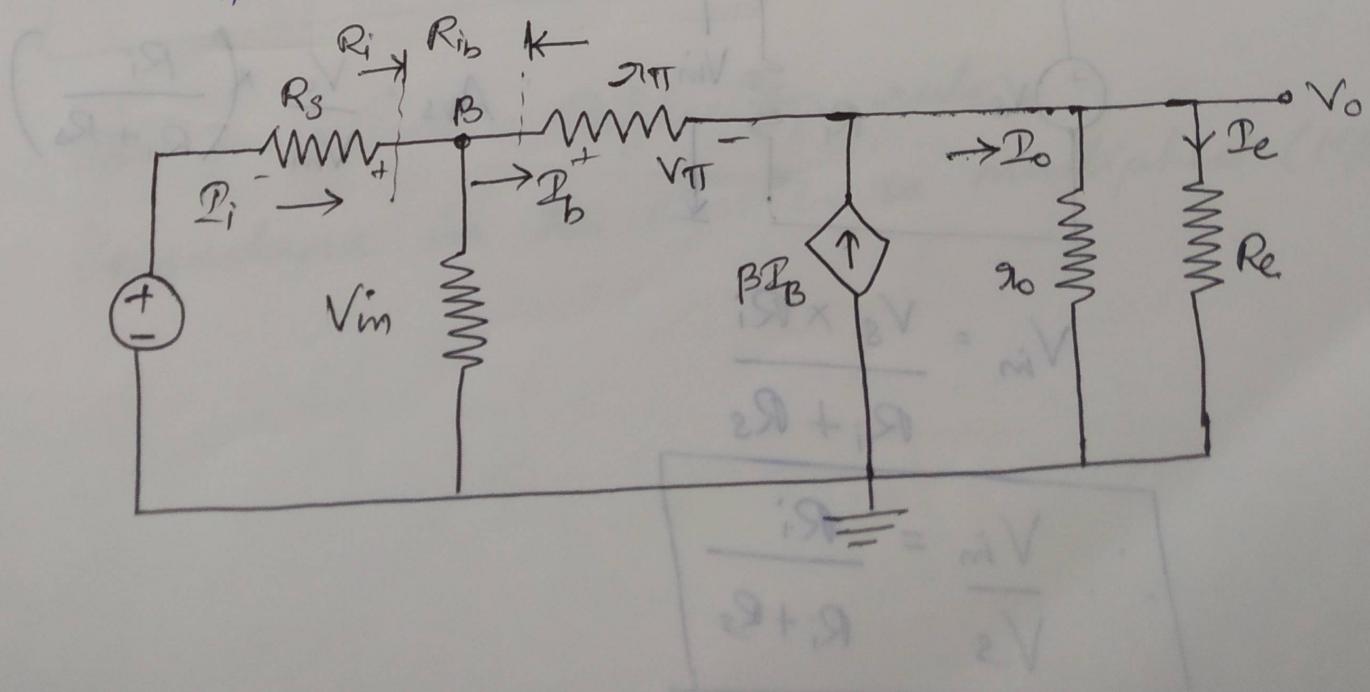- # The op is taken off the emitter with respect to ground and collector is connected to  $V_{CE}$ .
- # since  $V_{CE}$  is at signal ground in ac equivalent circuit, we have the name common collector
- # It is known as emitter follower, because the emitter voltage follows the voltage at the base terminal.
- # low op resistance & high  $\beta_p$  resistance



$$g_m = \frac{I_{CQ}}{\sqrt{T}} = \text{?}$$

# Voltage Gain  $A_v$  (open loop)

$$A_V = \frac{V_o}{V_m}$$

$$\therefore V_o = I_o (\tau_0 \parallel R_E) = (I_b + \beta I_B) (\tau_0 \parallel R_E)$$


$$V_m = I_b \tau_{\pi} + I_o (\tau_0 \parallel R_E)$$

$$= I_b \tau_{\pi} + I_b (1+\beta) (\tau_0 \parallel R_E)$$

$$\therefore A_V = \frac{V_o}{V_m} = \frac{I_b (1+\beta) (\tau_0 \parallel R_E)}{I_b (\tau_{\pi} + (1+\beta) (\tau_0 \parallel R_E))}$$

$$\boxed{A_V = \frac{(1+\beta) (\tau_0 \parallel R_E)}{\tau_{\pi} + (1+\beta) (\tau_0 \parallel R_E)}}$$

# loop gain (closed loop)

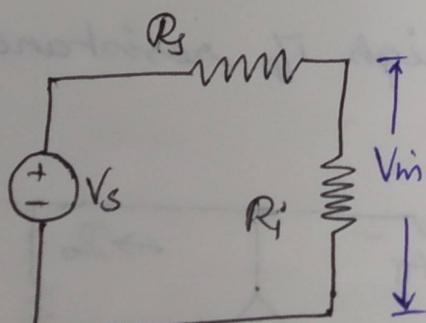

$$A_{VS} = \frac{V_o}{V_s} = \frac{V_o}{V_m} \times \frac{V_m}{V_s}$$

$$\therefore A_{VS} = \frac{V_o}{V_m} \times \left( \frac{R_i}{R_i + R_s} \right)$$

$$V_m = \frac{V_s \times R_i}{R_i + R_s}$$

$$\boxed{\therefore \frac{V_m}{V_s} = \frac{R_i}{R_i + R_s}}$$

$$A_{vE} = \frac{(1+\beta) (r_o \parallel R_E)}{r_{\pi} + (1+\beta) (r_o \parallel R_E)} * \frac{R_i}{R_i + R_s},$$

where  $R_1 \parallel R_2 \parallel R_{ib}$ .

- Voltage gain is +ve.  $\therefore$  o/p voltage at emitter is in phase with i<sub>P</sub> voltage. o/p follows i<sub>P</sub>

### # Input Impedance

$$R_i = R_1 \parallel R_2 \parallel R_{ib}.$$

$$\therefore R_{ib} = \frac{V_{in}}{I_b}$$

$$\begin{aligned} V_{in} &= I_b r_{\pi} + I_o (r_o \parallel R_E) \\ &= I_b r_{\pi} + (I_b + \beta I_B) (r_o \parallel R_E) \\ &= I_b [r_{\pi} + (1+\beta) r_o \parallel R_E] \end{aligned}$$

$$\therefore \frac{V_{in}}{I_b} = r_{\pi} + (1+\beta) r_o \parallel R_E = R_{ib}.$$


$$\boxed{\therefore R_i = R_1 \parallel R_2 \parallel r_{\pi} + (1+\beta) r_o \parallel R_E}$$

This is called, Reflection rule.

Impedance in the emitter is multiplied by  $(1+\beta)$
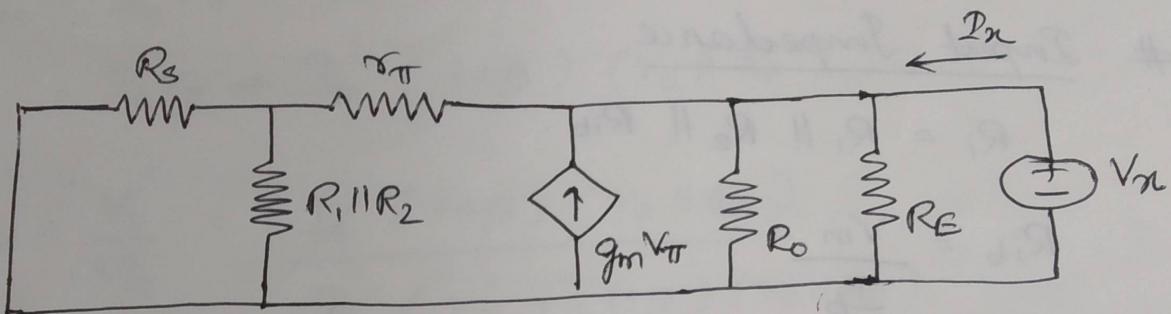
## # Output Impedance ( $R_o$ )

The independant voltage source is set to zero ( $V_S = 0$ ). A test voltage  $V_x$  is applied to the op terminals and the resulting test current is  $I_x$ .




$$\beta I_B = g_m V_\pi$$

$$R_o = \frac{V_x}{I_x}$$

Applying KCL at op

$$I_x + g_m V_\pi = \frac{V_x}{R_E} + \frac{V_x}{R_o} + \frac{V_x}{r_\pi + (R_s || R_1 || R_2)} \quad \text{--- (1)}$$

$$V_\pi = \frac{-V_x * r_\pi}{r_\pi + (R_s || R_1 || R_2)}$$

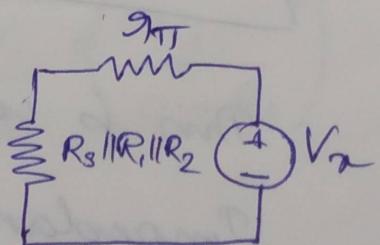

$$I_x = \frac{V_x g_m r_\pi}{r_\pi + (R_s || R_1 || R_2)} + \frac{V_x}{R_E} + \frac{V_x}{R_o} + \frac{V_x}{r_\pi + (R_s || R_1 || R_2)}$$

$$I_n = V_x \left[ \frac{1}{R_E} + \frac{1}{r_o} + \frac{(1 + g_m r_{\pi})}{r_{\pi} + (R_s \parallel R_1 \parallel R_2)} \right]$$

$$I_n = V_x \left[ \frac{1}{R_E} + \frac{1}{r_o} + \frac{1 + \beta}{r_{\pi} + (R_s \parallel R_1 \parallel R_2)} \right]$$

$$R_o = \frac{V_n}{I_n} = R_E \parallel r_o \parallel \frac{r_{\pi} + (R_s \parallel R_1 \parallel R_2)}{1 + \beta}$$

# Emitter follower is sometimes referred to as an impedance transformer, since the i/p impedance is large and o/p impedance is small

# This makes it an ideal voltage source, so the o/p is not loaded when used to drive another load

# This is used as o/p stage in multistage amplifier

# Small signal current gain  $A_i$

$$A_i = \frac{I_e}{I_i};$$

$$I_e = \frac{I_o R_o}{R_o + R_E}$$

$$I_o = I_b + \beta I_b = (1 + \beta) I_b$$

$$I_e = (1 + \beta) I_b \left( \frac{r_o}{r_o + R_E} \right)$$

$$I_b = I_i \times \frac{R_1 \parallel R_2}{R_{I_b} + (R_1 \parallel R_2)} \cdot \cancel{(1 + \beta)}$$

$$I_e = (1+\beta) I_i \cdot \frac{R_1 || R_2}{R_{ib} + (R_1 || R_2)} \cdot \frac{r_o}{r_o + R_E}$$

$$\Rightarrow \frac{I_e}{I_i} = (1+\beta) \cdot \frac{R_1 || R_2}{R_{ib} + (R_1 || R_2)} \cdot \left( \frac{r_o}{r_o + R_E} \right)$$

$$\Rightarrow \boxed{A_i = \frac{I_e}{I_i} = (1+\beta) \frac{R_1 || R_2}{R_{ib} + (R_1 || R_2)} \cdot \frac{r_o}{r_o + R_E}}$$

$$R_1 || R_2 \gg R_{ib} \quad r_o \gg R_E$$

$$\therefore A_i \approx (1+\beta)$$

# The small signal current gain is greater than 1.  $\therefore$  The circuit produces a small power gain.

## Multistage amplifiers


### Need for cascading

- 1) when amplification of single stage amplifier is not sufficient, or
  - 2) when the i/p or o/p impedance is not of correct magnitude for a particular application two or more stages are connected in cascade.
- such an amplifier with two or more stages is known as multistage amplifier.

### Limitations

- 1) The bandwidth of multistage amplifier is always less than that of a single stage amplifier.
- 2) Non-linear distortion is more in a multistage amplifier

## Two stage cascade amplifier

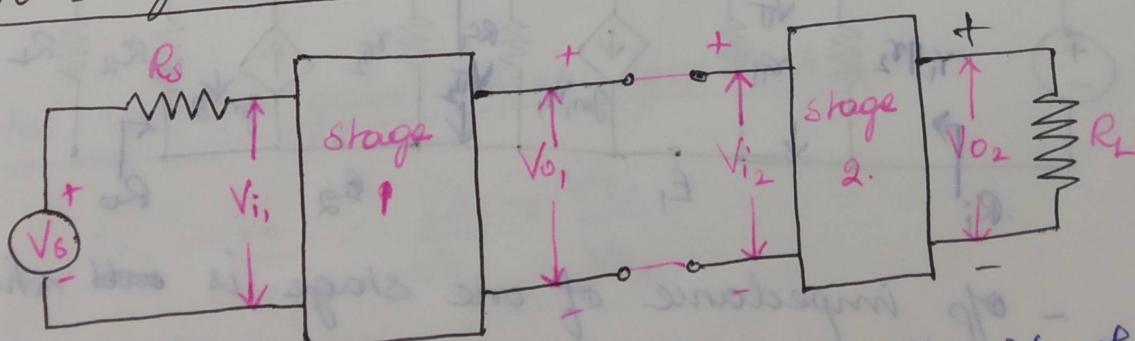

o/p of first stage is connected to the i/p of 2<sup>nd</sup> stage

$$A_v = \frac{V_{o2}}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \times \frac{V_{i2}}{V_{i1}}$$

$$= \frac{V_{o2}}{V_{i2}} \times \frac{V_{o1}}{V_{i1}}$$


$$V_{o1} = V_{i2}$$

$$\boxed{A_v = A_{v2} \cdot A_{v1}}$$


\* Voltage gain of multistage amplifier is the product of voltage gains of the individual stages.
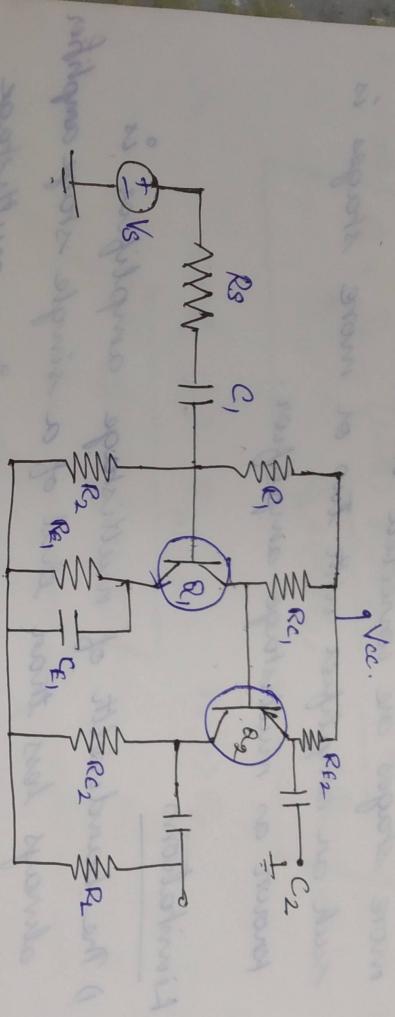
### 2 stage CE amplifier

- \* for ac analysis all capacitors are shorted & each transistors op. resistance ( $r_o$ ) is infinite.



AC equivalent circuit. Stage 1

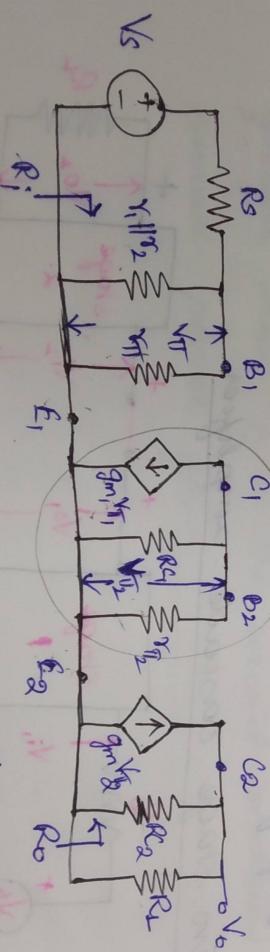

- op. impedance of one stage is ~~not~~ shunted by the input impedance of the next stage.

stage 2 :-

1) 2/p impedance  $R_{i_2}$

$$R_{i_2} = \infty$$

2) Voltage gain  $A_{V_2}$

$$A_{V_2} = \frac{V_o}{V_{\pi_2}} ; V_o = g_{m_2} V_{\pi_2} (R_{C_2} \parallel R_L)$$

$$(V_{in}) \leftarrow A_{V_2} = \frac{V_o}{V_{\pi_2}} = \frac{g_{m_2} V_{\pi_2} (R_{C_2} \parallel R_L)}{\sqrt{\pi_2}}$$

$$\boxed{A_{V_2} = g_{m_2} (R_{C_2} \parallel R_L)}$$

Stage 1 :-

1) Input impedance  $R_{i_1}$

$$R_{i_1} = R_1 \parallel R_2 \parallel \infty$$

2) Voltage gain  $A_{V_1}$

$$A_{V_1} = \frac{V_{\pi_2}}{V_{\pi_1}} = g_{m_1} V_{\pi_1} (R_{C_1} \parallel R_{\pi_2})$$

# Total voltage gain (open loop)  $A_{V_o}$

$$A_{V_o} = \frac{V_o}{V_{\pi_1}} = \frac{V_o}{V_{\pi_2}} \times \frac{V_{\pi_2}}{V_{\pi_1}}$$

$$= \frac{V_o}{V_{\pi_2}} \times \frac{V_{\pi_2}}{V_{\pi_1}}$$

$$= A_{V_1} \times A_{V_2}$$

$$\boxed{A_{V_o} = g_{m_1} (R_{C_1} \parallel R_{\pi_2}) g_{m_2} (R_{C_2} \parallel R_L)}$$

$$AV_s = \frac{V_o}{V_s} = \frac{V_o}{V_{T_2}} \times \frac{V_{T_2}}{V_{T_1}} \times \frac{V_{T_1}}{V_s}$$

$$= AV_2 \times AR_1 \times \frac{R_i}{R_i + R_s}$$

$$\therefore AV_s = g_m g_{m_2} (\gamma_C \parallel \gamma_{T_2}) (\gamma_{T_1} \parallel \gamma_L) \frac{R_i}{R_i + R_s}$$

3) O/p resistance ( $R_o$ )

$$R_o \approx RC_2$$

$$(AV_2 \parallel R_1 \parallel R_s) \text{ o/p } = \frac{AV_2}{1 + AV_2}$$

o/p (goal page) ncp section total \*

$$\frac{AV_2}{1 + AV_2} \times \frac{oV}{AV_2} = \frac{oV}{1 + AV_2} = oVA$$

$$\frac{AV_2}{1 + AV_2} \times \frac{oV}{AV_2} =$$

$$oVA \times MA$$

$$(C_2 \parallel C_3) \text{ o/p } (AV_2 \parallel R_1 \parallel R_s) \text{ o/p } = oVA$$

## Darlington Transistors.

- \* high input resistance
- \* improves current gain.

Small signal current gain  $A_i$

$$A_i = \frac{I_o}{I_i}$$

$$I_o = g_{m2}V_{\pi_2} + g_{m1}V_{\pi_1}$$

$$V_{\pi_1} = I_i V_{\pi_1}$$

$$\sqrt{V_{\pi_2}} = (I_i + g_{m1}V_{\pi_1}) \sqrt{V_{\pi_2}}$$

$$= (I_i + I_i g_{m1} \beta_1) \sqrt{V_{\pi_2}}$$

$$= (I_i + I_i \beta_1) \sqrt{V_{\pi_2}}$$

$$\sqrt{V_{\pi_2}} = I_i \sqrt{V_{\pi_2}} + I_i \beta_1 \sqrt{V_{\pi_2}}$$

Sub  $V_{\pi_1} + V_{\pi_2}$  in  $I_o$

$$\therefore I_o = g_{m2} (I_i \sqrt{V_{\pi_2}} + I_i \beta_1 \sqrt{V_{\pi_2}}) + g_{m1} I_i V_{\pi_1}$$

$$= I_i g_{m2} \sqrt{V_{\pi_2}} + I_i \beta_1 g_{m2} \sqrt{V_{\pi_2}} + I_i g_{m1} V_{\pi_1}$$

$$= I_i [\beta_2 + \beta_1 \beta_2 + \beta_1]$$

$$A_i = \frac{I_o}{I_i} = \beta_1 + \beta_2 + \beta_1 \beta_2$$

$$A_i = \beta_1 \beta_2$$

The overall current gain of a darlington pair is the product of individual current gains

↓ saturation off all

is very difficult



↓ more input

current required

$$-R_{\pi,2} = R_{\pi,1}$$

$$-R_{\pi,1} = R_{\pi,2}$$

$$-R_{\pi,1} - R_{\pi,2} = R$$

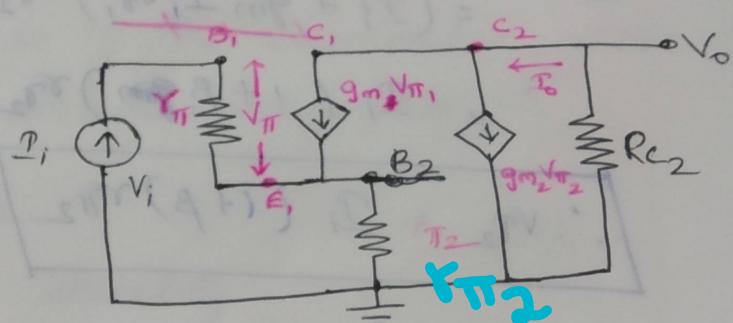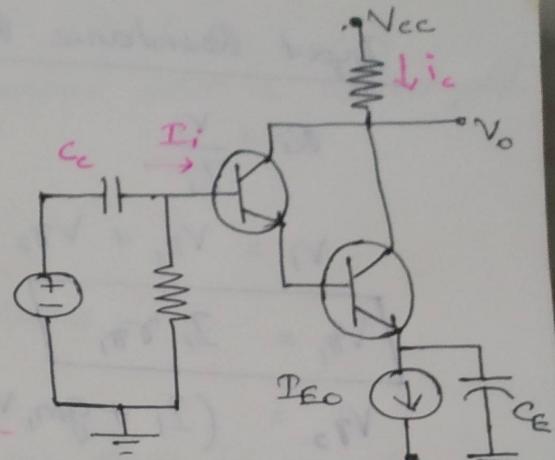

### Input Resistance $R_i$

$$R_i = \frac{V_i}{I_i}$$

$$V_i = V_{\pi_1} + V_{\pi_2}$$

$$\boxed{V_{\pi_1} = I_i \gamma_{\pi_1}}$$

$$\begin{aligned} V_{\pi_2} &= (I_i + g_m V_{\pi_1}) \gamma_{\pi_2} \\ &= (I_i + g_m I_i \gamma_{\pi_1}) \gamma_{\pi_2} \\ &= I_i (1 + \beta_1) \gamma_{\pi_2} \end{aligned}$$

$$g_m \gamma_{\pi} = \beta$$

$$\boxed{\therefore V_{\pi_2} = I_i (1 + \beta_1) \gamma_{\pi_2}}$$

Sub  $V_{\pi_1} + V_{\pi_2}$  in  $V_i$

$$\begin{aligned} V_i &= I_i \gamma_{\pi_1} + I_i (1 + \beta_1) \gamma_{\pi_2} \\ &= I_i (\gamma_{\pi_1} + [1 + \beta_1] \gamma_{\pi_2}) \end{aligned}$$

$$\boxed{R_i = \frac{V_i}{I_i} = \left[ \gamma_{\pi_1} + (1 + \beta_1) \gamma_{\pi_2} \right]}$$

$$\gamma_{\pi_1} = \frac{\beta_1}{g_m} = \frac{\beta V_T}{I_{CQ_1}}$$

$$\text{Let } I_{CQ_1} = \frac{I_{CQ_2}}{\beta_2}$$

$$\gamma_T = \frac{\beta_1 V_T \cdot \beta_2}{I_{CQ_2}}$$

$$\gamma_T = \beta_1 \gamma_{\pi_2}$$

$$R_i = \beta_1 \gamma_{\pi_2} + (1 + \beta_1) \gamma_{\pi_2}$$

$$\boxed{R_i \approx 2 \beta_1 \gamma_{\pi_2}}$$

The i/p resistance of darlington pair is large because of  $\beta$  multiplication

## Cascode Amplifier


- # It has a CE stage in series with a CB amplifier.
- #  $\alpha_1 = \text{CE}$ ;  $\alpha_2 = \text{CB}$ .

Features :-


- # It provides high  $\text{I}_p$  impedance.
- # High voltage gain
- # Improved  $\text{I}_p - \text{O}_p$  isolation as there is no direct coupling from  $\text{O}_p$  to  $\text{I}_p$ . This eliminates Miller effect and thus provides much BW.
- # high  $\text{O}_p$  resistance.
- # high slew rate & stability

Disadvantages.

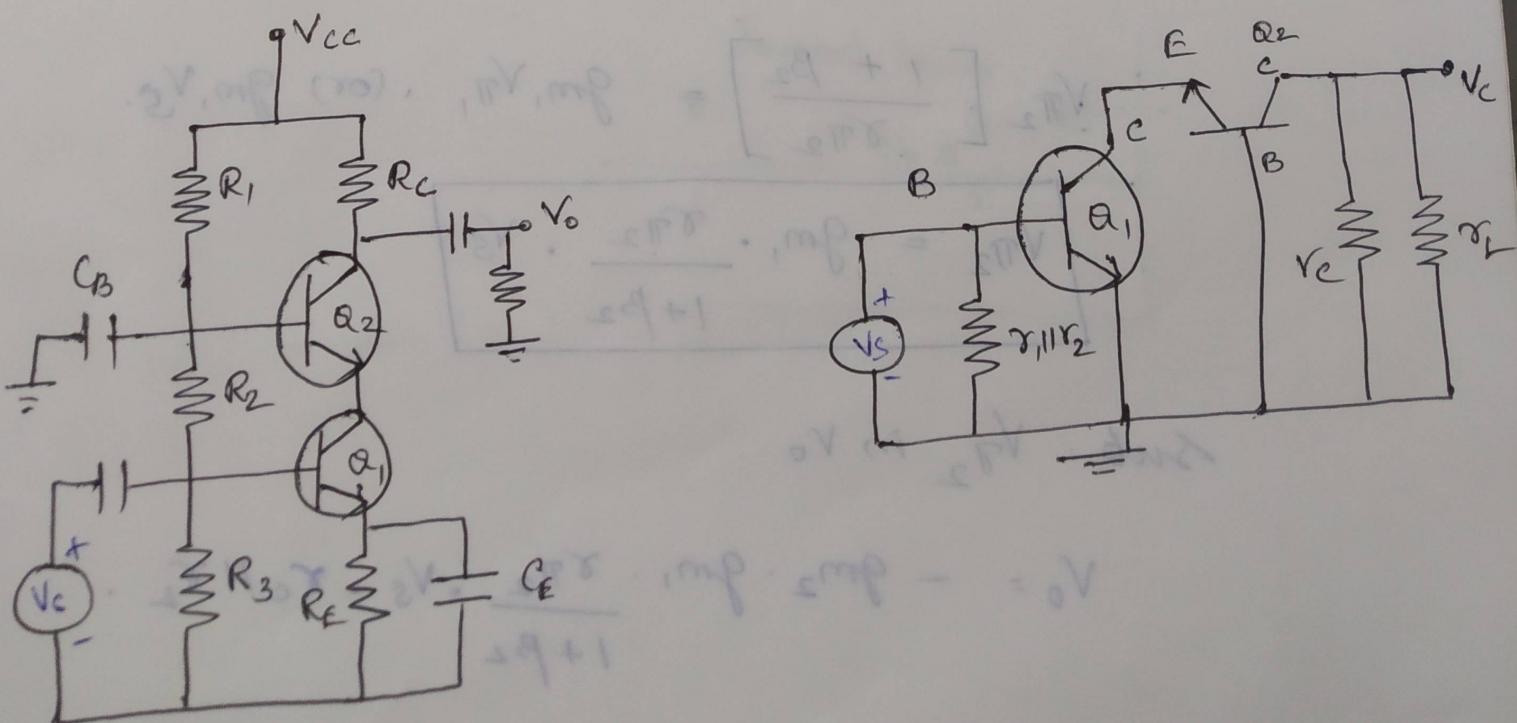- # high supply voltage is required &
- # need for 2 transistors.



AC equivalent circuit diagram.

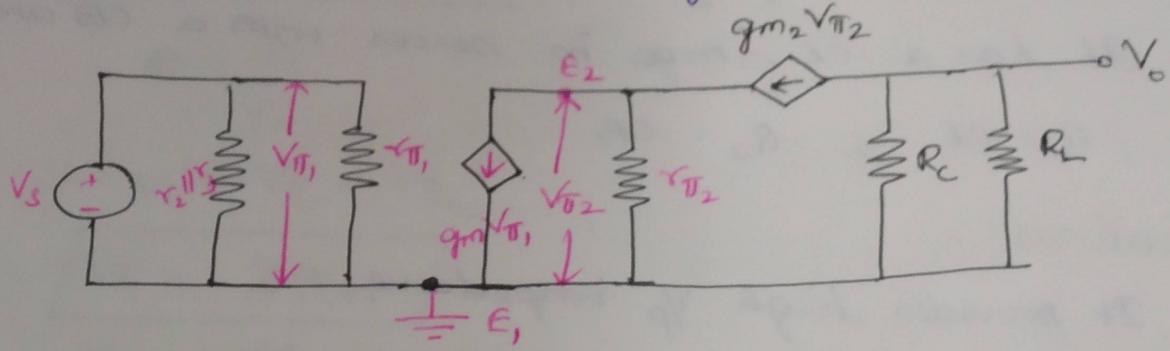

To find voltage gain  $A_V$

$$A_V = \frac{V_0}{V_S} ; V_0 = -gm_2 V_{\pi_2} (r_C \parallel r_L)$$

~~$$V_S = V_{\pi_1}$$~~

apply KCL to  $\epsilon_2$

$$gm_2 V_{\pi_2} + \frac{V_{\pi_2}}{r_{\pi_2}} = gm_1 V_{\pi_1} = gm_1 V_S$$

$$\therefore V_{\pi_2} \left[ gm_2 + \frac{1}{r_{\pi_2}} \right] = gm_1 V_{\pi_1} = gm_1 V_S$$

$$\therefore V_{\pi_2} \left[ \frac{1 + \beta_2}{r_{\pi_2}} \right] = gm_1 V_{\pi_1} . \text{(or)} gm_1 V_S$$

$$V_{\pi_2} = gm_1 \cdot \frac{r_{\pi_2}}{1 + \beta_2} \cdot V_S$$

Sub.  $V_{\pi_2}$  in  $V_0$

$$V_0 = -gm_2 \cdot gm_1 \cdot \frac{r_{\pi_2}}{1 + \beta_2} \cdot V_S \cdot r_C \parallel r_L$$


$$\therefore A_V = \frac{V_0}{V_s} = -g m_1 g m_2 \frac{\infty_{\pi_2}}{1 + \beta_2} (\infty_c / (\infty_L))$$

$$= -g m_1 (g m_2 \frac{\infty_{\pi_2}}{1 + \beta_2}) (\infty_c / (\infty_L))$$

$$A_V = \frac{V_0}{V_s} = -g m_1 \cdot \frac{\beta_2}{1 + \beta_2} (\infty_c / (\infty_L))$$

$$\left[ \because \beta_2 / (\beta_2 + 1) \approx 1 \right]$$


$$A_V = -g m_1 (\infty_c / (\infty_L))$$

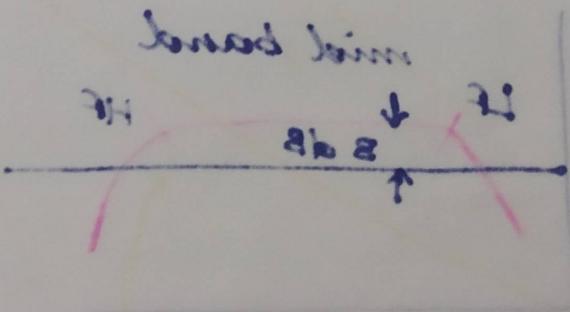

## Frequency Response analysis of Basic BJT CE amplifier
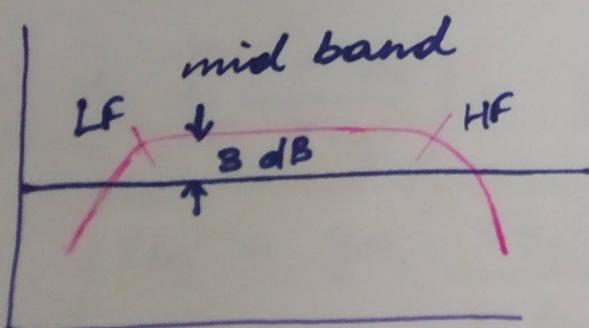
### Amplifier frequency response.

- \* All amplifier gain factors are functions of signal frequency.
- \* we have assumed that the signal frequency is high enough such that, coupling and bypass capacitors can be treated as short circuit and at the same time signal frequency is low enough such that the transistor capacitors and stray capacitors are open circuit



## Three ranges of frequency

1) Low frequency range:- ( $f < f_L$ )

The gain decreases as frequency decreases, because of coupling and bypass capacitors effects.

2) High frequency range:- ( $f > f_R$ )

stray capacitance and transistor capacitance effects cause gain to decrease as the frequency increases.

3) Midband range:-

Coupling and bypass capacitors act as short circuit and stray and transistors 'c' acts as open circuit. Gain is constant.



$$BW = f_H - f_L$$

$$\boxed{2V_{out} - = (2)V}$$

$$P_{out} = IV$$

frequency response: Transistor amplifier with capacitor circuit.

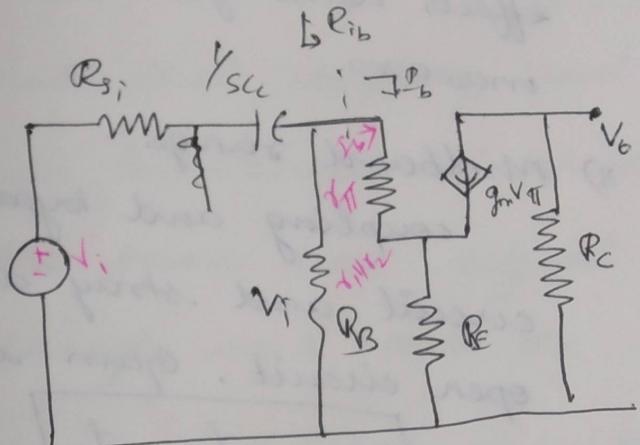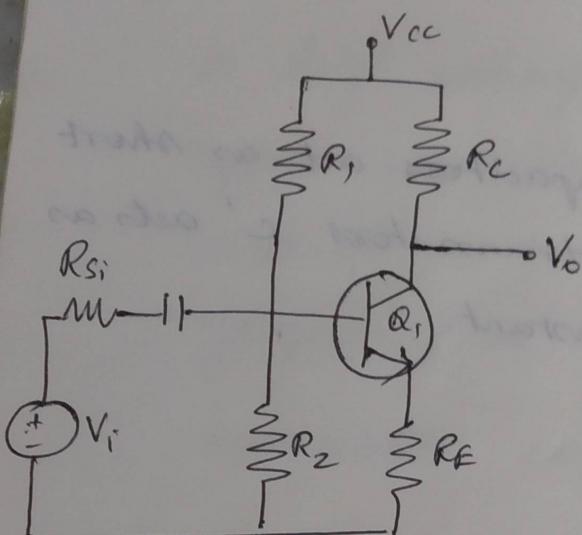- coupling
- bypass
- + load capacitor @ high frequencies.



To determine the transfer  $R_B = R_1 \parallel R_2$

To find  $A_{v(s)}$ )

$$A_{v(s)} = \frac{V_o(s)}{V_i(s)}$$

$V_o(s) = -g_m V_T R_c$

$$V_T = \beta_b V_T$$

from T/p circuit

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$R_{ib} = \frac{V_{i_1}}{I_b} \Rightarrow V_{i_1} = V_T + (I_b + g_m V_T) R_E$$


$$= I_b r_T + (I_b + g_m I_b r_T) R_E$$

$$= I_b [r_T + (1+\beta) R_E]$$

$$\boxed{\frac{V_{i_1}}{I_b} = r_T + (1+\beta) R_E}$$


$$R_i = R_1 \parallel R_2 \parallel r_T + (1+\beta) R_E$$

To find  $I_b$  in terms of  $I_i$

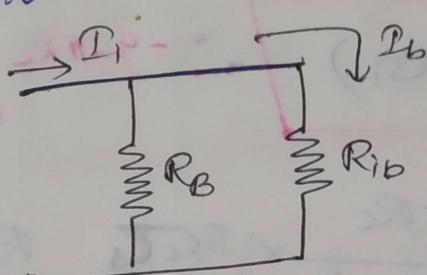

$$I_b = I_i \times \frac{R_B}{R_B + R_{ib}}$$

To find  $I_i$  in terms of  $V_i$

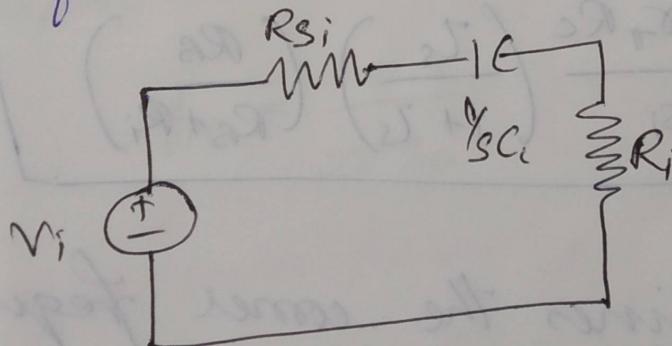

$$V_i = I_i R_{si} + \frac{I_i}{S C} + I_i R_i$$

$$= I_i \left[ R_{si} + \frac{1}{S C} + R_i \right]$$

$$\boxed{I_i = \frac{V_i}{R_{si} + R_i + \frac{1}{S C}}}$$

sub  $I_i$  in  $V_o$ .

$$V_o = -g_m R_C \circled{I_b} r_T$$

sub  $I_b$  in  $V_o$

$$V_o = -g_m R_C \cdot \frac{I_i R_B}{R_B + R_{ib}} \cdot r_T$$

sub  $P_i$  in  $V_o$ ,

$$\therefore V_o = -g_m R_c \cdot \frac{V_i}{(R_{S_i} + R_i) + \frac{1}{SC_c}} \cdot \frac{R_B}{R_B + R_{iB}} \cdot \gamma_T$$

$$f = \frac{1}{2\pi R C} = -g_m R_c \cdot \gamma_T \cdot \frac{V_i (SC_c)}{1 + SC_c (R_{S_i} + R_i)} \cdot \frac{R_B}{R_B + R_{iB}}$$

$$\omega = \frac{1}{2\pi (R_S + R_i)} \text{ rad/s} \quad \text{ie } \frac{V_o}{V_i} = -g_m \gamma_T \frac{R_c \cdot SC_c}{1 + SC_c (R_{S_i} + R_i)} \cdot \frac{R_B}{R_B + R_{iB}}$$

Let  $T_s = SC_c (R_i + R_{S_i})$   $\therefore -g_m \pi R_c \cdot \frac{SC_c}{1 + T_s} \cdot \frac{R_B}{R_B + R_i}$


$$A_V = \frac{V_o}{V_i} = \frac{-g_m \pi R_c}{C_c (R_i + R_{S_i})} \times \frac{SC_c T_s}{1 + T_s} \cdot \frac{R_B}{R_B + R_i}$$

$$A_{V_s} = -\frac{g_m \gamma_T R_c}{R_i + R_{S_i}} \left( \frac{T_s}{1 + T_s} \right) \left( \frac{R_B}{R_B + R_i} \right)$$

$T_s \rightarrow$  determines the corner frequency.

## COUPLING & LOAD CAPACITOR EFFECT
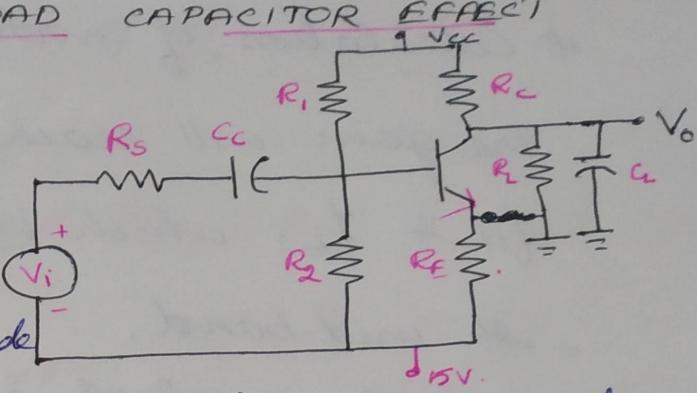
# The values of the coupling & load capacitances differ by orders of magnitude



- The corner frequencies are far apart and can be treated separately.

# Lower order frequency

$$f_L = \frac{1}{2\pi\tau_s} \rightarrow \text{time constant associated with coupling capacitor.}$$

lower corner frequency

$$\tau_s = (R_s + R_1 \parallel R_2 \parallel R_i) C_s$$

# Upper corner frequency

$$f_H = \frac{1}{2\pi\tau_p} \rightarrow \text{time constant associated with load capacitor.}$$

upper corner frequency

$$\tau_p = (R_E \parallel R_L) C_L$$


## \* Calculation of midband gain

The gain will reach maximum between  $f_H$  &  $f_L$ , which is the mid-band.

- At mid-band,

$e_c \rightarrow$  short circuited

$c_L \rightarrow$  open circuited

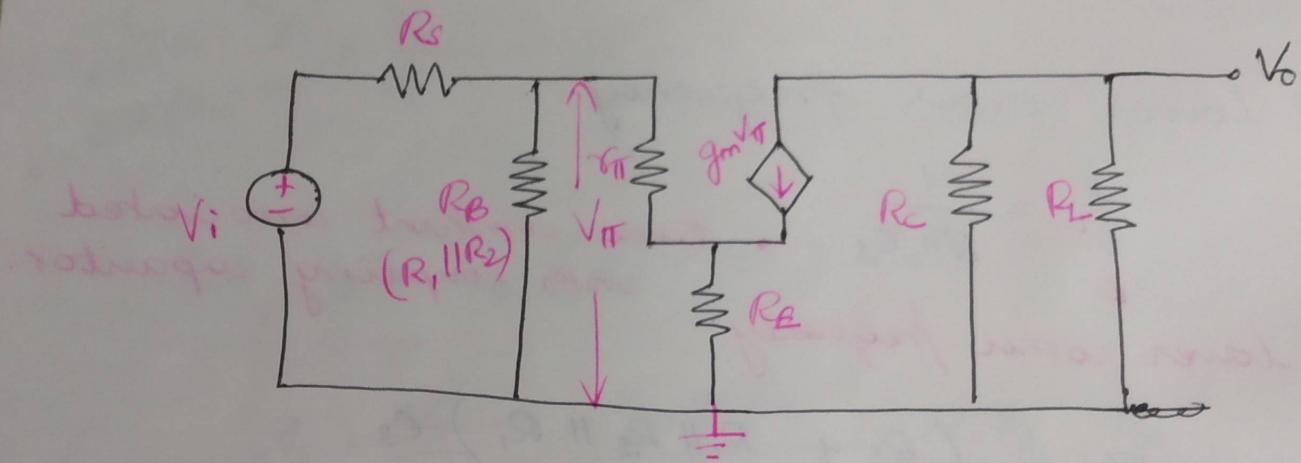

$$\text{Midband gain } A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m \cdot V_\pi \cdot (R_C \parallel R_L)$$


$$= -g_m \cdot \underline{I_b} \cdot V_\pi \cdot (R_C \parallel R_L)$$

$$\underline{I_b} = \frac{I_i \times R_B}{R_B + \underline{R_{ib}}}$$

$$\underline{R_{ib}} = V_\pi + (1 + \beta) R_E$$

$$\therefore V_o = -g_m \cdot V_\pi (R_C \parallel R_L) \cdot \underline{I_i} \cdot \frac{R_B}{R_B + \underline{R_{ib}}}$$

- To find  $I_i$  in terms of  $V_i$

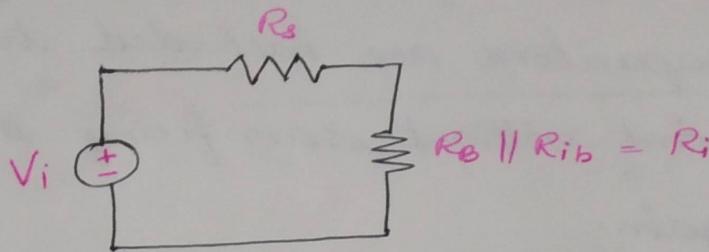

$$\therefore V_i = I_i (R_s + R_i)$$

$$\boxed{I_i = \frac{V_i}{R_s + R_i}}$$

sub in  $V_o$ :

$$\therefore V_o = -g_m \cdot r_{\pi} (R_C \parallel R_L) \cdot \frac{V_i}{R_s + R_i} \cdot \frac{R_B}{R_B + R_{ib}}.$$

$$\therefore \frac{V_o}{V_i} = -g_m r_{\pi} (R_C \parallel R_L) \cdot \frac{1}{R_s + R_i} \cdot \frac{R_B}{R_B + R_{ib}}.$$

$$\boxed{|Av| = \left| \frac{V_o}{V_i} \right| = g_m r_{\pi} (R_C \parallel R_L) \cdot \frac{1}{R_s + R_i} \cdot \frac{R_B}{R_B + R_{ib}}}.$$



- A figure of merit for an amplifier is the gain - BW product. Assuming the corner frequencies far apart, BW is

$$f_{BW} = f_H - f_L \approx f_H.$$

$$G_{IB} = |Av|_{\max} \cdot f_H.$$
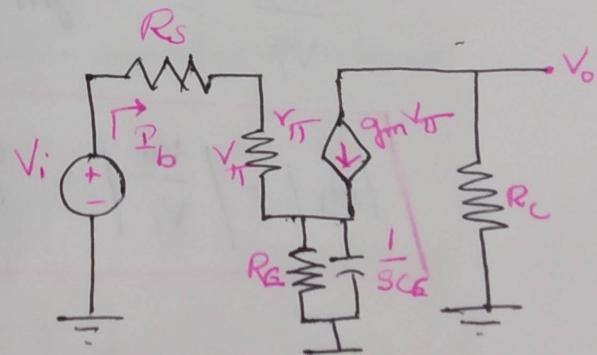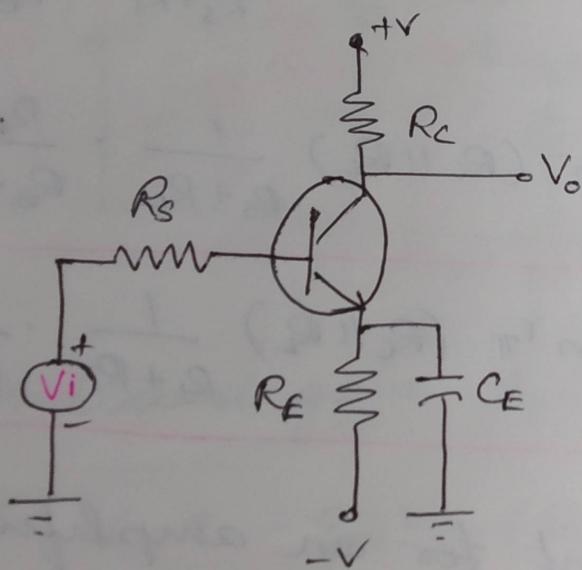
## BYPASS CAPACITOR EFFECT

- Bypass capacitors are included to stabilize the Q point without sacrificing the small signal gain.
- To choose a bypass capacitor we must determine the circuit response in the frequency range where these capacitors neither open nor short circuit.



The transfer function

$$A_v = \frac{V_o(s)}{V_i(s)}$$

$$V_o = -g_m V_T (R_c)$$

$$= -g_m R_b \gamma_T R_c$$

$$V_T = R_b \cdot \gamma_T$$

$$V_i = I_b \left[ R_s + r_{\pi} + \left( R_E \parallel \frac{1}{SCE} \right) (1+\beta) \right]$$

$$\Rightarrow I_b = \frac{V_i}{R_s + r_{\pi} + \left( R_E \parallel \frac{1}{SCE} \right) (1+\beta)}$$

$$\therefore V_o = -g_m \cdot r_{\pi} \cdot R_c \cdot \frac{V_i}{R_s + r_{\pi} + \left( R_E \parallel \frac{1}{SCE} \right) (1+\beta)}$$

$$\therefore \frac{V_o}{V_i} = -g_m \cdot r_{\pi} \cdot R_c \cdot \frac{1}{R_s + r_{\pi} + \left\{ \frac{R_E \cdot \frac{1}{SCE}}{\frac{R_E + \frac{1}{SCE}}{SCE}} \right\} (1+\beta)}$$

$$= -g_m \cdot r_{\pi} \cdot R_c \cdot \frac{1}{R_s + r_{\pi} + \left\{ \frac{R_E \cdot \frac{1}{SCE}}{\frac{SCE R_E + 1}{SCE}} \right\} (1+\beta)}$$

$$= -g_m \cdot r_{\pi} \cdot R_c \cdot \frac{1}{R_s + r_{\pi} + \left\{ \frac{R_E}{R_E SCE + 1} \right\} (1+\beta)}$$

$$= -\frac{g_m \cdot r_{\pi} \cdot R_c \cdot (1 + SCE R_E)}{R_s (1 + SCE R_E) + r_{\pi} (1 + SCE R_E) + R_E (1+\beta)}$$

$$= -\frac{g_m \cdot r_{\pi} \cdot R_c \cdot (1 + SCE R_E)}{R_s + R_s SCE R_E + r_{\pi} + r_{\pi} SCE R_E + R_E (1+\beta)}$$

$$= -\frac{g_m \cdot r_{\pi} \cdot R_c \cdot (1 + SCE R_E)}{R_s + r_{\pi} + R_E (1+\beta) + SCE R_E (R_s + r_{\pi})}$$

@  $w=0$ ,  $C_E$  is open circuited, hence, this eqn straight away goes to the final eqn directly

Taking  $R_s + r_\pi + (1+\beta)R_E$  out, in Dr.

$$\therefore \frac{V_o}{V_i} = \frac{-g_m \cdot r_\pi \cdot R_c (1 + S C_E R_E)}{R_s + r_\pi + (1+\beta)R_E \left[ 1 + \frac{S C_E R_E (R_s + r_\pi)}{R_s + r_\pi + (1+\beta)R_E} \right]}$$

$$\therefore A_v = \frac{-g_m \cdot r_\pi \cdot R_c \cdot (1 + \tau_A)}{R_s + r_\pi + (1+\beta)R_E \cdot (1 + \tau_B)}$$

where  $\tau_A = S C_E R_E$

$$\tau_B = \frac{S C_E R_E (R_s + r_\pi)}{R_s + r_\pi + (1+\beta)R_E}$$

# At  $\omega = 0$ ,  $C_E$  is open circuit.

$$\therefore |A_v|_{\omega=0} = \frac{g_m \cdot r_\pi \cdot R_c}{R_s + r_\pi + (1+\beta)R_E}$$

At  $\omega = \infty$ ,  $C_E$  is short circuited.

$$\therefore |A_v|_{\omega=\infty} = \frac{g_m \cdot r_\pi \cdot R_c}{R_s + r_\pi}$$

$R_E$  is short circuited by  $C_E$ .

# corner frequencies

$$f_A = \frac{1}{2\pi\tau_A}$$

$$f_B = \frac{1}{2\pi\tau_B}$$

