

# BOOTH ENCODING MULTIPLIER

Team Member:

Meng Zhang, Tianyu Feng

Ming Gao, Xintong Li

# OUTLINE.....

1


- Principle introduction

2

- Circuit Estimation

3

- Circuit Design

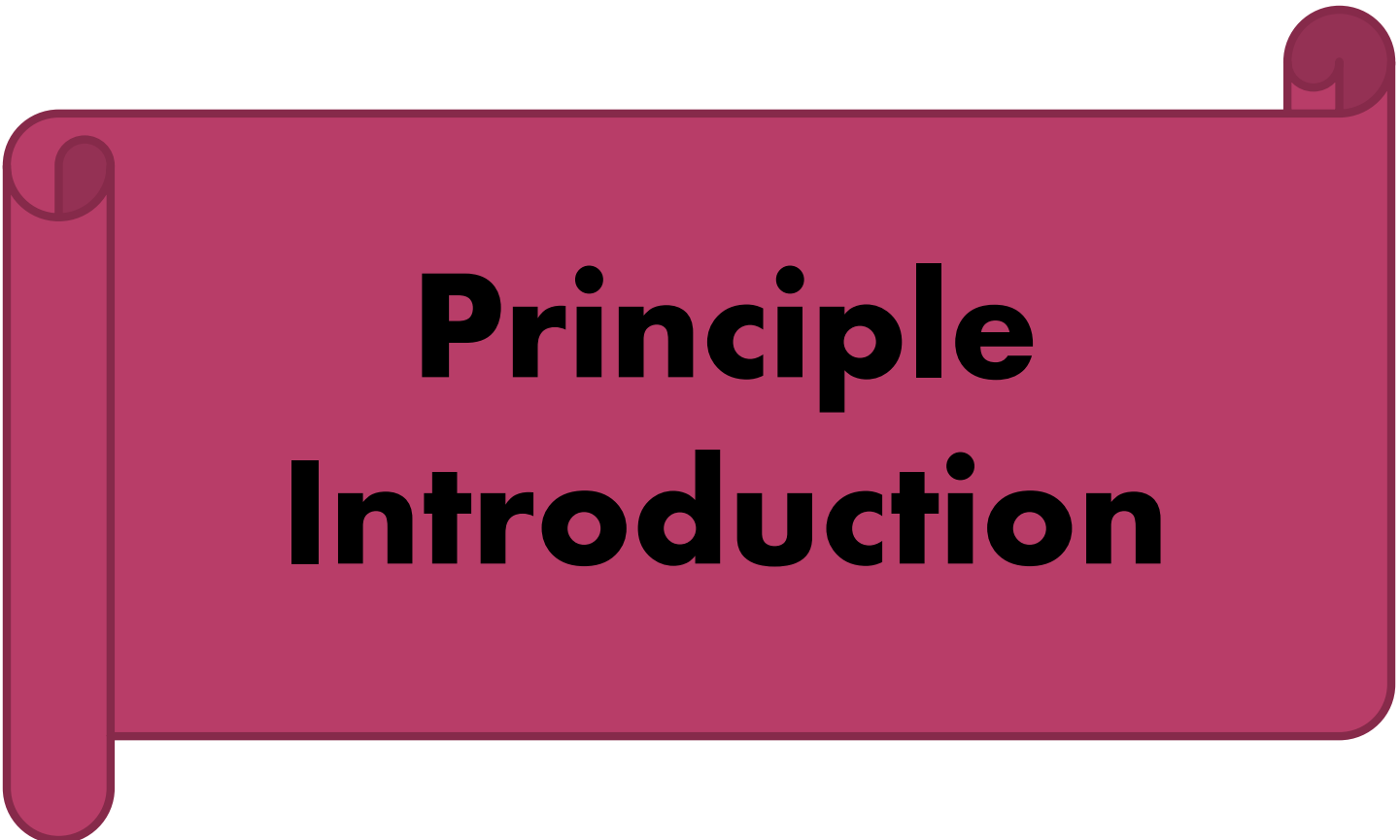


# **Principle Introduction**

# PROJECT SUMMARY

- ◉ In our project, we are aiming to build up a Booth Encoding Radix-4 8 bits Multiplier. Booth Encoding is an effective method which greatly increase the speed of our algebra.
- ◉ We also attempts to reduce the number of partial products generated in a multiplication process by using the modified Booth algorithm

# SYSTEM ARCHITECTURE

 

# ARCHITECTURE DESCRIPTION

The multiplier takes in 2 8-bits operands: the multiplier(MR) and the multiplicand (MD), then produces 16-bit multiplication result of the two as its output.

The architecture comprises four parts: Complement Generator, Booth Encoder, Partial Product and Carry Look-ahead Adder. We adapt the simplest way to demonstrate the multiplier.

# PRINCIPLE INTRODUCTION

## Booth encoder

- Booth's algorithm involves repeatedly adding one of two predetermined values to a product  $P$ , then performing a rightward arithmetic shift on  $P$ .


## Partial Product Generator

- A product formed by multiplying the multiplicand by one digit of the multiplier when the multiplier has more than one digit. Partial products are used as intermediate steps in calculating larger products.

## Carry look-ahead adder

- a type of adder used in digital logic. It can be contrasted with the simpler, but usually slower, *ripple carry adder*

# CHIP FLOORPLAN

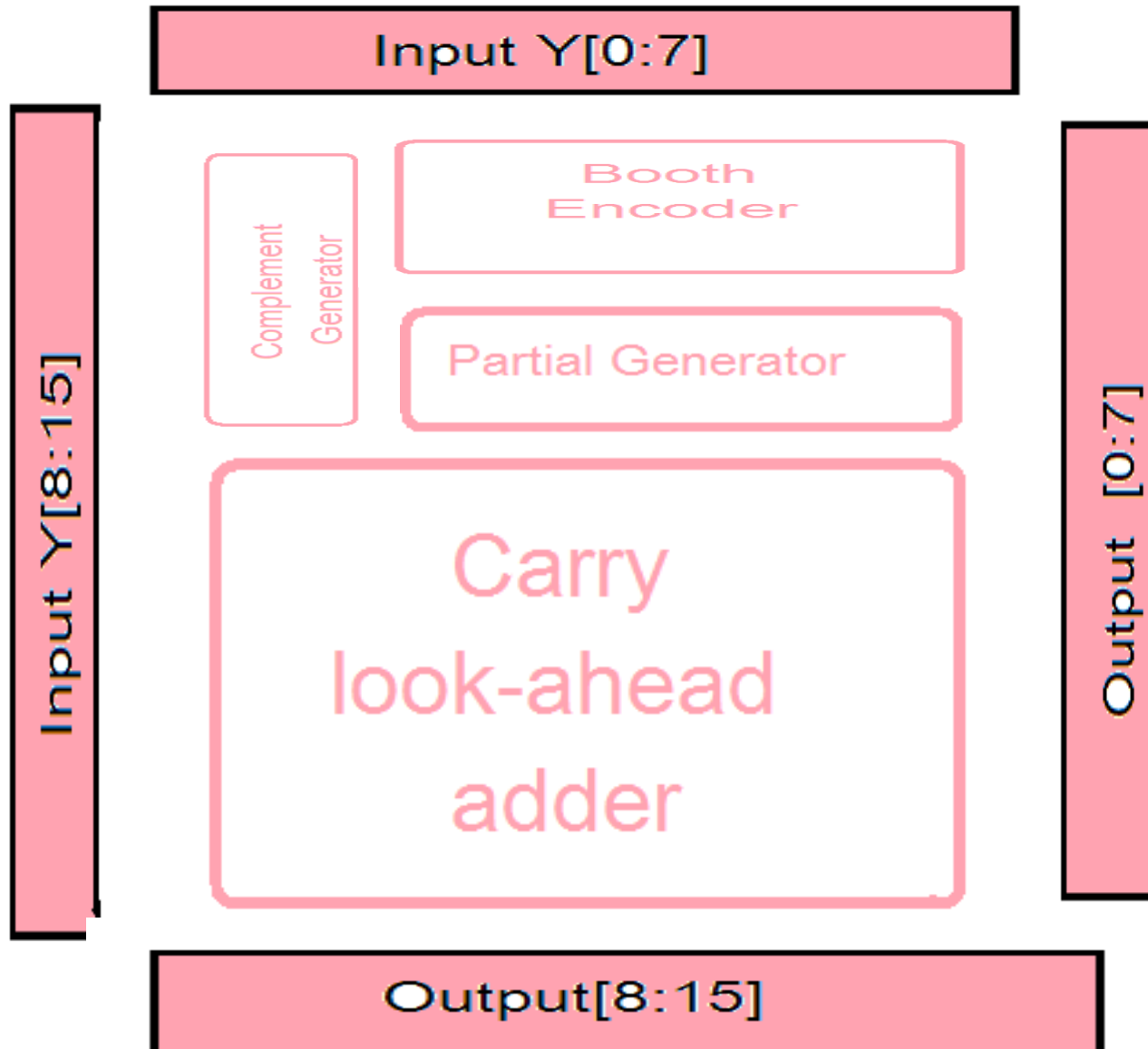



# FULL SYSTEM DESIGN BACKGROUND

- ◉ The multiplier has M-bits X and N-bits Y as input and generate M\*N-bits output Z.

$$X = \sum_{i=0}^{M-1} X_i 2^i$$

$$Y = \sum_{j=0}^{N-1} Y_j 2^j$$

$$Z = X \times Y = \sum_{i=0}^{M-1} \left( \sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right)$$

# FULL SYSTEM DESIGN BACKGROUND

$$X \times 00111110 = X \times (2^5 + 2^4 + 2^3 + 2^2 + 2^1) = X \times 62,$$


The number of partial product and the number of operations can be reduced to two by rewriting the equation as

$$X \times 00111110 = X \times (2^6 - 2^1) = X \times (64 - 2) = X \times 62$$

When Booth encounters the first digit of a block of ones (0 1), it follows this scheme.  
When Booth encounters the end of the block (1 0), it follows a subtraction.
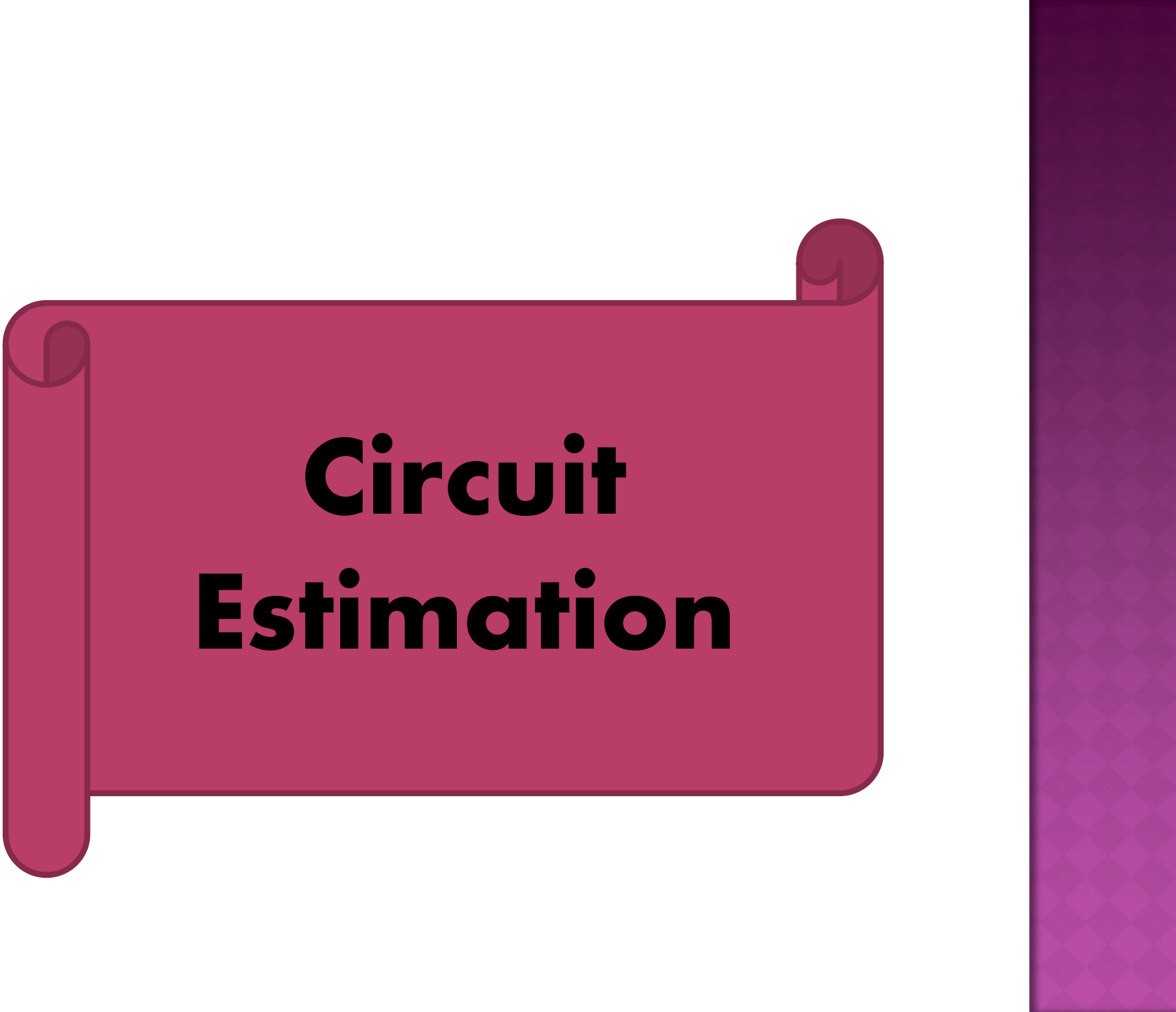
# FULL SYSTEM DESIGN BACKGROUND

- ◉ Booth Encoding algorithm...
- ◉ Do multiplication on both non-negative and negative operand.
- ◉ Decrease the number of partial product, which lead to substantially delay and area reduction.  
Shown as below:



# **Circuit Estimation**

# ESTIMATION:TRANSISTOR

| Gate Type | Transistor # | required # | Total transistor |
|-----------|--------------|------------|------------------|
| AND2      | 6            | 155        | 930              |
| XOR2      | 8            | 248        | 1984             |
| INV       | 2            | 478        | 956              |
| NAND2     | 4            | 263        | 1052             |
| NAND3     | 6            | 268        | 1608             |
| NAND4     | 8            | 175        | 600              |
| OR2       | 6            | 35         | 210              |
| Total     |              |            | 8140             |

# ESTIMATION: POWER & AREA

$$\begin{aligned} P(\text{dynamic}) &= \alpha C V^2 f \\ &= 0.1 * 5354 * 4 * 0.05 * 2 * 5 * 5 * 10^{-9} \\ &= 0.0053 \text{ mw/MHz} \end{aligned}$$

$$\begin{aligned} L &= 4 * 0.05 * 5354 = 1070.8 \text{ } \mu\text{m} \\ I &= 1070.8 * (0.02/2 + 0.002) = 12.8496 \text{ nA} \\ P(\text{static}) &= 5 * 12.8496 = 0.000064248 \text{ mW} \end{aligned}$$

Assuming the frequency is 100 MHz

$$P = 0.53 \text{ mw}$$


$$\text{Area} = 7.76 \text{ cm}^2$$



# Circuit Design

# SUB-CIRCUIT DESIGN


- Booth Encoder-Schematic

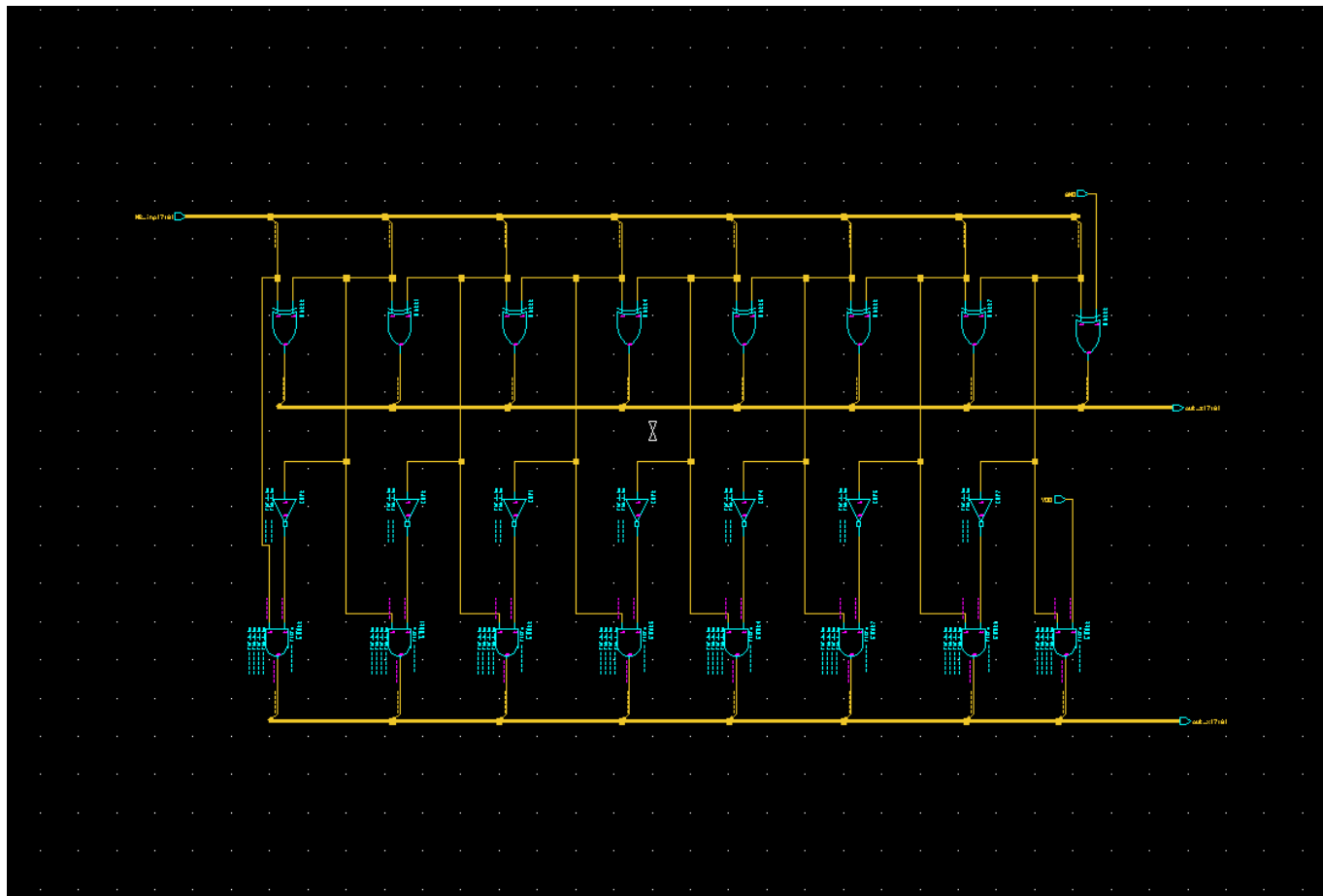




# SUB-CIRCUIT DESIGN

## ⦿ Booth Encoder- Layout

 


# SUB-CIRCUIT DESIGN

## Complement Generator-Schematic

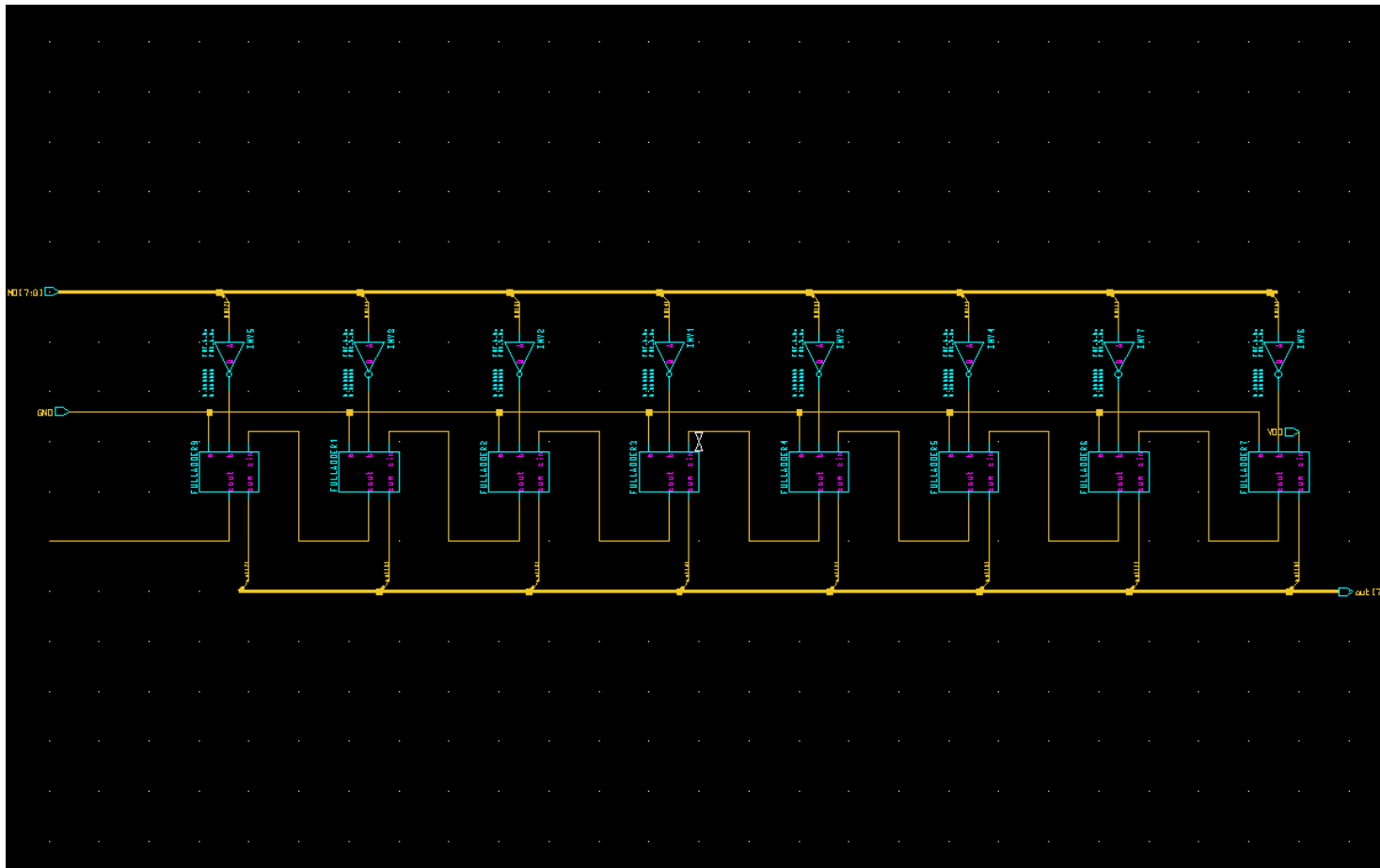


# SUB-CIRCUIT DESIGN

## ◉ Complement Generator-Layout

 


# SUB-CIRCUIT DESIGN

## Partial Products Generator-Schematic

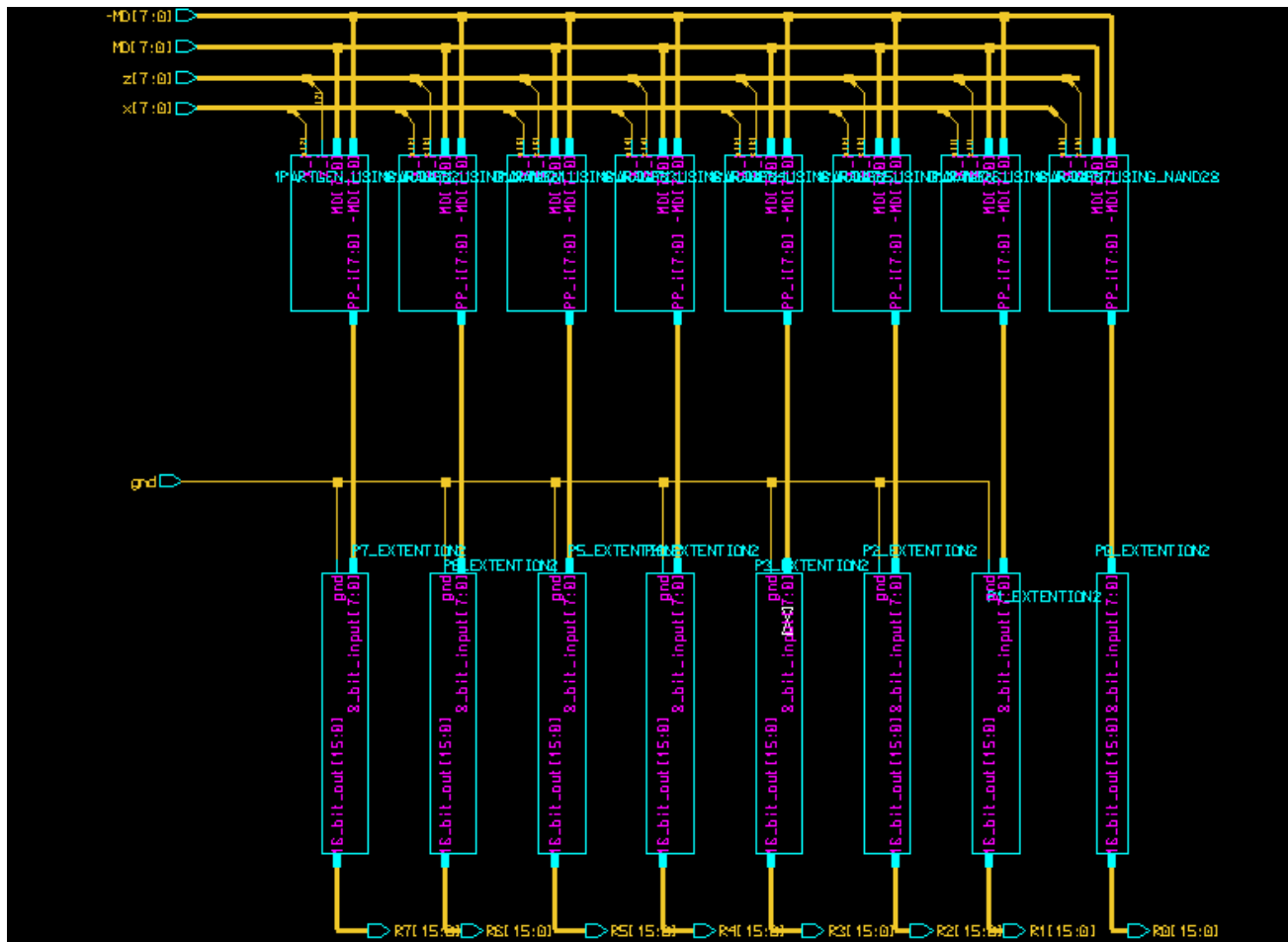


# SUB-CIRCUIT DESIGN

## Partial Products Generator-Layout

 


# SUB-CIRCUIT DESIGN

## ○ Carry Look-ahead Adders-Schematic

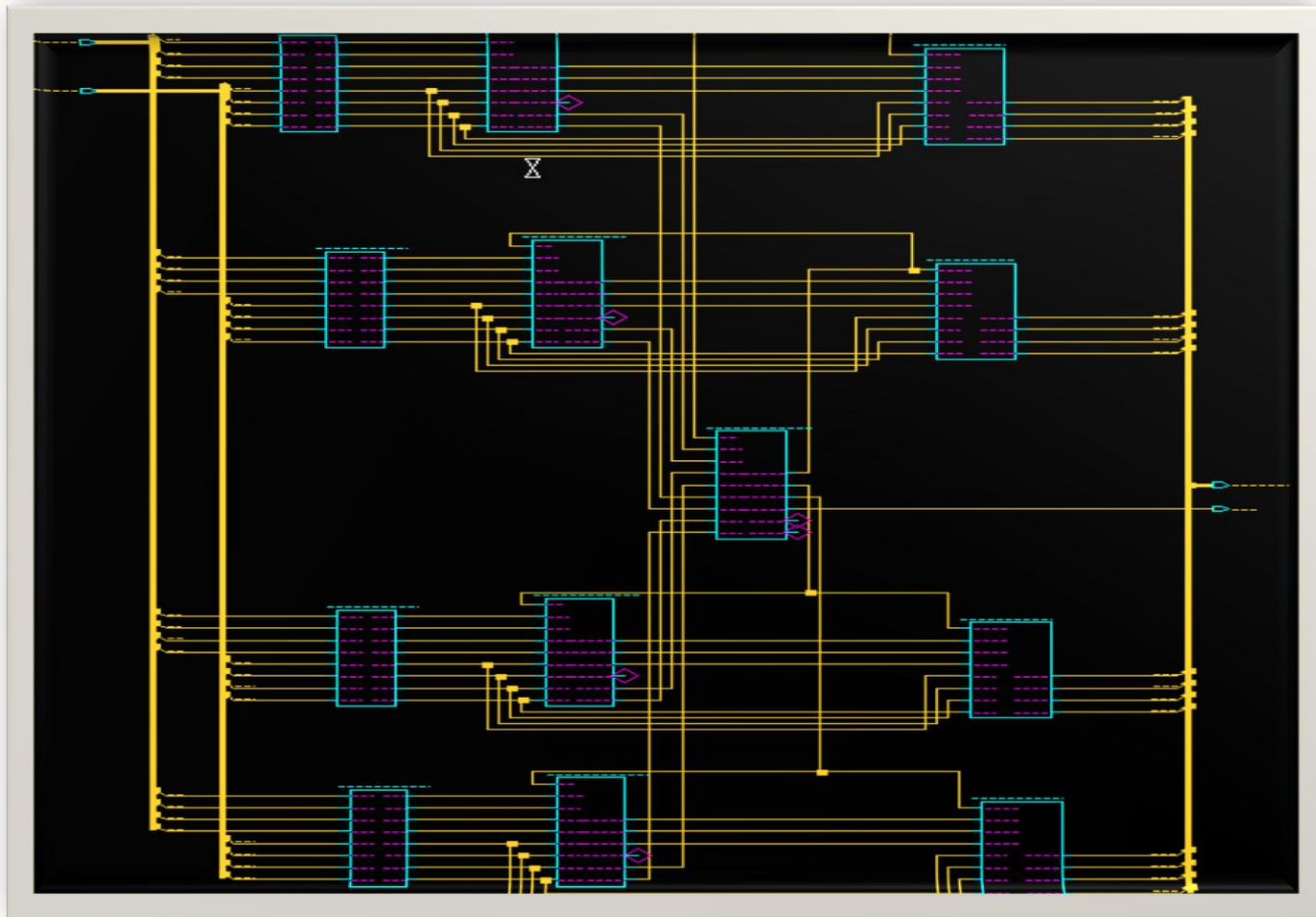


# SUB-CIRCUIT DESIGN

## ◉ Carry Look-ahead Adders-Layout

 

# SUB-CIRCUIT DESIGN


## Sum Generator-Schematic

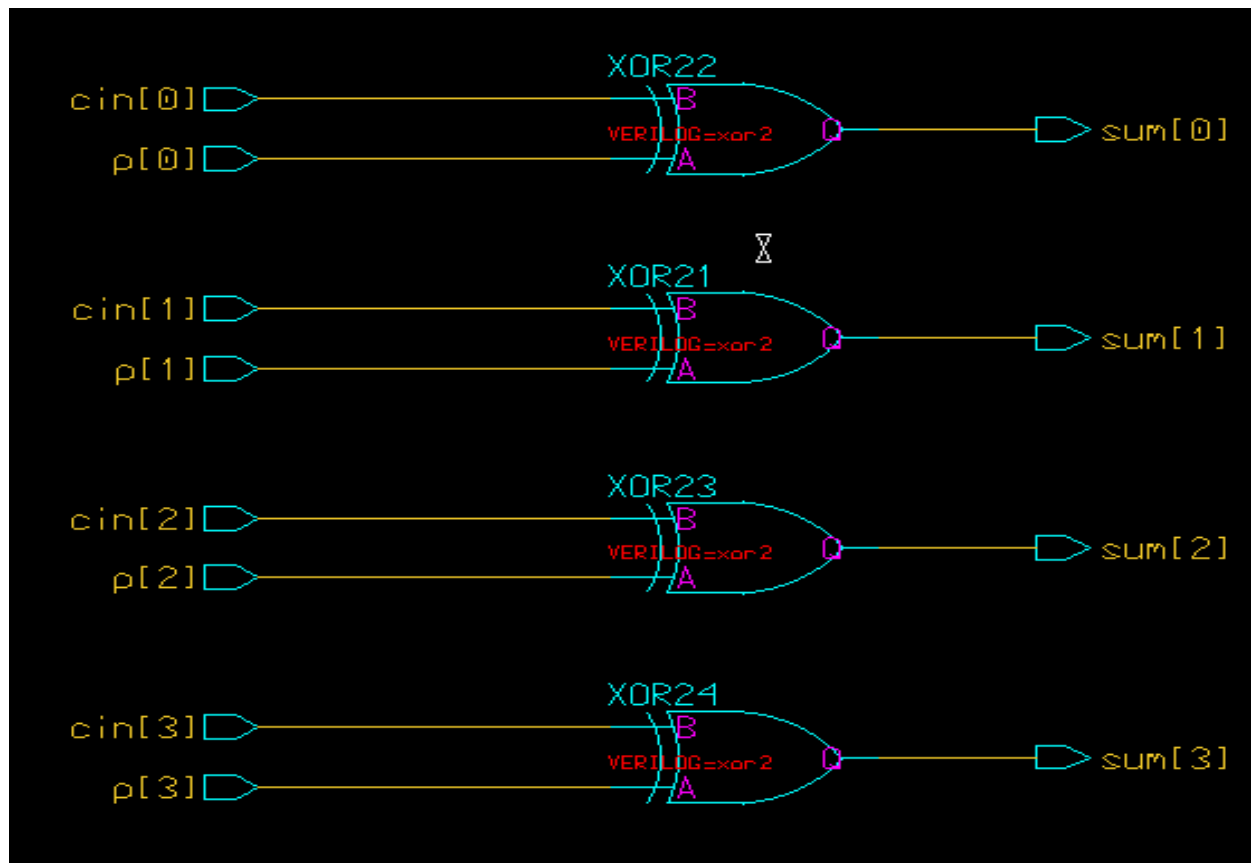




# SUB-CIRCUIT DESIGN

## Sum Generator-Layout

 

# FULL SYSTEM DESIGN


- Full system-schematic

 

# FULL SYSTEM DESIGN

## ◉ Digital simulation

Positive

 


Multiplier:21  
Multiplicand:74  
Product:1554

# FULL SYSTEM DESIGN

## ◉ Digital simulation

Minus

 


Multiplier:12

Multiplicand: -54( $202 - 2^8 = -54$ )


Product: -648( $64888 - 2^{16} = -648$ )

# FULL SYSTEM DESIGN

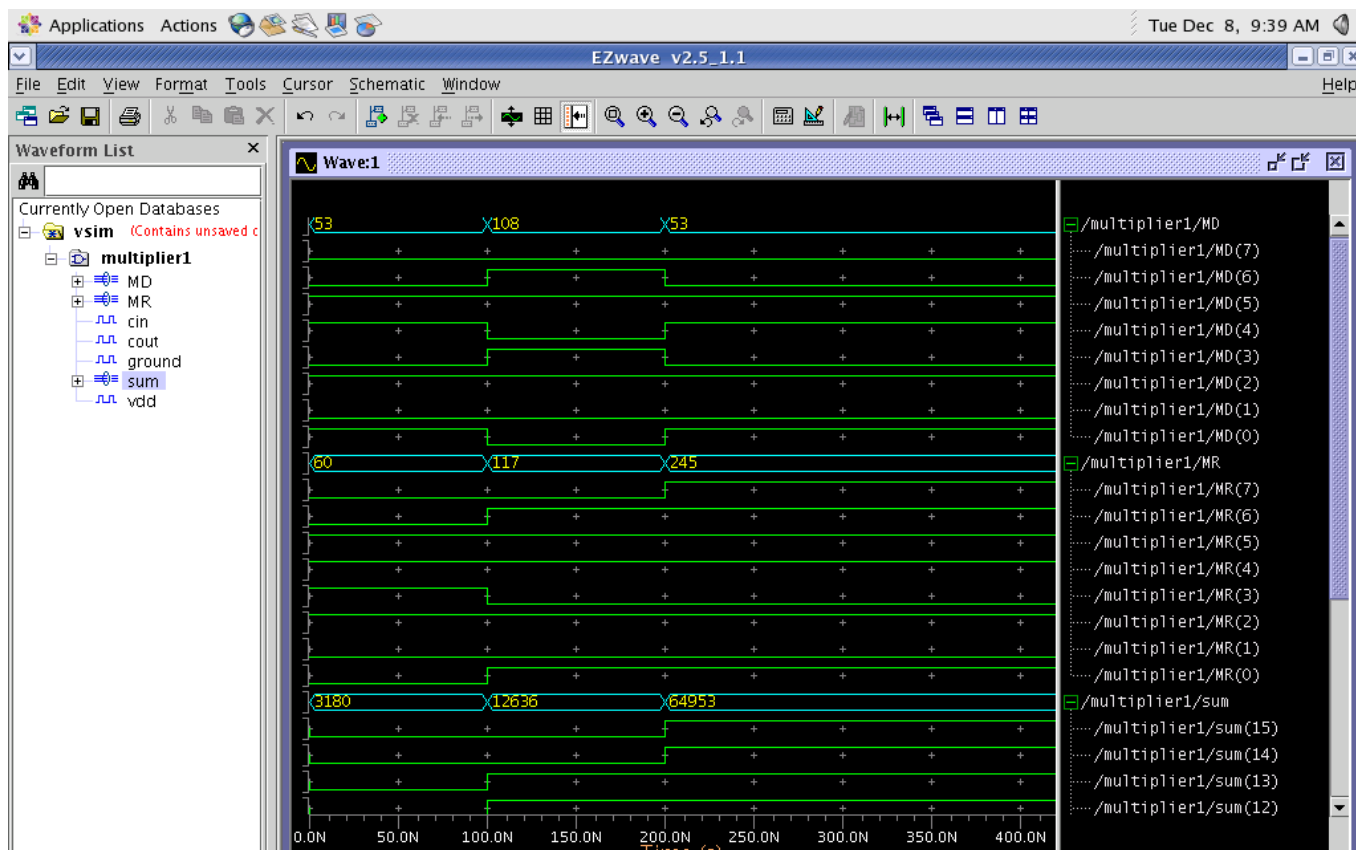


# FULL SYSTEM DESIGN

## ○ Digital simulation

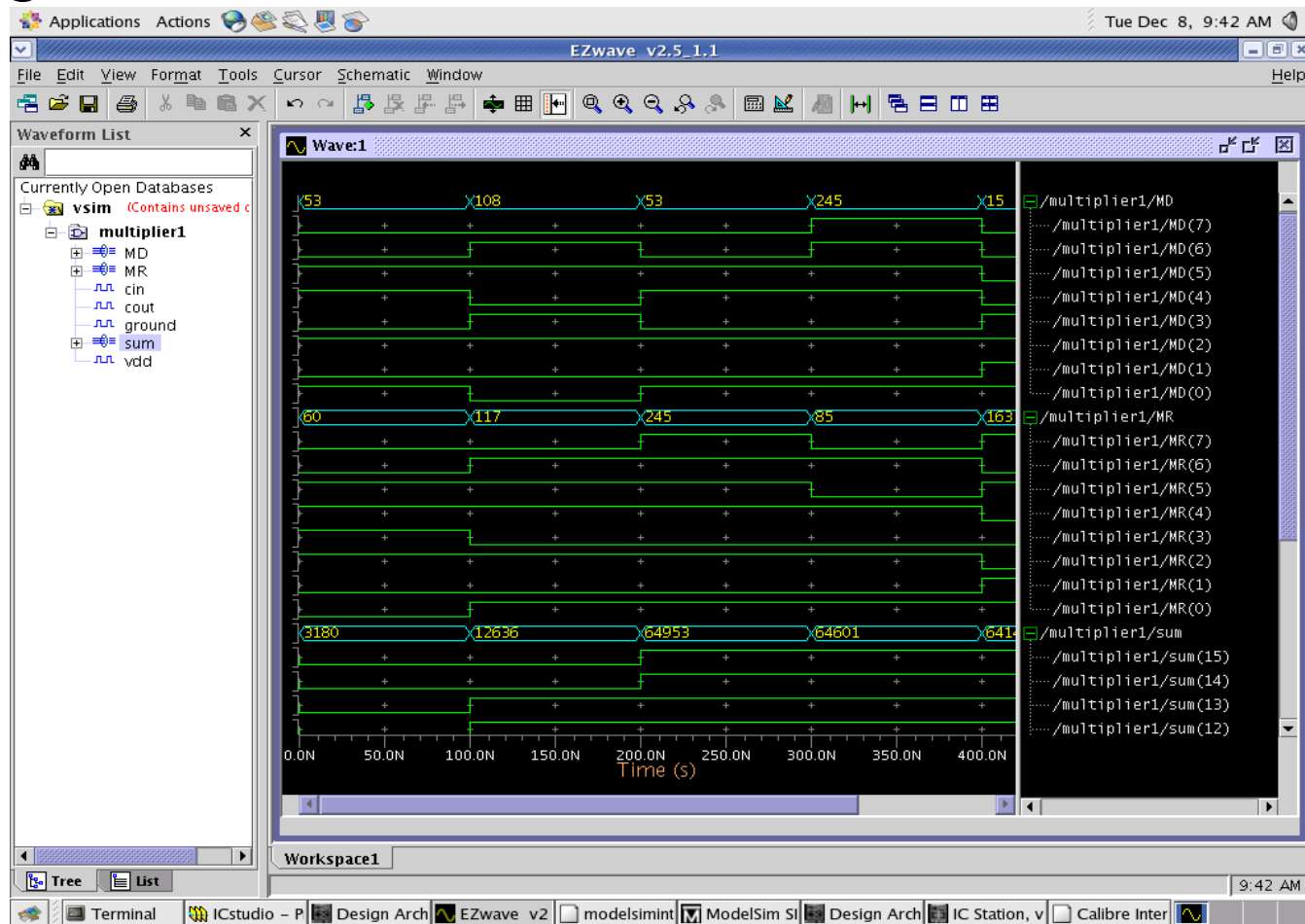


## ● Analog simulation

 

# FULL SYSTEM DESIGN


- Full system-layout

 



# FULL SYSTEM DESIGN

## ○ DRC Check

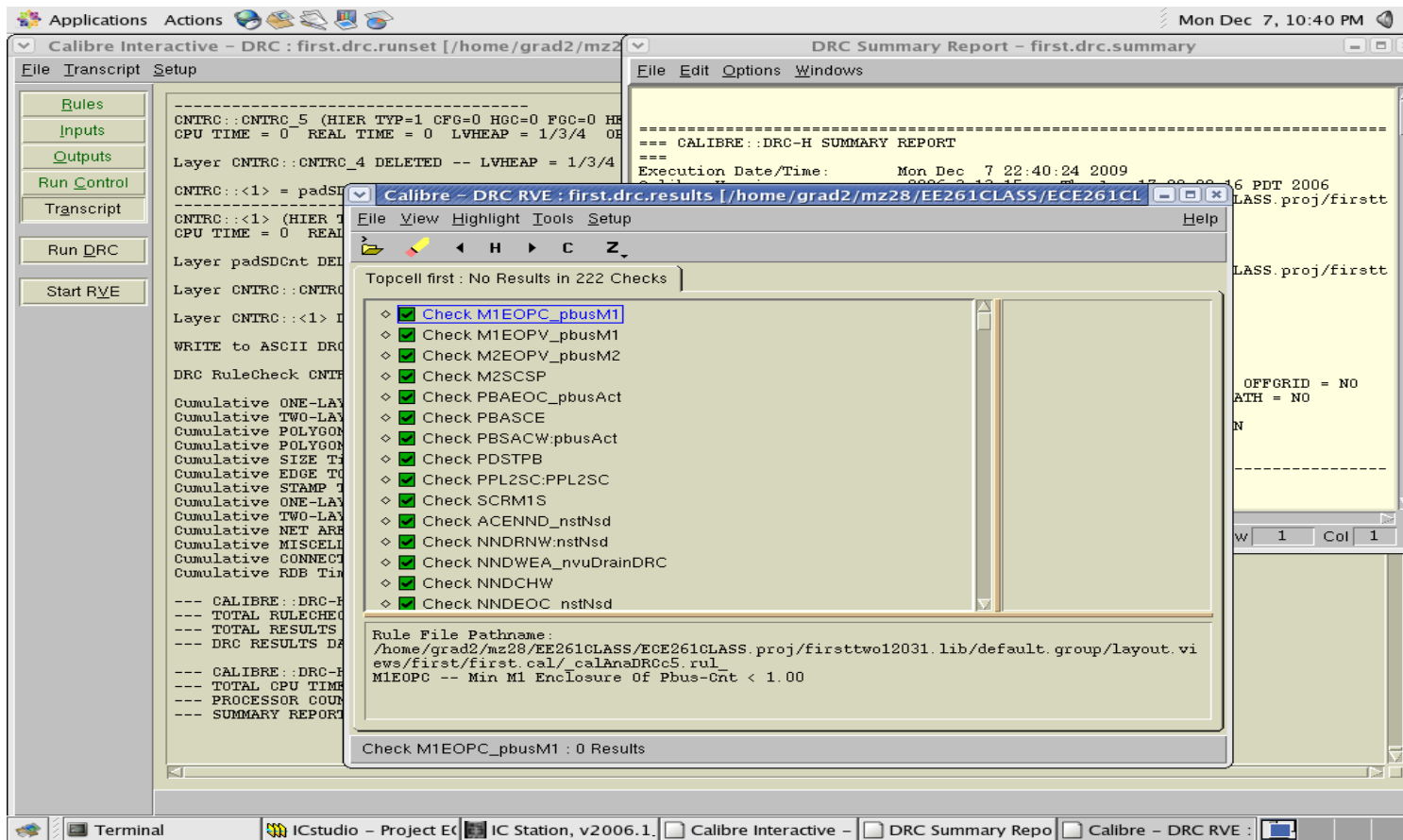

# FULL SYSTEM DESIGN

## ○ LVS Check

